

Solutions Manual

for

Microwave Engineering  
4<sup>th</sup> edition

David Pozar  
April 2011

# Chapter 1

**1.1**

This is an open-ended question where the focus of the answer may be largely chosen by the student or the instructor. Some of the relevant historical developments related to the early days of radio are listed here (as cited from T. S. Sarkar, R. J. Mailloux, A. A. Oliner, M. Salazar-Palma, and D. Sengupta, *History of Wireless*, Wiley, N.J., 2006):

1865: James Clerk Maxwell published his work on the unification of electric and magnetic phenomenon, including the introduction of the displacement current and the theoretical prediction of EM wave propagation.

1872: Mahlon Loomis, a dentist, was issued US Patent 129,971 for “aerial telegraphy by employing an ‘aerial’ used to radiate or receive pulsations caused by producing a disturbance in the electrical equilibrium of the atmosphere”. This sounds a lot like radio, but in fact Loomis was not using an RF source, instead relying on static electricity in the atmosphere. Strictly speaking this method does not involve a propagating EM wave. It was not a practical system.

1887-1888: Heinrich Hertz studied Maxwell’s equations and experimentally verified EM wave propagation using spark gap sources with dipole and loop antennas.

1893: Nikola Tesla demonstrated a wireless system with tuned circuits in the transmitter and receiver, with a spark gap source.

1895: Marconi transmitted and received a coded message over a distance of 1.75 miles in Italy.

1894: Oliver Lodge demonstrated wireless transmission of Morse code over a distance of 60 m, using coupled induction coils. This method relied on the inductive coupling between the two coils, and did not involve a propagating EM wave.

1897: Marconi was issued a British Patent 12,039 for wireless telegraphy.

1901: Marconi achieved the first trans-Atlantic wireless transmission.

1943: The US Supreme Court invalidated Marconi’s 1904 US patent on tuning using resonant circuits as being superseded by prior art of Tesla, Lodge, and Braun.

So it is clear that many workers contributed to the development of wireless technology during this time period, and that Marconi was not the first to develop a wireless system that relied on the propagation of electromagnetic waves. On the other hand, Marconi was very successful at making radio practical and commercially viable, for both shipping and land-based services.

**1.2**

$$E_y = E_0 \cos(\omega t - kx) , E_0 = 5 \text{ V/m} , f = 2.4 \text{ GHz} .$$

$$\epsilon_r = 2.54 , \chi_1 = 0.1 , \chi_2 = 0.15$$

a)  $\eta = n_0 / \sqrt{\epsilon_r} = 236.6 \Omega$

$$H_z = E_y / \eta = 0.0211 \cos(\omega t - k_z)$$

b)  $v_p = c / \sqrt{\epsilon_r} = 1.88 \times 10^8 \text{ m/sec}$

c)  $\lambda = v_p / f = 0.0784 \text{ m} , k = 2\pi/\lambda = 80.11 \text{ m}^{-1}$

d)  $\Delta\phi = k(\chi_2 - \chi_1) = 80.11(0.15 - 0.1) = 4.00 \text{ rad} = 229.5^\circ$

**1.3**

$$\bar{E} = E_0 (a \hat{x} + b \hat{y}) e^{-jk_0 z} ; a, b \text{ real}$$

Let  $\bar{E} = A (\hat{x} - j \hat{y}) e^{-jk_0 z} + B (\hat{x} + j \hat{y}) e^{-jk_0 z}$

where  $A, B$  are the amplitudes of the RCP and LCP components. Equating vector components gives

$$\hat{x}: A + B = a E_0$$

$$\hat{y}: -jA + jB = b E_0 , \text{ or } A - B = j b E_0$$

so

$$A = E_0(a + jb)/2$$

$$B = E_0(a - jb)/2$$

check: if  $a=1, b=2$  then  $A = (\frac{1}{2} + j) E_0, B = (\frac{1}{2} - j) E_0$

(agrees with Problem 1.5 from 3rd ed.)

**1.4** From eq. (1.76),

$$\bar{H} = \frac{1}{\eta_0} \hat{n} \times \bar{E} , \quad \bar{E} = \bar{E}_0 e^{-j\bar{k} \cdot \bar{r}}$$

$$\begin{aligned} \bar{S} &= \bar{E} \times \bar{H}^* = \frac{1}{\eta_0} \bar{E} \times \hat{n} \times \bar{E}^* \\ &= \frac{1}{\eta_0} [(\bar{E} \cdot \bar{E}^*) \hat{n} - (\bar{E} \cdot \hat{n}) \bar{E}^*] \quad (\text{from B.5}) \end{aligned}$$

Since  $\bar{k} \cdot \bar{E}_0 = k_0 \hat{n} \cdot \bar{E}_0 = 0$  from (1.69) and (1.74), we have

$$\bar{S} = \frac{\hat{n}}{\eta_0} \bar{E} \cdot \bar{E}^* = \frac{\hat{n}}{\eta_0} |E_0|^2 \text{ W/m}^2 \checkmark$$

**1.5**

Writing general plane wave fields in each region:

$$\begin{array}{ll} \bar{E}^i = \hat{x} e^{jk_0 z} & \bar{H}^i = \frac{j}{\eta_0} e^{jk_0 z} \quad \text{for } z < 0 \\ \bar{E}^r = \hat{x} \Gamma e^{jk_0 z} & \bar{H}^r = \frac{-j}{\eta_0} \Gamma e^{jk_0 z} \quad \text{for } z < 0 \\ \bar{E}^s = \hat{x} (A e^{jk_0 z} + B e^{-jk_0 z}) & \bar{H}^s = \frac{j}{\eta_0} (A e^{jk_0 z} - B e^{-jk_0 z}) \quad \text{for } 0 < z < d \\ \bar{E}^t = \hat{x} T e^{-jk_0(z-d)} & \bar{H}^t = \frac{j}{\eta_0} T e^{-jk_0(z-d)} \quad \text{for } z > d \end{array}$$

Now match  $E_x$  and  $H_y$  at  $z=0$  and  $z=d$  to obtain four equations for  $\Gamma, T, A, B$ :

$$z=0: \quad 1 + \Gamma = A + B \quad \frac{1}{\eta_0} (1 - \Gamma) = \frac{j}{\eta} (A - B)$$

$$z=d: \quad j(-A + B) = T \quad \frac{j}{\eta} (-A - B) = \frac{T}{\eta_0} \quad (\text{since } d = \lambda_0/4/\epsilon_r)$$

Solving for  $\Gamma$  gives

$$\Gamma = \frac{\eta^2 - \eta_0^2}{\eta^2 + \eta_0^2} \quad \checkmark$$

CHECK:

$$\lambda/4 \text{ TRANSFORMER} \Rightarrow Z_{in} = \eta^2/\eta_0 , \quad \Gamma = \frac{\eta^2/\eta_0 - \eta_0}{\eta^2/\eta_0 + \eta_0} = \frac{\eta^2 - \eta_0^2}{\eta^2 + \eta_0^2} .$$

**1.6**

The incident, reflected, and transmitted fields can be written as,

$$\bar{E}^i = E_0 (\hat{x} - j \hat{y}) e^{jk_0 z} \quad \bar{H}^i = j \frac{E_0}{\eta_0} (\hat{x} - j \hat{y}) e^{-jk_0 z} \quad (RHC) \quad (1)$$

$$\bar{E}^r = E_0 \Gamma (\hat{x} - j \hat{y}) e^{jk_0 z} \quad \bar{H}^r = j \frac{E_0}{\eta_0} \Gamma (\hat{x} - j \hat{y}) e^{jk_0 z} \quad (LHC) \quad (2)$$

$$\bar{E}^t = E_0 T (\hat{x} - j \hat{y}) e^{-jk_0 z} \quad \bar{H}^t = j \frac{E_0}{\eta} T (\hat{x} - j \hat{y}) e^{-jk_0 z} \quad (RHC) \quad (3)$$

Matching fields at  $z=0$  gives

$$\Gamma = \frac{\eta - \eta_0}{\eta + \eta_0}, \quad T = \frac{2\eta}{\eta + \eta_0}$$

The Poynting vectors are:  $(\hat{x} - j \hat{y}) \times (\hat{x} - j \hat{y})^* = 2j \hat{z}$

$$\text{For } z < 0: \bar{S}^- = (\bar{E}^i + \bar{E}^r) \times (\bar{H}^i + \bar{H}^r)^* = \frac{2\hat{z}|E_0|^2}{\eta_0} (1 - |\Gamma|^2 + \Gamma e^{2jk_0 z} + \Gamma^* e^{-2jk_0 z}) \checkmark$$

$$\text{For } z > 0: \bar{S}^+ = \bar{E}^t \times \bar{H}^t^* = \frac{2\hat{z}|E_0|^2|T|^2}{\eta^*} e^{-2k_0 z} \checkmark$$

at  $z=0$ ,

$$\bar{S}^- = \frac{2\hat{z}|E_0|^2}{\eta_0} (1 - |\Gamma|^2 + \Gamma - \Gamma^*) = \frac{2\hat{z}|E_0|^2}{\eta_0} (1 + \Gamma)(1 - \Gamma^*) \checkmark$$

$$\bar{S}^+ = 2\hat{z}|E_0|^2 \frac{4\eta}{|\eta + \eta_0|^2} \quad (\text{using } T = \frac{2\eta}{\eta + \eta_0})$$

$$= \frac{2\hat{z}|E_0|^2}{\eta_0} \left( \frac{2\eta}{\eta + \eta_0} \right) \left( \frac{2\eta_0}{\eta + \eta_0} \right)^* = \frac{2\hat{z}|E_0|^2}{\eta_0} (1 + \Gamma)(1 - \Gamma^*) \checkmark$$

Thus  $\bar{S}^- = \bar{S}^+$  at  $z=0$ , and power is conserved.

1.7

From Table 1.1,

$$\gamma = j\omega \sqrt{\mu_0 \epsilon} = 2\pi f \sqrt{\mu_0 \epsilon_0} \sqrt{5-j2} = j \frac{2\pi(1000)}{300} \sqrt{5.385} \angle -22^\circ$$
$$= 48.5 \angle 79^\circ = 9.25 + j47.6 = \alpha + j\beta \quad (\text{nepes/m, rad/m})$$


$$\eta = j\frac{\omega M}{\gamma} = \frac{j\omega \sqrt{\mu_0 \epsilon_0}}{j\omega \sqrt{\mu_0 \epsilon_0}} \sqrt{\frac{\mu_0}{\epsilon_0}} = \frac{\eta_0}{\sqrt{5-j2}} = \frac{377}{2.32 \angle -11^\circ} = 163 \angle 11^\circ \Omega$$

$$\Gamma = -1$$

$$\text{For } z < 0, \quad \bar{E} = \bar{E}^i + \bar{E}^r = 4\lambda (e^{-\gamma z} - e^{\gamma z})$$


$$|\bar{E}| = 4 |e^{-\alpha z} e^{-j\beta z} - e^{\alpha z} e^{j\beta z}|$$

$|\bar{E}|$  vs  $z$  is plotted below.

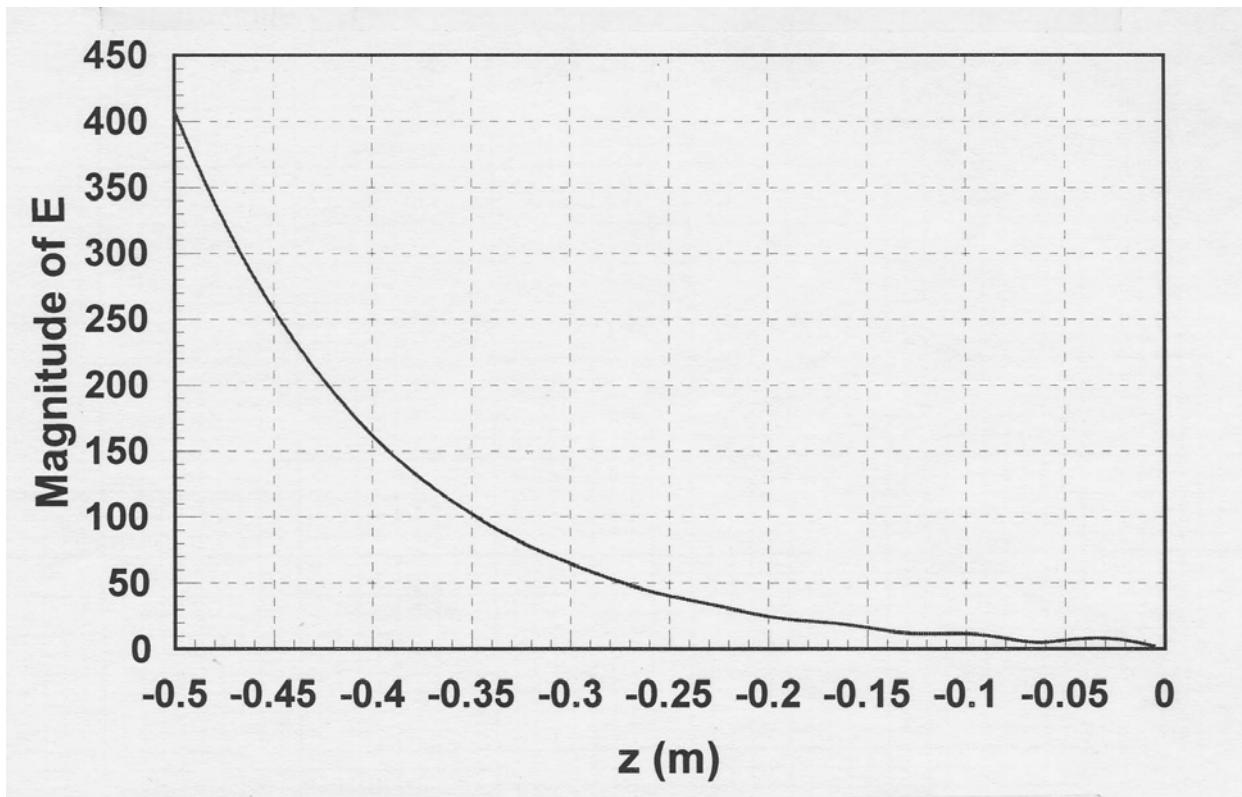

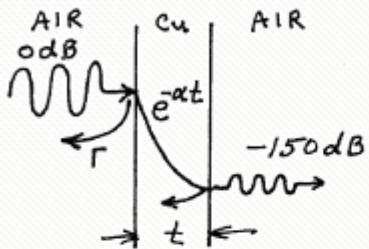1.8

The total loss through the sheet is the product of the transmission losses at the air-copper and copper-air interfaces, and the exponential loss through the sheet.



$$\delta_s = \sqrt{\frac{2}{\omega \mu_0}} = 2.09 \times 10^{-6} \text{ m} = \frac{1}{\alpha}$$

$$\eta_c = \frac{(1+j)}{\sigma \delta_s} = 8.2 \times 10^{-3} (1+j) \text{ n}$$

a) Power transfer from air into copper is given by,

$$|-\Gamma|^2, \quad \Gamma = \frac{\eta_c - \eta_0}{\eta_c + \eta_0} \approx \frac{8.2 \times 10^{-3} (1+j) - 377}{377} = -0.999956 + j 4.35E-5$$

This yields a power transfer of  $-40.6 \text{ dB}$  into the copper. By symmetry, the same transfer occurs for the copper-air interface.

b) the attenuation within the copper sheet is,

$$\begin{aligned} \text{copper att.} &= 150 \text{ dB} - 40.6 \text{ dB} - 40.6 \text{ dB} = 68.8 \text{ dB} \\ &= -20 \log e^{-t/\delta_s} \Rightarrow t = \underline{0.017 \text{ mm}} \quad \checkmark \end{aligned}$$

(J. Mead provided this correction on 9/04)

**1.9** From Table 1.1,

$$\gamma = j \omega \sqrt{\mu_0 \epsilon} = j \frac{2\pi(3000)}{300} \sqrt{3(1-j.1)} = 5.435 + j 108.964 = \alpha + j \beta \text{ m}^{-1}$$

$$\eta = \frac{\eta_0}{\sqrt{\epsilon_r(1-j.1)}} = 217.121 / 2.855^\circ$$

a)  $S_i = \text{Re} \left\{ \frac{|\bar{E}_i(z=0)|^2}{\eta^*} \right\} = 46.000 \text{ W/m}^2 \quad \checkmark$

$$\Gamma = -1 \text{ at } z=l=20 \text{ cm}$$

$$\bar{E}_r = \Gamma \bar{E}_i(z=l) e^{\gamma(z-l)} = -100 \hat{x} e^{-2\gamma l} e^{\gamma z}$$

$$S_r = \text{Re} \left\{ \frac{|\bar{E}_r(z=0)|^2}{\eta^*} \right\} = 0.595 \text{ W/m}^2 \quad \checkmark$$

b)  $\bar{E}_t = \bar{E}_i + \bar{E}_r$

$$\bar{E}_t(z=0) = 100 \hat{x} (1 - e^{-2\gamma l}), \bar{H}_t(z=0) = \frac{100 \hat{y}}{\eta} (1 + e^{-2\gamma l})$$

$$S_{in} = \text{Re} \left\{ \bar{E}_t \times \bar{H}_t^* \cdot \hat{z} \right\} = 45.584 \text{ W/m}^2$$

But  $S_i - S_r = 45.405 \text{ W/m}^2 \neq S_{in}$ . This is because  $S_i$  and  $S_r$  individually are not physically meaningful in a lossy medium.

(The above were computed using a FORTRAN program, with 6 digit precision. The error between  $S_i - S_r$  and  $S_{in}$  is only about 0.4% - this would be larger if the loss were greater.)

**1.10** As in Example 1.3, assume outgoing plane wave fields in each region. To get  $J_{sx}$ , we need  $H_y$ , since  $\hat{n} \times (\bar{H}_2 - \bar{H}_1) = \bar{J}_s$  ( $\hat{n} = \hat{z}$ ). Then we must have  $E_x$  to get  $\bar{s} = \bar{E} \times \bar{H}^* = \pm s \hat{z}$ . So the form of the fields must be,

$$\text{for } z < 0, \quad \bar{E}_1 = \hat{x} A e^{jk_0 z} \quad \text{for } z > 0, \quad \bar{E}_2 = \hat{x} B e^{-jk_0 z}$$

$$\bar{H}_1 = -\frac{j}{\eta_0} A e^{jk_0 z} \quad \bar{H}_2 = \frac{j}{\eta} B e^{-jk_0 z}$$

with  $k_0 = \omega \sqrt{\mu_0 \epsilon_0}$ ,  $k = \omega \sqrt{\mu_0 \epsilon_0 \epsilon_r}$ ,  $\eta_0 = \sqrt{\mu_0 / \epsilon_0}$ ,  $\eta = \sqrt{\mu_0 / \epsilon_0 \epsilon_r}$ , and  $A$  and  $B$  are unknown amplitudes to be determined.

The boundary conditions at  $z=0$  are, from (1.36) and (1.37),

$$(\bar{E}_2 - \bar{E}_1) \times \hat{n} = 0 \Rightarrow A = B$$

$$\hat{z} \times (\bar{H}_2 - \bar{H}_1) = \bar{J}_s \Rightarrow -\left(\frac{B}{\eta} + \frac{A}{\eta_0}\right) = J_s$$

$$\therefore A = B = \frac{-J_s \eta \eta_0}{\eta + \eta_0}$$

1.11

This current sheet will generate obliquely propagating plane waves. From (1.132)-(1.133), assume

$$\begin{aligned}\bar{E}_1 &= A (\hat{x} \cos \theta_1 + \hat{z} \sin \theta_1) e^{-jk_0(x \sin \theta_1 - z \cos \theta_1)} \\ \bar{H}_1 &= \frac{-A}{\eta_0} \hat{y} e^{-jk_0(x \sin \theta_1 - z \cos \theta_1)}\end{aligned}\quad \left. \right\} \text{for } z < 0$$

$$\begin{aligned}\bar{E}_2 &= B (\hat{x} \cos \theta_2 - \hat{z} \sin \theta_2) e^{-jk(x \sin \theta_2 + z \cos \theta_2)} \\ \bar{H}_2 &= \frac{B}{\eta} \hat{y} e^{-jk(x \sin \theta_2 + z \cos \theta_2)}\end{aligned}\quad \left. \right\} \text{for } z > 0$$

$$\text{with } k_0 = \omega / \sqrt{\mu_0 \epsilon_0}, \quad k = \sqrt{\epsilon_r} k_0, \quad \eta_0 = \sqrt{\mu_0 \epsilon_0}, \quad \eta = \eta_0 / \sqrt{\epsilon_r}.$$

Apply boundary conditions at  $z=0$ :

$$\hat{z} \times (\bar{E}_2 - \bar{E}_1) = 0 \implies A \cos \theta_1 e^{-jk_0 x \sin \theta_1} - B \cos \theta_2 e^{-jk x \sin \theta_2} = 0$$

$$\hat{z} \times (\bar{H}_2 - \bar{H}_1) = J_s \implies \frac{A}{\eta_0} e^{-jk_0 x \sin \theta_1} + \frac{B}{\eta} e^{-jk x \sin \theta_2} = -J_s e^{-j\beta x}$$

For phase matching we must have  $k_0 \sin \theta_1 = k \sin \theta_2 = \beta$

$$\therefore \theta_1 = \sin^{-1} \beta / k_0 \quad \theta_2 = \sin^{-1} \beta / k \quad (\text{must have } \beta < k_0)$$

Then,

$$A \cos \theta_1 = B \cos \theta_2, \quad \frac{A}{\eta_0} + \frac{B}{\eta} = -J_s$$

$$A = \frac{-J_s \eta \eta_0 \cos \theta_2}{\eta \cos \theta_2 + \eta_0 \cos \theta_1}, \quad B = \frac{-J_s \eta \eta_0 \cos \theta_1}{\eta \cos \theta_2 + \eta_0 \cos \theta_1}$$

Check: If  $\beta=0$ , then  $\theta_1=\theta_2=0$ , and  $A=B=\frac{-J_s \eta \eta_0}{\eta+\eta_0}$ ,

which agrees with Problem 1.10 ✓

1.12

This solution is identical to the parallel polarized dielectric case of Section 1.8, except for the definitions of  $k_1$ ,  $k_2$ ,  $\eta_1$ , and  $\eta_2$ . Thus,

$$k_0 \sin \theta_i = k_0 \sin \theta_r = k \sin \theta_t \quad ; \quad k = k_0 \sqrt{\mu_r}$$

$$\Gamma = \frac{\eta \cos \theta_t - \eta_0 \cos \theta_i}{\eta \cos \theta_t + \eta_0 \cos \theta_i}$$

$$T = \frac{2 \eta \cos \theta_i}{\eta \cos \theta_t + \eta_0 \cos \theta_i}$$

$$\eta = \eta_0 \sqrt{\mu_r}$$

There will be a Brewster angle if  $\Gamma=0$ . This requires that,

$$\eta \cos \theta_t = \eta_0 \cos \theta_i$$

$$\sqrt{\mu_r} \sqrt{1 - \left(\frac{k_0}{k}\right)^2 \sin^2 \theta_i} = \cos \theta_i = \sqrt{1 - \sin^2 \theta_i}$$

$$\mu_r \left(1 - \frac{1}{\mu_r} \sin^2 \theta_i\right) = 1 - \sin^2 \theta_i$$

or,  $\mu_r = 1$ . This implies a uniform region, so there is no Brewster angle for  $\mu_r \neq 1$ .

**1.13**

Again, this solution is similar to the perpendicular polarized case of section 1.8, except for the definition of  $k_1, k_2, \eta_1, \eta_2$ . Thus,

$$\Gamma = \frac{\eta \cos \theta_i - \eta_0 \cos \theta_t}{\eta \cos \theta_i + \eta_0 \cos \theta_t}, \quad T = \frac{2 \eta \cos \theta_i}{\eta \cos \theta_i + \eta_0 \cos \theta_t}$$

a Brewster angle exists if

$$\eta \cos \theta_i = \eta_0 \cos \theta_t$$

$$\sqrt{\mu_r} \sqrt{1 - \sin^2 \theta_i} = \sqrt{1 - \frac{1}{\mu_r} \sin^2 \theta_i}$$

$$\mu_r^2 - \mu_r \sin^2 \theta_i = \mu_r - \sin^2 \theta_i$$

$$\mu_r = (\mu_r + 1) \sin^2 \theta_i$$

$$\sin \theta_i = \sin \theta_b = \sqrt{\frac{\mu_r}{1 + \mu_r}} < 1 \quad \checkmark$$

Thus, a Brewster angle does exist for this case.

**1.14**

$$\bar{E} = 3\hat{x} - 2\hat{y} + 5\hat{z}$$

$$\bar{D} = [\epsilon] \bar{E} = \begin{bmatrix} 1 & 3j & 0 \\ -3j & 2 & 0 \\ 0 & 0 & 4 \end{bmatrix} \begin{bmatrix} 3 \\ -2 \\ 5 \end{bmatrix} = \begin{bmatrix} 3 - 6j \\ -4 - 9j \\ 20 \end{bmatrix} = (3 - 6j)\hat{x} + (-4 - 9j)\hat{y} + 20\hat{z}$$

1.15

$$D_x = \epsilon_0 (\epsilon_r E_x + j \times E_y)$$

$$D_y = \epsilon_0 (-j \times E_x + \epsilon_r E_y)$$

$$D_z = \epsilon_0 E_z$$

Then,

$$D_+ = D_x - j D_y = \epsilon_0 (\epsilon_r - k) E_x - j \epsilon_0 (\epsilon_r - k) E_y = \epsilon_0 (\epsilon_r - k) E_+$$

$$D_- = D_x + j D_y = \epsilon_0 (\epsilon_r + k) E_x + j \epsilon_0 (\epsilon_r + k) E_y = \epsilon_0 (\epsilon_r + k) E_-$$

OR,

$$\begin{bmatrix} D_+ \\ D_- \\ D_z \end{bmatrix} = \begin{bmatrix} (\epsilon_r - k) & 0 & 0 \\ 0 & (\epsilon_r + k) & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} E_+ \\ E_- \\ E_z \end{bmatrix}$$

From Maxwell's equations,

$$\begin{aligned} \nabla \times \bar{E} &= -j \omega \mu \bar{H} \\ \nabla \times \bar{H} &= j \omega \epsilon [\epsilon] \bar{E} \end{aligned} \quad \left\{ \begin{aligned} \nabla \times \nabla \times \bar{E} &= -j \omega \mu \nabla \times \bar{H} = \omega^2 \mu [\epsilon] \bar{E} \\ \nabla^2 \bar{E} + \omega^2 \mu [\epsilon] \bar{E} &= 0 \end{aligned} \right. \text{ (CARTESIAN)}$$

Expanding this wave equation gives,

$$\nabla^2 E_x + \omega^2 \mu \epsilon_0 (\epsilon_r E_x + j \times E_y) = 0 \quad (1)$$

$$\nabla^2 E_y + \omega^2 \mu \epsilon_0 (-j \times E_x + \epsilon_r E_y) = 0 \quad (2)$$

$$\nabla^2 E_z + k_0^2 E_z = 0 \quad (3)$$

Adding (1) + j(2) gives  $\nabla^2 (E_x + j E_y) + \omega^2 \mu \epsilon_0 [(\epsilon_r + k) E_x + j (\epsilon_r + k) E_y] = 0$ 

$$\nabla^2 E^+ + \omega^2 \mu \epsilon_0 (\epsilon_r + k) E^+ = 0$$

$$\therefore \beta_+ = k_0 \sqrt{\epsilon_r + k} \quad \checkmark$$

Adding (1) - j(2) gives  $\nabla^2 (E_x - j E_y) + \omega^2 \mu \epsilon_0 [(\epsilon_r - k) E_x - j (\epsilon_r - k) E_y] = 0$ 

$$\nabla^2 E^- + \omega^2 \mu \epsilon_0 (\epsilon_r - k) E^- = 0$$

$$\therefore \beta_- = k_0 \sqrt{\epsilon_r - k} \quad \checkmark$$

Note that the wave equations for  $E^+$ ,  $E^-$  must be satisfied simultaneously. Thus, for  $E^+$  we must have  $E^- = 0$ . This implies that  $E_y = j E_x = j E_0$ . The actual electric field is then,  $\bar{E}^+ = \hat{x} E_x + \hat{y} E_y = E_0 (\hat{x} + j \hat{y}) e^{-j \beta_+ z}$  (LHCP)

This is a LHCP wave. Similarly for  $\bar{E}^-$  we must have

$$E^+ = 0 : \quad \bar{E}^- = \hat{x} E_x + \hat{y} E_y = E_0 (\hat{x} - j \hat{y}) e^{j \beta_- z} \quad (\text{RHCP})$$

**1.16**

Comparing (1.118), (1.125), and (1.129) shows that


$$E_t = \frac{J_t}{\sigma} = \frac{J_s}{\sigma \delta s} = R_s J_s.$$

Thus  $\bar{E}_t = R_s \bar{J}_s = R_s \hat{n} \times \bar{H}$  is the desired surface impedance relation. Applying this to the surface integral of (1.155) gives, on  $\delta$ ,

$$\begin{aligned}
 & [(\bar{E}_1 \times \bar{H}_2) - (\bar{E}_2 \times \bar{H}_1)] \cdot \hat{n} = R_s [(\hat{n} \times \bar{H}_{1t}) \times \bar{H}_{2t} - (\hat{n} \times \bar{H}_{2t}) \times \bar{H}_{1t}] \\
 (\text{USING B.5}) \quad & = R_s [(\cancel{\bar{H}_{2t}} \cdot \cancel{\hat{n}}) \bar{H}_{1t} - (\cancel{\bar{H}_{2t}} \cdot \cancel{\hat{n}}) \bar{H}_{1t} - (\cancel{\bar{H}_{1t}} \cdot \cancel{\hat{n}}) \bar{H}_{2t} + (\cancel{\bar{H}_{1t}} \cdot \cancel{\hat{n}}) \bar{H}_{2t}] \\
 & = 0
 \end{aligned}$$

So (1.157) is obtained.

1.17

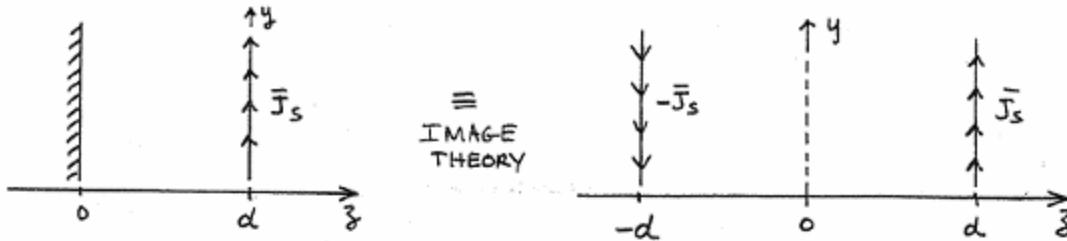

First find the fields due to the source at  $z=d$ . From (1.139) – (1.140),

$$\text{FOR } z < d, \quad \bar{E}_1 = A \hat{y} e^{-jk_0(x \sin \theta - z \cos \theta)}$$

$$\bar{H}_1 = \frac{A}{\eta_0} (\hat{x} \cos \theta + \hat{z} \sin \theta) e^{-jk_0(x \sin \theta - z \cos \theta)}$$

$$\text{FOR } z > d, \quad \bar{E}_2 = B \hat{y} e^{-jk_0(x \sin \theta + z \cos \theta)}$$

$$\bar{H}_2 = \frac{B}{\eta_0} (-\hat{x} \cos \theta + \hat{z} \sin \theta) e^{-jk_0(x \sin \theta + z \cos \theta)}$$

Apply boundary conditions at  $z=d$ :

$$\hat{z} \times [\bar{E}(d^+) - \bar{E}(d^-)] = 0 \Rightarrow A e^{jk_0 d \cos \theta} = B e^{-jk_0 d \cos \theta}$$

$$\hat{z} \times [\bar{H}(d^+) - \bar{H}(d^-)] = \bar{J}_s \Rightarrow [-B \cos \theta e^{-jk_0 d \cos \theta} - A \cos \theta e^{jk_0 d \cos \theta}]$$

$$e^{-jk_0 x \sin \theta} = \eta_0 J_0 e^{-j\beta x}$$

$$\text{For phase matching, } k_0 \sin \theta = \beta$$

$$\text{Then, } A = \frac{-\eta_0 J_0}{2 \cos \theta} e^{-jk_0 d \cos \theta} \quad B = \frac{-\eta_0 J_0}{2 \cos \theta} e^{jk_0 d \cos \theta}$$

$$\bar{E} = \frac{-\eta_0 J_0 \hat{y}}{2 \cos \theta} \begin{cases} e^{-jk_0 [x \sin \theta - (z-d) \cos \theta]} & z < d \\ e^{-jk_0 [x \sin \theta + (z-d) \cos \theta]} & z > d \end{cases}$$

The fields due to the source at  $z=-d$  can then be found by replacing  $d$  with  $-d$ , and  $J_0$  with  $-J_0$ :

$$\bar{E} = \frac{\eta_0 J_0 \hat{y}}{2 \cos \theta} \begin{cases} e^{-jk_0 [x \sin \theta - (z+d) \cos \theta]} & z < -d \\ e^{-jk_0 [x \sin \theta + (z+d) \cos \theta]} & z > -d \end{cases}$$

Combining these results gives the total fields:

$$\bar{E} = \frac{-j \eta_0 J_0 \hat{y}}{\cos \theta} \begin{cases} e^{-jk_0 x \sin \theta} e^{-jk_0 d} \sin(k_0 z \cos \theta) & 0 < z < d \\ e^{-jk_0 x \sin \theta} e^{-jk_0 z} \sin(k_0 d \cos \theta) & z > d \end{cases}$$

CHECK: If  $\beta=0$ , then  $\theta=0$  and we have,

$$\bar{E} = -j \eta_0 J_0 \hat{y} \begin{cases} e^{-jk_0 d} \sin k_0 z & \text{for } 0 < z < d \\ e^{-jk_0 z} \sin k_0 d & \text{for } z > d \end{cases}$$

This agrees with the results in (1.161) - (1.162).

1.18

$$\begin{aligned}
 \nabla \times \bar{E} &= \hat{\rho} \left( \frac{1}{\rho} \frac{\partial E_3}{\partial \phi} - \frac{\partial E_\phi}{\partial z} \right) + \hat{\phi} \left( \frac{\partial E_\rho}{\partial z} - \frac{\partial E_3}{\partial \rho} \right) + \hat{z} \left( \frac{1}{\rho} \left( \frac{\partial (\rho E_\phi)}{\partial \rho} \right) - \frac{\partial E_\rho}{\partial \phi} \right) \\
 \nabla \times \nabla \times \bar{E} &= \hat{\rho} \left[ -\frac{1}{\rho^2} \frac{\partial^2 E_\rho}{\partial \phi^2} - \frac{\partial^2 E_\rho}{\partial z^2} + \frac{\partial^2 E_3}{\partial \rho \partial z} + \frac{1}{\rho} \frac{\partial^2 E_\phi}{\partial \rho \partial \phi} + \frac{1}{\rho^2} \frac{\partial^2 E_\phi}{\partial \phi^2} \right] \\
 &\quad + \hat{\phi} \left[ -\frac{\partial^2 E_\phi}{\partial z^2} + \frac{1}{\rho} \frac{\partial^2 E_3}{\partial \phi \partial z} - \frac{\partial^2 E_\phi}{\partial \rho^2} - \frac{1}{\rho} \frac{\partial E_\phi}{\partial \rho} + \frac{E_\phi}{\rho^2} - \frac{1}{\rho^2} \frac{\partial E_\rho}{\partial \phi} + \frac{1}{\rho} \frac{\partial^2 E_\rho}{\partial \phi \partial \rho} \right] \\
 &\quad + \hat{z} \left[ -\frac{\partial^2 E_3}{\partial \rho^2} - \frac{1}{\rho^2} \frac{\partial^2 E_3}{\partial \phi^2} + \frac{\partial^2 E_\rho}{\partial \rho \partial z} + \frac{1}{\rho} \frac{\partial^2 E_\phi}{\partial \phi \partial z} + \frac{1}{\rho} \frac{\partial E_\rho}{\partial z} - \frac{1}{\rho} \frac{\partial E_3}{\partial \rho} \right] \\
 \nabla \cdot (\nabla \cdot \bar{E}) &= \hat{\rho} \left[ \frac{\partial^2 E_\rho}{\partial \rho^2} + \frac{\partial^2 E_3}{\partial \rho \partial z} + \frac{1}{\rho} \frac{\partial^2 E_\phi}{\partial \rho \partial \phi} + \frac{1}{\rho} \frac{\partial E_\rho}{\partial \rho} - \frac{1}{\rho^2} \frac{\partial E_\phi}{\partial \phi} - \frac{E_\rho}{\rho^2} \right] \\
 &\quad + \hat{\phi} \left[ \frac{1}{\rho} \frac{\partial^2 E_3}{\partial \phi \partial z} + \frac{1}{\rho^2} \frac{\partial^2 E_\phi}{\partial \phi^2} + \frac{1}{\rho} \frac{\partial^2 E_\rho}{\partial \rho \partial \phi} + \frac{1}{\rho^2} \frac{\partial E_\rho}{\partial \phi} \right] \\
 &\quad + \hat{z} \left[ \frac{\partial^2 E_3}{\partial z^2} + \frac{1}{\rho} \frac{\partial^2 E_\phi}{\partial \phi \partial z} + \frac{\partial^2 E_\rho}{\partial \rho \partial z} + \frac{1}{\rho} \frac{\partial E_\rho}{\partial z} \right]
 \end{aligned}$$

If we apply  $\nabla^2$  to the cylindrical components of  $\bar{E}$  we get:

$$\begin{aligned}
 \nabla^2 \bar{E} &\stackrel{?}{=} \hat{\rho} \nabla^2 E_\rho + \hat{\phi} \nabla^2 E_\phi + \hat{z} \nabla^2 E_3 \quad (\text{THIS IS NOT A VALID STEP!}) \\
 &= \hat{\rho} \left[ \frac{1}{\rho} \frac{\partial E_\rho}{\partial \rho} + \frac{\partial^2 E_\rho}{\partial \rho^2} + \frac{1}{\rho^2} \frac{\partial^2 E_\rho}{\partial \phi^2} + \frac{\partial^2 E_\rho}{\partial z^2} \right] \\
 &\quad + \hat{\phi} \left[ \frac{1}{\rho} \frac{\partial E_\phi}{\partial \rho} + \frac{\partial^2 E_\phi}{\partial \rho^2} + \frac{1}{\rho^2} \frac{\partial^2 E_\phi}{\partial \phi^2} + \frac{\partial^2 E_\phi}{\partial z^2} \right] \\
 &\quad + \hat{z} \left[ \frac{1}{\rho} \frac{\partial E_3}{\partial \rho} + \frac{\partial^2 E_3}{\partial \rho^2} + \frac{1}{\rho^2} \frac{\partial^2 E_3}{\partial \phi^2} + \frac{\partial^2 E_3}{\partial z^2} \right]
 \end{aligned}$$

Note that the  $\hat{\rho}$  and  $\hat{\phi}$  components of  $\nabla \times \nabla \times \bar{E}$  and  $\nabla \cdot (\nabla \cdot \bar{E}) - \nabla^2 \bar{E}$  do not agree. This is because  $\hat{\rho}$  and  $\hat{\phi}$  are not constant vectors, so  $\nabla^2 \bar{E} \neq \hat{\rho} \nabla^2 E_\rho + \hat{\phi} \nabla^2 E_\phi + \hat{z} \nabla^2 E_3$ . The  $\hat{z}$  components are equal.

## Chapter 2

**2.1**

$$i(t, z) = 1.8 \cos(3.77 \times 10^9 t - 18.13z) \text{ mA}$$

$$\omega = 3.77 \times 10^9 \text{ rad/sec}, \beta = 18.13 \text{ m}^{-1}, Z_0 = 75 \Omega$$

$$a) f = \omega/2\pi = 3.77 \times 10^9 / 2\pi = 600 \text{ MHz}$$

$$b) V_p = \omega/\beta = 2.08 \times 10^8 \text{ m/sec}$$

$$c) \lambda = 2\pi/\beta = 0.346 \text{ m}$$

$$d) \epsilon_r = (c/V_p)^2 = 2.08 \text{ (Teflon)}$$

$$e) I(z) = 1.8 e^{-j\beta z} \text{ (mA)}$$

$$f) v(t, z) = 0.135 \cos(\omega t - \beta z) \text{ V.}$$

**2.2**

$$R = 4.0 \Omega/\text{m}, G = 0.02 \text{ S/m}, L = 0.5 \mu\text{H/m}, C = 200 \text{ pF/m}$$

$$f = 800 \text{ MHz}, l = 30 \text{ cm}$$

$$Y = \sqrt{(R+j\omega L)(G+j\omega C)} = 0.540 + j 50.268 \text{ 1/m}$$

$$Z_0 = \sqrt{(R+j\omega L)/(G+j\omega C)} = 49.99 + j 0.46 \Omega$$

$$\text{with } R=G=0, \beta = \omega \sqrt{LC} = 50.265 \text{ rad/m}$$

$$Z_0 = \sqrt{L/C} = 50.0 \Omega$$

Note that  $\beta, Z_0$  w/o loss are very close to values with loss.

$$\text{For } l = 30 \text{ cm, att} = \alpha l = 0.162 \text{ dB} \left( \frac{8.686 \text{ dB}}{\text{m}} \right) = 1.4 \text{ dB}$$

**2.3** From Table 2.1:

$$L = \frac{\mu_0}{2\pi} \ln \frac{b}{a} = 2.40 \times 10^{-7} \text{ H/m}$$

$$C = \frac{2\pi\epsilon_0\epsilon_r}{\ln b/a} = 9.64 \times 10^{-11} \text{ Fd/m}$$

$$R = \frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right) = 3.76 \text{ } \Omega/\text{m}$$

$$G = \frac{2\pi\omega\epsilon_0\epsilon_r \tan\delta}{\ln b/a} = 2.42 \times 10^{-4} \text{ S/m}$$

$$R_s = \sqrt{\frac{\mu_0}{2\pi}} = 0.00825 \text{ } \Omega$$

For small loss,  $Z_0 = \sqrt{L/C} = 49.9 \text{ } \Omega \checkmark$

From (2.85a),  $\alpha \approx \frac{1}{2} \left( \frac{R}{Z_0} + G Z_0 \right) = 0.044 \text{ np/m} = 0.38 \text{ dB/m} \checkmark$

From RG-402V cable data:  $Z_0 = 50 \Omega$ ,  $\alpha = 13 \text{ dB/100 ft}$   
 $= 0.426 \text{ dB/m}$

Check using formulas from Example 2.7: (difference due to braided outer conductor, not solid)

$$Z_0 = \sqrt{\frac{\mu}{\epsilon}} \frac{\ln b/a}{2\pi} = 49.9 \text{ } \Omega \checkmark$$

$$\alpha_C = \frac{R_s}{2\pi \ln b/a} \left( \frac{1}{a} + \frac{1}{b} \right) = 0.0376 \text{ np/m} = 0.326 \text{ dB/m} \checkmark$$

$$\alpha_d = \frac{\omega\epsilon_0\epsilon_r}{2} \eta \tan\delta = 0.00605 \text{ np/m} = 0.052 \text{ dB/m}$$

$$\alpha_T = 0.378 \text{ dB/m} \checkmark$$


Also verified with Serenade.

**2.4**

Using the formulas of Problem 2.3, with  $\alpha \approx \frac{1}{2}(R/Z_0 + GZ_0)$ :

$f$	$R_s(\omega)$	$R(\omega)$	$G(s)$	$\alpha (Np/m)$	$\alpha (dB/m)$
1 MHz	$2.6 \times 10^{-4}$	0.118	$2.42 \times 10^{-7}$	$1.19 \times 10^{-3}$	0.0103
10 MHz	$8.25 \times 10^{-4}$	0.376	$2.42 \times 10^{-6}$	$3.82 \times 10^{-3}$	0.0332
100 MHz	$2.6 \times 10^{-3}$	1.18	$2.42 \times 10^{-5}$	$1.24 \times 10^{-3}$	0.1078
1 GHz	$8.25 \times 10^{-3}$	3.76	$2.42 \times 10^{-4}$	$4.365 \times 10^{-2}$	0.379
10 GHz	$2.6 \times 10^{-2}$	11.8	$2.42 \times 10^{-3}$	$1.785 \times 10^{-1}$	1.55
100 GHz	$8.25 \times 10^{-3}$	37.6	$2.42 \times 10^{-2}$	1.96	17.0

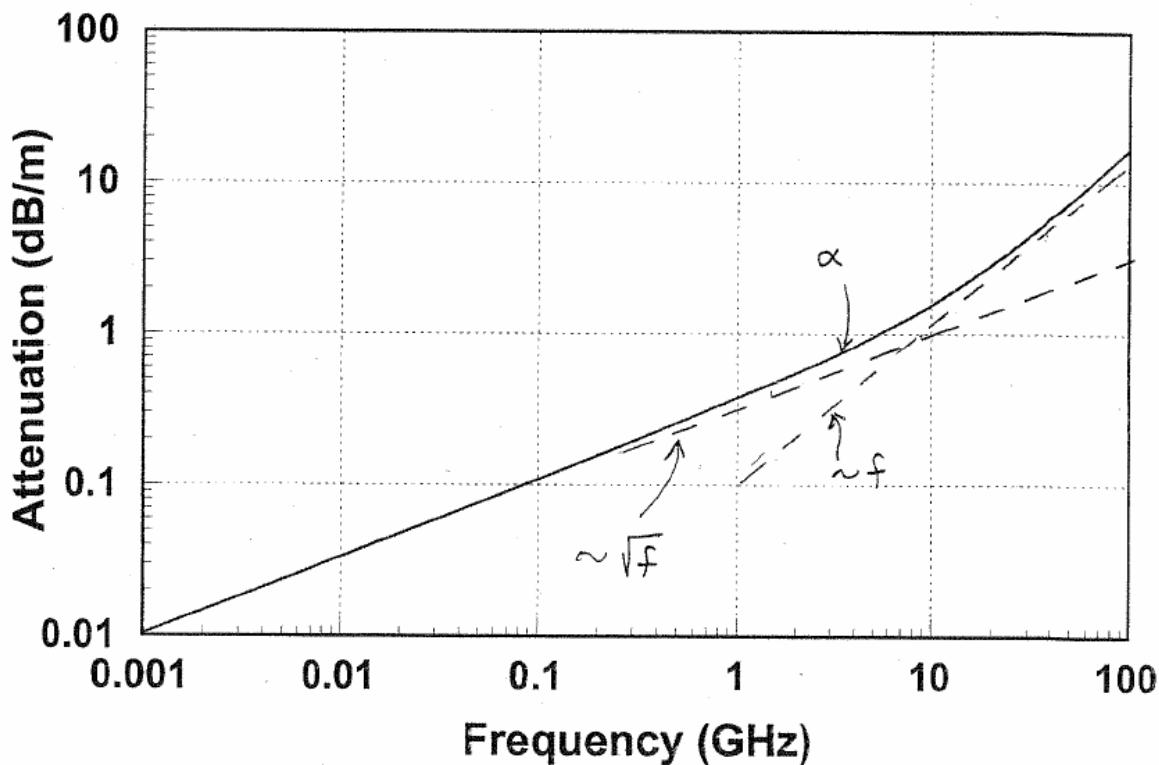Results are plotted below (with additional data points). Note that the frequency dependence is between  $\sqrt{f}$  ( $R \sim \sqrt{f}$ ), and  $f$  ( $G \sim f$ ), at low and high frequencies.



2.5

Ignoring fringing fields,  $E$  and  $\bar{H}$  can be assumed as,

$$E_y = \frac{-V_0}{d} \text{ V/m}, \quad H_x = \frac{V_0}{d\eta} = \frac{I_0}{W} \text{ A/m}, \quad \eta = \sqrt{\mu/\epsilon}$$

$$\text{Then } \bar{E} \times \bar{H}^* = \frac{1}{2} |s| \quad \text{and} \quad I_0 = V_0 \left( \frac{W}{\eta d} \right)$$

From (2.17) - (2.20),

$$L = \frac{\mu_0}{I_0^2} \int_S |\bar{H}|^2 ds = \frac{\mu_0}{I_0^2} \int_{x=0}^W \int_{y=0}^d \left( \frac{I_0}{W} \right)^2 dx dy = \frac{\mu_0 d}{W} \text{ H/m}$$

$$C = \frac{\epsilon}{V_0^2} \int_S |\bar{E}|^2 ds = \frac{\epsilon}{V_0^2} \int_{x=0}^W \int_{y=0}^d \left( \frac{-V_0}{d} \right)^2 dx dy = \frac{\epsilon W}{d} \text{ Fm/m}$$

$$R = \frac{R_s}{I_0^2} \int_{c_1+c_2} |\bar{H}|^2 dl = \frac{2R_s}{I_0^2} \int_{x=0}^W \left( \frac{I_0}{W} \right)^2 dx = \frac{2R_s}{W} \text{ R/m}$$

$$G = \frac{\omega \epsilon''}{V_0^2} \int_S |\bar{E}|^2 ds = \frac{\omega \epsilon''}{V_0^2} \int_{x=0}^W \int_{y=0}^d \left( \frac{-V_0}{d} \right)^2 dx dy = \frac{\omega \epsilon'' W}{d} \text{ s/m}$$

These results agree with those in Table 2.1

2.6

Assume  $E_z = H_z = 0$ ,  $\partial/\partial x = \partial/\partial y = 0$ .

Then Maxwell's curl equations reduce to,

$$-\frac{\partial E_y}{\partial z} = -j\omega\mu H_x \quad (1) \qquad -\frac{\partial H_y}{\partial z} = j\omega\epsilon E_x \quad (3)$$

$$\frac{\partial E_x}{\partial z} = -j\omega\mu H_y \quad (2) \qquad \frac{\partial H_x}{\partial z} = j\omega\epsilon E_y \quad (4)$$

Since  $E_x = 0$  at  $y=0$  and  $y=d$ , and  $\partial/\partial y = 0$ , we must have  $E_x \equiv 0$ . Then (3) implies  $H_y \equiv 0$ . So we have,

$$\frac{\partial E_y}{\partial z} = j\omega\mu H_x \qquad \frac{\partial H_x}{\partial z} = j\omega\epsilon E_y$$

Now let  $E_y = \frac{1}{d} V(z)$  and  $H_x = \frac{-1}{W} I(z)$ .

Then the voltage and current are,

$$V(z) = \int_{y=0}^d E_y dy \qquad I(z) = \int_{x=0}^W (\hat{y} \times \vec{H}) \cdot \hat{z} dx = - \int_{x=0}^W H_x dx$$

Then,

$$\left. \begin{aligned} \frac{\partial V}{\partial z} &= -j \frac{\omega\mu d}{W} I(z) \implies L = \frac{\mu d}{W} \\ \frac{\partial I(z)}{\partial z} &= j \frac{\omega\epsilon W}{d} V(z) \implies C = \frac{\epsilon W}{d} \end{aligned} \right\} \begin{array}{l} \text{agree with} \\ \text{Table 2.1} \end{array}$$

**2.7** Using KVL:

$$-V(z) + R \frac{\Delta z}{2} i(z) + L \frac{\Delta z}{2} \frac{\partial i(z)}{\partial t} + R \frac{\Delta z}{2} i(z+\Delta z) + L \frac{\Delta z}{2} \frac{\partial i(z+\Delta z)}{\partial t} + V(z+\Delta z) = 0$$

divide by  $\Delta z$  and let  $\Delta z \rightarrow 0$ :

$$\frac{\partial V(z)}{\partial z} = -R i(z) - L \frac{\partial i(z)}{\partial t} \quad \checkmark$$

Using KCL:

$$i(z) - \Delta z \left[ G + C \frac{\partial}{\partial t} \right] \left[ V(z) - \frac{\Delta z}{2} (R + L \frac{\partial}{\partial t}) i(z) \right] - i(z+\Delta z) = 0$$

divide by  $\Delta z$  and let  $\Delta z \rightarrow 0$ :

$$\frac{\partial i(z)}{\partial z} = -G V(z) - C \frac{\partial V(z)}{\partial t} \quad \checkmark$$

These results agree with (2.2a,b).

**2.8**  $Z_L = Z_L/Z_0 = 0.400 - j0.267$

From Smith chart,  $\Gamma_L = 0.461 \angle 215^\circ$

$$\text{SWR} = 2.71$$

$$\Gamma_{in} = 0.461 \angle 359^\circ \quad \checkmark$$

$$Z_{in} = 203 - j5.2 \Omega$$

**2.9**

$$\lambda_g = \lambda_0 / \sqrt{\epsilon_r} = \frac{300}{3000 \sqrt{2.56}} = 6.25 \text{ cm}$$

$$l = \frac{2.0 \text{ cm}}{6.25 \text{ cm}/\lambda_g} = 0.320 \lambda_g \quad \beta l = \frac{2\pi}{\lambda_g} (0.32 \lambda_g) = 115.2^\circ$$


Smith chart solution:  $Z_{in} = 18.98 - j20.55 \Omega \quad \checkmark$

$$\Gamma_{in} = 0.62 \angle 212^\circ \quad \checkmark$$

$$\Gamma_L = 0.62 \angle 83^\circ \quad \checkmark$$

$$\text{SWR} = 4.27 \quad \checkmark$$

These results were verified with the analytical formulas.

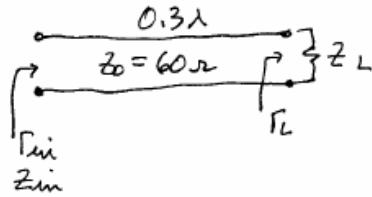**2.10**

$$\Gamma_L = 0.4/60^\circ = 0.2 + j 0.3464$$

$$Z_L = Z_0 \frac{1 + \Gamma_L}{1 - \Gamma_L} = 60 \frac{1.2 + j 0.3464}{0.8 - j 0.3464} = \frac{74.94/16.1^\circ}{0.8718/-23.4^\circ} = 66.3 + j 54.7 \Omega \quad \checkmark$$

$$\Gamma_{in} = \Gamma_L e^{-j\beta l} = 0.4/60-216^\circ = 0.4/156^\circ = 0.4/204^\circ \quad \checkmark$$

$$Z_{in} = 26.6 - j 10.3 \Omega \quad \checkmark \quad (\text{Smith Chart})$$

**2.11**

$$C: Z_{oc} = -j/\omega C = -j 12.73 \Omega = -j Z_0 \cot \beta l \quad C = 5 \mu F$$

$$\tan \beta l = 100/12.73 \Rightarrow \beta l = 82.74^\circ \quad \checkmark$$

$$\lambda_0 = 0.12 \text{ m}, \beta = 2\pi\sqrt{\epsilon_r}/\lambda_0 = 3854^\circ/\text{m} \Rightarrow l = 2.147 \text{ cm} \quad \checkmark$$

$$L: Z_{oc} = j\omega L = +j 78.5 \Omega = -j Z_0 \cot \beta l \quad L = 5 \mu H$$

$$\tan \beta l = -100/78.5 \Rightarrow \beta l = 128.1^\circ \Rightarrow l = 3.324 \text{ cm} \quad \checkmark$$

These results were verified with Serenade.

**2.12**

$$|\Gamma| = \frac{S-1}{S+1} = \frac{0.5}{2.5} = 0.2$$

$$|\Gamma| = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = \left| \frac{100 - Z_0}{100 + Z_0} \right| \quad (Z_0 \text{ real})$$

$$\text{So either, } \frac{100 - Z_0}{100 + Z_0} = 0.2 \Rightarrow Z_0 = 2 \cdot \frac{1 - \Gamma}{1 + \Gamma} = 100 \left( \frac{1.2}{1.2} \right) = 66.7 \Omega \quad \checkmark$$

or

$$\frac{100 - Z_0}{100 + Z_0} = -0.2 \Rightarrow Z_0 = 2 \cdot \frac{1 - \Gamma}{1 + \Gamma} = 100 \left( \frac{1.2}{-0.8} \right) = 150 \Omega \quad \checkmark$$

**2.13**

$$Z_{SC} = j Z_0 \tan \beta l \quad , \quad Z_{OC} = -j Z_0 \cot \beta l$$

$$Z_{SC} \cdot Z_{OC} = Z_0^2 \Rightarrow Z_0 = \sqrt{Z_{SC} Z_{OC}}$$

**2.14**

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{30 + j40}{130 + j40} = \frac{50 \angle 53^\circ}{136 \angle 17^\circ} = 0.367 \angle 36^\circ \quad \checkmark$$

$$P_{LOAD} = P_{INC} - P_{REF} = P_{INC} (1 - |\Gamma|^2) = 30 [1 - (0.367)^2] = 25.9 \text{ W} \quad \checkmark$$

**2.15**

$$RL = -20 \log |\Gamma|$$

$$SWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$|\Gamma| = 10^{RL/20}$$

$$|\Gamma| = \frac{SWR - 1}{SWR + 1}$$

SWR	$ \Gamma $	RL(dB)
1.00	0.0	$\infty$
1.01	.005	46.0
1.02	.01	40.0
1.05	.024	32.3
1.07	.0316	30.0
1.10	.0476	26.4
1.20	.091	20.8
1.22	.100	20.0
1.50	.200	14.0
1.92	.316	10.0
2.00	.333	9.5
2.50	.429	7.4

**2.16**

$$V_g = 15 \text{ V RMS}, Z_g = 75 \Omega, Z_0 = 75 \Omega, Z_L = 60 - j 40 \Omega, l = 0.7 \lambda.$$

a)  $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{-15 - j 40}{135 - j 40} = \frac{42.7 / -10.6^\circ}{140.8 / -16.5^\circ} = 0.303 / -94^\circ = -0.021 - j 0.302$

$$P_L = \left(\frac{V_g}{2}\right)^2 \frac{1}{Z_0} (1 - |\Gamma|^2) = 0.681 \text{ W } \checkmark$$

This method is actually based on  $P_L = P_{in} (1 - |\Gamma|^2)$ . It is the simplest method, but only applies to lossless lines.

b)  $Z_{in} = Z_0 \frac{Z_L + j Z_0 \tan \beta l}{Z_0 + j Z_L \tan \beta l} = 75 \frac{60 + j 190.8}{198.1 + j 184.7} = 75 \frac{200 / 72.5^\circ}{270.8 / 143^\circ}$   
 $= 55.4 / 29.5^\circ = 48.2 + j 27.3 \Omega$

$$P_L = \left| \frac{V_g}{Z_g + Z_{in}} \right|^2 \operatorname{Re}(Z_{in}) = \left| \frac{15}{123.2 + j 27.3} \right|^2 (48.2) = 0.681 \text{ W } \checkmark$$

This method computes  $P_L = P_{in} = |I_{in}|^2 R_{in}$ , and also applies only to lossless lines.

c)  $V(z) = V^+ (e^{-j\beta z} + \Gamma e^{j\beta z})$   
 $V_L = V(0) = V^+ (1 + \Gamma) \quad V^+ = \frac{V_g}{2} = 7.5 \text{ V}$   
 $= 7.5 (1 - 0.021 - j 0.302)$   
 $= 7.68 / -17^\circ$

$$P_L = \left| \frac{V_L}{Z_L} \right|^2 \operatorname{Re}(Z_L) = \left( \frac{7.68}{72.1} \right)^2 (60) = 0.681 \text{ W } \checkmark$$


This method computes  $P_L = |I_L|^2 R_L$ , and applies to lossy as well as lossless lines. Note the concept that  $V^+ = V_g/2$  requires a good understanding of the transmission line equations, and only applies here because  $Z_g = Z_0$ .

**2.17**

$$Z_L = jX$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{jX - Z_0}{jX + Z_0}$$

$$|\Gamma|^2 = \Gamma \Gamma^* = \frac{(jX - Z_0)}{(jX + Z_0)} \frac{(-jX - Z_0)}{(-jX + Z_0)} = \frac{X^2 - jZ_0 X + jZ_0 X + Z_0^2}{X^2 + Z_0^2} = 1 \quad \checkmark$$

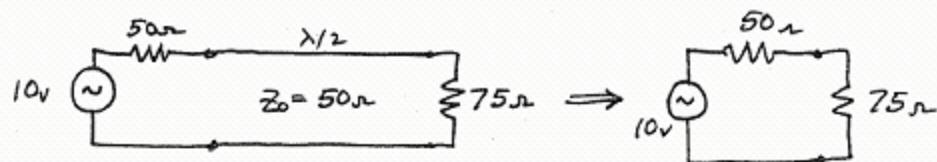**2.18**

$$\text{POWER DELIVERED BY SOURCE} = \frac{1}{2} \frac{(10)^2}{50+75} = 0.400 \text{ W} \quad \checkmark$$

$$\text{POWER DISSIPATED IN } 50\Omega \text{ LOAD} = \frac{1}{2} (50) \left( \frac{10}{50+75} \right)^2 = 0.160 \text{ W} \quad \checkmark$$

$$\text{POWER TRANSMITTED DOWN LINE} = \frac{1}{2} (75) \left( \frac{10}{50+75} \right)^2 = 0.240 \text{ W} \quad \checkmark$$

$$\text{INCIDENT POWER} = \frac{1}{2} (50) \left( \frac{10}{50+50} \right)^2 = 0.250 \text{ W} \quad \checkmark$$

$$\text{REFLECTED POWER} = P_{\text{INC}} |\Gamma|^2 = .250 \left| \frac{75-50}{75+50} \right|^2 = 0.010 \text{ W} \quad \checkmark$$

—  $P_{\text{INC}} - P_{\text{REF}} = .250 - .010 = 0.240 = P_{\text{TRANS}} \quad \checkmark$

$$P_{\text{DISS}} + P_{\text{TRANS}} = .160 + .240 = 0.400 = P_{\text{SOURCE}} \quad \checkmark$$

2.19

$$\Gamma = \frac{-20-j40}{180-j40} = \frac{44.7 \angle -116.6^\circ}{184.4 \angle -12.5^\circ} = 0.24 \angle -104^\circ = -0.058-j0.233 \checkmark$$

$$V_L = 10 \frac{80-j40}{180-j40} = 10 \frac{89.4 \angle -26^\circ}{184 \angle -12.5^\circ} = 4.86 \angle -13.5^\circ$$

$$V(z) = V^+ [e^{-j\beta z} + \Gamma e^{j\beta z}] \quad V^+ = 10 \frac{100}{100+100} = 5V \quad \checkmark$$


So  $V(z) = 5 [e^{-j\beta z} + \Gamma e^{j\beta z}]$

$$V_{MAX} = 5(1+|\Gamma|) = 5(1.24) = 6.2 \text{ at } z = -0.355\lambda$$

$$V_{MIN} = 5(1-|\Gamma|) = 5(.76) = 3.8 \text{ at } z = -0.105\lambda$$

These results repeat every  $\lambda/2$ .

$|V(z)|$  is plotted below:

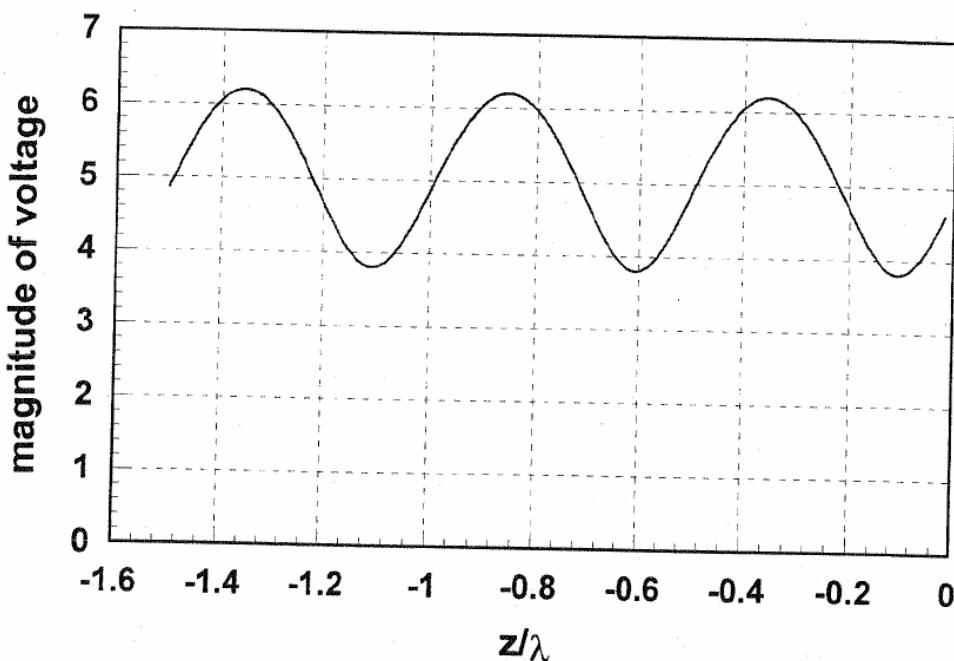


**2.20**

$$Z_0 = 50 \Omega, Z_L = 60 + j50 \Omega, \lambda = 0.4\lambda$$

From Smith chart, ( $Z_L = 1.2 + j1.0$ )

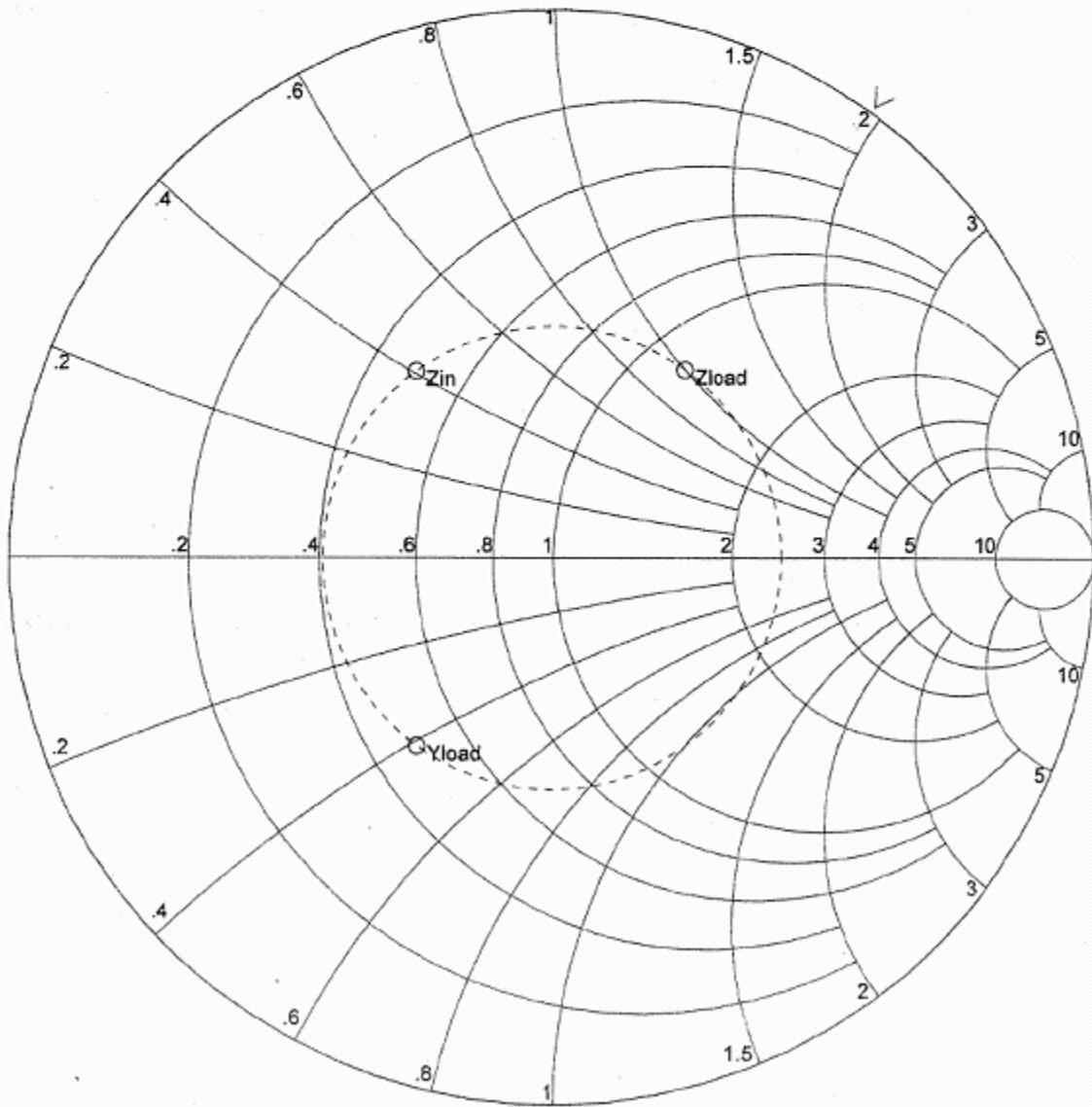- a) SWR = 2.46 ✓
- b)  $\Gamma = 0.422 \angle 54^\circ$  ✓
- c)  $Y_L = (1.492 - j.410)/50 = 9.84 - j8.2 \text{ mS}$  ✓
- d)  $Z_{in} = 24.5 + j20.3 \Omega$
- e)  $\lambda_{min} = 0.325\lambda$
- f)  $\lambda_{max} = 0.075\lambda$



**2.21**

- a)  $\ell = 0$  or  $\ell = 0.5\lambda$  ✓
- b)  $\ell = 0.25\lambda$  ✓
- c)  $\ell = 0.125\lambda$  ✓
- d)  $\ell = 0.406\lambda$  ✓
- e)  $\ell = 0.021\lambda$  ✓

These results check  
with  $Z_{in} = jZ_0 \tan \beta l$ .

**2.22**

- a)  $\ell = 0.25\lambda$  ✓
- b)  $\ell = 0\lambda$  or  $0.5\lambda$  ✓
- c)  $\ell = 0.375\lambda$  ✓
- d)  $\ell = 0.656\lambda - 0.5\lambda = 0.156\lambda$  ✓
- e)  $\ell = 0.271\lambda$  ✓

(add  $\lambda/4$  to results of P.2.22)

(also check with  
 $Z_{in} = -jZ_0 \cot \beta l$ )

**2.23**

$\lambda = 4.2 \text{ cm}$ . From the Smith chart,  $l_{min} = .9/4.2 = 0.214\lambda$   
from the load, so  $Z_L = 2-j.9 \Rightarrow \underline{\underline{Z_L = 100-j45 \Omega}}$  ✓

Analytically, using (2.58)-(2.60),

$$\Gamma = |\Gamma| e^{j\theta}, \quad |\Gamma| = \frac{2.5-j}{2.5+j} = 0.428$$

$$\theta = \pi + 2\beta l_{min} = 180 + 2(360)(.214) = -26^\circ \quad \checkmark$$

Then,


$$Z_L = \frac{1+0.428 \angle -26^\circ}{1-0.428 \angle -26^\circ} (50) = 50 \frac{1.4 \angle -7.7^\circ}{0.643 \angle 17^\circ} = 109 \angle -25^\circ$$

$$= \underline{\underline{99-j46 \Omega}}$$

**2.24**

$$Z_L = \sqrt{40(75)} = 54.77 \Omega$$

The VSWR is plotted vs  $f/f_0$  below:

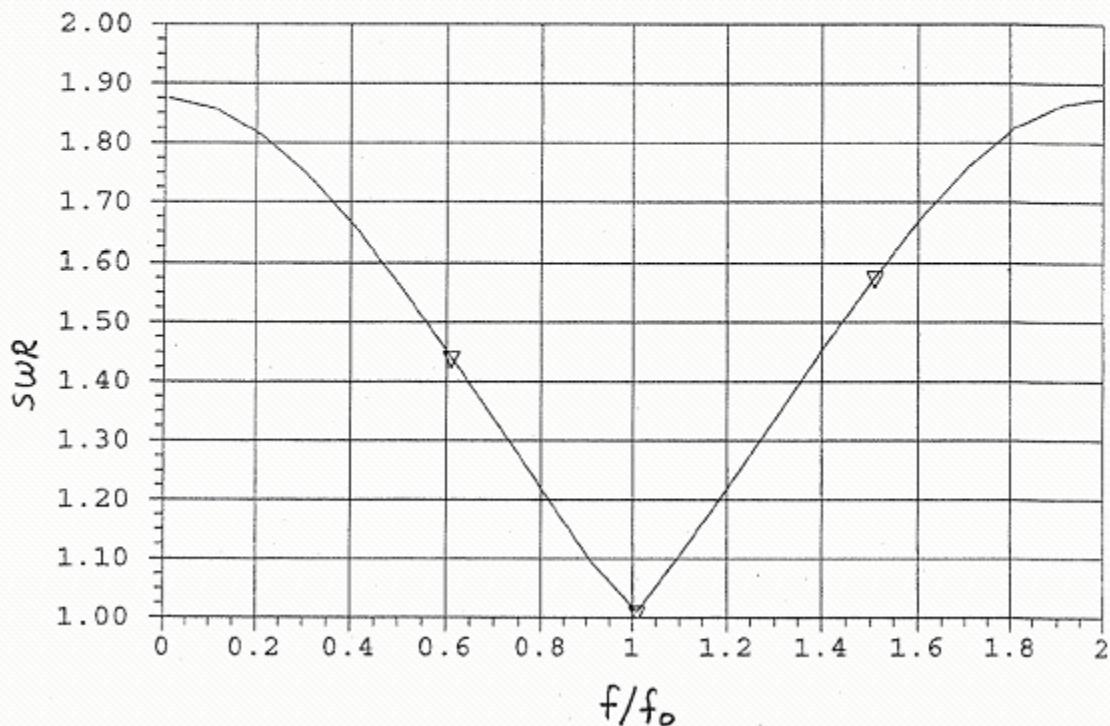

**2.25**

On the  $\lambda/4$  transformer, the voltage can be expressed as,

$$V(z) = V^+ e^{-j\beta z} + \Gamma V^- e^{j\beta z}, \quad \Gamma = \frac{R_L - \sqrt{Z_0 R_L}}{R_L + \sqrt{Z_0 R_L}}$$

$$\text{at } z = -l, \quad V(-l) = V^i = V^+ [e^{j\beta l} + \Gamma e^{-j\beta l}]$$

$$V^+ = \frac{V^i}{[e^{j\beta l} + \Gamma e^{-j\beta l}]} \quad , \quad V^- = \Gamma V^+$$

(assuming  $V^i$  with a phase reference at  $z = -l$ .)

2.26

From (2.70),

$$V_o^+ = V_g \frac{Z_{in}}{Z_{in} + Z_g} \frac{1}{(e^{j\beta l} + \Gamma_x e^{-j\beta l})}$$

From (2.67),

$$Z_{in} = Z_0 \frac{1 + \Gamma_x e^{-2j\beta l}}{1 - \Gamma_x e^{-2j\beta l}}$$

Then,

$$\begin{aligned} \frac{Z_{in}}{Z_{in} + Z_g} &= \frac{Z_0(1 + \Gamma_x e^{-2j\beta l})}{Z_0(1 + \Gamma_x e^{-2j\beta l}) + Z_g(1 - \Gamma_x e^{-2j\beta l})} \\ &= \frac{Z_0(e^{j\beta l} + \Gamma_x e^{-j\beta l}) e^{j\beta l}}{(Z_0 + Z_g) + \Gamma_x(Z_0 - Z_g) e^{-2j\beta l}} \\ &= \frac{Z_0(e^{j\beta l} + \Gamma_x e^{-j\beta l}) e^{j\beta l}}{(Z_0 + Z_g) \left[ 1 + \Gamma_x \frac{Z_0 - Z_g}{Z_0 + Z_g} e^{-2j\beta l} \right]} \end{aligned}$$

Thus,

$$V_o^+ = V_g \frac{Z_0 e^{-j\beta l}}{(Z_0 + Z_g)(1 - \Gamma_x \Gamma_g e^{-2j\beta l})}, \text{ since } \Gamma_g = \frac{Z_g - Z_0}{Z_g + Z_0}.$$

2.27

$$\frac{\partial \alpha_c}{\partial a} = \frac{R_s}{2\eta} \left[ \frac{1}{a} \left( \frac{1}{\ln b/a} \right)^2 \left( \frac{1}{a} + \frac{1}{b} \right) + \frac{1}{\ln b/a} \left( -\frac{1}{a^2} \right) \right] = 0$$

$$a \left( \frac{1}{a} + \frac{1}{b} \right) = \ln b/a$$

$$(1 + b/a) = b/a \ln b/a$$

If  $x = b/a$ , then  $1 + x = x \ln x$ .

(If  $\frac{\partial \alpha_c}{\partial b}$  is taken, the same result is obtained if  $x = a/b$ )

Now solve this equation for  $x$ :

Using interval-halving method:

$x$	$x \ln x - x - 1$
1	-2.0
2	-1.6
3	-0.704
4	.545
3.5	-0.115
3.6	.011
3.55	-0.052
→ 3.59	-0.01

For  $x = \frac{b}{a} = 3.59$ ,

$$Z_0 = \frac{\eta}{2\pi} \ln \frac{b}{a} = \frac{377}{\sqrt{\epsilon_r}} \ln(3.59) = \frac{76.7}{\sqrt{\epsilon_r}} \approx 77 \Omega \text{ for } \epsilon_r = 1.$$


Thus, for an air dielectric, minimum attenuation occurs for a characteristic impedance near  $77 \Omega$ .

**2.28**

The skin depth of copper at 10 GHz is  $\delta_s = 6.60 \times 10^{-7} \text{ m}$ .

Then, compute  $\frac{\alpha'c}{\alpha c} = 1 + \frac{2}{\pi} \tan^{-1} 1.4 \left( \frac{\Delta}{\delta_s} \right)^2$  (2.107)

The results are plotted below.

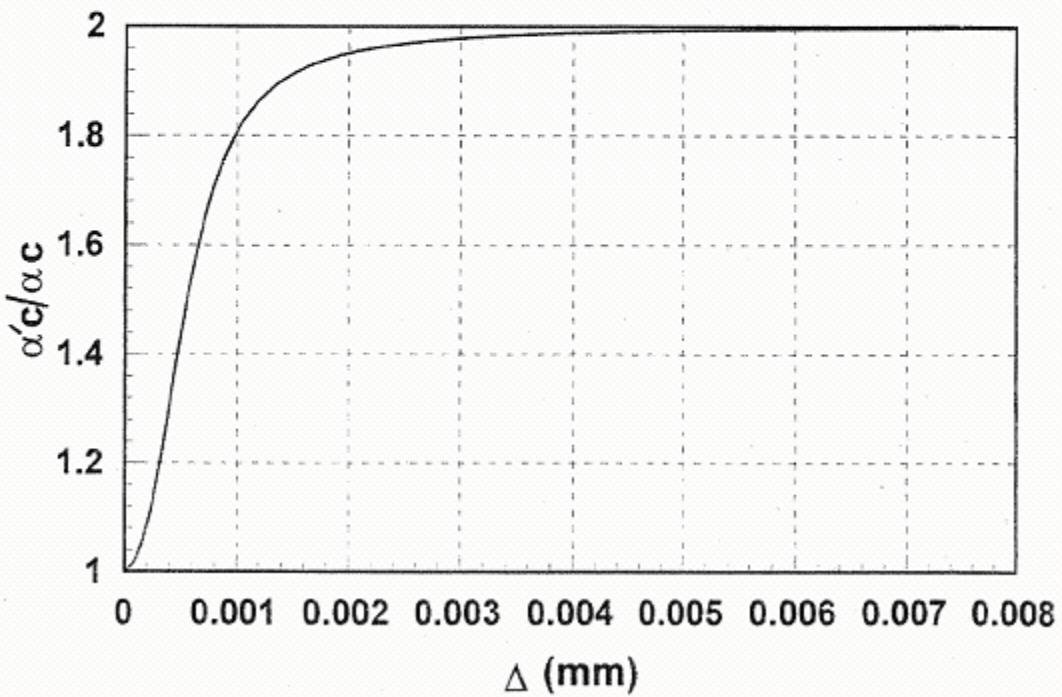

**2.29** Since the generator is matched to the line,

$$V_o^+ = \frac{V_g}{2} e^{-\gamma l} \quad (\text{phase reference at } z=0)$$

$$\alpha = 0.5 \text{ dB}/\lambda = 0.0576 \text{ nepers}/\lambda$$

$$\gamma l = (\alpha + j\beta)l = 0.1325 + j108^\circ \quad \checkmark$$

$$\text{Thus } |V_o^+| = \frac{10}{2} e^{-\alpha l} = 4.38 \text{ V.}$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{100 - 50}{100 + 50} = 0.333 \quad , \quad \Gamma(l) = \Gamma e^{-2\gamma l}$$

From (2.92) - (2.94) we then have,

$$\begin{aligned} P_{in} &= \frac{|V_o^+|^2}{2Z_0} [1 - |\Gamma(l)|^2] e^{2\alpha l} = \frac{(4.38)^2}{100} \left[ e^{2(0.1325)} - (0.333)^2 e^{-2(0.1325)} \right] \\ &= 0.2337 \text{ W} \quad (\text{power delivered to line}) \end{aligned}$$

$$P_L = \frac{|V_o^+|^2}{2Z_0} (1 - |\Gamma|^2) = \frac{(4.38)^2}{100} [1 - (0.333)^2] = 0.1706 \text{ W} \quad (\text{power to load})$$

$$P_{loss} = P_{in} - P_L = 0.2337 - 0.1706 = 0.0631 \text{ W}$$

The input impedance is,

$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l} = 50 \frac{100 + 50(0.845 + j2.19)}{50 + 100(0.845 + j2.19)} = 32.5 - j12.4 \Omega$$

The input current is,

$$I_{in} = \frac{V_g}{R_g + Z_{in}} = \frac{10}{82.5 - j12.4} = 0.1199 / 8.5^\circ \text{ A}$$

The generator power is,

$$P_s = \frac{1}{2} V_g |I_{in}| = 5(0.1199) = 0.600 \text{ W}$$

Power lost in  $R_g$  is,


$$P_{Rg} = \frac{1}{2} |I_{in}|^2 R_g = \frac{1}{2} (0.1199)^2 (50) = 0.3594 \text{ W}$$

CHECK:

$$P_L + P_{loss} + P_{Rg} = 0.1706 + 0.0631 + 0.3594 = 0.5931 \text{ W} \approx P_s \quad \checkmark$$

$$P_{in} + P_{Rg} = 0.2337 + 0.3594 = 0.5931 \text{ W} \approx P_s \quad \checkmark$$

2.30

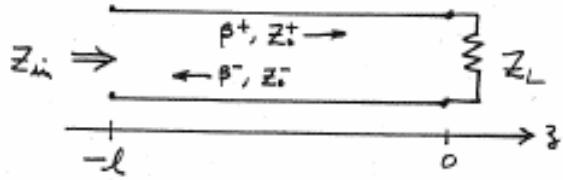

$$V(z) = V_0^+ e^{-j\beta^+ z} + V_0^- e^{j\beta^- z}$$

$$I(z) = \frac{V_0^+}{Z_0^+} e^{-j\beta^+ z} - \frac{V_0^-}{Z_0^-} e^{j\beta^- z}$$

at  $z=0$  (load),  $V(0) = V_0^+ + V_0^-$

$$I(0) = \frac{V_0^+}{Z_0^+} - \frac{V_0^-}{Z_0^-}$$

$$Z_L = \frac{V(0)}{I(0)} = \frac{V_0^+ + V_0^-}{V_0^+/Z_0^+ - V_0^-/Z_0^-} = \frac{l + V_0^-/V_0^+}{\frac{1}{Z_0^+} - \frac{V_0^-}{V_0^+} \frac{1}{Z_0^-}}$$

as usual, let  $\Gamma(0) = V_0^-/V_0^+$ . Then,

$$Z_L \left( \frac{1}{Z_0^+} - \Gamma \frac{1}{Z_0^-} \right) = 1 + \Gamma$$

$$\frac{Z_L}{Z_0^+} - 1 = \Gamma \left( 1 + \frac{Z_L}{Z_0^-} \right)$$

$$\Gamma = \Gamma(0) = \frac{Z_L - Z_0^-}{Z_L + Z_0^+} \quad (\text{at load})$$

The input impedance is,

$$Z_{in} = \frac{V(-l)}{I(-l)} = \frac{V_0^+ [e^{j\beta^+ l} + \Gamma e^{-j\beta^- l}]}{V_0^+ [\frac{1}{Z_0^+} e^{j\beta^+ l} - \Gamma \frac{1}{Z_0^-} e^{-j\beta^- l}]}$$

$$= \frac{(Z_L + Z_0^+) e^{j\beta^+ l} + (Z_L - Z_0^-) e^{-j\beta^- l}}{\frac{1}{Z_0^+} (Z_L + Z_0^+) e^{j\beta^+ l} - \frac{1}{Z_0^-} (Z_L - Z_0^-) e^{-j\beta^- l}}$$

This result does not simplify much further. From (2.42),  
 $\Gamma(-l) = \Gamma(0) e^{j(\beta^- + \beta^+) l}$  (reflection coefficient at the input)

**2.31**

The incident wave amplitude is  $v_i^+ = 10 \frac{50}{25+50} = 6.67 \text{ v}$   
 The reflection coefficients are ,

$$\Gamma_L = \frac{100-50}{100+50} = 0.333, \quad \Gamma_g = \frac{25-50}{25+50} = -0.333$$

$$v_i^- = \Gamma_L v_i^+ = 2.22 \text{ v}$$


$$v_2^+ = v_i^- \Gamma_g = -0.740 \text{ v}$$

$$v_2^- = v_2^+ \Gamma_L = -0.246 \text{ v}$$

at  $z = l/2$  and  $t = 3l/v_p$ ,

$$v_T = 6.67 + 2.22 - 0.740$$

$$= \underline{8.15 \text{ v}}$$

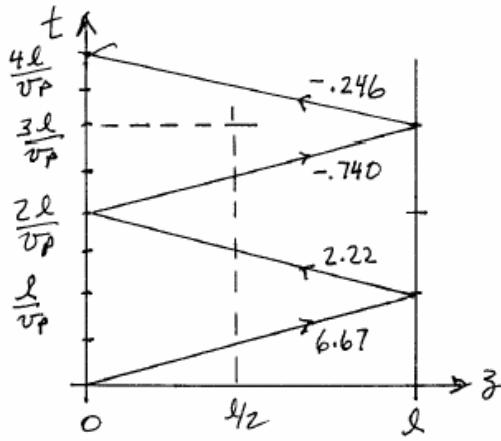

## Chapter 3

### 3.1

#### Variation on coax:

#1.



Square Coax (actually used in micromachined circuits). Easier to fabricate in micromachined form, using deposition and vias. TEM mode, so dispersion is low. Losses can be low if dielectric loss is small and metallization is good. Higher order modes will exist above cutoff frequency.

#2.



coax with two dielectric cores. Will not be strictly TEM, thus slightly dispersive. May also allow control of  $Z_0$  without changing  $a, b$ , possibly for use as  $\lambda/4$  matching section without discontinuity in diameters. More expensive than standard coax.

#### Variation on microstrip:

#1

~~AIR~~ air-filled microstrip may be supported with foam spacers. No dielectric loss, light weight, pure TEM mode, low dispersion, fewer higher order modes. Lower cost.

#2



covered microstrip - provides physical protection of metallization. More expensive, higher dielectric loss, heavier. These drawbacks would be minimized if the top layer was very thin.

**3.2** Let  $k_c^2 = k^2 - \beta^2$

$H_x$ : multiply (3.3a) by  $\omega\epsilon$ , multiply (3.4b) by  $\beta$ , and add:

$$\omega\epsilon \frac{\partial E_3}{\partial y} - j\beta^2 H_x - \beta \frac{\partial H_3}{\partial x} = -j\omega^2 \mu\epsilon H_x$$

$$H_x = \frac{j}{k_c^2} \left[ \omega\epsilon \frac{\partial E_3}{\partial y} - \beta \frac{\partial H_3}{\partial x} \right] \checkmark$$

$H_y$ : multiply (3.3b) by  $-\omega\epsilon$ , multiply (3.4a) by  $\beta$ , and add:

$$\omega\epsilon \frac{\partial E_3}{\partial x} + \beta \frac{\partial H_3}{\partial y} + j\beta^2 H_y = j\omega^2 \mu\epsilon H_y$$

$$H_y = \frac{-j}{k_c^2} \left[ \omega\epsilon \frac{\partial E_3}{\partial x} + \beta \frac{\partial H_3}{\partial y} \right] \checkmark$$

$E_x$ : multiply (3.3b) by  $-\beta$ , multiply (3.4a) by  $\omega\mu$ , and add:

$$j\beta^2 E_x + \beta \frac{\partial E_3}{\partial x} + \omega\mu \frac{\partial H_3}{\partial y} = j\omega^2 \mu\epsilon E_x$$

$$E_x = \frac{-j}{k_c^2} \left[ \beta \frac{\partial E_3}{\partial x} + \omega\mu \frac{\partial H_3}{\partial y} \right] \checkmark$$

$E_y$ : multiply (3.3a) by  $\beta$ , multiply (3.4b) by  $\omega\mu$ , and add:

$$\beta \frac{\partial E_3}{\partial y} + j\beta^2 E_y - \omega\mu \frac{\partial H_3}{\partial x} = j\omega^2 \mu\epsilon E_y$$

$$E_y = \frac{-j}{k_c^2} \left[ \beta \frac{\partial E_3}{\partial y} - \omega\mu \frac{\partial H_3}{\partial x} \right] \checkmark$$

**3.3**

From (3.66) - (3.67),

$$H_3 = B_n \cos \frac{n\pi y}{d} e^{-j\beta z}$$

$$H_y = \frac{j\beta}{k_c} B_n \sin \frac{n\pi y}{d} e^{-j\beta z}$$

From (3.71),

$$P_o = \frac{\omega\mu d W \beta}{4 k_c^2} / B_n |^2 \quad \text{for } n > 0, \beta \text{ real.}$$

From (2.97), the power lost in both plates is,

$$P_L = 2 \left( \frac{R_s}{2} \right) \int |H_t|^2 ds = R_s \int_{z=0}^1 \int_{x=0}^W [ |H_y(y=0)|^2 + |H_z(y=0)|^2 ] dx dz \\ = R_s W |B_n|^2$$

Then,  $\alpha_c = \frac{P_L}{2 P_0} = \frac{2 R_s k_c^2}{k d \eta \beta}$ . (agrees with (3.72)) ✓

**3.4** From Appendix I,  $a = 1.07 \text{ cm}$ ,  $b = 0.43 \text{ cm}$ .

$$\left. \begin{array}{l} f_{c10} = \frac{C}{2a} = 14.02 \text{ GHz} \\ f_{c20} = \frac{C}{a} = 28.04 \text{ GHz} \\ f_{c01} = \frac{C}{2b} = 34.88 \text{ GHz} \end{array} \right\} \text{LOWEST ORDER MODES}$$

The fractional BW from  $f_{c10}$  to  $f_{c20}$  is  $\frac{(28-14)}{(28+14)/2} = 67\%$

The fractional BW of the recommended operating range of 18.0-26.5 GHz is  $\frac{(26.5-18.0)}{(26.5+18.0)/2} = 38\%$  (reduction of 29%)

**3.5**

K-band guide,  $\ell = 10 \text{ cm}$ ,  $\epsilon_r = 2.55$ ,  $\tan \delta = 0.0015$   
 copper,  $f = 15 \text{ GHz}$ .  $a = 1.07 \text{ cm}$ ,  $b = 0.43 \text{ cm}$ ,  $\sigma = 5.8 \times 10^7$

$$f_{c_{10}} = \frac{c}{2a\sqrt{\epsilon_r}} = 8.78 \text{ GHz} \checkmark, f_{c_{20}} = 17.6 \text{ GHz} \text{ (one prop. mode)}$$

$$k = \sqrt{\epsilon_r} k_0 = 501.67 \text{ m}^{-1}$$

$$R_s = \sqrt{\frac{\omega_0}{2\sigma}} = 0.03195 \Omega$$

$$\beta_{10} = \sqrt{k^2 - (\pi/a)^2} = 406.78 \text{ m}^{-1} \checkmark$$

$$\eta = 377/\sqrt{\epsilon_r} = 236.1 \Omega$$

$$\text{From (3.29)} \quad \alpha_d = \frac{k^2 \tan \delta}{2\beta} = 0.464 \text{ nph/m} = 4.03 \text{ dB/m} \checkmark$$

$$\text{From (3.96)} \quad \alpha_c = \frac{R_s}{a^3 b \beta k \eta} (2b\pi^2 + a^3 k^2) = 0.0495 \text{ nph/m} = 0.430 \text{ dB/m} \checkmark$$

$$\text{Loss} = (\alpha_c + \alpha_d) \ell = 0.446 \text{ dB}$$

$$\Delta\phi = \beta \ell = 2330.7^\circ$$

**3.6**

In the section of guide of width  $a/2$ , the  $TE_{10}$  mode is below cutoff (evanescent), with an attenuation constant  $\alpha$ :

$$k = \frac{2\pi (12,000)}{300} = 251.3 \text{ m}^{-1} \checkmark$$

$$\alpha = \sqrt{\left(\frac{\pi}{a/2}\right)^2 - k^2} = \sqrt{\left(\frac{2\pi}{0.02286}\right)^2 - (251.3)^2} = 111.3 \text{ naper/m} \checkmark$$

To obtain 100 dB attenuation (ignoring reflections),

$$-100 \text{ dB} = 20 \log e^{-\alpha \ell}$$

$$10^{-5} = e^{-\alpha \ell}$$

$$\ell = \frac{11.5}{111.3} = 0.103 \text{ m} = \underline{10.3 \text{ cm}} \checkmark$$

**3.7** The TE<sub>10</sub> H-fields from (3.89) are:

$$H_x = \frac{j\beta a A}{\pi} \sin \frac{\pi x}{a} e^{-j\beta z}$$

$$H_y = 0$$

$$H_z = A \cos \frac{\pi x}{a} e^{-j\beta z}$$

$\bar{J}_s = \hat{n} \times \bar{H}$ , so the surface currents are,

$$\text{ON BOTTOM WALL: } \hat{n} = \hat{y}; \quad \bar{J}_s = -\hat{z} \frac{j\beta a A}{\pi} \sin \frac{\pi x}{a} e^{j\beta z} + \hat{x} A \cos \frac{\pi x}{a} e^{-j\beta z} \quad \checkmark$$

$$\text{ON TOP WALL: } \hat{n} = -\hat{y}; \quad \bar{J}_s = \hat{z} \frac{j\beta a A}{\pi} \sin \frac{\pi x}{a} e^{-j\beta z} - \hat{x} A \cos \frac{\pi x}{a} e^{j\beta z} \quad \checkmark$$

$$\text{ON LEFT SIDE WALL: } \hat{n} = \hat{x}, x=0; \quad \bar{J}_s = -\hat{y} A e^{j\beta z}$$

$$\text{ON RIGHT SIDE WALL: } \hat{n} = -\hat{x}, x=a; \quad \bar{J}_s = -\hat{y} A e^{-j\beta z}$$

Note that the top and bottom currents are the negative of each other.

Along the centerline of the top or bottom (broad) walls,  $x=a/2$ , so the surface currents can be reduced to,

$$\bar{J}_s = \pm \hat{z} \frac{j\beta a A}{\pi} e^{-j\beta z},$$

which shows that current flow is only in the longitudinal direction. Thus a narrow longitudinal slot will not break any current lines, and will have a negligible effect on the operation of the waveguide.

3.8

From (3.101),

$$\begin{aligned}\bar{E} \times \bar{H}^* \cdot \hat{z} &= E_x H_y^* - E_y H_x^* \\ &= \frac{\omega \epsilon \beta m^2 \pi^2}{a^2 k_c^4} |B|^2 \cos^2 \frac{m\pi x}{a} \sin^2 \frac{n\pi y}{b} \\ &\quad + \frac{\omega \epsilon \beta n^2 \pi^2}{b^2 k_c^4} |B|^2 \sin^2 \frac{m\pi x}{a} \cos^2 \frac{n\pi y}{b}\end{aligned}$$

So the power flow down the guide is,

$$P_0 = \frac{1}{2} \int_{x=0}^a \int_{y=0}^b \bar{E} \times \bar{H}^* \cdot \hat{z} dx dy = \frac{\omega \epsilon \beta \pi^2 |B|^2}{2 k_c^4} \left( \frac{m^2}{a^2} + \frac{n^2}{b^2} \right) \frac{ab}{4} = \frac{\omega \epsilon \beta ab}{8 k_c^2} |B|^2$$

The power loss in the walls is,

$$\begin{aligned}P_L &= \frac{R_s}{2} \int_t^s |\bar{H}_t|^2 ds = R_s \left\{ \int_{x=0}^a |H_x(y=0)|^2 dx + \int_{y=0}^b |H_y(x=0)|^2 dy \right\} \\ &= R_s \left\{ \frac{\omega^2 \epsilon^2 n^2 \pi^2}{b^2 k_c^4} |B|^2 \frac{a}{2} + \frac{\omega^2 \epsilon^2 m^2 \pi^2}{a^2 k_c^4} |B|^2 \frac{b}{2} \right\} \\ &= R_s \frac{\omega^2 \epsilon^2 \pi^2}{2 k_c^4} |B|^2 \left( \frac{n^2 a}{b^2} + \frac{m^2 b}{a^2} \right)\end{aligned}$$

So the attenuation is,

$$\begin{aligned}\alpha_c &= \frac{P_L}{2P_0} = \frac{R_s \omega^2 \epsilon^2 \pi^2 4 k_c^2}{2 k_c^4 \omega \epsilon \beta a b} \left( \frac{n^2 a}{b^2} + \frac{m^2 b}{a^2} \right) \\ &= \frac{2 R_s k \pi^2}{k_c^2 \beta \eta} \left( \frac{n^2}{b^3} + \frac{m^2}{a^3} \right) \text{ nepau/m } \checkmark\end{aligned}$$

**3.9**

From (3.109), the propagation constant is a solution of,

$$k_a \tan k_d t + k_d \tan k_a (a-t) = 0,$$

where

$$\beta = \sqrt{k_0^2 - k_a^2} = \sqrt{\epsilon_r k_0^2 - k_d^2} \quad (3.106)$$

Since  $\beta=0$  at cutoff, we have that  $k_a=k_0$ , and  $k_d=\sqrt{\epsilon_r} k_0$ . Thus we must find the root of the following equation:

$$f(k_0) = k_0 \tan \sqrt{\epsilon_r} k_0 t + \sqrt{\epsilon_r} k_0 \tan k_0 t = 0 \quad (\text{since } t=a/2)$$

We know that  $k_c=k_0$  must be between  $k_c$  of the empty guide, and  $k_c$  for the completely filled guide:

$$k_c(\text{EMPTY}) = \frac{\pi}{a} = 137 \text{ m}^{-1}$$

$$k_c(\text{ILLED}) = \frac{\pi}{\sqrt{\epsilon_r} a} = 92 \text{ m}^{-1}$$

$k_0$	$f(k_0)$
95	-1366
100	-362
105	-44
110	171
106	2.3
105.9	-2.25
✓ → 105.95	.017

This result is accurate to at least four figures, and agrees with a result given in the Waveguide Handbook.

The cutoff frequency is,

$$f_c = \frac{k_c c}{2\pi} = 5.06 \text{ GHz}$$

**3.10**

The lowest order mode will have an  $H_3$  component which is even in  $x$ , and no variation in  $y$ . Thus,  $H_3$  can be written as,

$$h_3(x, y) = \begin{cases} A \cos k_d x & \text{for } |x| < w/2 \quad (k_c = k_d) \\ B e^{-k_a |x|} & \text{for } |x| > w/2 \quad (k_c = j k_a) \end{cases}$$

where  $k_d$  and  $k_a$  are the cutoff wavenumbers in the dielectric and air regions, respectively, satisfying

$$\beta = \sqrt{\epsilon_r k_0^2 - k_d^2} = \sqrt{k_0^2 - k_a^2} \quad (\text{phase matching})$$

Next, we need  $e_y$ , from (3.19d):

$$e_y(x, y) = \frac{j \omega u}{k_0^2} \frac{\partial h_3}{\partial x} = \begin{cases} -j \frac{\omega u A}{k_d} \sin k_d x & \text{for } |x| < w/2 \\ \frac{j \omega u B}{k_a} e^{-k_a x} & \text{for } x > w/2 \end{cases}$$

Matching  $h_3$  and  $e_y$  at  $x=w/2$  gives,

$$A \cos k_d w/2 = B e^{-k_a w/2}$$

$$-\frac{A}{k_d} \sin k_d w/2 = \frac{B}{k_a} e^{-k_a w/2}$$

Setting the determinant of these equations to zero gives,

$$k_a \tan k_d w/2 + k_d = 0.$$

A TEM mode cannot exist by itself because of the impossibility of phase matching at  $x=w/2$ . (For a TEM mode,  $\beta=k$  in both regions, which is not possible.)

3.11

Maxwell's curl equations are,

$$\nabla \times \vec{E} = -j\omega \mu \vec{H} \quad , \quad \nabla \times \vec{H} = j\omega \epsilon \vec{E}$$

The  $\rho$  and  $\phi$  components in cylindrical form are,

$$\frac{1}{\rho} \frac{\partial E_3}{\partial \phi} - \frac{\partial E_\phi}{\partial z} = -j\omega \mu H_\rho \quad \frac{1}{\rho} \frac{\partial H_3}{\partial \phi} - \frac{\partial H_\phi}{\partial z} = j\omega \epsilon E_\rho$$

$$\frac{\partial E_\rho}{\partial z} - \frac{\partial E_3}{\partial \rho} = -j\omega \mu H_\phi \quad \frac{\partial H_\rho}{\partial z} - \frac{\partial H_3}{\partial \rho} = j\omega \epsilon E_\phi$$

Now assume  $\vec{E}(\rho, \phi, z) = \vec{e}(\rho, \phi) e^{-j\beta z}$

$$\vec{H}(\rho, \phi, z) = \vec{h}(\rho, \phi) e^{-j\beta z}$$

Then  $\partial/\partial z \rightarrow -j\beta$ , and the above equations reduce to:

$$\frac{1}{\rho} \frac{\partial E_3}{\partial \phi} + j\beta E_\phi = -j\omega \mu H_\rho \quad (1) \quad \frac{1}{\rho} \frac{\partial H_3}{\partial \phi} + j\beta H_\phi = j\omega \epsilon E_\rho \quad (3)$$

$$-j\beta E_\rho - \frac{\partial E_3}{\partial \rho} = -j\omega \mu H_\phi \quad (2) \quad -j\beta H_\rho - \frac{\partial H_3}{\partial \rho} = j\omega \epsilon E_\phi \quad (4)$$

Multiply (2) by  $-j\beta$ , multiply (3) by  $\omega \mu$ , and add:

$$j\beta^2 E_\rho + \beta \frac{\partial E_3}{\partial \rho} + \frac{\omega \mu}{\rho} \frac{\partial H_3}{\partial \phi} = j\omega^2 \mu \epsilon E_\rho$$

$$E_\rho = \frac{-j}{k_c^2} \left[ \beta \frac{\partial E_3}{\partial \rho} + \frac{\omega \mu}{\rho} \frac{\partial H_3}{\partial \phi} \right]$$

Multiply (1) by  $j\beta$ , multiply (4) by  $\omega \mu$ , and add:

$$\frac{\beta}{\rho} \frac{\partial E_3}{\partial \phi} + j\beta^2 E_\phi - \omega \mu \frac{\partial H_3}{\partial \rho} = j\omega^2 \mu \epsilon E_\phi$$

$$E_\phi = \frac{-j}{k_c^2} \left[ \frac{\beta}{\rho} \frac{\partial E_3}{\partial \phi} - \omega \mu \frac{\partial H_3}{\partial \rho} \right]$$

Multiply (1) by  $\omega \epsilon$ , multiply (4) by  $\beta$ , and add:

$$\frac{\omega \epsilon}{\rho} \frac{\partial E_3}{\partial \phi} - j\beta^2 H_\rho - \beta \frac{\partial H_3}{\partial \rho} = -j\omega^2 \mu \epsilon H_\rho$$

$$H_\rho = \frac{j}{k_c^2} \left[ \frac{\omega \epsilon}{\rho} \frac{\partial E_3}{\partial \phi} - \beta \frac{\partial H_3}{\partial \rho} \right]$$

$$\omega \epsilon \frac{\partial E_2}{\partial \rho} + \frac{\beta}{\rho} \frac{\partial H_2}{\partial \phi} + j\beta^2 H_\phi = j\omega^2 \mu \epsilon H_\phi$$

$$H_\phi = \frac{-j}{k_c} \left[ \omega \epsilon \frac{\partial E_2}{\partial \rho} + \frac{\beta}{\rho} \frac{\partial H_2}{\partial \phi} \right]$$

$$\text{with } k_c^2 = k^2 - \beta^2.$$

These results agree with those of (3.110). ✓

**3.12**

Let  $A=1, B=0$  in (3.141). Then the transverse fields are,

$$E_\rho = \frac{-j\beta n}{k_c} \sin n\phi J_n(k_c\rho) e^{-j\beta z}$$

$$E_\phi = \frac{-j\beta n}{k_c^2 \rho} \cos n\phi J_n(k_c\rho) e^{-j\beta z}$$

$$H_\rho = \frac{j\omega \epsilon n}{k_c^2 \rho} \cos n\phi J_n(k_c\rho) e^{-j\beta z}$$

$$H_\phi = -\frac{j\omega \epsilon}{k_c} \sin n\phi J_n(k_c\rho) e^{-j\beta z}$$

$$\bar{E} \times \bar{H}^* \cdot \hat{z} = E_\rho H_\phi^* - E_\phi H_\rho^*$$

The power flow down the guide is, for  $n > 0$ ,

$$\begin{aligned} P_0 &= \frac{1}{2} \int_{\rho=0}^a \int_{\phi=0}^{2\pi} \left[ \frac{\rho \omega \epsilon}{k_c^2} \sin^2 n\phi J_n'^2(k_c\rho) + \frac{\beta \omega \epsilon n^2}{k_c^4 \rho^2} \cos^2 n\phi J_n^2(k_c\rho) \right] \rho d\phi d\rho \\ &= \frac{\beta \omega \epsilon \pi}{2 k_c^2} \int_{\rho=0}^a \left[ J_n'^2(k_c\rho) + \frac{n^2}{k_c^2 \rho^2} J_n^2(k_c\rho) \right] \rho d\rho \quad \begin{matrix} \text{Let } x = k_c \rho \\ dx = k_c d\rho \\ k_c a = r_{nm} \end{matrix} \\ &= \frac{\beta \omega \epsilon \pi}{2 k_c^4} \int_{x=0}^{r_{nm}} \left[ J_n'^2(x) + \frac{n^2}{x^2} J_n^2(x) \right] x dx = \frac{\beta \omega \epsilon \pi}{4 k_c^4} r_{nm}^2 J_n'^2(r_{nm}) \quad (\text{SEE C.16}) \end{aligned}$$

The power lost in the conducting wall is,

$$\begin{aligned} P_L &= \frac{R_s}{2} \int_{\rho=a}^1 \int_{\phi=0}^{2\pi} |H_\phi(\rho=a)|^2 a d\phi dz = \frac{a R_s}{2} \frac{\omega^2 \epsilon^2}{k_c^2} J_n'^2(r_{nm}) \int_{\phi=0}^{2\pi} \sin^2 n\phi d\phi \\ &= \frac{a R_s \omega^2 \epsilon^2 \pi}{2 k_c^2} J_n'^2(r_{nm}) \end{aligned}$$

The attenuation is then,

$$\alpha_C = \frac{P_L}{2P_0} = \frac{a R_s \omega^2 \epsilon^2 \pi 4 k_c^4}{4 k_c^2 \beta \omega \epsilon r_{nm}^2} = \frac{a R_s \omega k_c^2}{\beta r_{nm}^2} = \frac{k R_s}{\beta \eta a} \text{ nepers/m. ✓}$$

3.13

$a = 0.4 \text{ cm}$ ,  $\epsilon_r = 1.50$ , Copper,  $\tan \delta = 0.0002$

$$\text{TE}_{11}: f_c = \frac{\rho_{11}' c}{2\pi a \sqrt{\epsilon_r}} = 17.94 \text{ GHz} \checkmark$$

$$\text{TM}_{01}: f_c = \frac{\rho_{01} c}{2\pi a \sqrt{\epsilon_r}} = 23.44 \text{ GHz} \checkmark$$

$$\text{TE}_{21}: f_c = \frac{\rho_{21}' c}{2\pi a \sqrt{\epsilon_r}} = 29.76 \text{ GHz} \checkmark$$

$$\text{TE}_{01}: f_c = \frac{\rho_{01}' c}{2\pi a \sqrt{\epsilon_r}} = 37.35 \text{ GHz.} \checkmark$$

$$\text{at } 20 \text{ GHz, } k_0 = 418.88 \text{ m}^{-1}, \beta = \sqrt{\epsilon_r k_0^2 - (\rho_{11}'/a)^2} = 226.63 \text{ m}^{-1} \checkmark$$

$$\alpha_d = \frac{\epsilon_r k_0^2 \tan \delta}{2\beta} = 0.116 \text{ nF/m} = 1.01 \text{ dB/m} \checkmark$$

$$R_s = 0.0369 \Omega \quad \alpha_c = \frac{R_s}{2k_0 \eta_0 \beta} \left( \frac{k^2}{k_c^2} + \frac{k^2}{\rho_{11}'^2 - 1} \right) = 0.083 \text{ nF/m} = 0.721 \text{ dB/m} \checkmark$$

**3.14**

From (3.153),  $\Phi(\rho, \phi) = \frac{V_0 \ln b/\rho}{\ln b/a}$

From (3.13) and Appendix,

$$\bar{E}(\rho, \phi) = -\nabla_t \Phi(\rho, \phi) = -\left(\hat{\rho} \frac{\partial \Phi}{\partial \rho} + \hat{\phi} \frac{1}{\rho} \frac{\partial \Phi}{\partial \phi}\right) = \frac{V_0 \hat{\rho}}{\rho \ln b/a}$$

Then,

$$\bar{E}(\rho, \phi, z) = \bar{E}(\rho, \phi) e^{j\beta z} = \frac{V_0 \hat{\rho} e^{j\beta z}}{\rho \ln b/a} \quad (4.155) \text{ of 1st Ed.}$$

From (3.18),

$$\bar{H}(\rho, \phi) = \frac{1}{\eta} \hat{z} \times \bar{E}(\rho, \phi) = \frac{V_0 \hat{\phi}}{\eta \rho \ln b/a}$$

Then,

$$\bar{H}(\rho, \phi, z) = \frac{V_0 \hat{\phi} e^{j\beta z}}{\eta \rho \ln b/a} \quad (4.157) \text{ of 1st Ed.}$$

The potential between the two conductors is,

$$V_{ab} = \int_{\rho=a}^b E_p(\rho, \phi, z) d\rho = V_0 e^{j\beta z} \quad (4.158) \text{ of 1st Ed.}$$

The current on the inner conductor is,

$$I_a = \int_{\phi=0}^{2\pi} H_\phi(a, \phi, z) a d\phi = \frac{2\pi V_0 e^{j\beta z}}{\eta \ln b/a} \quad (4.159) \text{ of 1st Ed.}$$

The characteristic impedance is,

$$Z_0 = \frac{V_{ab}}{I_a} = \frac{\eta \ln b/a}{2\pi} \quad (4.162) \text{ of 1st Ed.}$$

**3.15** The solution is similar to the TE mode case for the coax, but with  $e_z$  in place of  $h_z$ :

$$e_z(r, \phi) = (A \sin n\phi + B \cos n\phi) [C J_n(k_c r) + D Y_n(k_c r)]$$

Then the boundary condition that  $e_z = 0$  at  $r=a$  and at  $r=b$  yields two equations:

$$C J_n(k_c a) + D Y_n(k_c a) = 0$$

$$C J_n(k_c b) + D Y_n(k_c b) = 0$$

or,

$$J_n(k_c a) Y_n(k_c b) = J_n(k_c b) Y_n(k_c a)$$

For the  $TM_{01}$  mode,  $n=0$ . Let  $x = k_c a$ . Then for  $b=2a$ , we have that  $k_c b = 2x$ , and so the above equation can be written as,

$$f(x) = J_0(x) Y_0(2x) - J_0(2x) Y_0(x) = 0$$

We know that  $k_c$  should be greater than  $k_c$  for a circular waveguide of radius  $b$ , for which  $k_{c01} = P_{01}/b = 2.405/2a$ , which implies that  $x = 1.2$ . So we can begin the root search at  $x=1.2$ . Using a table of Bessel functions gives the following results in only a few minutes:

$x$	$J_0(x)$	$Y_0(x)$	$J_0(2x)$	$Y_0(2x)$	$f(x)$
1.2	.671	.228	.003	.510	.342
1.5	.512	.382	-.260	.377	.292
2.0	.224	.510	-.397	-.017	.198
3.1	-.292	.343	.202	-.248	.003
3.2	-.320	.307	.243	-.200	-.011

Linear interpolation between  $x=3.1$  and 3.2 gives a more accurate value for the root:

$$\begin{aligned} f(x) &\approx .003 + \frac{.003 - (-.011)}{3.1 - 3.2} (x - 3.1) \\ &\approx .437 - .14x = 0 \end{aligned}$$

$$x = \frac{.437}{.14} = \underline{\underline{3.12}} = \underline{\underline{k_c a}}$$

3.16

From (3.175),

$$\bar{E} \times \bar{H}^* \cdot \hat{z} = -E_y H_x^* = \begin{cases} \frac{\omega \mu_0 \beta |B|^2}{k_c^2} \sin^2 k_c x & \text{for } 0 \leq x \leq d \\ \frac{\omega \mu_0 \beta |B|^2}{h^2} \cos^2 k_c d e^{-2h(x-d)} & \text{for } d \leq x < \infty \end{cases}$$

The power flow is,

$$\begin{aligned} P_0 &= \frac{1}{2} \int_{x=0}^{\infty} \int_{y=0}^1 \bar{E} \times \bar{H}^* \cdot \hat{z} dy dx \\ &= \frac{\omega \mu_0 \beta |B|^2}{2 k_c^2} \int_{x=0}^d \sin^2 k_c x dx + \frac{\omega \mu_0 \beta |B|^2}{2 h^2} \cos^2 k_c d \int_{x=d}^{\infty} e^{-2h(x-d)} dx \\ &= \frac{\omega \mu_0 \beta |B|^2}{2} \left[ \frac{1}{k_c^2} \left( \frac{x}{2} - \frac{\sin 2k_c x}{4k_c} \right) \Big|_0^d + \frac{\cos^2 k_c d}{h^2} \left( \frac{e^{-2h(x-d)}}{-2h} \right) \Big|_d^{\infty} \right] \\ &= \frac{\omega \mu_0 \beta |B|^2}{2} \left[ \frac{1}{k_c^2} \left( \frac{d}{2} - \frac{\sin 2k_c d}{4k_c} \right) + \frac{\cos^2 k_c d}{2h^3} \right] \end{aligned}$$

The power loss is,

$$\begin{aligned} P_L &= \frac{R_s}{2} \int_S |\bar{H}_t|^2 ds = \frac{R_s}{2} \int_{y=0}^1 \int_{z=0}^1 \left[ |H_x(x=0)|^2 + |H_z(x=0)|^2 \right] dz dy \\ &= \frac{R_s}{2} |B|^2 \end{aligned}$$

So the attenuation is,

$$\begin{aligned} \alpha_c &= \frac{P_L}{2P_0} = \frac{2R_s}{4\omega\mu_0\beta \left[ \frac{1}{k_c^2} \left( \frac{d}{2} - \frac{\sin 2k_c d}{4k_c} \right) + \frac{\cos^2 k_c d}{2h^3} \right]} \\ &= \frac{R_s}{k_0 \mu_0 \beta \left[ \frac{d}{k_c^2} - \frac{\sin 2k_c d}{2k_c^3} + \frac{\cos^2 k_c d}{h^3} \right]} \quad \checkmark \end{aligned}$$

**3.17** Following the derivation in Section 3.6 for the TM surface waves of a dielectric slab:

$$k_c^2 = \mu_r k_0^2 - \beta^2 \quad \text{for } 0 \leq y \leq d$$

$$n^2 = \beta^2 - k_c^2 \quad \text{for } y > d$$

Then,

$$E_z(x, y) = \begin{cases} A \sin k_c y & \text{for } 0 \leq y \leq d \\ B e^{-hy} & \text{for } y > d \end{cases}$$

This form of  $E_z$  is selected to satisfy  $E_z = 0$  at  $y=0$ , and to have exponential decay for  $y \rightarrow \infty$  (radiation condition). Next, we need  $H_x$  ( $H_y = E_x = H_z = 0$ ): From (3.23a),

$$H_x = \frac{j\omega \epsilon_0}{k_c^2} \frac{\partial E_z}{\partial y} = \begin{cases} \frac{j\omega \epsilon_0}{k_c} A \cos k_c y & \text{for } 0 \leq y \leq d \\ \frac{j\omega \epsilon_0}{h} B e^{-hy} & \text{for } y > d \end{cases}$$

at  $y=d$ :

$$E_z \text{ continuous} \Rightarrow A \sin k_c d = B e^{-hd}$$

$$H_x \text{ continuous} \Rightarrow \frac{A}{k_c} \cos k_c d = \frac{B}{h} e^{-hd}$$

or,

$$h \cos k_c d = k_c \sin k_c d$$

$$h = k_c \tan k_c d \quad \checkmark$$

and,

$$h^2 + k_c^2 = (\mu_r - 1) k_0^2 \quad \checkmark$$

These two equations must be solved simultaneously to find  $h$  and  $k_c$ .

**3.18**

$$T M_{0m} \text{ mode. } H_z = 0 \quad E_z(p, \phi, z) = e_z(p, \phi) e^{j\beta z}$$

(No TEM mode can be supported by this line because of the impossibility of phase matching at  $p=b$ )

$$\left( \frac{\partial^2}{\partial p^2} + \frac{1}{p} \frac{\partial}{\partial p} + \frac{1}{p^2} \frac{\partial^2}{\partial \phi^2} + k_c^2 \right) e_z(p, \phi) = 0$$

$$\frac{\partial}{\partial \phi} e_z = 0 \text{ for } n=0 \text{ modes} \Rightarrow E_\phi = H_\phi = 0.$$

Thus,

$$e_z(p, \phi) = \begin{cases} A J_0(k_d p) + B Y_0(k_d p) & \text{for } a \leq p \leq b \\ C J_0(k_a p) + D Y_0(k_a p) & \text{for } b \leq p \leq c \end{cases}$$

$$\text{where } \beta^2 = \epsilon_r k_0^2 - k_d^2 = k_0^2 - k_a^2.$$

The boundary conditions are:

$$e_z = 0 \text{ at } p=a \text{ and } p=c.$$

$$e_z \text{ and } H_\phi \text{ are continuous at } p=b.$$

From (3.110d),

$$H_\phi = -j \frac{w \epsilon}{k_c^2} \frac{\partial E_z}{\partial p},$$

So we get the following four equations:

$$A J_0(k_d a) + B Y_0(k_d a) = 0$$

$$C J_0(k_a c) + D Y_0(k_a c) = 0$$

$$A J_0(k_d b) + B Y_0(k_d b) = C J_0(k_a b) + D Y_0(k_a b)$$

$$\epsilon_r k_d [A J'_0(k_d b) + B Y'_0(k_d b)] = k_a [C J'_0(k_a b) + D Y'_0(k_a b)]$$

$k_a$  and  $k_d$  can be expressed in terms of  $\beta$ , and  $\beta$  can be found so that the determinant of the above system of equations vanishes. This is as far as we can go without actual values for  $a, b, c$ , and  $\epsilon_r$ .

**3.19**

STRIPLINE:  $100\Omega$ ,  $b = 1.02\text{mm}$ ,  $\epsilon_r = 2.2$ , copper,  $\tan \delta = 0.001$   
 $f = 5\text{GHz}$ .

$$\lambda_g = \lambda_0 / \sqrt{\epsilon_r} = c / \sqrt{\epsilon_r} f = 4.045 \text{ cm}$$

$$\sqrt{\epsilon_r} Z_0 = 148.3 > 120 \Omega$$

$$x = \frac{30\pi}{\sqrt{\epsilon_r} Z_0} - 0.441 = 0.194$$

$$W/b = .85 - \sqrt{1.6-x} = 0.213 \Rightarrow W = 0.2174 \text{ mm}$$

(PCAAD:  $W = 0.218 \text{ mm}$ )

$$\begin{aligned} \alpha_d &= 0.0067 \text{ dB/cm} \\ \alpha_c &= 0.044 \text{ dB/cm} \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{PCAAD}$$

**3.20**

MICROSTRIP:  $100\Omega$ ,  $d = 0.51\text{mm}$ ,  $\epsilon_r = 2.2$ , copper  
 $\tan \delta = 0.001$ ,  $f = 5\text{GHz}$ .

$$\text{First try } W/d < 2 : A = \frac{Z_0}{60} \sqrt{\frac{\epsilon_{r+1}}{2}} + \frac{\epsilon_{r-1}}{\epsilon_{r+1}} (2.3 + 1.1/\epsilon_r) = 2.213$$

$$W/d = \frac{8e^A}{e^{2A} - 2} = .896 \Rightarrow W = 0.457 \text{ mm} \quad \checkmark$$

$$\epsilon_e = \frac{\epsilon_{r+1}}{2} + \frac{\epsilon_{r-1}}{2} \frac{1}{\sqrt{1 + 12d/W}} = 1.758 \quad \checkmark$$

$$\lambda_g = c / \sqrt{\epsilon_r} f = 4.525 \text{ cm}$$

$$\begin{aligned} \alpha_d &= 0.0048 \text{ dB/cm} \\ \alpha_c &= 0.017 \text{ dB/cm} \end{aligned} \quad \left. \begin{array}{l} \\ \end{array} \right\} \text{PCAAD}$$

**3.21**

$$\lambda_0 = 0.12 \text{ m}, \beta = 2\pi/\sqrt{\epsilon_r} / \lambda_0 = 3986.7^\circ/\text{m} \quad (f = 2.5 \text{ GHz})$$

C = 5 pF: From P2.11,  $\beta l = 82.74^\circ \Rightarrow l = 2.0754 \text{ cm}$  ( $Z_{in} = -j12.73 \Omega$ )

L = 5 nH: From P2.11,  $\beta l = 128.1^\circ \Rightarrow l = 3.2132 \text{ cm}$  ( $Z_{in} = +j78.5 \Omega$ )

From SERENADE:

LOSSLESS: C:  $Z_{in} = -j12.63 \Omega \checkmark$

L:  $Z_{in} = +j78.7 \Omega \checkmark$

LOSSY: C:  $Z_{in} = 0.27 - j12.82 \Omega$

( $t = 0.5 \text{ mil}$ ) L:  $Z_{in} = 0.66 + j76.7 \Omega$

**3.22**

$$k_0 = \frac{2\pi f}{c} = 104.7 \text{ m}^{-1} \quad ; \quad R_s = \sqrt{\frac{WU}{Z_0}} = \sqrt{\frac{2\pi(5 \times 10^9)(4\pi \times 10^{-7})}{2(5.813 \times 10^7)}} = 0.018 \Omega$$

MICROSTRIP CASE :

First try  $W/d > 2$ : From (3.197),  $B = \frac{377\pi}{2Z_0\sqrt{\epsilon_r}} = 8.0$ 

$$W/d = \frac{2}{\pi} \left[ B - 1 - \ln(2B-1) + \frac{\epsilon_r-1}{2\epsilon_r} \left\{ \ln(B-1) + .39 - \frac{.61}{\epsilon_r} \right\} \right] = 3.09 > 2$$

$$W = 3.09(1.6 \text{ cm}) = \underline{0.494 \text{ cm}}$$

$$\text{From (3.195), } \epsilon_e = \frac{\epsilon_r+1}{2} + \frac{\epsilon_r-1}{2} \frac{1}{\sqrt{1+12d/W}} = 1.87 \Rightarrow \lambda_g = \frac{c}{\sqrt{\epsilon_e} f} = \underline{4.38 \text{ cm}}$$

From (3.198),

$$\alpha_d = \frac{k_0 \epsilon_r (\epsilon_e - 1)}{2 \sqrt{\epsilon_e (\epsilon_r - 1)}} \tan \delta = \underline{0.061 \text{ nepers/m}}$$

From (3.199),

$$\alpha_c = \frac{R_s}{Z_0 W} = \underline{0.073 \text{ nepers/m}}$$

Total MS Loss:

$$\text{LOSS} = (.061 + .073) \left( \frac{m}{m} \right) \left( \frac{1}{16\lambda_g} \right) \left( \frac{.0438 \frac{m}{\lambda_g}}{\text{nepers}} \right) \left( \frac{8.686 \text{ dB}}{\text{nepers}} \right)$$

$$= \underline{0.82 \text{ dB}}$$

STRIPLINE CASE :

$$\text{From (3.180), } \sqrt{\epsilon_r} Z_0 = \sqrt{2.2}(50) = 74 < 120. \quad \chi = \frac{30\pi}{\sqrt{\epsilon_r} Z_0} - .441 = 0.833$$

$$W/b = \chi = 0.833 \Rightarrow W = .833(3.2 \text{ cm}) = \underline{0.267 \text{ cm}}$$

$$\lambda_g = \frac{c}{\sqrt{\epsilon_r} f} = \underline{4.045 \text{ cm}} \quad A = 1 + \frac{2W}{b-t} + \frac{1}{\pi} \frac{b+t}{b-t} \ln \left( \frac{2b-t}{t} \right) = 4.73$$

From (3.181),

$$\alpha_c = \frac{2.7 \times 10^{-3} R_s \epsilon_r Z_0}{30\pi b} A = \underline{0.084 \text{ nepers/m}}$$

From (3.30),

$$\alpha_d = \frac{k \tan \delta}{2} = \frac{\sqrt{2.2}(104.7)(0.01)}{2} = \underline{0.078 \text{ nepers/m}}$$

Total S.L. Loss:

$$\text{LOSS} = (.084 + .078) \left( \frac{m}{m} \right) \left( \frac{1}{16\lambda_g} \right) \left( \frac{.04045 \frac{m}{\lambda_g}}{\text{nepers}} \right) \left( \frac{8.686 \text{ dB}}{\text{nepers}} \right)$$

$$= \underline{0.91 \text{ dB}}$$

Thus the microstrip line should be used.

**3.23**

$$H_3(x, y, z) = h_3(x, y) e^{-j\beta z} \quad ; \quad h_3 \text{ real}, \beta \text{ real}$$

From (3.19),

$$H_x = \frac{-j\beta}{k_c^2} \frac{\partial h_3}{\partial x} e^{-j\beta z}$$

$$H_y = \frac{-j\beta}{k_c^2} \frac{\partial h_3}{\partial y} e^{-j\beta z}$$

$$E_x = \frac{j\omega u}{k_c^2} \frac{\partial h_3}{\partial y} e^{-j\beta z}$$

$$E_y = j\frac{\omega u}{k_c^2} \frac{\partial h_3}{\partial x} e^{-j\beta z}$$

$$\begin{aligned} \bar{E} \times \bar{H}^* &= (E_x H_y^* - E_y H_x^*) \hat{z} - E_x H_3^* \hat{y} + E_y H_3^* \hat{x} \\ &= \frac{\omega u \beta}{k_c^4} \left[ \left( \frac{\partial h_3}{\partial y} \right)^2 + \left( \frac{\partial h_3}{\partial x} \right)^2 \right] \hat{z} + j \frac{\omega u}{k_c^2} \left( \frac{\partial h_3}{\partial y} \hat{y} + \frac{\partial h_3}{\partial x} \hat{x} \right) h_3 \end{aligned}$$

So if  $h_3$  is real (or a real function times a complex constant), there is real power flow only in the  $z$ -direction.

**3.24**

Write the incident, reflected, and transmitted  $TE_{10}$  fields as follows:

$$E_y^i = E_0 \sin \frac{\pi x}{a} e^{-j\beta_a z}$$

$$E_y^r = E_0 \Gamma \sin \frac{\pi x}{a} e^{j\beta_a z}$$

$$H_x^i = \frac{-E_0}{Z_a} \sin \frac{\pi x}{a} e^{-j\beta_a z}$$

$$H_x^r = \frac{E_0 \Gamma}{Z_a} \sin \frac{\pi x}{a} e^{j\beta_a z}$$

$$E_y^t = E_0 T \sin \frac{\pi x}{a} e^{-j\beta_d z}$$

$$H_x^t = \frac{-E_0 T}{Z_d} \sin \frac{\pi x}{a} e^{-j\beta_d z}$$

$$\text{where } \beta_a = \sqrt{k_0^2 - (\pi/a)^2}$$

$$Z_a = k_0 \eta_0 / \beta_a$$

$$\beta_d = \sqrt{G_r k_0^2 - (\pi/a)^2}$$

$$Z_d = k_0 \eta_0 / \beta_d$$

Match fields at  $z=0$  to obtain:

$$1 + \Gamma = T \quad (\text{E}_y \text{ continuous})$$

$$\frac{1}{Z_a} (-1 + \Gamma) = \frac{-T}{Z_d} \quad (H_x \text{ continuous})$$

Solving for  $\Gamma$  gives,


$$\Gamma = \frac{Z_d - Z_a}{Z_d + Z_a}$$

which agrees with the transmission line theory result if  $Z_{TE}$  is used as  $Z_0$  in each region. ✓

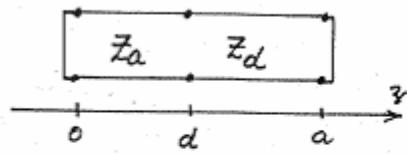**3.25**  $Z_{TM} = \eta \beta / k = \eta_0 \beta / k_0 \sqrt{\epsilon_r}$

for  $0 < x < d$ ,  $Z_a = \eta_0 k_x a / k_0$

for  $d < x < a$ ,  $Z_d = \eta_0 k_x d / \sqrt{\epsilon_r} k_0$



$$\beta = \sqrt{\epsilon_r k_0^2 - k_x^2 - (\pi n_b)^2} = \sqrt{k_0^2 - k_x^2 - (\pi n_b)^2}$$

Applying (3.215):

$$Z_a \tan \beta a d + Z_d \tan \beta_d (a - b) = 0$$


The m-th root of this equation applies to the  $TM_{mn}$  mode.

**3.26**

$$Z_a = k_y a \eta_0 / k_0 = -j h \eta_0 / k_0$$

$$Z_d = k_y d \eta_0 / k_0 = k_y d \eta_0 / k_0$$
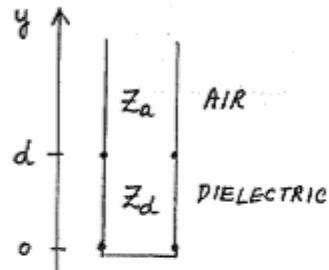
$$\beta = \sqrt{\epsilon_r k_0^2 - k_y^2} = \sqrt{k_0^2 - k_y^2 a} = \sqrt{k_0^2 + h^2}$$



Applying (3.215):

$$Z_a + j Z_d \tan k_y d = 0$$

$$h = k_y d \tan k_y d = 0$$

This agrees with the solution to Problem 3.17, with  $k_c = k_y d$ . ✓

**3.27**For X-band guide,  $a = 2.286 \text{ cm}$ .

$$k = \frac{2\pi f \sqrt{\epsilon_r}}{c} = \frac{2\pi (9500) \sqrt{2.08}}{300} = 287. \text{ m}^{-1} \checkmark$$

$$\beta = \sqrt{k^2 - (\pi/a)^2} = 252. \text{ m}^{-1} \checkmark$$

$$\text{speed of light in Teflon} = \frac{c}{\sqrt{\epsilon_r}} = \frac{3 \times 10^8}{\sqrt{2.08}} = 2.08 \times 10^8 \text{ m/sec} \checkmark$$

$$\text{phase velocity} = v_p = \frac{\omega}{\beta} = \frac{2\pi (9.5 \times 10^9)}{252} = 2.37 \times 10^8 \text{ m/sec} \checkmark$$

From (3.231),

$$\begin{aligned} \text{group velocity} &= v_g = \left( \frac{d\beta}{d\omega} \right)^{-1} = \left( \frac{d\beta}{dk} \frac{dk}{d\omega} \right)^{-1} = \left( \frac{k}{\beta} \sqrt{\mu\epsilon} \right)^{-1} \\ &= \frac{\beta}{k\sqrt{\mu\epsilon}} = \frac{252 (2.08 \times 10^8)}{287} = 1.83 \times 10^8 \text{ m/sec} \end{aligned}$$

Note that  $v_g < \frac{c}{\sqrt{\epsilon_r}} < v_p$ .**3.28**

$$P_{MAX} = C a^2 \ln \frac{b}{a}$$

$$\frac{d P_{MAX}}{da} = 2a \ln \frac{b}{a} - \frac{a^2}{a} = 0$$

$$2 \ln \frac{b}{a} - 1 = 0$$

$$2 \ln x = 1$$

$$\ln x = 0.5$$

$$x = 1.65$$

$$Z_0 = \frac{377}{2\pi} \ln \frac{b}{a} = \frac{120\pi}{2\pi} \left(\frac{1}{2}\right) = 30 \Omega$$

3.29

alumina,  $\epsilon_r = 9.9$ ,  $d = 2.0 \text{ mm}$ ,  $W = 1.93 \text{ mm}$   
 $Z_0 = 50 \Omega$ ,  $\epsilon_e = 6.771$

$$f_{T1} = \frac{c}{2\pi d} \sqrt{\frac{2}{\epsilon_r - 1}} \tan^{-1} \epsilon_r = 11.3 \text{ GHz}$$

$$f_{T2} = \frac{c}{4d \sqrt{\epsilon_r - 1}} = 12.5 \text{ GHz}.$$

$$f_{T3} = \frac{c}{\sqrt{\epsilon_r} (2W+d)} = 16.3 \text{ GHz}$$

$$f_{T4} = \frac{c}{2d \sqrt{\epsilon_r}} = 23.8 \text{ GHz}.$$


It would be advisable to keep the operating frequency below 10 GHz for this line.

## Chapter 4

**4.1**

Using a transmission line analogy gives,


$$\Gamma = \frac{Z_2 - Z_1}{Z_2 + Z_1}$$

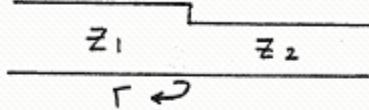

where  $Z_1 = k_0 n_0 / \beta_1$ ,  $Z_2 = k_0 n_0 / \beta_2$ .

But  $\beta_1 = \beta_2 = \sqrt{k_0^2 - (\pi/a)^2}$  in both regions, since only the height (b) of the guide changes. Thus,  $\Gamma = 0$  from above. This is obviously not correct, as  $E_y$  should be zero for  $b/2 < y < b$ . Higher order  $TE_{1n}$  modes must be considered, in a mode matching procedure. This will result in a solution where  $\Gamma \neq 0$ . Consideration of only the dominant mode is not adequate.

**4.2**

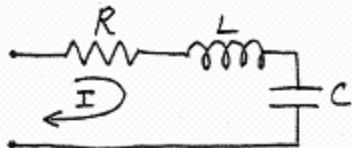

$$P_d = \frac{1}{2} |I|^2 R \implies R = \frac{P_d}{\frac{1}{2} |I|^2}$$


$$W_m = \frac{1}{4} L |I|^2 \implies L = \frac{2 W_m}{\frac{1}{2} |I|^2}$$

$$W_e = \frac{1}{4} C |V_c|^2 = \frac{1}{4 \omega^2 C} |I|^2 \implies \frac{1}{\omega^2 C} = \frac{2 W_e}{\frac{1}{2} |I|^2}$$

The input impedance is,

$$Z_{in} = R + j(\omega L + \frac{1}{\omega C}) = \frac{P_d + 2j\omega(W_m - W_e)}{\frac{1}{2} |I|^2} \quad \checkmark$$

In agreement with (4.17)

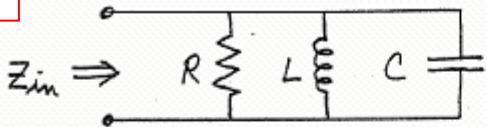**4.3**

$$Z = \frac{1}{\frac{1}{R} + \frac{1}{j\omega L} + j\omega C} = \frac{1}{\frac{1}{R} + j\omega(C - \frac{1}{\omega^2 L})}$$

$$Z(-\omega) = \frac{1}{\frac{1}{R} - j\omega(C - \frac{1}{\omega^2 L})} = Z^*(\omega) \quad \checkmark$$

**4.4**

$$V_1 = 10 \angle 90^\circ$$

$$I_1 = 0.2 \angle 90^\circ$$

$$V_2 = 8 \angle 0^\circ$$

$$I_2 = 0.16 \angle -90^\circ$$

$$Z_0 = 50 \Omega$$

$$V_n^+ = (V_n + Z_0 I_n)/2$$

$$V_n^- = (V_n - Z_0 I_n)/2$$

$$V_1^+ = \frac{1}{2} [10j + 50(0.2j)] = 10 \angle 90^\circ$$

$$V_1^- = \frac{1}{2} [10j - 50(0.2j)] = 0$$

$$V_2^+ = \frac{1}{2} [8 + 50(-0.16j)] = 4 - 4j = 5.66 \angle -45^\circ$$

$$V_2^- = \frac{1}{2} [8 - 50(-0.16j)] = 4 + 4j = 5.66 \angle +45^\circ$$

$$Z_{in}^{(1)} = \frac{V_1}{I_1} = \frac{10j}{0.2j} = 50 \Omega$$

$$Z_{in}^{(2)} = \frac{V_2}{I_2} = \frac{8}{-0.16j} = 50j = 50 \angle 90^\circ \Omega$$

**4.5**

$$\begin{aligned} P_{in} &= \frac{1}{2} [V]^t [I]^* = \frac{1}{2} [V]^t [Y]^* [V]^* \\ &= \frac{1}{2} \sum_{n=1}^N \sum_{m=1}^N V_m Y_{mn}^* V_n^* \end{aligned}$$

If lossless,  $\operatorname{Re}\{P_{in}\}=0$ . Since the  $V_m$ 's are independent, we first let all  $V_m=0$ , except for  $V_n$ . Then,

$$\begin{aligned} P_{in} &= \frac{1}{2} V_n Y_{nn}^* V_n^* = \frac{1}{2} |V_n|^2 Y_{nn}^* \\ \therefore \operatorname{Re}\{Y_{nn}^*\} &= \operatorname{Re}\{Y_{nn}\} = 0 \quad \checkmark \end{aligned}$$

Now let all port voltages be zero except for  $V_m$  and  $V_n$ . Then,

$$P_{in} = \frac{1}{2} V_m Y_{mn}^* V_n^* + \frac{1}{2} V_n Y_{nm}^* V_m^*$$

So,

$$\operatorname{Re}\{V_m Y_{mn}^* V_n^* + V_n Y_{nm}^* V_m^*\} = 0$$

If  $Y_{mn}=Y_{nm}$  (reciprocal), then

$$\operatorname{Re}\{Y_{mn}^* (V_m V_n^* + V_n V_m^*)\} = \operatorname{Re}\{Y_{mn}^* [(V_m V_n^* + (V_m V_n^*)^*)]\} = 0$$

Since  $A+A^*$  is real, we must have  $\operatorname{Re}\{Y_{mn}\}=0 \quad \checkmark$

**4.6**

Let  $[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$ , and show that  $Z_{ij}$ 's can be found such that  $P_{in}=0$ , but not all  $Z_{ij}$ 's are pure imaginary.

$$\begin{aligned} P_{in} &= \frac{1}{2} [I]^t [Z]^t [I]^* = \frac{1}{2} (I_1 Z_{11} I_1^* + I_1 Z_{21} I_2^* + I_2 Z_{12} I_1^* + I_2 Z_{22} I_2^*) \\ &= \frac{1}{2} (Z_{11} |I_1|^2 + Z_{22} |I_2|^2 + Z_{21} I_1 I_2^* + Z_{12} I_2 I_1^*) \end{aligned}$$

To be lossless, we must have  $\operatorname{Re}\{Z_{11}\} = \operatorname{Re}\{Z_{22}\} = 0$ .


$$\text{Also, } \operatorname{Re}\{Z_{21} I_1 I_2^* + Z_{12} I_2 I_1^*\} = 0.$$

This will occur if  $Z_{12} = -Z_{21}^*$  (since  $\operatorname{Re}\{A-A^*\}=0$ ).

For example, if  $Z_{12} = a+jb$ , then  $Z_{21} = -a+jb$ .

Thus,  $[Z]$  is not symmetric, and the answer is NO.

4.7

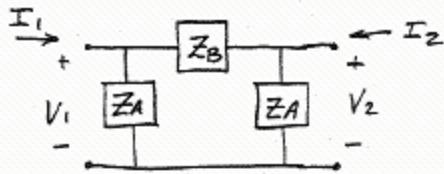

From (4.28),

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{V_1}{V_1 \left( \frac{2Z_A + Z_B}{Z_A(Z_A + Z_B)} \right)} = \frac{Z_A(Z_A + Z_B)}{2Z_A + Z_B} = Z_{22} \quad (\text{BY SYMMETRY})$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{I_1 Z_{11} \left( \frac{Z_A}{Z_A + Z_B} \right)}{I_1} = \frac{Z_A^2}{2Z_A + Z_B} = Z_{12} \quad (\text{BY RECIPROCITY})$$

From (4.29),

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0} = \frac{I_1}{I_1 \left( \frac{Z_A Z_B}{Z_A + Z_B} \right)} = \frac{Z_A + Z_B}{Z_A Z_B} = Y_{22} \quad (\text{BY SYMMETRY})$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0} = -\frac{V_1 / Z_B}{V_1} = -\frac{1}{Z_B} = Y_{12} \quad (\text{BY RECIPROCITY})$$

CHECK:  $[Z][Y] = [Y] ?$ 

$$Z_{11} Y_{11} + Z_{12} Y_{21} = \frac{(Z_A + Z_B)^2}{Z_B(2Z_A + Z_B)} - \frac{Z_A^2}{Z_B(2Z_A + Z_B)} = \frac{2Z_A Z_B + Z_B^2}{Z_B(2Z_A + Z_B)} = 1 \quad \checkmark$$

$$Z_{11} Y_{12} + Z_{12} Y_{22} = \frac{-Z_A(Z_A + Z_B)}{Z_B(2Z_A + Z_B)} + \frac{Z_A(Z_A + Z_B)}{Z_B(2Z_A + Z_B)} = 0 \quad \checkmark$$

Similarly for the T-network. The results are,


$$Z_{11} = Z_{22} = \frac{Y_A + Y_B}{Y_A Y_B} \quad \checkmark \qquad Z_{12} = Z_{21} = \frac{-1}{Y_B} \quad \checkmark$$

$$Y_{11} = Y_{22} = \frac{Y_A(Y_A + Y_B)}{2Y_A + Y_B} \quad \checkmark$$

$$Y_{12} = Y_{21} = \frac{Y_A^2}{2Y_A + Y_B} \quad \checkmark$$

**4.8**

Model the two-port as below:

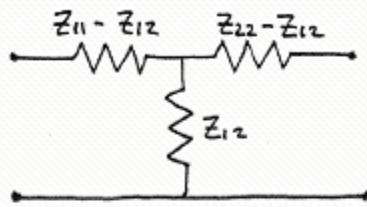

Then,

$$Z_{sc}^{(1)} = Z_{11} - Z_{12} + \frac{Z_{12}(Z_{22} - Z_{12})}{Z_{22}} = Z_{11} - Z_{12}^2/Z_{22}$$

$$Z_{sc}^{(2)} = Z_{22} - Z_{12}^2/Z_{11}$$

$$Z_{oc}^{(1)} = Z_{11} \quad \checkmark$$

$$Z_{oc}^{(2)} = Z_{22} \quad \checkmark$$

From the first equation,

$$Z_{12}^2 = -(Z_{sc}^{(1)} - Z_{11})Z_{22} = (Z_{oc}^{(1)} - Z_{sc}^{(1)})Z_{oc}^{(2)}.$$

**4.9**

From Table 4.1 the ABCD parameters for a transmission line section are,

$$A = D = \cos \beta l, \quad B = j Z_0 \sin \beta l, \quad C = j Y_0 \sin \beta l.$$


Now use Table 4.2 to convert to Z-parameters:

$$Z_{11} = \frac{A}{C} = \frac{\cos \beta l}{j Y_0 \sin \beta l} = -j Z_0 \cot \beta l \quad \checkmark$$

$$Z_{12} = Z_{21} = \frac{1}{C} = -j Z_0 \csc \beta l \quad \checkmark$$

$$Z_{22} = \frac{D}{C} = \frac{\cos \beta l}{j Y_0 \sin \beta l} = -j Z_0 \cot \beta l \quad \checkmark$$

4.10

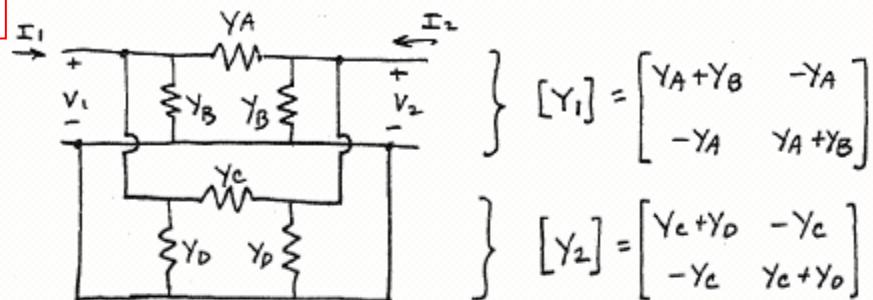


Adding  $[Y]$  matrices gives:

$$[Y] = [Y_1] + [Y_2] = \begin{bmatrix} Y_A + Y_B + Y_c + Y_D & -Y_A - Y_c \\ -Y_A - Y_c & Y_A + Y_B + Y_c + Y_D \end{bmatrix}$$

By direct calculation, we obtain similar results:

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} = Y_A + Y_B + Y_c + Y_D \quad \checkmark \quad Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0} = -(Y_A + Y_c) \quad \checkmark$$

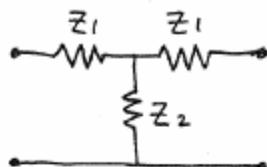
Now apply to bridged-T network (Example 5.7 of 1st edition)



$$[Z_A] = \begin{bmatrix} z_1 + z_2 & z_2 \\ z_2 & z_1 + z_2 \end{bmatrix}$$

$$[Y_A] = \frac{1}{D} \begin{bmatrix} z_1 + z_2 & -z_2 \\ -z_2 & z_1 + z_2 \end{bmatrix} \quad \checkmark$$

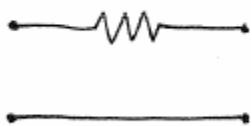
$$D = (z_1 + z_2)^2 - z_2^2 = z_1^2 + 2z_1z_2 \quad \checkmark$$



$$[Y_B] = \begin{bmatrix} 1/z_3 & -1/z_3 \\ -1/z_3 & 1/z_3 \end{bmatrix} \quad \checkmark$$

$$[Y_{TOT}] = [Y_A] + [Y_B] = \begin{bmatrix} \frac{1}{z_3} + \frac{z_1 + z_2}{D} & -(\frac{1}{z_3} + \frac{z_2}{D}) \\ -(\frac{1}{z_3} + \frac{z_2}{D}) & \frac{1}{z_3} + \frac{z_1 + z_2}{D} \end{bmatrix} \quad \checkmark$$

4.11

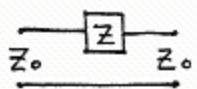


From Table 4.1,  $\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$

convert to  $[s]$  using Table 4.2:

$$S_{11} = \frac{1 + Z/Z_0 - 1}{1 + Z/Z_0 + 1} = \frac{Z}{2Z_0 + Z} ; S_{12} = \frac{Z}{1 + Z/Z_0 + 1} = \frac{ZZ_0}{2Z_0 + Z}$$
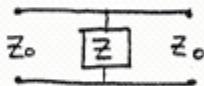
$$1 - S_{11} = \frac{2Z_0}{2Z_0 + Z} = S_{12} \checkmark$$



From Table 4.1,  $\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 1/Z & 1 \end{bmatrix}$


convert to  $[s]$ :

$$S_{11} = \frac{1 - Z_0/Z - 1}{1 + Z_0/Z + 1} = \frac{-Z_0}{2Z + Z_0} ; S_{12} = \frac{Z}{1 + Z_0/Z + 1} = \frac{Z}{2Z + Z_0}$$

$$1 + S_{11} = \frac{2Z}{2Z + Z_0} = S_{12} \checkmark$$

**4.12**

Define wave amplitudes as shown:

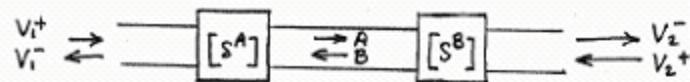

Then,

$$\begin{bmatrix} V_i^- \\ A \end{bmatrix} = [S^A] \begin{bmatrix} V_i^+ \\ B \end{bmatrix} \quad \begin{bmatrix} B \\ V_2^- \end{bmatrix} = [S^B] \begin{bmatrix} A \\ V_2^+ \end{bmatrix} \quad \begin{bmatrix} V_i^- \\ V_2^- \end{bmatrix} = [S] \begin{bmatrix} V_i^+ \\ V_2^+ \end{bmatrix}$$

$$S_{21} = \left. \frac{V_2^-}{V_i^+} \right|_{V_2^+=0}. \text{ When } V_2^+=0, \text{ we have } B = S_{11}^B A, V_2^- = S_{21}^B A.$$

Then,

$$A = S_{21}^A V_i^+ + S_{22}^A B = S_{21}^A V_i^+ + S_{22}^A S_{11}^B A$$


$$\frac{V_2^-}{S_{21}^B} = S_{21}^A V_i^+ + S_{22}^A S_{11}^B \frac{V_2^-}{S_{21}^B}$$

$$V_i^- \left( 1 - \frac{S_{22}^A S_{11}^B}{S_{21}^B} \right) = S_{21}^A V_i^+$$

So,

$$S_{21} = \frac{S_{21}^A S_{11}^B}{1 - S_{22}^A S_{11}^B} \checkmark$$

SIGNAL FLOWGRAPH SOLUTION:

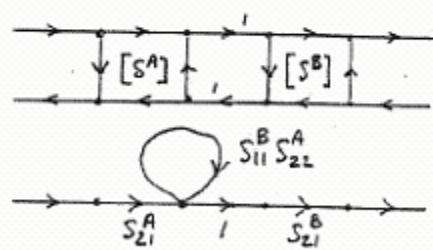

$$\therefore S_{21} = \frac{S_{21}^A S_{11}^B}{1 - S_{11}^B S_{22}^A} \checkmark$$

**4.13**

a)  $[S] = \begin{bmatrix} S_{11} & S_{21} \\ S_{21} & S_{22} \end{bmatrix}$   $S_{12}=S_{21}$  since reciprocal

$[S]$  is unitary if lossless, so

1st Row:  $|S_{11}|^2 + |S_{21}|^2 = 1$  (or 1st col)  
 $|S_{21}|^2 = 1 - |S_{11}|^2 \checkmark$

b)  $[S] = \begin{bmatrix} S_{11} & S_{21} \\ 0 & S_{22} \end{bmatrix}$   $S_{12} \neq S_{21}$  since nonreciprocal

1st Row:  $|S_{11}|^2 + |S_{21}|^2 = 1$   
1st Col.:  $|S_{11}|^2 = 1$   
 $\therefore |S_{21}| = 0$

4.14

a) To be lossless,  $[S]$  must be unitary. From 1st row :

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 + |S_{14}|^2 = (.178)^2 + (.6)^2 + (.4)^2 = 0.552 \neq 1$$

so the network is not lossless.

b) The  $[S]$  matrix is symmetric, so it is reciprocal.

c) When ports 2, 3, 4 are matched,  $\Gamma = S_{11}$ .

$$\text{so } R_L = -20 \log |\Gamma| = -20 \log (.178) = 15.0 \text{ dB}$$

d) For ports 1 and 3 terminated with  $Z_0$ , we have

$$V_1^+ = 0, V_3^+ = 0, \text{ so } V_4^- = S_{42} V_2^+$$

$$IL = -20 \log |S_{42}| = -20 \log (.3) = 10.5 \text{ dB}$$

phase delay =  $+45^\circ$

e) For a short at port 3,  $Z_0$  on other ports, we have

$$V_2^+ = V_4^+ = 0$$

$$V_3^+ = -V_3^-$$

$$V_1^- = S_{11} V_1^+ + S_{13} V_3^+ = S_{11} V_1^+ - S_{13} V_3^-$$

$$V_3^- = S_{31} V_1^+$$

Then,

$$\begin{aligned}\Gamma^{(1)} &= \frac{V_1^-}{V_1^+} = S_{11} - S_{13} S_{31} = 0.178j - (.4/45)(.4/45) \\ &= 0.178j - .16j = 0.018j = 0.018 \angle 90^\circ\end{aligned}$$

**4.15** A matched, reciprocal, 3-port network has an [S] matrix of the following form:

$$[S] = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix}$$

If the network is lossless, then [S] must be unitary:

$$|S_{12}|^2 + |S_{13}|^2 = 1 \quad (1) \qquad S_{13} S_{23}^* = 0 \quad (4)$$

$$|S_{12}|^2 + |S_{23}|^2 = 1 \quad (2) \qquad S_{12} S_{13}^* = 0 \quad (5)$$

$$|S_{13}|^2 + |S_{23}|^2 = 1 \quad (3) \qquad S_{12} S_{23}^* = 0 \quad (6)$$


To show that a contradiction exists, assume that  $S_{12} = 0$ , in order to satisfy (5) and (6). Then from (1),  $|S_{13}|^2 = 1$ , and from (3),  $|S_{23}| = 0$ . But then (2) will be contradicted. Similarly, a contradiction will follow if we let  $S_{13} = 0$ , or  $S_{23} = 0$ .

A circulator is an example of a nonreciprocal, lossless, matched 3-port network.

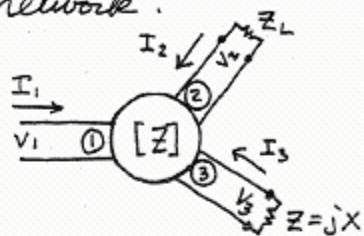4.16

For this problem it is easiest to use the  $Z$ -matrix for a lossless reciprocal 3-port network:

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} jX_{11} & jX_{12} & jX_{13} \\ jX_{12} & jX_{22} & jX_{23} \\ jX_{13} & jX_{23} & jX_{33} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix}$$



If we terminate port 3 in a reactance  $jX$ ,

then  $V_3 = -jX I_3$ . Then we must find  $jX$  so that  $V_2 = 0$  for  $V_1 \neq 0$ . If  $V_2 = 0$ , then  $I_2 = 0$ :

$$V_3 = jX_{13} I_1 + jX_{33} I_3 = -jX I_3$$

$$I_3 = \frac{-X_{13} I_1}{X_{33} + X}$$

$$V_2 = jX_{12} I_1 + jX_{23} I_3 = \left( jX_{12} - \frac{jX_{23} X_{13}}{X_{33} + X} \right) I_1 = 0$$

So,

$$X_{12} X_{33} + X X_{12} - X_{13} X_{23} = 0$$

$$X = \frac{X_{13} X_{23} - X_{12} X_{33}}{X_{12}} \quad \checkmark$$

CHECK: The input impedance at Port 1 is,

$$Z_{in}^{(1)} = \frac{V_1}{I_1} = \frac{jX_{11} I_1 + jX_{13} I_3}{I_1} = jX_{11} + jX_{13} \left( \frac{-X_{13}}{X_{33} + X} \right)$$

$$= j \left( X_{11} - \frac{X_{13}^2}{X_{33} + X} \right) \quad \text{which is pure imaginary} \quad \checkmark$$

4.17

$$\begin{bmatrix} V_1^- \\ V_2^- \\ V_3^- \end{bmatrix} = \begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{12} & S_{11} & S_{13} \\ S_{13} & S_{13} & S_{33} \end{bmatrix} \begin{bmatrix} V_1^+ \\ V_2^+ \\ V_3^+ \end{bmatrix}$$

Assume the network is fed at port 1, so  $V_1^+ \neq 0$ . Port 2 is terminated in a matched load, so  $V_2^+ = 0$ . Port 3 is terminated in a reactive load, so  $V_3^+ = e^{j\phi} V_3^-$ . We must find  $e^{j\phi}$  so that  $V_1^-/V_1^+ = 0$ .

$$V_3^- = S_{13} V_1^+ + S_{33} V_3^+ = e^{j\phi} V_3^+$$

$$V_3^+ = \frac{S_{13} V_1^+}{e^{-j\phi} - S_{33}}$$

$$V_1^- = S_{11} V_1^+ + S_{13} V_3^+ = S_{11} V_1^+ + \frac{S_{13}^2 V_1^+}{e^{-j\phi} - S_{33}}$$

$$\frac{V_1^-}{V_1^+} = S_{11} + \frac{S_{13}^2}{e^{-j\phi} - S_{33}} = 0 \Rightarrow e^{-j\phi} = S_{33} - \frac{S_{13}^2}{S_{11}} . \checkmark$$

We should also verify that this quantity has unit magnitude:

$$|S_{33} - S_{13}^2/S_{11}|^2 = \frac{|S_{11}|^2 |S_{33}|^2 - |S_{13}|^4 - S_{11}^* S_{33}^* S_{13}^2 - S_{11} S_{33} S_{13}^{*2}}{|S_{11}|^2}$$

The unitary properties of  $[S]$  lead to four equations:

$$|S_{11}|^2 + |S_{12}|^2 + |S_{13}|^2 = 1$$

$$S_{11} S_{12}^* + S_{12} S_{11}^* + |S_{13}|^2 = 0$$

$$2 |S_{13}|^2 + |S_{33}|^2 = 1$$

$$S_{12} S_{13}^* + S_{11} S_{13}^* + S_{13} S_{33}^* = 0$$

Eliminating  $S_{12}$  from the two equations on the right yields,

$$-2 |S_{11}|^2 - \frac{S_{11} S_{13}^* S_{33}}{S_{13}} - \frac{S_{11}^* S_{13} S_{33}^*}{S_{13}^*} + |S_{13}|^2 = 0$$


$$\text{or, } -S_{11} S_{13}^{*2} S_{33} - S_{11}^* S_{13}^2 S_{33}^* = 2 |S_{11}|^2 |S_{13}|^2 - |S_{13}|^4$$

$$\text{Then, } |S_{33} - S_{13}^2/S_{11}|^2 = \frac{|S_{11}|^2 |S_{33}|^2 + |S_{13}|^4 + 2 |S_{11}|^2 |S_{13}|^2 - 2 |S_{13}|^4}{|S_{11}|^2}$$

$$= |S_{33}|^2 + 2 |S_{13}|^2 = 1 \checkmark$$

**4.18**

signal flow graph solution :

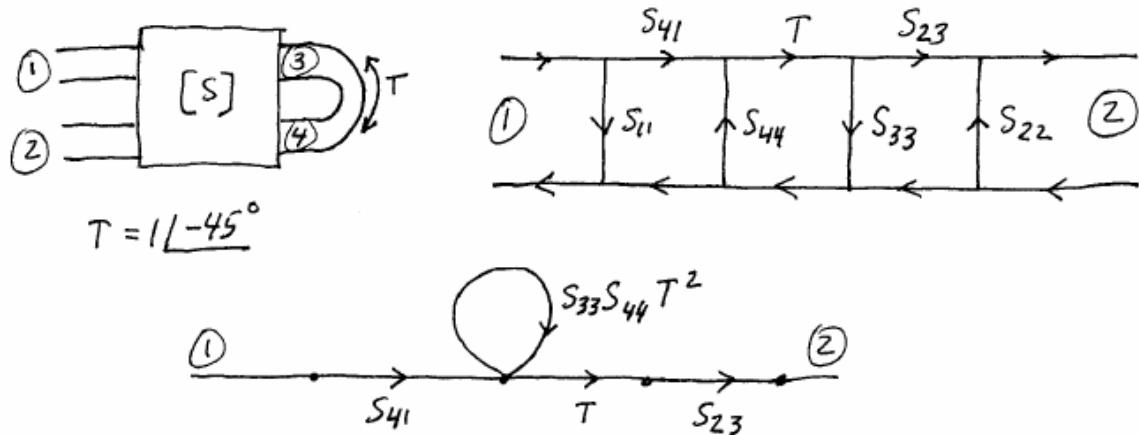

$$T_{21} = \frac{S_{41} S_{23}}{1 - S_{33} S_{44} T^2} = \frac{(1.4 \angle 45^\circ)(0.7 \angle -45^\circ)}{1 - (0.6 \angle 45^\circ)(0.5 \angle 45^\circ)(1 \angle -90^\circ)} = 0.4 \angle -90^\circ$$

$$IL = -20 \log(0.4) = 7.96 \text{ dB}$$

$$\text{delay} = +90^\circ.$$

**4.19**

From (4.62),

$$S'_{ij} = \frac{\sqrt{Z_{0j}}}{\sqrt{Z_{0i}}} S_{ij}$$

So,


$$S'_{11} = S_{11} \checkmark$$

$$S'_{12} = \sqrt{\frac{Z_{02}}{Z_{01}}} S_{12} \checkmark$$

$$S'_{21} = \sqrt{\frac{Z_{01}}{Z_{02}}} S_{21} \checkmark$$

$$S'_{22} = S_{22} \checkmark$$

4.20

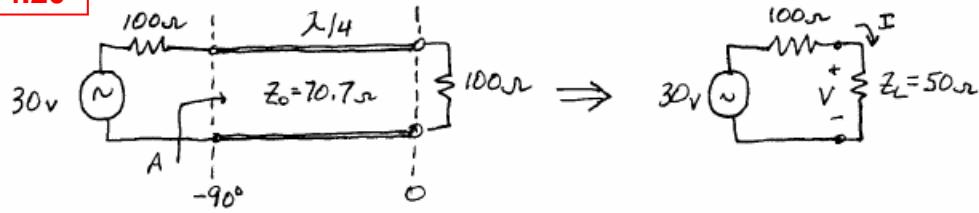

$$Z_{in}(\text{at } A) = (70.7)^2 / 100 = 50 \Omega$$

with reference at A : Let  $Z_R = Z_L^* = 50 \Omega$ . Then  $\Gamma_p = 0$  (not copy mat.)

$$V = 30 \frac{50}{150} = 10 V$$

$$I = \frac{30}{150} = 0.2 A$$

$$a = \frac{1}{2\sqrt{R_R}} (V + Z_R I) = \frac{1}{2\sqrt{50}} (10 + 10) = 1.414$$

$$P_L = \frac{1}{2} |a|^2 = 1 W \quad \checkmark$$

with reference at B : Let  $Z_R = Z_L^* = 100 \Omega$ . Then  $\Gamma_p = 0$

$$\Gamma = \frac{100 - Z_0}{100 + Z_0} = 0.1716$$

$$V(z) = V_o^+ (e^{-j\beta z} + \Gamma e^{+j\beta z})$$

$$V(-90^\circ) = 10 = V_o^+ (j - 0.1716j)$$

$$V_o^+ = -j 12.07$$


$$V(0) = V_o^+ (1 + \Gamma) = -j 14.14$$

$$I(0) = -j 14.14$$

$$a = \frac{1}{2\sqrt{100}} (-j 14.14 - j 14.14) = -j 1.414$$


$$P_L = \frac{1}{2} |a|^2 = 1 W \quad \checkmark$$

4.21

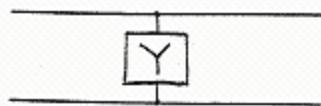

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = 1 \quad C = \frac{I_1}{V_2} \Big|_{I_2=0} = Y \quad$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} = 0 \quad D = \frac{I_1}{I_2} \Big|_{V_2=0} = 1$$

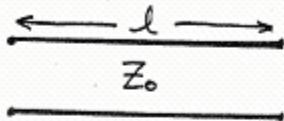

for  $I_2=0$ ,  $V_1 = V^+ (e^{j\beta l} + e^{-j\beta l}) = V^+ 2 \cos \beta l$   
 $V_2 = 2V^+ = V_1 / \cos \beta l$

So,

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = \cos \beta l \quad$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{V_1}{Z_{in} V_2} = \frac{\cos \beta l}{-j Z_0 \cot \beta l} = j Y_0 \sin \beta l$$


for  $V_2=0$ ,  $V_1 = V^+ (e^{j\beta l} - e^{-j\beta l}) = V^+ 2j \sin \beta l$

$$I_2 = \frac{2V^+}{Z_0}$$

So,

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} = j Z_0 \sin \beta l \quad$$

$$D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{V_1}{Z_{in} I_2} = \frac{B}{Z_{in}} = \frac{j Z_0 \sin \beta l}{j Z_0 \tan \beta l} = \cos \beta l$$

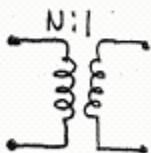

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{N V_2}{V_2} = N \quad$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} = 0 \quad$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = 0 \quad$$

$$D = \frac{I_1}{I_2} \Big|_{V_2=0} = \frac{1}{N}$$

**4.22** NOTE: Difference in signs for  $Z$  and  $ABCD$ .

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = \frac{V_1}{V_2} \frac{V_2}{I_1} \Big|_{I_2=0} = A/C \quad \checkmark$$

for  $I_1=0$ ,  $V_1 = AV_2 - BI_2$   
 $0 = CV_2 - DI_2 \Rightarrow V_2 = DI_2/C$

$$V_1 = \left( \frac{AD}{C} - B \right) I_2$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} = \frac{AD - BC}{C} \quad \checkmark$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = 1/C \quad \checkmark$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0} = D/C \quad \checkmark$$

**4.23**

DIRECT CALCULATION:

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{V_1}{V_1 \frac{1/Y}{Z+ZY}} = 1+ZY$$

$$B = \frac{V_1}{I_2} \Big|_{V_2=0} = \frac{V_1}{V_1/Z} = Z$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = \frac{I_1}{I_1/Y} = Y$$


$$D = \frac{I_1}{I_2} \Big|_{V_2=0} = 1 \quad \text{CHECK: } AD - BC = 1+ZY - ZY = 1 \quad \checkmark$$

CALCULATION USING CASCADE: (From Table 4.1)

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} = \begin{bmatrix} 1+ZY & Z \\ Y & 1 \end{bmatrix} \quad \checkmark$$

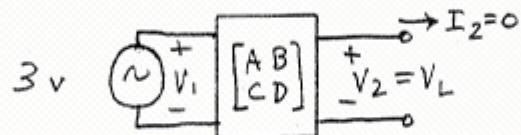**4.24** Using Table 4.1, the ABCD matrix of the cascade of four components (including load) is,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & 50 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 & 0 \\ 0 & 2 \end{bmatrix} \begin{bmatrix} 0 & j50 \\ j/50 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ V_{25} & 1 \end{bmatrix} = \begin{bmatrix} 3j & 25j \\ j/25 & 0 \end{bmatrix}$$





$$V_1 = AV_2 + BI_2 = AV_2 = AV_L$$

$$V_L = \frac{V_1}{A} = \frac{3}{3j} = 1 \angle -90^\circ \quad \checkmark$$

(verified with Serenade)

4.25

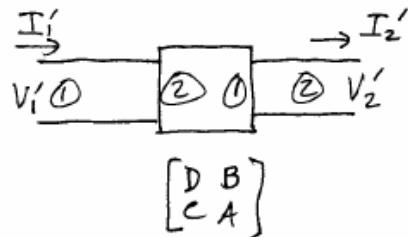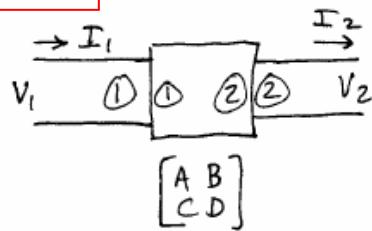

$$I_1' = -I_2, \quad I_2' = -I_1$$

$$V_1' = V_2, \quad V_2' = V_1$$

$$\begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_1' \\ -I_1' \end{bmatrix}$$

inverting:

$$\begin{bmatrix} V_1' \\ -I_1' \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}^{-1} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix} = \begin{bmatrix} D & -B \\ -C & A \end{bmatrix} \begin{bmatrix} V_2' \\ -I_2' \end{bmatrix}$$


since  $AD - BC = 1$  if reciprocal.

Rewriting:

$$\begin{bmatrix} V_1' \\ I_1' \end{bmatrix} = \begin{bmatrix} D & B \\ C & A \end{bmatrix} \begin{bmatrix} V_2' \\ I_2' \end{bmatrix}$$


Example:

original

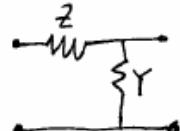

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} = \begin{bmatrix} 1+ZY & Z \\ Y & 1 \end{bmatrix}$$

reversed

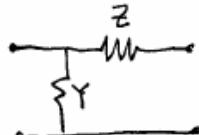

$$\begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix} \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 1 & Z \\ Y & 1+ZY \end{bmatrix}$$

$$\text{so } A' = D, \quad B' = B, \quad C' = C, \quad D' = A \quad \checkmark$$

**4.26**

$$V_1 = A V_2 - B I_2$$

$$V_n = V_n^+ + V_n^-$$

$$I_1 = C V_2 - D I_2$$

$$I_n = (V_n^+ - V_n^-)/Z_0$$

So,

$$V_1^+ + V_1^- = A(V_2^+ + V_2^-) - B(V_2^+ - V_2^-)/Z_0$$

$$V_1^+ - V_1^- = C(V_2^+ + V_2^-)Z_0 - D(V_2^+ - V_2^-)$$

For  $V_2^+ = 0$ ,

$$V_1^+ + V_1^- = (A + B/Z_0)V_2^-$$

$$V_1^+ - V_1^- = (CZ_0 + D)V_2^-$$

eliminate  $V_2^+$ :

$$V_1^+ + V_1^- = \frac{A + B/Z_0}{CZ_0 + D} (V_1^+ - V_1^-)$$

$$V_1^- (CZ_0 + D + A + B/Z_0) = V_1^+ (A + B/Z_0 - CZ_0 - D)$$

$$S_{11} = \left. \frac{V_1^-}{V_1^+} \right|_{V_2^+=0} = \frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D} \quad \checkmark$$

eliminate  $V_1^-$ :

$$2V_1^+ = (A + B/Z_0 + CZ_0 + D)V_2^-$$

$$S_{21} = \left. \frac{V_2^-}{V_1^+} \right|_{V_2^+=0} = \frac{2}{A + B/Z_0 + CZ_0 + D} \quad \checkmark$$

for  $V_1^+ = 0$  the above set reduces to,

$$\begin{aligned} V_1^- &= (A - B/Z_0) V_2^+ + (A + B/Z_0) V_2^- \\ - V_1^- &= (C Z_0 - D) V_2^+ + (C Z_0 + D) V_2^- \end{aligned}$$

eliminate  $V_1^-$ :

$$(A - B/Z_0 + C Z_0 - D) V_2^+ + (A + B/Z_0 + C Z_0 + D) V_2^- = 0$$

$$S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{V_1^+ = 0} = \frac{-A + B/Z_0 - C Z_0 + D}{A + B/Z_0 + C Z_0 + D} \quad \checkmark$$

eliminate  $V_2^-$ :

$$\frac{V_1^-}{A + B/Z_0} - \frac{A - B/Z_0}{A + B/Z_0} V_2^+ = \frac{-V_1^-}{C Z_0 + D} - \frac{C Z_0 - D}{C Z_0 + D} V_2^+$$

$$V_1^- \left( \frac{1}{A + B/Z_0} + \frac{1}{C Z_0 + D} \right) = V_2^+ \left( \frac{A - B/Z_0}{A + B/Z_0} - \frac{C Z_0 - D}{C Z_0 + D} \right)$$

$$S_{12} = \left. \frac{V_1^-}{V_2^+} \right|_{V_1^+ = 0} = \frac{\frac{A - B/Z_0}{A + B/Z_0} - \frac{C Z_0 - D}{C Z_0 + D}}{\frac{1}{A + B/Z_0} + \frac{1}{C Z_0 + D}} = \frac{2(AD - BC)}{A + B/Z_0 + C Z_0 + D} \quad \checkmark$$

These results agree with Table 4.2.

4.27

a) Using the S-parameters, the transmission coefficient from Port 1 to Port 4 is,

$$\begin{aligned} T &= \frac{V_4^-}{V_1^+} = \frac{1}{V_1^+} \left( \frac{-1}{\sqrt{2}} \right) (V_2^+ + jV_3^+) = \frac{1}{V_1^+} \left( \frac{-1}{\sqrt{2}} \right) (\Gamma V_2^- + j\Gamma V_3^-) \\ &= \frac{1}{V_1^+} \left( \frac{-1}{\sqrt{2}} \right) \left( \frac{-1}{\sqrt{2}} \right) (\Gamma) (j+j) V_1^+ = j \Gamma \quad \checkmark \end{aligned}$$


$$\text{attenuation} = |T| = |\Gamma| = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|$$

at port 1 the reflected wave is,

$$V_1^- = \frac{-1}{\sqrt{2}} (jV_2^+ + V_3^+) = \frac{-1}{\sqrt{2}} \Gamma (jV_2^- + V_3^-) = \frac{1}{2} \Gamma (-1+i) V_1^+ = 0 \quad \checkmark$$


b)

$Z_L/Z_0$	atten.(dB)
0	0
0.172	3
1	$\infty$
5.83	3
$\infty$	0

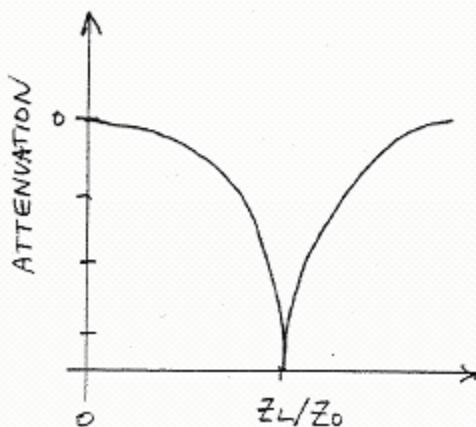


4.28

The signal flowgraph is as follows:

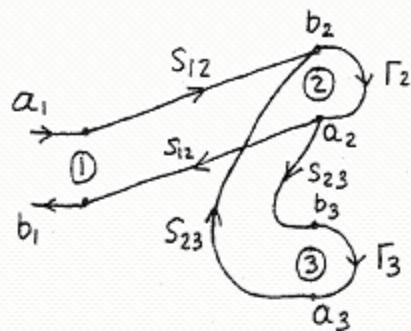


$$\text{Let } \Gamma_{in} = \frac{b_1}{a_1}$$

Using the reduction rules:

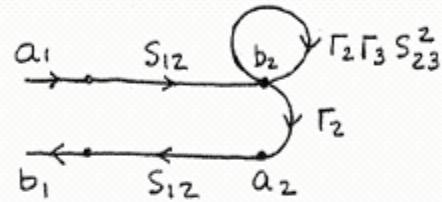
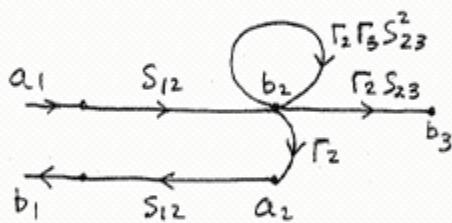
$$b_2 = a_1 \frac{S_{12}}{1 - \Gamma_2 \Gamma_3 S_{23}^2} \quad \checkmark$$



$$b_3 = a_2 \frac{\Gamma_2 \Gamma_3 S_{23}^2}{1 - \Gamma_2 \Gamma_3 S_{23}^2} \quad \checkmark$$

$$b_3 = b_2 \Gamma_2 S_{23}$$

Then,


$$\begin{aligned} \frac{P_2}{P_1} &= \frac{b_2^2 - a_2^2}{a_1^2 - b_1^2} = \frac{b_2^2 (1 - |\Gamma_2|^2)}{a_1^2 (1 - |\Gamma_{in}|^2)} = \frac{|S_{12}|^2 (1 - |\Gamma_2|^2)}{\left|1 - \Gamma_2 \Gamma_3 S_{23}^2\right|^2 \left(1 - \frac{|S_{12}|^2 |\Gamma_2|^2}{\left|1 - \Gamma_2 \Gamma_3 S_{23}^2\right|^2}\right)} \\ &= \frac{|S_{12}|^2 (1 - |\Gamma_2|^2)}{\left|1 - \Gamma_2 \Gamma_3 S_{23}^2\right|^2 - |S_{12}^2 \Gamma_2|^2} \quad \checkmark \end{aligned}$$

$$\begin{aligned} \frac{P_3}{P_1} &= \frac{b_3^2 - a_3^2}{a_1^2 - b_1^2} = \frac{b_3^2 (1 - |\Gamma_3|^2)}{a_1^2 (1 - |\Gamma_{in}|^2)} = \frac{|S_{12}|^2 |\Gamma_2 S_{23}|^2 (1 - |\Gamma_3|^2)}{\left|1 - \Gamma_2 \Gamma_3 S_{23}^2\right|^2 \left(1 - \frac{|S_{12}^2 \Gamma_2|^2}{\left|1 - \Gamma_2 \Gamma_3 S_{23}^2\right|^2}\right)} \\ &= \frac{|S_{12}|^2 |S_{23}|^2 |\Gamma_2|^2 (1 - |\Gamma_3|^2)}{\left|1 - \Gamma_2 \Gamma_3 S_{23}^2\right|^2 - |S_{12}^2 \Gamma_2|^2} \quad \checkmark \end{aligned}$$

(verified by direct calculation using S-parameters)

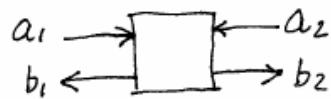4.29

$$\begin{bmatrix} a_1 \\ b_1 \end{bmatrix} = \begin{bmatrix} T_{11} & T_{12} \\ T_{21} & T_{22} \end{bmatrix} \begin{bmatrix} b_2 \\ a_2 \end{bmatrix}$$



$$\left. \begin{array}{l} a_1 = T_{11}b_2 + T_{12}a_2 \\ b_1 = T_{21}b_2 + T_{22}a_2 \end{array} \right\} \text{T-parameters}$$

$$\left. \begin{array}{l} b_1 = S_{11}a_1 + S_{12}a_2 \\ b_2 = S_{21}a_1 + S_{22}a_2 \end{array} \right\} \text{s-parameters}$$

$$T_{11} = \left. \frac{a_1}{b_2} \right|_{a_2=0} = 1/S_{21} \quad \checkmark$$

$$T_{12} = \left. \frac{a_1}{a_2} \right|_{b_2=0} = -S_{22}/S_{21} \quad \checkmark$$

$$T_{21} = \left. \frac{b_1}{b_2} \right|_{a_2=0} = S_{11}/S_{21} \quad \checkmark$$

$$\begin{aligned} T_{22} &= \left. \frac{b_1}{a_2} \right|_{b_2=0} = S_{11} \frac{a_1}{a_2} + S_{12} = S_{11} \left( \frac{-S_{22}}{S_{21}} \right) + S_{12} = S_{12} - S_{11} S_{22} / S_{21} \\ &= \frac{S_{12} S_{21} - S_{11} S_{22}}{S_{21}} \quad \checkmark \end{aligned}$$

**4.30**

$$Z_{oc} = -j Z_0 \cot \beta d \approx \frac{-j Z_0}{\beta d} = \frac{-j Z_0 C}{\omega \sqrt{\epsilon_r} d} = \frac{-j}{\omega C_f}$$

$$\therefore d \approx \frac{Z_{oc} C_f}{\omega \sqrt{\epsilon_r}} \quad (\text{agrees with T. Edwards, p. 123})$$

For  $C_f = 0.075 \mu F$ ,  $\epsilon_r = 1.894$ ,  $Z_0 = 50 \Omega$ ,

this gives  $d = 0.082 \text{ cm}$

(Using  $\epsilon_r = 2.2$ ,  $d = 0.158 \text{ cm}$ ,  $W = 0.487 \text{ cm}$ )

The Hammerstad & Bekkadal approximation gives

$$d = 0.412d \left( \frac{\epsilon_r + 3}{\epsilon_r - 2.58} \right) \frac{\sqrt{W + .262d}}{W + .813d} = 0.075 \text{ cm}$$

**4.31**

The complex reflected power can be computed using

(4.88):

$$\begin{aligned} P_r &= \int_s \bar{E}^r \times \bar{H}^{r*} \cdot \hat{z} ds = - \int_{x=0}^a \int_{y=0}^b E_y^r H_x^{r*} dx dy \\ &= -b \int_{x=0}^a \left[ \sum_n A_n \sin \frac{n\pi x}{a} e^{j\beta_n^a z} \right] \left[ \sum_m \frac{A_m^*}{Z_m^{a*}} \sin \frac{m\pi x}{a} e^{-j\beta_m^{a*} z} \right] dx \\ &= -\frac{ab}{2} \sum_{n=1}^{\infty} \frac{|A_n|^2}{Z_n^{a*}} e^{j(\beta_n^a - \beta_n^{a*}) z} \end{aligned}$$

The only propagating mode is the  $n=1$  ( $TE_{10}$ ) mode, so  $\beta_1^a$  is real, and  $\beta_n^a$  is imaginary for  $n>1$ . Let  $\alpha_n = j\beta_n = \sqrt{(n\pi/a)^2 - k_0^2}$  for  $n>1$ . Then  $Z_1^a = k_0 \eta_0 / \beta_1^a$ , and  $Z_n^a = k_0 \eta_0 / \beta_n^a = j k_0 \eta_0 / \alpha_n$  for  $n>1$ .

Then  $P_r = -\frac{ab}{2} \left[ \frac{|A_1|^2 \beta_1^a}{k_0 \eta_0} - j \sum_{n=2}^{\infty} \frac{|A_n|^2 \alpha_n}{k_0 \eta_0} e^{2\alpha_n z} \right]$  for  $z < 0$ .

So we see that  $\operatorname{Im}\{P_r\} > 0$ , indicating an inductive load.

4.32

This solution is essentially the same as the analysis in Section 4.6. Let  $d = (a-c)/2$

$$E_y^i = \sin \frac{\pi x}{a} e^{-j\beta_i^a z}$$

$$H_x^i = \frac{-1}{z_i^a} \sin \frac{\pi x}{a} e^{-j\beta_i^a z}$$

$$E_y^r = \sum_{n=1}^{\infty} A_n \sin \frac{n\pi x}{a} e^{j\beta_n^a z}$$

odd

$$H_x^r = \sum_{n=1}^{\infty} \frac{A_n}{z_n^a} \sin \frac{n\pi x}{a} e^{j\beta_n^a z}$$

odd

$$E_y^t = \sum_{n=1}^{\infty} B_n \sin \frac{n\pi}{c} (x-d) e^{-j\beta_n^c z}$$

odd

$$H_x^t = - \sum_{n=1}^{\infty} \frac{B_n}{z_n^c} \sin \frac{n\pi}{c} (x-d) e^{-j\beta_n^c z}$$

$$\text{where } \beta_n^a = \sqrt{k_0^2 - (n\pi/a)^2}, \quad \beta_n^c = \sqrt{k_0^2 - (n\pi/c)^2}$$

The solution has the same form as (4.97):

$$\frac{a}{2} A_m + \sum_{n=1}^{\infty} \sum_{k=1}^{\infty} \frac{2 z_k^c I_{km} I_{kn}}{c z_n^a} A_n = \sum_{k=1}^{\infty} \frac{2 z_k^c I_{km} I_{k1}}{c z_1^a} - \frac{a}{2} S_{m1}$$

for  $m = 1, 3, 5, \dots$ ,

and,

$$I_{mn} = \int_{x=d}^{d+c} \sin \frac{m\pi}{c} (x-d) \sin \frac{n\pi x}{a} dx$$

$$S_{mn} = \begin{cases} 1 & \text{for } m=n \\ 0 & \text{for } m \neq n \end{cases}$$

4.33

From (4.110) the source current is,

$$\bar{J}_s = \hat{x} \frac{2B^+ m\pi}{a} \cos \frac{m\pi x}{a} \sin \frac{n\pi y}{b} + \hat{y} \frac{2B^+ n\pi}{b} \sin \frac{m\pi x}{a} \cos \frac{n\pi y}{b}$$

From Table 3.2, the transverse fields for  $\pm$  traveling TM<sub>mn</sub> modes are,

$$E_x = \frac{\mp j\beta m\pi}{k_c^2 a} C^\pm \cos \frac{m\pi x}{a} \sin \frac{n\pi y}{b} e^{\mp j\beta z}$$

$$E_y = \frac{\mp j\beta n\pi}{k_c^2 b} C^\pm \sin \frac{m\pi x}{a} \cos \frac{n\pi y}{b} e^{\mp j\beta z}$$

$$H_x = \frac{j\omega \epsilon m\pi}{k_c^2 b} C^\pm \sin \frac{m\pi x}{a} \cos \frac{n\pi y}{b} e^{\mp j\beta z}$$

$$H_y = \frac{-j\omega \epsilon n\pi}{k_c^2 a} C^\pm \cos \frac{m\pi x}{a} \sin \frac{n\pi y}{b} e^{\mp j\beta z}$$

where  $C^\pm$  are the unknown amplitudes. At  $z=0$ ,  $E_t$  is continuous, so  $C^+ = -C^-$ . Also,  $\hat{z} \times (\bar{H}^+ - \bar{H}^-) = \bar{J}_s$ , or  $H_y^+ - H_y^- = J_{sy}$  and  $-H_x^+ + H_x^- = J_{sx}$ . So,

$$J_{sx}: \quad \frac{-j\omega \epsilon m\pi}{k_c^2 a} (C^+ - C^-) = 2B^+ \frac{m\pi}{a} \Rightarrow C^+ - C^- = \frac{k_c^2 B^+}{-j\omega \epsilon}$$

$$J_{sy}: \quad \frac{j\omega \epsilon n\pi}{k_c^2 b} (-C^+ + C^-) = 2B^+ \frac{n\pi}{b} \Rightarrow C^+ - C^- = \frac{k_c^2 B^+}{j\omega \epsilon} \quad \checkmark$$

Since these fields satisfy Maxwell's equations and the boundary conditions, they must form the unique solution.

4.34

Following Example 4.8:

$$\bar{I}(x, y, z) = I(y) \delta(x - a/2) \delta(z) \quad \text{for } 0 < y < d.$$

$$\bar{e}_1 = \hat{y} \sin \frac{\pi x}{a}, \quad \bar{h}_1 = \frac{-\hat{x}}{z_1} \sin \frac{\pi x}{a}, \quad Z_1 = k_0 N_0 / \beta_1$$

From (4.119),

$$P_1 = \frac{ab}{Z_1}$$

From (4.118),

$$\begin{aligned} A_{i^+} &= \frac{-1}{P_1} \int_v \sin \frac{\pi x}{a} e^{j\frac{B_1}{k} z} I(y) \delta(x - a/2) \delta(z) dx dy dz \\ &= \frac{-I_0}{P_1} \int_{y=0}^d \frac{\sin k(d-y)}{\sin k d} dy = \frac{-I_0}{P_1 \sin k d} \int_0^d \sin k w dw \\ &\quad (\text{let } w = d-y) \\ &= \frac{I_0 Z_1 (\cos kd - 1)}{kab \sin kd} \end{aligned}$$

The total power flow in the TE<sub>10</sub> mode is,

$$P = \frac{ab |A_{i^+}|^2}{2Z_1},$$

for both + and - traveling waves, since  $|A_{i^+}| = |A_{i^-}|$ .

Then the radiation resistance is,

$$R_{in} = \frac{2P}{I_0^2} = \frac{ab |A_{i^+}|^2}{I_0^2 Z_1} = \frac{Z_1}{ab} \frac{(1 - \cos kd)^2}{k^2 \sin^2 kd}.$$

$$= \frac{Z_1}{k^2 ab} \frac{(2 \sin^2 \frac{kd}{2})^2}{4 \sin^2 \frac{kd}{2} \cos^2 \frac{kd}{2}} = \frac{Z_1}{k^2 ab} \tan^2 \frac{kd}{2} \quad \checkmark$$

4.35

Following Example 4.8:

$$\bar{J}(x, y, z) = I \delta(z) [\delta(x - a/4) - \delta(x - 3a/4)] \hat{y} \quad \text{for } 0 < y < b$$

From Table 3.2,

$$TE_{10}: \bar{E}_1 = \hat{y} \sin \frac{\pi x}{a} \quad \bar{h}_1 = -\frac{\hat{x}}{z_1} \sin \frac{\pi x}{a} \quad z_1 = k_0 n_0 / \beta_1$$

$$TE_{20}: \bar{E}_2 = \hat{y} \sin \frac{2\pi x}{a} \quad \bar{h}_2 = -\frac{\hat{x}}{z_2} \sin \frac{2\pi x}{a} \quad z_2 = k_0 n_0 / \beta_2$$

$$P_1 = ab/z_1 \quad \beta_1 = \sqrt{k_0^2 - (\pi/a)^2}$$

$$P_2 = ab/z_2 \quad \beta_2 = \sqrt{k_0^2 - (2\pi/a)^2}$$

From (4.118):


$$A_1^+ = \frac{-I}{P_1} \int_v \bar{E}_1^- \cdot \bar{J} dv = -\frac{Ib}{P_1} (\sin \frac{\pi}{4} - \sin \frac{3\pi}{4}) = 0 \quad \checkmark$$

$$A_2^+ = \frac{-I}{P_2} \int_v \bar{E}_2^- \cdot \bar{J} dv = -\frac{Ib}{P_2} (\sin \frac{\pi}{2} - \sin \frac{3\pi}{2}) = -\frac{2Ib}{a}$$

Since the excitation has an odd symmetry about the center of the guide, it will only excite modes that have an electric field with an odd symmetry about  $x=a/2$ . This implies the  $TE_{m0}$  modes, for  $m$  even, will be excited. The  $TE_{10}$  mode is not excited.

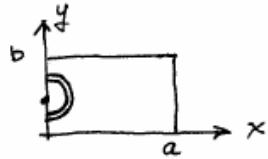**4.36** By image theory, the half-loop on the side wall can be replaced with a full loop without the wall. For a small loop, the equivalent magnetic dipole moment is,

$$\bar{P}_m = \frac{j}{8} I_0 \pi R_0^2 \delta(x) \delta(y - b/2) \delta(z)$$



$$\begin{aligned}\bar{M} &= j\omega\mu_0 \bar{P}_m \\ &= \frac{j}{8} j\omega\mu_0 I_0 \pi R_0^2 \delta(x) \delta(y - b/2) \delta(z) \text{ V/m}^2\end{aligned}$$

For the TE<sub>10</sub> mode,

$$\bar{e}_1 = \hat{y} \sin \frac{\pi x}{a}$$

$$\bar{h}_1 = -\frac{\hat{x}}{z_1} \sin \frac{\pi x}{a}$$

$$h_{z1} = \frac{j\pi}{k_0 \eta_0 a} \cos \frac{\pi x}{a}$$

where  $z_1 = k_0 \eta_0 / \beta_1$ ,  $\beta_1 = ab/z_1$ ,

From (4.128),

$$A_1^+ = \frac{1}{\beta_1} \int_v (-\bar{h}_1 + \hat{z} h_{z1}) \cdot \bar{M} e^{j\beta_1 z} dv$$

$$= \frac{z_1}{ab} \int_v h_{z1} M dv = \frac{-\pi^2 z_1 I_0 R_0^2}{a^2 b} = A_1^-$$

These results are for a full loop - reduce by  $\frac{1}{2}$  for half-loop.

4.37

FIRST SOLUTION: (all fields and currents are  $TE_{10}$ )

$$E_y = B \sin \frac{\pi x}{a} [e^{-j\beta z} - e^{j\beta z}] = -2jB \sin \frac{\pi x}{a} \sin \beta z \quad 0 < z < d$$

$$H_x = \frac{B}{Z_1} \sin \frac{\pi x}{a} [-e^{-j\beta z} - e^{j\beta z}] = -\frac{2B}{Z_1} \sin \frac{\pi x}{a} \cos \beta z \quad 0 < z < d$$

This satisfies  $E_y = 0$  at  $z = 0$ .

$$E_y = C \sin \frac{\pi x}{a} e^{-j\beta(z-d)} \quad z > d$$

$$H_x = \frac{C}{Z_1} \sin \frac{\pi x}{a} e^{-j\beta(z-d)} \quad z > d$$

at  $z = d$ ,  $E_y$  is continuous, so

$$-2jB \sin \beta d = C$$

at  $z = d$ ,  $\hat{z} \times (\bar{H}^+ - \bar{H}^-) = \bar{J}_s$ , or

$$\frac{C}{Z_1} + \frac{2B}{Z_1} \cos \beta d = \frac{2\pi A}{a}$$

Solving for  $B, C$ :

$$B = \frac{\pi Z_1 A}{a} e^{-j\beta d}, \quad C = \frac{\pi Z_1 A}{a} (e^{-2j\beta d} - 1)$$

SECOND SOLUTION: (Using (4.105) and (4.106b)):

$E_y$  due to  $J_{sy}$  at  $z = d$ :

$$E_y^\pm = \frac{-\pi Z_1 A}{a} \sin \frac{\pi x}{a} e^{\mp j\beta(z-d)}$$

$E_y$  due to  $-J_{sy}$  at  $z = -d$ :

$$E_y^\pm = \frac{\pi Z_1 A}{a} \sin \frac{\pi x}{a} e^{\mp j\beta(z+d)}$$

For  $0 < z < d$ ,

$$E_y = \frac{\pi Z_1 A}{a} \sin \frac{\pi x}{a} [e^{-j\beta(z+d)} - e^{j\beta(z-d)}] = \frac{-2j\pi Z_1 A}{a} e^{-j\beta d} \sin \frac{\pi x}{a} \sin \beta z \quad \checkmark$$

For  $z > d$ ,

$$E_y = \frac{\pi Z_1 A}{a} \sin \frac{\pi x}{a} [e^{-j\beta(z+d)} - e^{-j\beta(z-d)}] = \frac{-2j\pi Z_1 A}{a} \sin \beta d \sin \frac{\pi x}{a} e^{-j\beta z} \quad \checkmark$$

These results agree with those from the first solution.

## Chapter 5


**5.1**

a)  $Z_L = 150 - j200 \Omega$

$\beta_L = 1.5 - j2$  inside  $1+jx$  circle

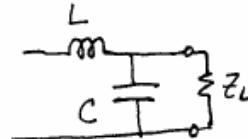
#1  $b_1 = 0.107 \Rightarrow C = \frac{b}{2\pi f Z_0} = 0.0568 \mu F \checkmark$

$$\chi_1 = 1.78 \Rightarrow L = \frac{\chi Z_0}{2\pi f} = 9.44 \mu H \checkmark$$


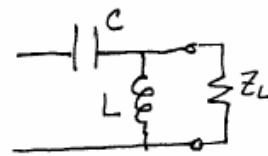
#2  $b_2 = -0.747 \Rightarrow L = \frac{-Z_0}{2\pi f b} = 7.10 \mu H \checkmark$

$$\chi_2 = -1.78 \Rightarrow C = \frac{-1}{2\pi f \chi Z_0} = 0.298 \mu F \checkmark$$




b)  $Z_L = 20 - j90 \Omega$

$\beta_L = 0.2 - j1.9$  outside  $1+jx$  circle

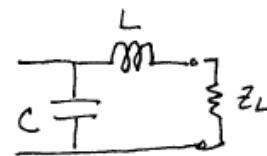
#1  $\chi_1 = 1.30 \Rightarrow L = \frac{\chi Z_0}{2\pi f} = 6.90 \mu H \checkmark$

$$b_1 = 2.00 \Rightarrow C = \frac{b}{2\pi f Z_0} = 1.06 \mu F \checkmark$$


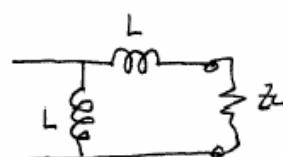
#2  $\chi_2 = 0.5 \Rightarrow L = \frac{-Z_0}{2\pi f} = 2.65 \mu H \checkmark$

$$b_2 = -2.00 \Rightarrow L = \frac{-Z_0}{2\pi f b} = 2.65 \mu H \checkmark$$



verified w/ PCTAD 7.0

**5.2****5.3** Analytical Solutions:

$$\text{From (5.9), } t = \frac{80 \pm \sqrt{100[(75-100)^2 + (80)^2]}/75}{100-75} = 3.2 \pm 3.87j$$

$$t_1 = 7.07j, \quad t_2 = -0.67j$$

From (5.10) the possible stub positions are,

$$d_1 = \frac{\lambda}{2\pi} \tan^{-1} t_1 = 0.2276 \lambda$$

$$d_2 = \frac{\lambda}{2\pi} (\pi + \tan^{-1} t_2) = 0.4059 \lambda$$

From (5.8b) the required stub susceptances are,

$$B = \frac{R_L^2 t - (Z_0 - X_L t)(X_L + Z_0 t)}{Z_0 [R_L^2 + (X_L + Z_0 t)^2]}$$

$$B_1 = 0.0129, \quad B_2 = -0.0129$$

From (5.11a) the o.c. stub lengths are,

$$l_1 = \frac{-\lambda}{2\pi} \tan^{-1}(B_1 Z_0) = 0.3776 \lambda \quad (\lambda/2 added to get l_1 > 0)$$

$$l_2 = \frac{-\lambda}{2\pi} \tan^{-1}(B_2 Z_0) = 0.1224 \lambda$$

**5.4**

Use  $B_1, B_2$  from Problem 5.3 with (5.11b) :

$$l_1 = \frac{\lambda}{2\pi} \tan^{-1} \frac{1}{Z_0 B_1} = 0.1276 \lambda \checkmark$$

$$l_2 = \frac{\lambda}{2\pi} \tan^{-1} \frac{1}{Z_0 B_2} = 0.3724 \lambda \checkmark \quad (\lambda/2 \text{ added to get } l_2 > 0)$$

**5.5**

Smith chart solutions :

The normalized load impedance is  $\bar{z}_L = 1.2 + j0.8$

The stub positions and required reactances are,

$$d_1 = 0.346 - 0.172 = 0.174 \lambda \checkmark, \quad x_1 = +j0.753$$

$$d_2 = (.5 - .172) + 0.153 = 0.481 \lambda \checkmark, \quad x_2 = -j0.753$$

open ckt stub lengths are,

$$l_1 = .25 + .103 = 0.353 \lambda \checkmark$$

$$l_2 = .397 - .25 = 0.147 \lambda \checkmark$$

verified w/ PCAAID 7.0


**5.6**

The required stub lengths for s.c. stubs are  $\lambda/4$  longer (or shorter) than the o.c. stub lengths :

$$l_1 = .353 - .25 = 0.103 \lambda \checkmark$$

$$l_2 = .147 + .25 = 0.397 \lambda \checkmark$$

5.7

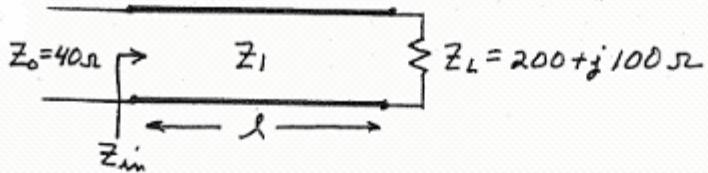

To match this load, we must find  $Z_1$  and  $l$  so that  $Z_{in} = Z_0 = 40 \Omega$ :

$$Z_{in} = 40 = Z_1 \frac{(200 + j100) + jZ_1 t}{Z_1 + j(200 + j100)t}, \text{ with } t = \tan \beta l.$$

$$(40Z_1 - 4000t) + j8000t = 200Z_1 + j(100 + Z_1 t)Z_1,$$

Equating real and imaginary parts gives two equations for the two unknowns,  $Z_1$  and  $t$ : (if they exist!)

$$\text{Re: } 40Z_1 - 4000t = 200Z_1 \Rightarrow Z_1 = -25t$$

$$\text{Im: } 8000t = Z_1(100 + Z_1 t)$$

$$8000t = -25t(100 - 25t^2)$$

$$t = \pm \sqrt{16.8} = \pm 4.10 \quad (\text{use } -4.10 \text{ so that } Z_1 > 0) \checkmark$$

$$\text{Then, } \beta l = \tan^{-1}(-4.10) = -76.3^\circ \equiv 104^\circ \Rightarrow l = 0.288\lambda$$

The characteristic impedance is then,

$$Z_1 = -25(-4.10) = 102.5 \Omega \checkmark$$

(Note: Not all load impedances can be matched in this way - a good exam problem to determine which impedances can be matched using this technique!)

**5.8** From (2.91) the impedance of a terminated lossy line is,

$$Z_{in} = Z_0 \frac{Z_L + Z_0 \tanh \gamma l}{Z_0 + Z_L \tanh \gamma l}, \quad \gamma l = \alpha l + j\beta l$$

For  $Z_L = \infty$  (o.c.), the normalized input admittance is,

$$Y_{in} = \tanh \gamma l = \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tanh \alpha l \tan \beta l}$$

The normalized input susceptance is,

$$B_{in} = \frac{\tan \beta l (1 - \tanh^2 \alpha l)}{1 + \tanh^2 \alpha l \tan^2 \beta l} \quad (\text{at this point, we could find max. } B_{in} \text{ by calculating } B_{in} \text{ vs. } l)$$

Since maximum susceptance for a lossless line is obtained for  $\beta l = \pi/2$ , we expect  $\beta l$  to be close to  $\pi/2$  for the lossy case. So let  $\beta l = \pi/2 + \Delta$ , where  $\Delta$  is small. Also,  $\alpha l$  is small, so we have  $\tanh \alpha l \approx \alpha l$ , and  $\tan \beta l = -\cot \Delta \approx -1/\Delta$ .

Then,

$$B_{in} \approx \frac{-\frac{1}{\Delta} (1 - \alpha^2 l^2)}{1 + \alpha^2 l^2 / \Delta^2} \approx \frac{-1}{\Delta + \alpha^2 l^2 / \Delta}$$

To maximize  $B_{in}$ , we can minimize  $\Delta + \alpha^2 l^2 / \Delta$  with respect to  $l$ :

$$\frac{d}{dl} (\Delta + \alpha^2 l^2 / \Delta) = \frac{d\Delta}{dl} + \frac{2\alpha^2 l}{\Delta} + \alpha^2 l^2 \left( \frac{-1}{\Delta^2} \right) \frac{d\Delta}{dl} = 0$$

or, since  $\frac{d\Delta}{dl} = \beta$ ,

$$\beta + \frac{2\alpha^2 l}{\Delta} - \frac{\alpha^2 l^2}{\Delta^2} \beta = 0$$

since  $\Delta = \beta l - \pi/2$ , we have,

$$l^2 \beta (\alpha^2 + \beta^2) - \pi l (\alpha^2 + \beta^2) + \beta \frac{\pi^2}{4} = 0$$

Solve for  $l$ :

$$l = \frac{\pi(\alpha^2 + \beta^2) \pm \sqrt{\pi^2(\alpha^2 + \beta^2)^2 - \beta^2\pi^2(\alpha^2 + \beta^2)}}{2\beta(\alpha^2 + \beta^2)}$$

$$= \frac{\pi}{2\beta} \pm \frac{\pi\alpha}{2\beta\sqrt{\alpha^2 + \beta^2}} \approx \frac{\pi}{2\beta} \pm \frac{\pi\alpha}{2\beta^2} \quad (\text{since } \alpha^2 \ll \beta^2)$$

Then,

$$\Delta = \beta l - \pi/2 \approx \frac{\pi\alpha}{2\beta} \approx \alpha l \quad (\text{since } \beta \approx \pi/2l)$$

The corresponding value of  $b_{in}$  is,

$$b_{in}^{MAX} = \frac{\pm 1}{\alpha l + \alpha l} = \frac{\pm 1}{2\alpha l} = \frac{\pm 2}{\alpha \lambda} \quad (\text{since } l \approx \lambda/4)$$

$$\text{For } \alpha = 0.01 \text{ neper}/\lambda, \quad b_{in}^{MAX} = \frac{\pm 2}{0.01} = \underline{\pm 200}$$

(This checks with direct calculation of  $y_{in}$  vs.  $l$ .)

The reactance of a short-circuited line is the dual case of the above problem, so  $x_{in}^{MAX} = \pm 200$ .

**5.9 Smith chart solution:**

1. plot  $y_L = 0.4 + j1.2$  on admittance chart
2. plot rotated  $1+jb$  circle
3. add a stub susceptance of  $j0.6$  or  $-j1.0$  to move to rotated  $1+jb$  circle
4. move  $\lambda/8$  toward generator, to  $1+jb$  circle
5. add a stub susceptance of  $+j3.0$  or  $-j1.0$  to move to center of chart.
6. the O.C. stub lengths are,

$$l_1 = 0.086\lambda \quad \text{or} \quad l_1 = 0.375\lambda$$

$$l_2 = 0.198\lambda \quad \text{or} \quad l_2 = 0.375\lambda$$

(see attached Smith chart for first solution)


Analytic solution:  $t = \tan \beta d = 1$

$$b_1 = -b_L + 1 \pm \sqrt{2g_L - g_L^2} = 0.6, -1.0$$

$$b_2 = \frac{1}{g_L} \left[ \pm \sqrt{2g_L - g_L^2} + g_L \right] = 3.0, -1.0$$

$$l_1 = \frac{\lambda}{2\pi} \tan^{-1} b_1 = 0.086\lambda \quad \text{or} \quad l_1 = 0.375\lambda$$
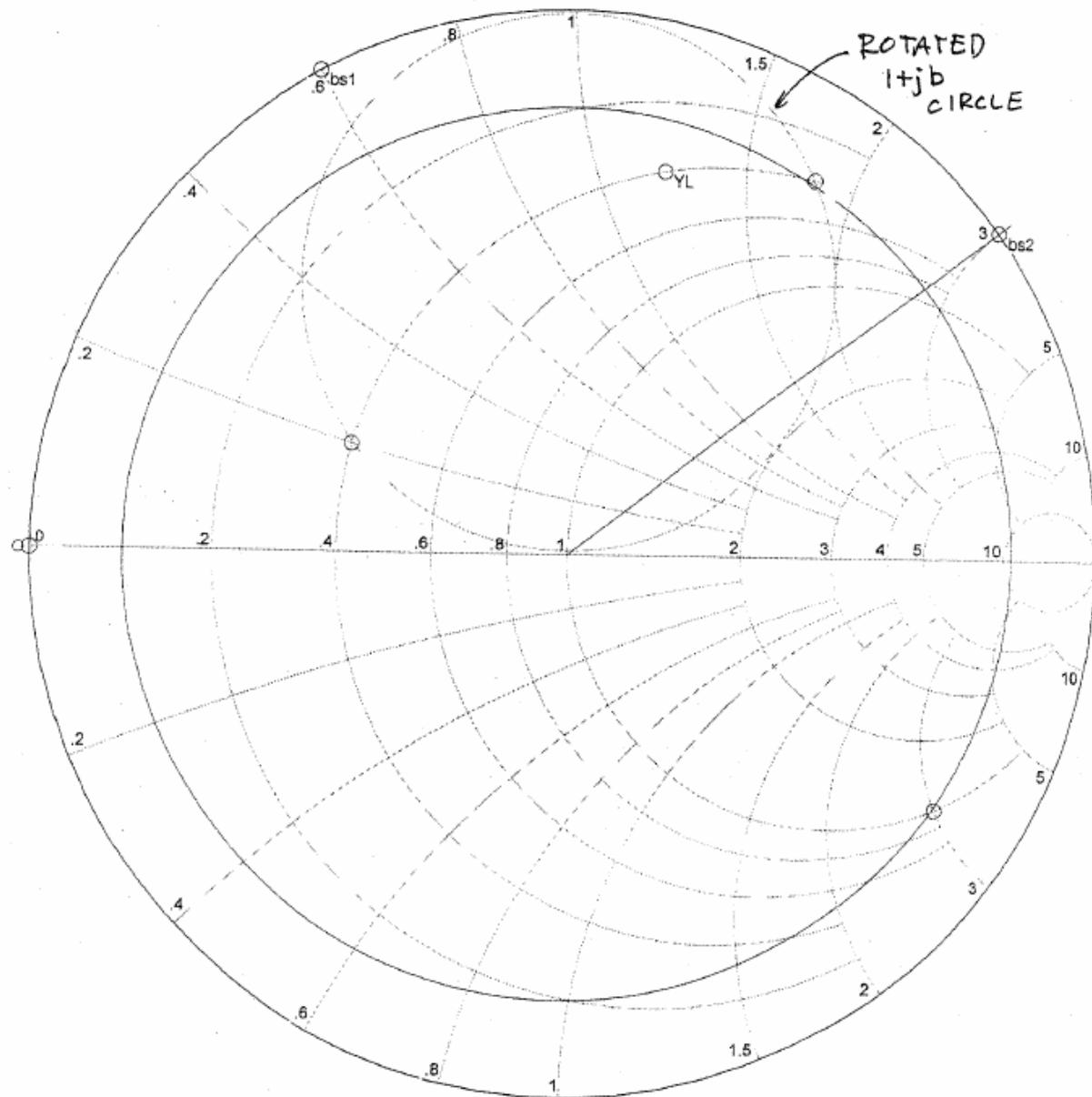
$$l_2 = \frac{\lambda}{2\pi} \tan^{-1} b_2 = 0.198\lambda \quad \text{or} \quad l_2 = 0.375\lambda$$



Smith chart for P. 5.9 (#1)

**5.10** Analytic Solution : let  $t = \tan \beta d = \tan 135^\circ = -1.0$

From (5.22) the first stub susceptance is

$$b_1 = -b_L + \frac{1 \pm \sqrt{(1+t^2)g_L - g_L^2 t^2}}{t} = -3 \text{ or } -1.4 \quad \checkmark$$

From (5.23) the second stub susceptance is


$$b_2 = \frac{\pm \sqrt{(1+t^2)g_L - g_L^2 t^2} + g_L}{g_L t} = -3 \text{ or } 1.0 \quad \checkmark$$

The S.C. stub lengths are, from (5.24b),

$$l_1 = 0.051\lambda \text{ or } 0.0987\lambda$$

$$l_2 = 0.051\lambda \text{ or } 0.375\lambda$$

**5.11**

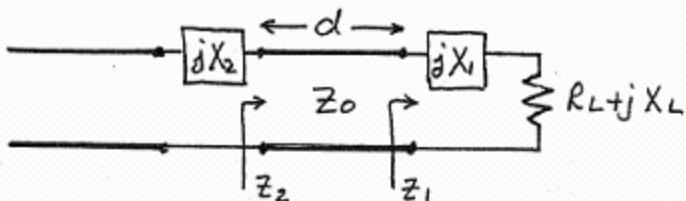

$$Z_1 = R_L + j(X_L + X_1)$$

$$Z_2 = Z_0 \frac{R_L + j(X_L + X_1 + Z_0 t)}{Z_0 + j t (R_L + j X_L + j X_1)} = Z_0 \quad t = \tan \beta d$$

Solving for  $R_L$ :

$$R_L = Z_0 \frac{1+t^2}{2t^2} \left[ 1 \pm \sqrt{\frac{1-4t^2(Z_0-X_L t-X_1 t)^2}{Z_0(1+t^2)^2}} \right]$$

So we must have,

$$0 \leq R_L \leq Z_0 \frac{1+t^2}{2t^2} = \frac{Z_0}{\sin^2 \beta d}$$

The first stub reactance is,

$$X_1 = -X_L + \frac{Z_0 \pm \sqrt{(1+t^2)R_L Z_0 - R_L^2 t^2}}{t}$$

The second stub reactance is,

$$X_2 = \frac{\pm Z_0 \sqrt{Z_0 R_L (1+t^2) - R_L^2 t^2} + R_L Z_0}{R_L t}$$

The stub lengths are given by,

$$l_{oc} = \frac{1}{2\pi} \tan^{-1} \left( \frac{Z_0}{X} \right) \quad , \quad l_{sc} = \frac{1}{2\pi} \tan^{-1} \left( \frac{X}{Z_0} \right)$$

5.12

Using the Smith chart ( $Z_0 = 100 \Omega$ )


a) A single short-circuited shunt stub:

at  $f_0$ ,  $d_1 = 0.152\lambda$  ✓  $d_2 = 0.348\lambda$  ✓

$b_1 = -0.7$        $b_2 = +0.7$

$l_1 = 0.153\lambda$  ✓  $l_2 = 0.347\lambda$  ✓

$|\Gamma_1| = 0$        $|\Gamma_2| = 0$

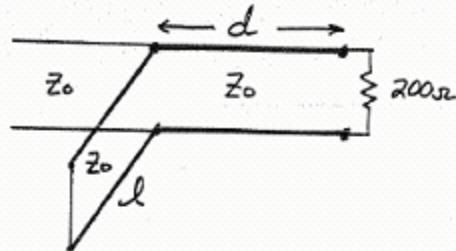


b) A single short-circuited series stub:

at  $f_0$ ,  $d_1 = 0.098\lambda$  ✓  $d_2 = 0.402\lambda$  ✓

$X_1 = 0.7$        $X_2 = -0.7$

$l_1 = 0.097\lambda$  ✓  $l_2 = 0.403\lambda$  ✓

$|\Gamma_1| = 0$        $|\Gamma_2| = 0$

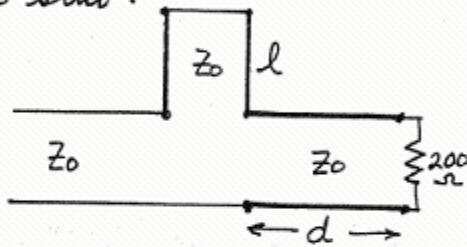c) a double short-circuited shunt stub: (let  $d = \lambda/8$ )at  $f_0$ ,


$b_1 = 0.14$        $b'_1 = 1.85$

$l_1 = 0.272\lambda$  ✓       $l'_1 = 0.421\lambda$  ✓



$b_2 = -0.73$        $b'_2 = 2.75$

$l_2 = 0.15\lambda$  ✓       $l'_2 = 0.444\lambda$  ✓

$|\Gamma| = 0$        $|\Gamma'| = 0$

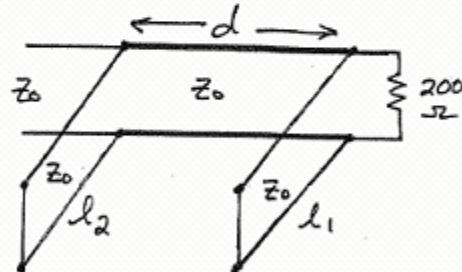

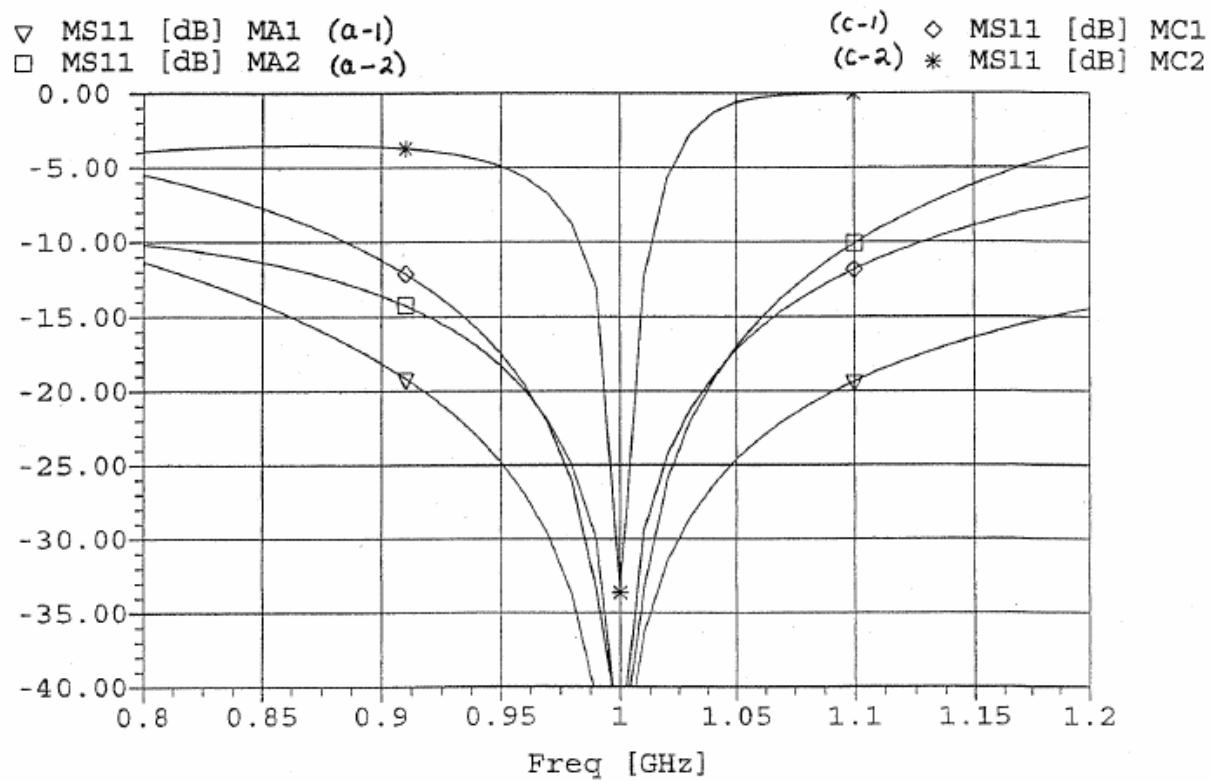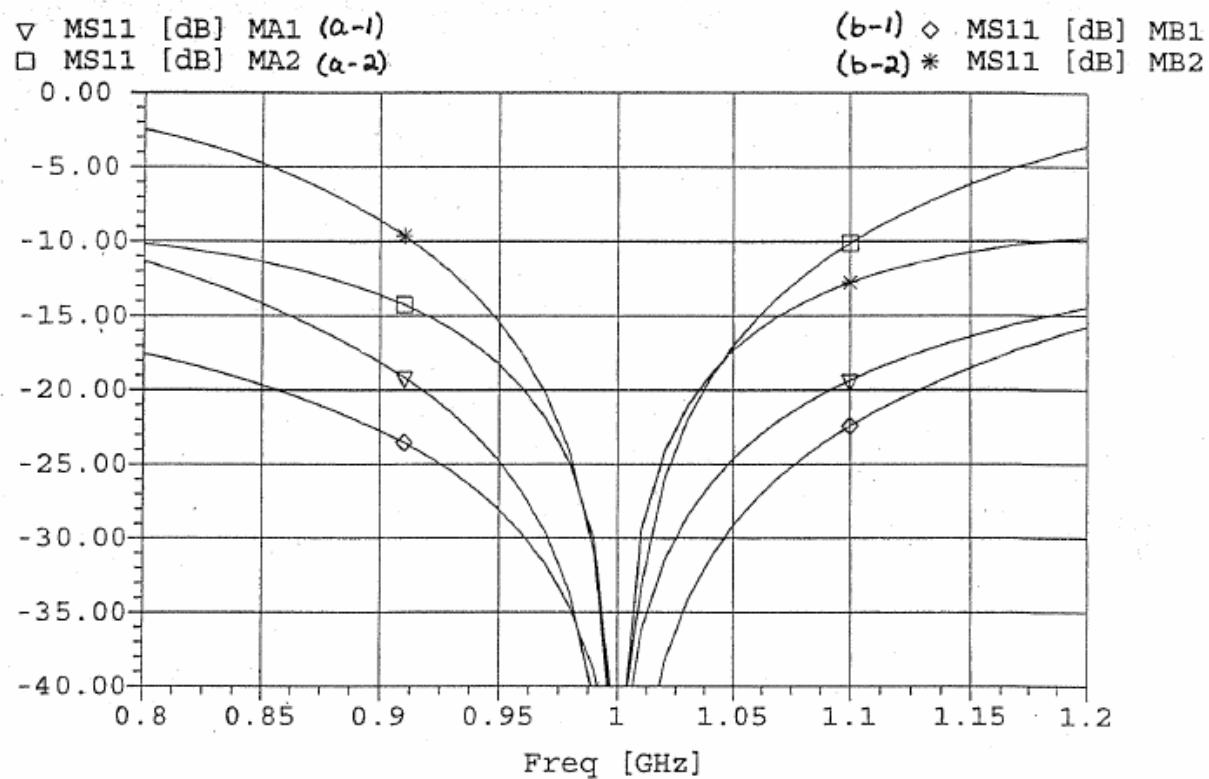Plots of return loss vs.  $f/f_0$  for these six solutions are shown on the following page. (only 4 curves could be plotted per graph). These results show that the tuner of solution (b-1), the series stub tuner, gives the best bandwidth. This is probably because the stub length and line length are shortest for this case, giving the smallest frequency variation.



**5.13**

An SWR of 2 corresponds to a reflection coefficient magnitude of,

$$\Gamma_m = \frac{s-1}{s+1} = \frac{1}{3}$$


Then from (5.33) the bandwidth is,

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[ \frac{\Gamma_m}{\sqrt{1-\Gamma_m^2}} \frac{2\sqrt{Z_0 Z_L}}{|Z_L - Z_0|} \right] = 71\%$$

MICROSTRIP LAYOUT:

$$\epsilon_r = 2.2, d = 0.159 \text{ cm}, f = 4 \text{ GHz}$$

First try  $w/d < 2$ :

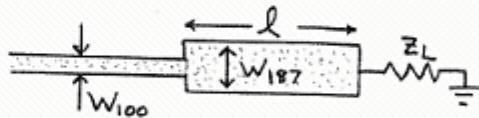

for  $w_{100}$ ,  $A_{100} = 2.213$ ,  $w_{100}/d = 0.896 < 2$  (OK),  $w_{100} = 0.142 \text{ cm}$

for  $w_{187}$ ,  $A_{187} = 4.047$ ,  $w_{187}/d = 0.140 < 2$  (OK),  $w_{187} = 0.022 \text{ cm}$

From (3.195),  $\epsilon_e$  for  $w_{187}$  is  $\epsilon_e = 1.66$ .

Then the physical length of the  $\lambda/4$  transformer is,

$$l = \frac{\lambda_g}{4} = \frac{c}{4\sqrt{\epsilon_e} f} = 1.455 \text{ cm} \checkmark$$


**5.14**

From (5.34) and (5.36), the partial reflection coefficients are,

$$\Gamma_1 = \frac{Z_2 - Z_1}{Z_2 + Z_1} = \frac{150 - 100}{150 + 100} = 0.2 ; \quad \Gamma_3 = \frac{Z_L - Z_2}{Z_L + Z_2} = \frac{225 - 150}{225 + 150} = 0.2$$

Since the approximate expression for  $\Gamma$  in (5.42) is identical to the numerator for the exact expression in (5.41), the greatest error will occur when the denominator of (5.41) departs from unity to the greatest extent. This occurs for  $\theta = 0$  or  $180^\circ$ . Then (5.41) gives the exact  $\Gamma$  as 0.384, while (5.42) gives the approximate  $\Gamma = 0.4$ . Thus the error is about 4%.

5.15

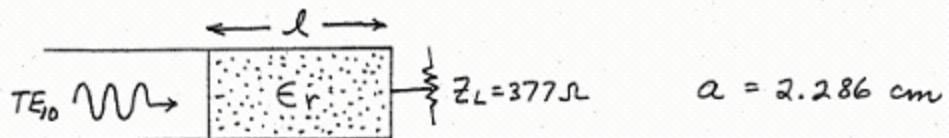

$$k_0 = \frac{2\pi f}{c} = 209.4 \text{ m}^{-1}$$

In the air-filled guide,

$$\beta_a = \sqrt{k_0^2 - (\pi/a)^2} = 158.0 \text{ m}^{-1}$$

$$Z_a = \frac{k_0 \eta_0}{\beta_a} = \frac{(209.4)(377)}{158} = 499.6 \Omega$$

So the matching section impedance must be,

$$Z_m = \sqrt{Z_a Z_L} = \sqrt{(499.6)(377)} = 434.0 \Omega$$

$$= \frac{k_m \eta_m}{\beta_m} = \frac{k_0 \eta_0}{\beta_m}$$

so the propagation constant of the matching section must be,

$$\beta_m = \frac{k_0 \eta_0}{Z_m} = \frac{(209.4)(377)}{434} = 181.9 \text{ m}^{-1}$$

$$= \sqrt{\epsilon_r k_0^2 - (\pi/a)^2}$$

Solving for  $\epsilon_r$ :


$$\epsilon_r = \frac{\beta_m^2 + (\pi/0.2286)^2}{(209.4)^2} = 1.185$$

The physical length of the matching section is,

$$l = \frac{\lambda_g}{4} = \frac{2\pi}{4\beta_m} = \frac{\pi}{2\beta_m} = 0.86 \text{ cm}$$

(Note that this type of matching is not possible if  $Z_L > Z_a$ .)

5.16

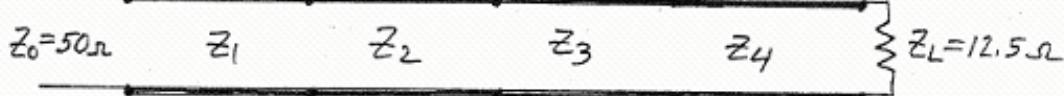

a) Using (5.53):

$$n=0: \ln z_1/z_0 = 2^{-4} C_0^4 \ln 12.5/50 \Rightarrow z_1 = 45.85 \Omega$$

$$n=1: \ln z_2/z_1 = 2^{-4} C_1^4 \ln 12.5/50 \Rightarrow z_2 = 32.42 \Omega$$

$$n=2: \ln z_3/z_2 = 2^{-4} C_2^4 \ln 12.5/50 \Rightarrow z_3 = 19.28 \Omega$$

$$n=3: \ln z_4/z_3 = 2^{-4} C_3^4 \ln 12.5/50 \Rightarrow z_4 = 13.63 \Omega$$

$$\text{Check: } n=4: \ln z_5/z_4 = 2^{-4} C_4^4 \ln 12.5/50 \Rightarrow z_5 = 12.50 \Omega = z_L \checkmark$$

Can also check with data in Table 5.1, Using  $z_4/z_0 = 4$ , which gives  $z_1 = 13.65 \Omega$ ,  $z_2 = 19.30 \Omega$ ,  $z_3 = 32.38 \Omega$ ,  $z_4 = 45.79 \Omega$   
(source and load are reversed in this case)



From (5.55),  $A \approx \frac{1}{2^{N+1}} \ln z_4/z_0 = -0.0433$

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[ \frac{1}{2} \left( \frac{z_0}{z_4} \right)^{1/N} \right] = 69\% \quad (\text{agrees with plot})$$


b) Microstrip line widths and lengths:

$Z_c$	W(cm.)	$\epsilon_r$	$\lambda_g/4(\text{cm})$
45.85	0.356	3.239	4.16
32.42	0.597	3.402	4.06
19.28	1.175	3.627	3.94
13.63	1.781	3.756	3.87

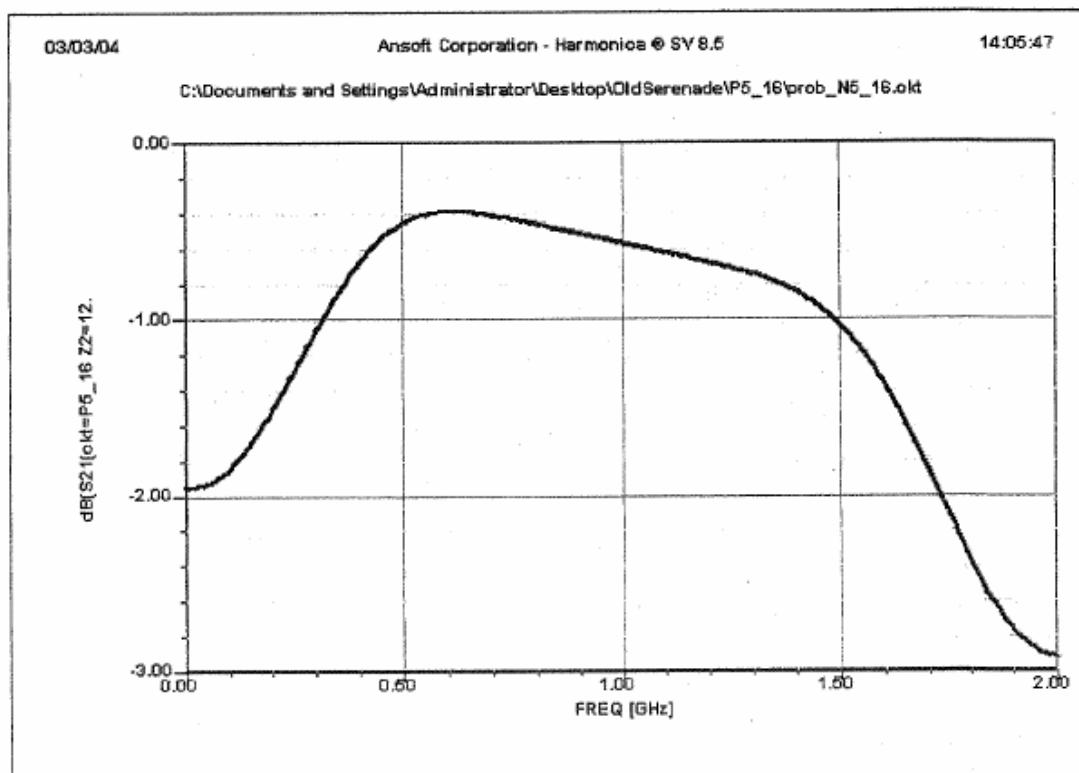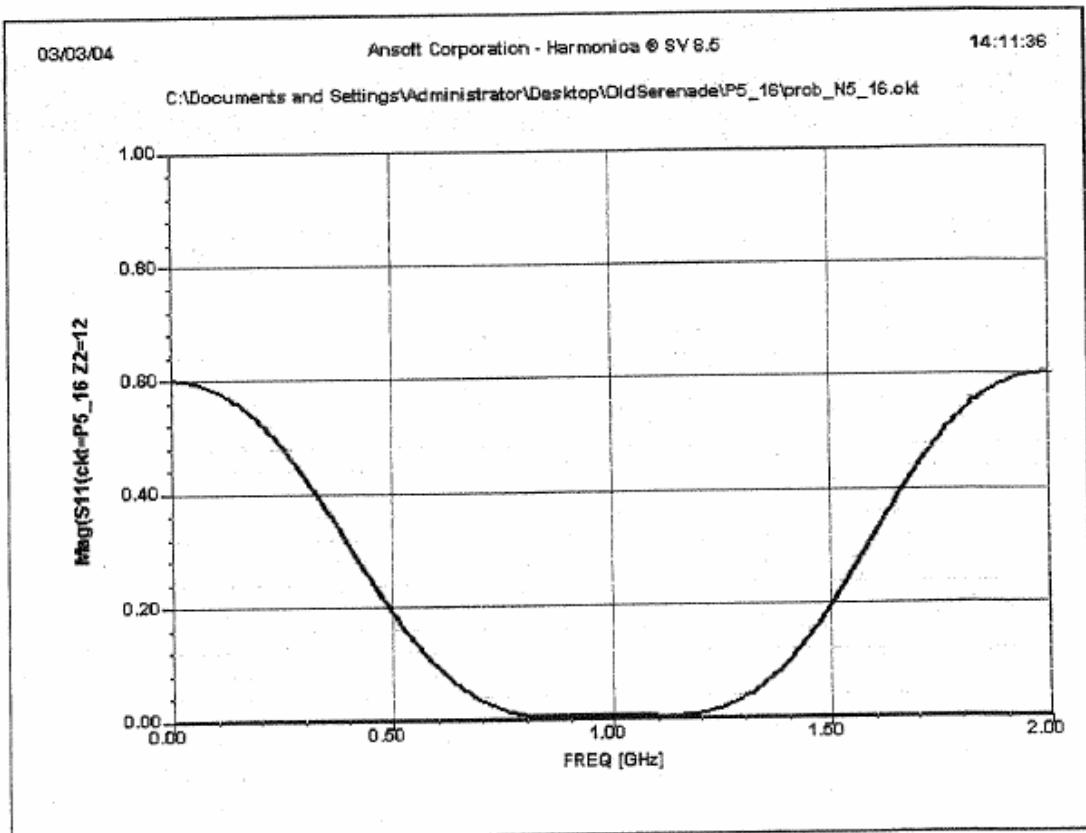Results from Serenade modeling of parts a) and b)  
are shown on the following page. Note the good  
match, and the insertion loss of about 0.5dB.



5.17

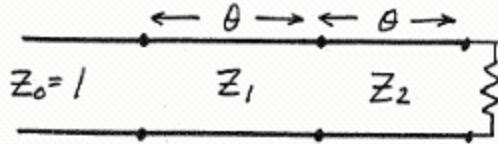

From (5.50) the desired input reflection coefficient response is ( $N=2$ ):

$$\Gamma(\theta) = 2A(1 + \cos 2\theta)$$

From the above circuit, we have that  $\Gamma(0) = \frac{R-1}{R+1} = 0.2$ , so  $A = 0.2/4 = 0.05$ .

Now we calculate the input reflection coefficient of the above circuit using ABCD matrices and conversion to S-parameters:

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos\theta & jZ_1 \sin\theta \\ jY_1 \sin\theta & \cos\theta \end{bmatrix} \begin{bmatrix} \cos\theta & jZ_2 \sin\theta \\ jY_2 \sin\theta & \cos\theta \end{bmatrix}$$

$$= \begin{bmatrix} \cos^2\theta - Z_1 Y_2 \sin^2\theta & j(Z_1 + Z_2) \cos\theta \sin\theta \\ j(Y_1 + Y_2) \sin\theta \cos\theta & \cos^2\theta - Y_1 Z_2 \sin^2\theta \end{bmatrix}$$

Using Table 4.2 to convert to s-parameters gives the input reflection coefficient as,

$$\begin{aligned} \Gamma(\theta) &= S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} = \frac{A+B-C-D}{S} + \frac{4\Gamma_L / S^2}{1 - \frac{-A+B-C+D}{S} \Gamma_L} \\ &= \frac{(A+B-C-D)[S - \Gamma_L(-A+B-C+D)] + 4\Gamma_L}{S[S - \Gamma_L(-A+B-C+D)]} \end{aligned}$$

where  $S = A+B+C+D$ ,  $\Gamma_L = \frac{R-1}{R+1}$ .

This result can be equated to  $2A(1 + \cos 2\theta)$ , and solved for  $Z_1$  and  $Z_2$ , but this is a very lengthy procedure. Instead, we will first evaluate both expressions at  $\theta = 90^\circ$ :

$$\Gamma(90^\circ) = 0, \text{ and } \begin{bmatrix} A & B \\ C & D \end{bmatrix} \Big|_{\theta=90^\circ} = \begin{bmatrix} -z_1 y_2 & 0 \\ 0 & -y_1 z_2 \end{bmatrix}$$

So  $\Gamma(0)$  reduces to the following equation:

$$(-z_1 y_2 + y_1 z_2) [-(y_1 z_2 + z_1 y_2) - \Gamma_L (z_1 y_2 - y_1 z_2)] + 4\Gamma_L = 0$$

$$(z_1^2 y_2^2 - y_1^2 z_2^2) + \Gamma_L (z_1^2 y_2^2 + y_1^2 z_2^2 + 2) = 0$$

$$(z_1^4 - z_2^4) + \Gamma_L (z_1^4 + z_2^4 + 2z_1^2 z_2^2) = 0$$

$$(z_1^2 - z_2^2) + \Gamma_L (z_1^2 + z_2^2) = 0$$

$$z_2^2 = z_1^2 \frac{1 + \Gamma_L}{1 - \Gamma_L} = z_1^2 R \Rightarrow z_2 = z_1 \sqrt{R} \quad (\text{for } z_0 = 1)$$

Another equation is harder to find, so we will make use of the fact that the transformer will be symmetric:

$$\frac{z_1 - 1}{z_1 + 1} = \frac{R - z_2}{R + z_2} = \frac{R/z_2 - 1}{R/z_2 + 1}$$

$$\text{Thus, } \frac{R}{z_2} = z_1 \text{ or } z_1 = \underline{R^{1/4}} \quad (\text{for } z_0 = 1)$$

If  $R = 1.5$ , these results reduce to,

$$z_1 = (1.5)^{1/4} = 1.1067 \quad \checkmark$$

$$z_2 = 1.1067 \sqrt{1.5} = 1.3554 \quad \checkmark$$


which agree with Table 5.1

**5.18** From (5.55), the fractional bandwidth is,

$$\frac{\Delta f}{f_0} = 2 - \frac{4}{\pi} \cos^{-1} \left[ \frac{1}{2} \left( \frac{Z_L}{A} \right)^{1/N} \right], \text{ with } A = 2^{-N} \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right|$$

$\frac{Z_L}{Z_0}$	N=1		N=2		N=4	
	A	$\Delta f/f_0 \cdot \%$	A	$\Delta f/f_0 \cdot \%$	A	$\Delta f/f_0 \cdot \%$
1.5	0.1000	200	0.0500	200	0.0125	200
2.0	0.1667	82	0.0833	113	0.0208	137
3.0	0.2500	52	0.1250	87	0.0313	117
4.0	0.3000	43	0.1500	78	0.0375	110
5.0	0.3333	39	0.1667	74	0.0417	106
6.0	0.3571	36	0.1786	71	0.0446	104

This data is plotted in the graph below.

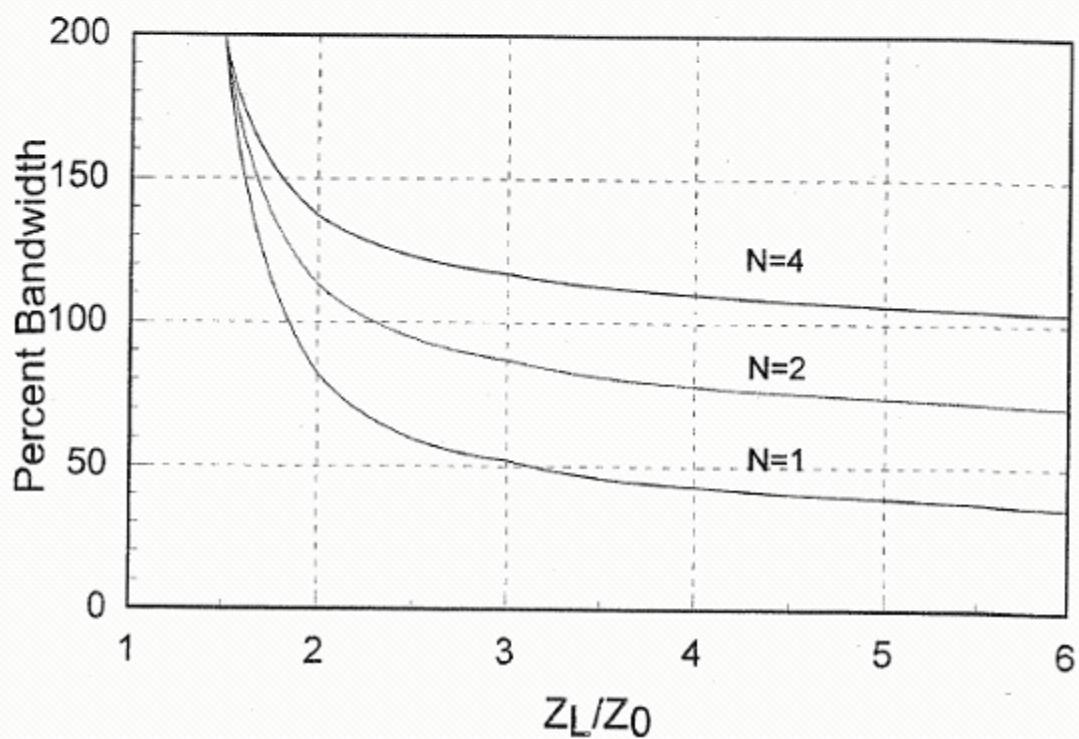

**5.19**  $Z_0 = 50 \Omega, Z_L = 30 \Omega, SWR_{Max} = 1.25$

$$|\Gamma_m| = \frac{SWR_m - 1}{SWR_m + 1} = 0.111 = A$$

$$\begin{aligned} \text{From (5.61), } \Gamma(\theta) &= 2e^{-j4\theta} \left[ \Gamma_0 \cos 4\theta + \Gamma_1 \cos 2\theta + \frac{1}{2} \Gamma_2 \right] \\ &= A e^{-j4\theta} T_4 (\sec \theta_m \cos \theta) \\ &= A e^{-j4\theta} \left[ \sec^4 \theta_m (\cos 4\theta + 4 \cos 2\theta + 3) - 4 \sec^2 \theta_m \cdot \right. \\ &\quad \left. (\cos 2\theta + 1) + 1 \right] \end{aligned}$$

From (5.63),

$$\begin{aligned} \sec \theta_m &= \cosh \left[ \frac{1}{N} \cosh^{-1} \left( \left| \frac{\ln Z_L/Z_0}{2\Gamma_m} \right| \right) \right] \\ &= \cosh \left[ \frac{1}{4} \cosh^{-1} \left( \frac{1}{2(1.11)} \ln \frac{30}{50} \right) \right] = 1.0687 \end{aligned}$$

so,

$$\theta_m = \cos^{-1} \left( \frac{1}{\sec \theta_m} \right) = 20.66^\circ$$

Equate  $\cos 4\theta$  terms:

$$2\Gamma_0 = A \sec^4 \theta_m \Rightarrow \Gamma_0 = 0.07246 = \Gamma_4$$

Equate  $\cos 2\theta$  terms:

$$2\Gamma_1 = A (4 \sec^4 \theta_m - 4 \sec^2 \theta_m) \Rightarrow \Gamma_1 = 0.03607 = \Gamma_3$$

Equate constant terms:

$$\Gamma_2 = A (3 \sec^4 \theta_m - 4 \sec^2 \theta_m + 1) = 0.03831$$

Compute  $Z_n$ 's : (reverse  $Z_L$  and  $Z_0$ )

$$Z_1 = Z_L \frac{1 + \Gamma_0}{1 - \Gamma_0} = 34.69 \Omega$$

$$Z_2 = Z_1 \frac{1 + \Gamma_1}{1 - \Gamma_1} = 37.29 \Omega$$

$$Z_3 = Z_2 \frac{1 + \Gamma_2}{1 - \Gamma_2} = 40.26 \Omega$$

$$Z_4 = Z_3 \frac{1 + r_3}{1 - r_3} = 43.27 \Omega$$


check :  $Z_5 = Z_4 \frac{1 + r_4}{1 - r_4} = 50.03 \Omega \approx Z_0 \checkmark$

From (5.64) the bandwidth is ,

$$\frac{\Delta f}{f_0} = 2 - \frac{4R_m}{\pi} = 154\%$$

From the graph ,
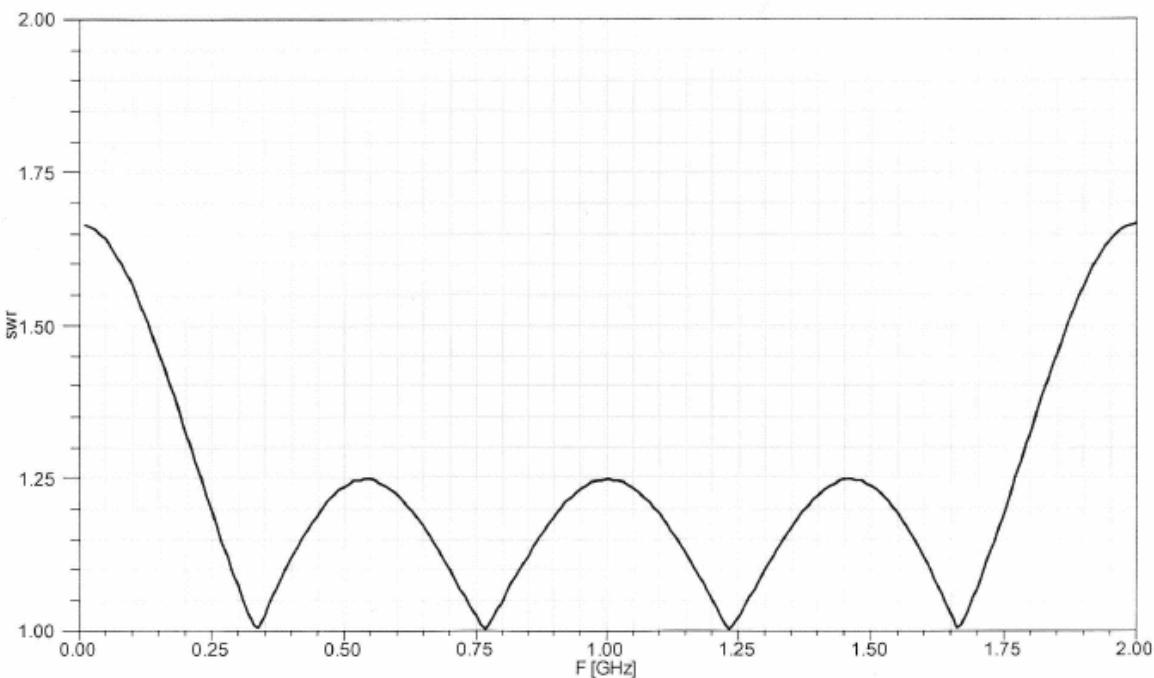
$$\frac{\Delta f}{f_0} \approx \frac{1.77 - .225}{1} = 154.5\% \checkmark$$



**5.20** From (5.61) and (5.60b),

$$\Gamma(\theta) = A e^{-2j\theta} T_2(\sec \theta m \cos \theta) = A e^{-2j\theta} [\sec^2 \theta m (1 + \cos 2\theta) - 1]$$

$$\Gamma(0) = A T_2(\sec \theta m) = \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| = \frac{R-1}{R+1} = 0.2 \quad ; \quad A = \Gamma_m = 0.05$$

As in Problem 5.17, we will evaluate  $\Gamma(\theta)$  for  $\theta = 90^\circ$ .

Then  $\Gamma(90^\circ) = \Gamma_m$ . Also, as in Problem 5.17, from symmetry we have that  $Z_1 Z_2 = R$ . Then,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} -Z_1^2/R & 0 \\ 0 & -R/Z_1^2 \end{bmatrix} \quad (Z_0 = 1)$$

$$\begin{aligned} \Gamma(90^\circ) = \Gamma_m &= \frac{\left(-Z_1^2/R + R/Z_1^2\right)\left[-\left(Z_1^2/R + R/Z_1^2\right) - \Gamma_\ell\left(Z_1^2/R - R/Z_1^2\right)\right] + 4\Gamma_\ell}{-\left(Z_1^2/R + R/Z_1^2\right)\left[-\left(Z_1^2/R + R/Z_1^2\right) - \Gamma_\ell\left(Z_1^2/R - R/Z_1^2\right)\right]} \\ &= \frac{(R^2 - Z_1^4)\left[-(Z_1^4 + R^2) - \Gamma_\ell(Z_1^4 - R^2)\right] + 4\Gamma_\ell R^2 Z_1^4}{(Z_1^4 + R^2)\left[(Z_1^4 + R^2) + \Gamma_\ell(Z_1^4 - R^2)\right]} \end{aligned}$$

$$\begin{aligned} \Gamma_m (Z_1^4 + R^2)^2 + \Gamma_m \Gamma_\ell (Z_1^4 + R^2)(Z_1^4 - R^2) &= -(R^2 - Z_1^4)(Z_1^4 + R^2) + \Gamma_\ell (Z_1^4 - R^2)^2 + 4\Gamma_\ell R^2 Z_1^4 \\ Z_1^8 (\Gamma_m - 1)(\Gamma_\ell + 1) + 2Z_1^4 R^2 (\Gamma_m - \Gamma_\ell) - R^4 (\Gamma_m + 1)(\Gamma_\ell - 1) &= 0 \end{aligned}$$

For  $\Gamma_m = 0.05$ ,  $\Gamma_\ell = 0.2$ ,  $R = 1.5$ :

$$-1.140 Z_1^8 - 0.6750 Z_1^4 + 4.2525 = 0$$

$$Z_1^4 = \frac{0.675 \pm 4.455}{-2.280} = 1.65789 \Rightarrow Z_1 = 1.1347 Z_0 \checkmark$$

$$Z_2 = R/Z_1 = 1.3219 Z_0 \checkmark$$

These results agree with Table 5.2.

5.21

$$|\Gamma(\theta)| = A(0.1 + \cos^2 \theta), \quad 0 < \theta < \pi$$

From (5.46a), for  $N=2$ ,

$$\begin{aligned} |\Gamma(\theta)| &= 2(\Gamma_0 \cos 2\theta + \frac{1}{2}\Gamma_1) = A(0.1 + \cos^2 \theta) \\ &= A(0.6 + 0.5 \cos 2\theta) \end{aligned}$$

$$\text{When } \theta=0, \quad |\Gamma(0)| = 1.1A = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{1.5-1}{1.5+1} = 0.2 \implies A = 0.182$$

Equating coefficients of  $\cos 2\theta$ :

$$2\Gamma_0 = 0.5A \implies \Gamma_0 = 0.0455$$

Equating constant terms:

$$\Gamma_1 = 0.6A = 0.109$$

so the characteristic impedances are,

$$Z_1 = Z_0 \frac{1 + \Gamma_0}{1 - \Gamma_0} = 1.095 Z_0$$

$$Z_2 = Z_1 \frac{1 + \Gamma_1}{1 - \Gamma_1} = 1.245 Z_1 = 1.363 Z_0$$


CHECK: at  $\theta=\pi/2$ , the input impedance to the transformer will be,

$$Z_{in} = \frac{Z_1^2}{(Z_2^2/Z_L)} = \frac{Z_L Z_0 Z_1^2}{Z_2^2} = 0.968 Z_0$$

So the input reflection coefficient is,

$$\Gamma_{in} = \left| \frac{Z_{in} - Z_0}{Z_{in} + Z_0} \right| = 0.016$$

which is reasonably close to  $|\Gamma(\pi/2)| = 0.1A = 0.018$

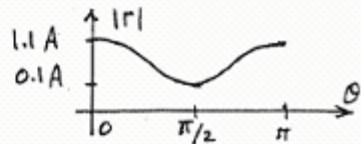

**5.22**

$$\frac{d(\ln z/z_0)}{dz} = A \sin \frac{\pi z}{L}$$

$$\ln(z/z_0) = B - \frac{LA}{\pi} \cos \frac{\pi z}{L}$$

$$z(z) = C e^{-\frac{LA}{\pi} \cos \frac{\pi z}{L}}$$

$$z(0) = z_0 = C e^{-LA/\pi}, \quad z(L) = z_L = C e^{+LA/\pi}$$

Solve for  $C, A$  to get,

$$C = \sqrt{z_0 z_L}$$

$$A = \frac{-\pi}{2L} \ln(z_0/z_L) \quad \checkmark$$


From (5.67),

$$\begin{aligned} \Gamma(\theta) &= \frac{1}{2} \int_{z=0}^L e^{-2j\beta z} \frac{d}{dz} (\ln z/z_0) dz \\ &= \frac{1}{2} \int_{z=0}^L A \sin \frac{\pi z}{L} e^{-2j\beta z} dz \\ &= \frac{A}{2} \frac{e^{-2j\beta L} \left[ -2j\beta \sin \frac{\pi L}{L} - \frac{\pi}{L} \cos \frac{\pi L}{L} \right]}{(\pi/L)^2 - 4\beta^2} \Big|_0^L \\ &= \frac{\pi A}{2L} e^{-j\beta L} \frac{(e^{-j\beta L} + e^{j\beta L})}{(\pi/L)^2 - 4\beta^2} \end{aligned}$$

So,

$$|\Gamma(\theta)| = \frac{\pi^2}{2} \left| \ln \frac{z_0}{z_L} \right| \left| \frac{\cos \beta L}{\pi^2 - (2\beta L)^2} \right| \quad \checkmark$$

This result is plotted as shown:

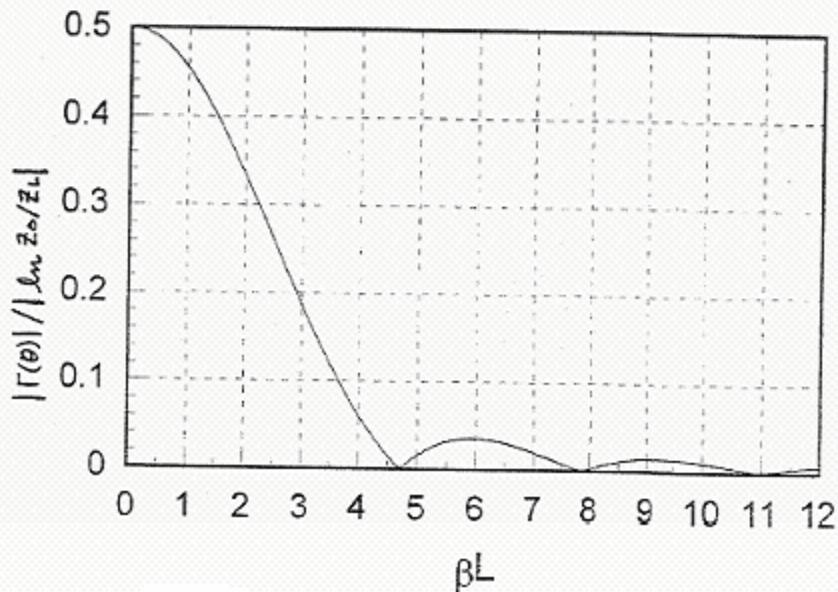

5.23


From (5.68),  $Z(z) = Z_0 e^{\alpha z}$  for  $0 < z < L$ .

$$\alpha = \frac{1}{L} \ln \frac{Z_L}{Z_0} = \frac{0.693}{L}$$

From (5.70),

$$|\Gamma(\theta)| = \frac{1}{2} \left| \ln \frac{Z_L}{Z_0} \right| \left| \frac{\sin \beta L}{\beta L} \right| = 0.346 \left| \frac{\sin \beta L}{\beta L} \right| \quad \checkmark$$

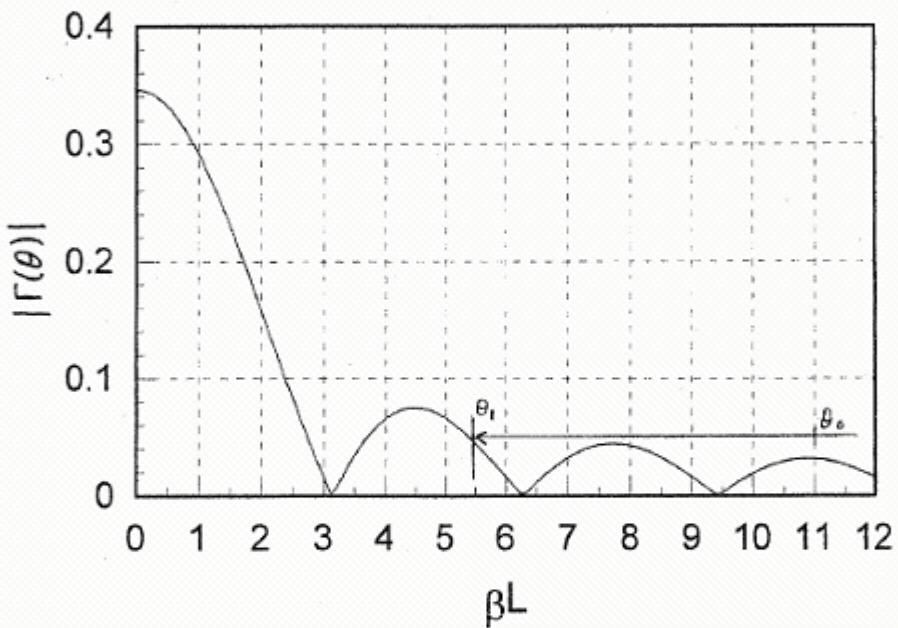This result is plotted in the graph shown below:



We see that the lower frequency limit for  $|\Gamma| \leq 0.05$  is  $\theta_1 = 5.5$ . To obtain 100% bandwidth, we must have,

$$\frac{\theta_2 - \theta_1}{(\theta_1 + \theta_2)/2} = 1, \text{ or } \theta_2 = 3\theta_1 = 16.5$$

Then at the center frequency,

$$\theta_0 = \frac{\theta_1 + \theta_2}{2} = 11.0 = \beta L$$

So,

$$L = \frac{11\lambda_0}{2\pi} = 1.75\lambda_0 \quad \checkmark$$

From (5.64),  $\theta_m$  for a Chebyshev transformer with 100% bandwidth is,

$$\frac{\Delta f}{f_0} = 2 - \frac{4\theta_m}{\pi} = 1 \implies \theta_m = \pi/4.$$

Then from (5.63),

$$\operatorname{slc} \theta_m = \cosh \left[ \frac{1}{N} \cosh^{-1} \left( \frac{1}{\Gamma_m} \left| \frac{Z_L - Z_0}{Z_L + Z_0} \right| \right) \right]$$

$$1.414 = \cosh \left[ \frac{1}{N} (2.5846) \right] \Rightarrow N = 2.93 \Rightarrow \underline{N = 3}$$

So  $N=3$  sections would be required, for a length of  $3\lambda_0/4$  at the center frequency.


This is much shorter than the exponential taper matching section.

**5.24**

From Figure 5.22 the Bode-Fano limit for a parallel RC load is,

$$\int_0^\infty \ln \frac{1}{|\Gamma(w)|} dw \leq \frac{\pi}{RC}$$

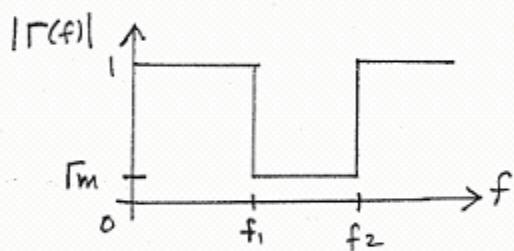The optimum reflection coefficient magnitude response will be as shown:




$$\text{Thus, } \ln \frac{1}{\Gamma_m} \leq \frac{\pi}{2WRC} = \frac{\pi}{2\pi(10.6-3.1)\times 10^9 (75)(0.6\times 10^{-12})} \\ \leq 1.48$$

$$\Gamma_m > 0.228 \Rightarrow RL < \underline{6.4 \text{ dB}}$$

5.25

L-section matching solution:

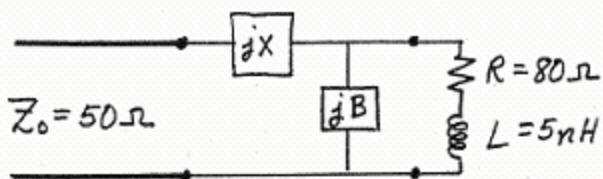

at  $f = 2 \text{ GHz}$ ,  $Z_L = 80 + j 63 \Omega$ ,  $\bar{Z}_L = 1.6 + j 1.26$  (INSIDE  $1 + j X$ )


a Smith chart solution gives,

$$jB = -j 1.8 \Rightarrow \text{INDUCTOR with } L = 22.1 \text{nH. } \checkmark$$

$$jX = -j 1.25 \Rightarrow \text{CAPACITOR with } C = 1.27 \text{ pF. } \checkmark$$

The input reflection coefficient magnitude is plotted below, where it is seen that the bandwidth for  $|\Gamma| < 0.1$  is 20%.

▽ MS11 [mag]

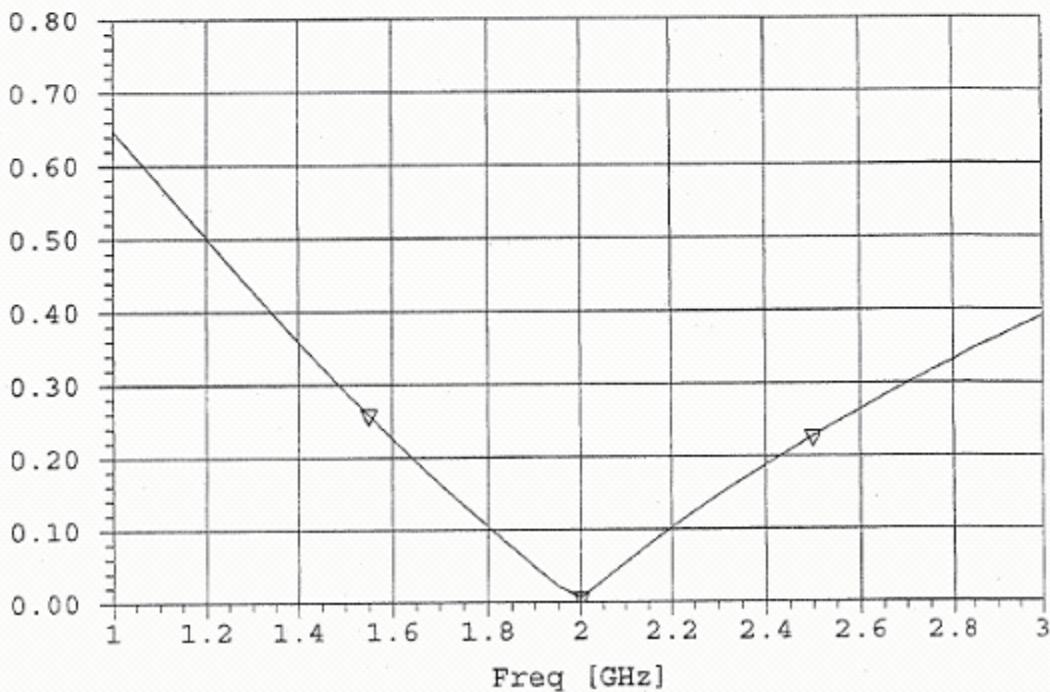

Bode - Fano limit:

From Figure 5.22d, the Bode-Fano criteria gives a bandwidth limit of


$$\Delta\omega = \frac{\pi R}{L} \frac{1}{\ln V_m} = 2.18 \times 10^{10} = \omega_2 - \omega_1$$

$$\frac{\Delta f}{f_0} = \frac{f_2 - f_1}{f_0} = \frac{2.18 \times 10^{10}}{2\pi (2 \times 10^9)} = 174\%$$

This is considerably more than the bandwidth of the L-section match.

## Chapter 6

6.1

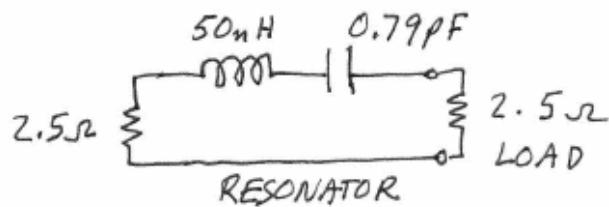


$$f_0 = \frac{1}{2\pi\sqrt{LC}} = 800 \text{ MHz}$$

$$Q_0 = \frac{\omega_0 L}{R} = 100$$

$$Q_e = \frac{\omega_0 L}{R_L} = 100$$

$$Q_L = 50$$

6.2

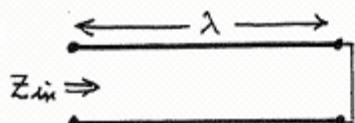

$$\ell = \lambda = \frac{2\pi V_p}{\omega_0} \quad \text{for } \omega = \omega_0$$

This circuit has a series-type resonance, like the short-circuited  $\pi$  resonator. Thus, let

$$\beta\ell = \frac{\omega_0 l}{V_p} + \frac{\Delta\omega l}{V_p} = 2\pi \left( 1 + \frac{\Delta\omega}{\omega_0} \right)$$

Then from (6.24) the input impedance is,

$$Z_{in} \approx Z_0 \frac{\alpha\ell + j2\pi \frac{\Delta\omega}{\omega_0}}{1 + j2\pi \frac{\Delta\omega}{\omega_0}} \approx Z_0 \left( \alpha\ell + j2\pi \frac{\Delta\omega}{\omega_0} \right) = R + jL\Delta\omega$$

$$\text{Thus, } R = Z_0\alpha\ell, \quad L = \frac{\pi Z_0}{\omega_0}.$$

And,

$$Q = \frac{\omega_0 L}{R} = \frac{\pi Z_0}{Z_0 \alpha\ell} = \frac{\pi}{\alpha\ell} = \frac{\beta}{2\alpha} \quad (\text{since } \ell = \lambda = \frac{2\pi}{\beta} \text{ at res.})$$

6.3

$$l = \frac{\lambda}{4} = \frac{\pi v_p}{2\omega_0} \text{ for } \omega = \omega_0$$

This circuit has a series-type resonance, like the short-circuited  $\lambda/2$  line. So let,

$$\beta l = \frac{\omega_0 l}{v_p} + \frac{\Delta \omega l}{v_p} = \frac{\pi}{2} \left( 1 + \frac{\Delta \omega}{\omega_0} \right)$$

Then,

$$\tan \beta l = \tan \frac{\pi}{2} \left( 1 + \frac{\Delta \omega}{\omega_0} \right) = -\cot \frac{\Delta \omega \pi}{2\omega_0} \approx -\frac{2\omega_0}{\pi \Delta \omega}$$

The input impedance is,


$$\begin{aligned} Z_{in} &= Z_0 \frac{1 + j \tan \beta l \tanh \alpha l}{\tanh \alpha l + j \tan \beta l} \approx \frac{1 - j \frac{2\omega_0}{\pi \Delta \omega} \alpha l}{\alpha l - j \frac{2\omega_0}{\pi \Delta \omega}} \\ &\approx Z_0 \frac{\alpha l + j \frac{\pi \Delta \omega}{2\omega_0}}{1 + j \frac{\pi \Delta \omega}{2\omega_0} \alpha l} \approx Z_0 \left( \alpha l + j \frac{\pi \Delta \omega}{2\omega_0} \right) = R + j L \Delta \omega \end{aligned}$$

$$\therefore R = Z_0 \alpha l \quad , \quad L = \frac{\pi Z_0}{4\omega_0}$$

Then,

$$Q = \frac{\omega_0 L}{R} = \frac{\pi}{4\alpha l} = \frac{\beta}{2\alpha}$$


(since  $l = \frac{\lambda}{4} = \frac{\pi}{2\beta}$  at resonance)

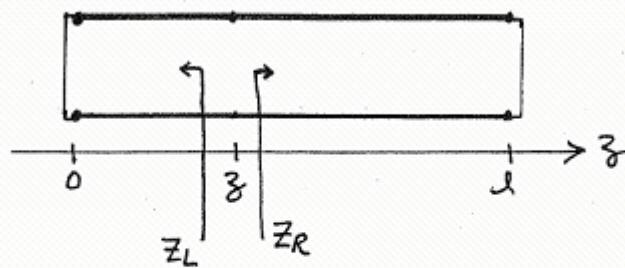**6.4**

$$\beta l = \pi$$

$$Z_L = j Z_0 \tan \beta l$$

$$Z_R = j Z_0 \tan \beta(l-z) = j Z_0 \tan(\pi - \beta l) = -j Z_0 \tan \beta l = Z_L^* \quad \checkmark$$

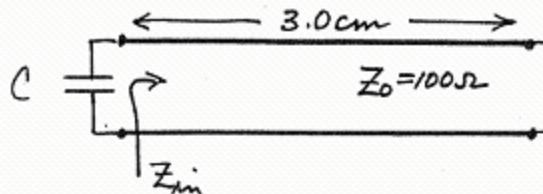**6.5**

$$f_0 = 6 \text{ GHz}$$

$$\beta = \frac{2\pi f}{c} = 125.7 \text{ m}^{-1} \text{ for an air-filled line}$$

$$\beta l = (125.7)(0.03) = 216^\circ \quad \checkmark$$


$$Z_{in} = j Z_0 \tan \beta l = j(100) \tan 216^\circ = j 72.6 \Omega = j \omega L \quad \checkmark$$

To achieve resonance we must have,

$$Z_{in} = (j X_C)^* = \frac{j}{\omega C}$$

$$\text{So, } C = \frac{1}{\omega X_{in}} = 0.365 \mu F \quad \checkmark$$

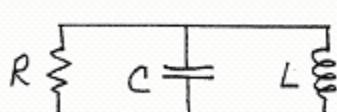The equivalent circuit at 6 GHz, with the shunt resistor, is as follows:



$$R = 10,000 \Omega$$


$$C = 0.365 \mu F$$

$$L = \frac{X_{in}}{\omega} = \frac{72.6}{2\pi(6 \times 10^9)} = 1.93 \text{ nH} \quad \checkmark$$

So the Q is,

$$Q = \omega R C = 2\pi(6 \times 10^9)(10,000)(0.365 \times 10^{-12}) = 138. \quad \checkmark$$

6.6

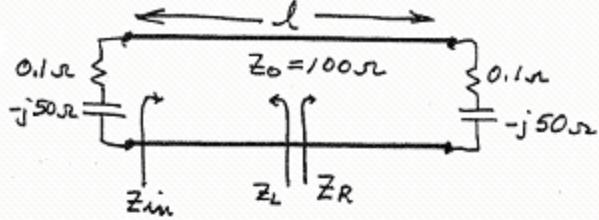

Since the resonator is symmetrical, at the midpoint of the line we must have,  $Z_L = Z_R^* = Z_R$ , or  $\operatorname{Im}\{Z_R\} = 0$ :

Let  $t = \tan \beta l/2$  and  $Z_L = R_L + jX_L$ . ( $R_L = 0.1$ ,  $X_L = -50$ .)

$$\begin{aligned} Z_R &= Z_0 \frac{Z_L + jZ_0 t}{Z_0 + jZ_L t} = Z_0 \frac{R_L + j(X_L + Z_0 t)}{(Z_0 - X_L t) + jR_L t} \\ &= Z_0 \frac{R_L(Z_0 - X_L t) + R_L t(X_L + Z_0 t) + j(X_L + Z_0 t)(Z_0 - X_L t) - jR_L^2 t}{(Z_0 - X_L t)^2 + (R_L t)^2} \end{aligned}$$

$$\begin{aligned} \operatorname{Im}\{Z_R\} &= 0 \Rightarrow (X_L + Z_0 t)(Z_0 - X_L t) - R_L^2 t = 0 \\ &\quad -X_L Z_0 t^2 + (Z_0^2 - X_L^2 - R_L^2)t + Z_0 X_L = 0 \\ &\quad 5000t^2 + 7500t - 5000 = 0 \end{aligned}$$


$$t^2 + 1.5t - 1 = 0$$

$$t = \frac{-1.5 \pm \sqrt{(1.5)^2 + 4}}{2} = -0.75 \pm 1.25 = \begin{cases} 0.50 \Rightarrow \beta l = 53.1^\circ \\ -2.00 \Rightarrow \beta l = -126.9^\circ = 53.1^\circ \end{cases}$$


So,

$$l = \frac{53.1^\circ}{360^\circ} \lambda = 0.148\lambda \quad \tan \beta l = 1.332$$

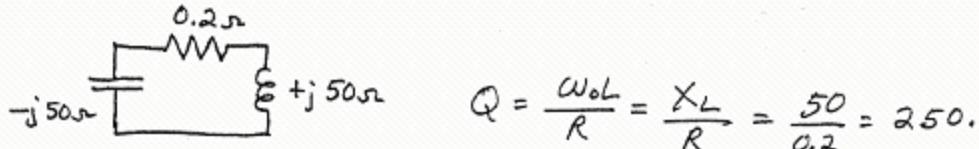CHECK:  $Z_{in} = 100 \frac{(0.1 - j50) + j133.2}{100 + j(0.1 - j50)(1.332)} = 0.1 + j50 \Omega \quad \checkmark$



6.7

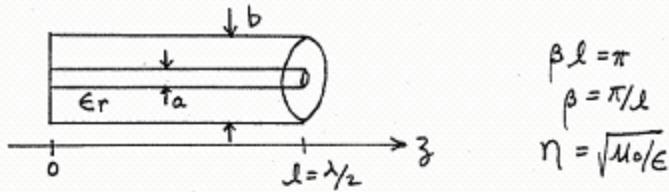

From Section 2.2 the TEM fields of a coaxial line are,

$$\bar{E}^{\pm} = \hat{p} \frac{V_0}{\rho \ln b/a} e^{\mp j\beta z}, \quad \bar{H}^{\pm} = \pm \hat{\phi} \frac{V_0}{\eta \ln b/a} e^{\mp j\beta z}$$

$E_p = 0$  at  $z=0$  in the resonator, so the standing wave fields can be written as,

$$E_p = \frac{V_0}{\rho \ln b/a} [e^{-j\beta z} - e^{j\beta z}] = \frac{-2j V_0}{\rho \ln b/a} \sin \beta z$$

$$H_\phi = \frac{V_0}{\eta \ln b/a} [e^{-j\beta z} + e^{j\beta z}] = \frac{2V_0}{\eta \ln b/a} \cos \beta z$$

From (1.84) and (1.86) the time-average stored electric and magnetic energies are,

$$W_e = \frac{\epsilon}{4} \int_V |E|^2 dV = \frac{\epsilon}{4} \int_{\rho=a}^b \int_{\phi=0}^{2\pi} \int_{z=0}^l \left( \frac{2V_0}{\rho \ln b/a} \right)^2 \sin^2 \frac{\pi z}{l} \rho dz d\phi d\rho$$

$$= \frac{\pi \epsilon V_0^2}{\ln b/a}$$

$$W_m = \frac{\mu_0}{4} \int_V |\bar{H}|^2 dV = \frac{\mu_0}{4} \int_{\rho=a}^b \int_{\phi=0}^{2\pi} \int_{z=0}^l \left( \frac{2V_0}{\eta \ln b/a} \right)^2 \cos^2 \frac{\pi z}{l} \rho dz d\phi d\rho$$

$$= \frac{\pi \mu_0 V_0^2}{\eta^2 \ln b/a} = \frac{\pi \epsilon V_0^2}{\ln b/a} = W_e \checkmark$$

**6.8**

$$Z_{in} = \frac{Z_0^2}{Z_L} = \frac{Z_0^2}{R + j(\omega L - \frac{1}{\omega C})} = \frac{1}{\frac{R}{Z_0^2} + j\omega\left(\frac{L}{Z_0^2} - \frac{1}{\omega^2 C Z_0^2}\right)}$$

The input impedance of a parallel RLC circuit is,

$$Z_{in} = \frac{1}{\frac{1}{R'} + \frac{1}{j\omega C'} + j\omega L'} = \frac{1}{\frac{1}{R'} + j\omega(C' - \frac{1}{\omega^2 L'})}$$

Thus the original circuit acts as a parallel  $R'L'C'$  resonator with  $R' = Z_0^2/R$ ,  $C' = L/Z_0^2$ ,  $L' = C Z_0^2$ .

(This is the basis for using  $\lambda/4$  lines as impedance and admittance inverters.)

**6.9**

air-filled, aluminium, X-band,

$d = 2.0\text{cm}$ ,  $a = 2.286\text{cm}$ ,  $b = 1.016\text{cm}$

$$\tau_{al} = 3.816 \times 10^7 \text{ s/m}$$

$$f_{101} = \frac{c}{2\pi} \sqrt{\left(\frac{\pi}{a}\right)^2 + \left(\frac{\pi}{d}\right)^2} = 9.965\text{GHz} \quad R_s = \sqrt{\frac{\omega M_0}{2\sigma}} = 0.0321\Omega$$

$$k = 208.7 \text{ m}^{-1}$$

$$f_{202} = \frac{c}{2\pi} \sqrt{\left(\frac{\pi}{a}\right)^2 + \left(\frac{2\pi}{d}\right)^2} = 16.372\text{GHz} \quad R_s = \sqrt{\frac{\omega M_0}{2\sigma}} = 0.0412\Omega$$

$$k = 342.9 \text{ m}^{-1}$$

$$\begin{aligned} \text{From (6.46), } & (2d^2a^3b + 2bd^3 + d^2a^3d + ad^3) = \\ & = 34.54 + 48.17d^2 \text{ cm}^4 \end{aligned}$$

$$Q_{101} = \frac{k^3 a^3 d^3 b \eta_0}{2\pi^2 R_s} \frac{1}{(34.54 + 48.17)10^{-8}} = 6349, \checkmark$$

$$Q_{102} = \frac{k^3 a^3 d^3 b \eta_0}{2\pi^2 R_s} \frac{1}{(34.54 + 48.17)10^{-8}} = 7987, \checkmark$$

verified w/ RECCAVITY FOR

6.10

From Table 3.2, the magnetic fields of the TM<sub>11</sub> waveguide mode are,

$$H_x^{\pm} = \frac{B^{\pm}}{b} \sin \frac{\pi x}{a} \cos \frac{\pi y}{b} e^{\mp j\beta z}$$

$$H_y^{\pm} = \frac{B^{\pm}}{a} \cos \frac{\pi x}{a} \sin \frac{\pi y}{b} e^{\mp j\beta z}$$

To have current maxima at  $z=0, d$  the cavity fields must be,

$$H_x = \frac{A}{b} \sin \frac{\pi x}{a} \cos \frac{\pi y}{b} \cos \frac{\pi z}{d}$$

$$H_y = \frac{A}{a} \cos \frac{\pi x}{a} \sin \frac{\pi y}{b} \cos \frac{\pi z}{d}$$

The stored magnetic energy is,

$$W_m = \frac{\mu_0}{4} \int_V |\vec{H}|^2 dv = \frac{\mu_0}{4} A^2 \frac{a}{2} \frac{b}{2} \frac{d}{2} \left( \frac{1}{b^2} + \frac{1}{a^2} \right) = \frac{abd\mu_0 A^2}{32} \left( \frac{1}{a^2} + \frac{1}{b^2} \right)$$

The power lost in the walls is,

$$\begin{aligned}
 P_L &= \frac{R_s}{2} \int_s |\vec{H}_t|^2 ds = R_s \left\{ \int_{x=0}^a \int_{z=0}^d |H_x(y=0)|^2 dz dx + \int_{y=0}^b \int_{z=0}^d |H_y(x=0)|^2 dy dz + \right. \\
 &\quad \left. + \int_{x=0}^a \int_{y=0}^b [ |H_x(z=0)|^2 + |H_y(z=0)|^2 ] dx dy \right\} \\
 &= \frac{A^2 R_s}{4} \frac{a^3 d + b^3 d + a^3 b + a b^3}{a^2 b^2}
 \end{aligned}$$

Then,

$$Q = \frac{\omega_0 (W_e + W_m)}{P_L} = \frac{2\omega_0 W_m}{P_L} = \frac{\kappa_0 \eta_0}{4 R_s} \frac{abd (a^2 + b^2)}{(a^3 d + b^3 d + a^3 b + a b^3)} \quad \checkmark$$

**6.11** From Section 3.3 the transverse fields of the  $TE_{10}$  mode in the two regions can be written as,

$$E_y = \begin{cases} A \sin \frac{\pi x}{a} \sin \beta_a z & \text{for } 0 < z < d-t \\ B \sin \frac{\pi x}{a} \sin \beta_d (d-z) & \text{for } d-t < z < d \end{cases}$$

$$H_x = \begin{cases} -j \frac{A}{Z_a} \sin \frac{\pi x}{a} \cos \beta_a z & \text{for } 0 < z < d-t \\ -j \frac{B}{Z_d} \sin \frac{\pi x}{a} \cos \beta_d (d-z) & \text{for } d-t < z < d \end{cases}$$

where  $\beta_a = \sqrt{k_0^2 - (\pi/a)^2}$ ,  $\beta_d = \sqrt{\epsilon_r k_0^2 - (\pi/a)^2}$

$$Z_a = k_0 \eta_0 / \beta_a, \quad Z_d = k_0 \eta_0 / \beta_d = k_0 \eta_0 / \beta_d$$

Continuity of  $E_y, H_x$  at  $z=d-t$ :

$$E_y: \quad A \sin \beta_a (d-t) = B \sin \beta_d t$$

$$H_x: \quad \frac{A}{Z_a} \cos \beta_a (d-t) = \frac{B}{Z_d} \cos \beta_d t$$

Divide to obtain:

$$Z_a \tan \beta_a (d-t) = Z_d \tan \beta_d t$$

$$\beta_d \tan \beta_a (d-t) = \beta_a \tan \beta_d t$$

This equation can be solved for  $k_0$ .  $\beta_a$  and  $\beta_d$  are functions of  $k_0$  as given above.

6.12

$$TM \text{ modes : } (\nabla^2 + k^2) E_z = 0$$

$$\text{Let } E_z(x, y, z) = X(x) Y(y) Z(z).$$

Substitute into wave equation and divide by XYZ:

$$\frac{1}{X} \frac{d^2 X}{dx^2} + \frac{1}{Y} \frac{d^2 Y}{dy^2} + \frac{1}{Z} \frac{d^2 Z}{dz^2} + k^2 = 0$$

By the separation of variables argument,

$$\frac{1}{X} \frac{d^2 X}{dx^2} = -k_x^2 \Rightarrow X(x) = A \cos k_x x + B \sin k_x x$$

$$\frac{1}{Y} \frac{d^2 Y}{dy^2} = -k_y^2 \Rightarrow Y(y) = C \cos k_y y + D \sin k_y y$$

$$\frac{1}{Z} \frac{d^2 Z}{dz^2} = -k_z^2 \Rightarrow Z(z) = E \cos k_z z + F \sin k_z z$$

$$\text{with } k^2 = k_x^2 + k_y^2 + k_z^2.$$

Now,  $E_z = 0$  for  $x=0, a$  and  $y=0, b$ . Therefore,

$A = C = 0$  and  $k_x = \frac{m\pi}{a}$ ,  $k_y = \frac{n\pi}{b}$ . To enforce the remaining boundary conditions, we need  $E_x$  or  $E_y$ : From Maxwell's equations,

$$E_x = \frac{1}{k^2 - k_z^2} \frac{\partial^2 E_z}{\partial x \partial z} = \frac{1}{k^2 - k_z^2} (B k_x \cos k_x x) (D \sin k_y y) \cdot (-k_z E \sin k_z z + k_z F \cos k_z z)$$

For  $E_x = 0$  at  $z=0, d$  we must have  $F = 0$ , and  $k_z = \frac{l\pi}{d}$ .

$$\text{Thus, } k^2 = \left(\frac{m\pi}{a}\right)^2 + \left(\frac{n\pi}{b}\right)^2 + \left(\frac{l\pi}{d}\right)^2,$$

which determines the resonant frequencies. The solution for TE modes is similar.

6.13

From Table 3.5 the fields of the  $TM_{nmo}$  mode are ( $\beta = 0$ ):

$$E_z = A \sin n\phi J_n(k_c p)$$

$$H_p = \frac{j\omega \epsilon}{k_c^2 p} A \cos n\phi J_n(k_c p)$$

$$H_\phi = -j\frac{\omega \epsilon}{k_c} A \sin n\phi J_n'(k_c p), \quad k_c = \Phi_{nm}/a = k$$

The stored electric energy is,

$$\begin{aligned} W_e &= \frac{\epsilon}{4} \int_V |\vec{E}|^2 dV = \frac{A^2 \epsilon}{4} \int_{p=0}^a \int_{\phi=0}^{2\pi} \int_{z=0}^d \sin^2 n\phi J_n^2(k_c p) p dp d\phi dz \\ &= \frac{A^2 \epsilon}{4} \pi d \frac{a^2}{2} J_n'^2(\Phi_{nm}) = \frac{A^2 a^2 \pi d \epsilon}{8} J_n'^2(\Phi_{nm}) \quad (\text{using C.14}) \end{aligned}$$

The power loss due to finite conductivity is,

$$\begin{aligned} P_L &= \frac{R_s}{2} \int_s |\vec{H}_t|^2 ds \\ &= \frac{R_s}{2} \left\{ \int_{\phi=0}^{2\pi} \int_{z=0}^d |H_\phi(p=a)|^2 ad\phi dz + 2 \int_{p=0}^a \int_{\phi=0}^{2\pi} [ |H_p|^2 + |H_\phi|^2 ] pdp d\phi \right\} \\ &= \frac{A^2 R_s}{2} \left\{ \frac{\pi ad}{\eta^2} J_n'^2(\Phi_{nm}) + \frac{2\pi}{\eta^2} \frac{\Phi_{nm}^2}{2k_c^2} J_n'^2(\Phi_{nm}) \right\} \\ &= \frac{A^2 R_s \pi}{2\eta^2} (ad + a^2) J_n'^2(\Phi_{nm}) \end{aligned}$$

Then,  $Q_C = \frac{2\omega W_e}{P_L} = \frac{\omega \epsilon \pi d \epsilon (2\eta^2)}{4R_s \pi \alpha (d+a)} = \frac{ad k \eta}{2R_s(d+a)}$

The power lost in the dielectric is,

$$P_d = \frac{\omega \epsilon''}{2} \int_V |\vec{E}|^2 dV = \frac{\omega \epsilon}{2} \tan \delta \int_V |\vec{E}|^2 dV = \frac{2k W_e}{\eta \epsilon} \tan \delta$$

So,  $Q_d = \frac{2\omega W_e}{P_L} = \frac{1}{\tan \delta} \quad (\text{as in (6.48)})$

**6.14**

From Figure 6.10, maximum  $Q$  for the  $TE_{111}$  mode occurs for  $2a/d \approx 1.7$ . From (6.53a) the resonant frequency is,

$$f_{111} = \frac{c}{2\pi\sqrt{\epsilon_r}} \sqrt{\left(\frac{p'_{11}}{a}\right)^2 + \left(\frac{\pi}{d}\right)^2} = \frac{3 \times 10^8}{2\pi\sqrt{1.5}} \sqrt{\left(\frac{1.841}{a}\right)^2 + \left(\frac{1.7\pi}{2a}\right)^2}$$

$$= \frac{1.264 \times 10^8}{a} = 6 \times 10^9 \text{ Hz} \Rightarrow a = 2.107 \text{ cm}$$

$$d = \frac{2a}{1.7} = 2.479 \text{ cm}$$

$$\sigma_{AU} = 4.1 \times 10^7 \text{ S/m}, R_s = \sqrt{\frac{\omega_{AU}}{2\pi}} = 0.024 \Omega$$

$$k = 2\pi f \sqrt{\epsilon_r}/c = 153.9 \text{ m}^{-1}$$

$$\beta = \frac{\pi}{d} = 126.7 \text{ m}^{-1}$$

From (6.57) the unloaded  $Q$  is, (due to conductor losses)

$$Q_c = \frac{(ka)^3 \eta ad \left[ 1 - \left( \frac{1}{p'_{11}} \right)^2 \right]}{4(p'_{11})^2 R_s \left\{ \frac{ad}{2} \left[ 1 + \left( \frac{\beta a}{p'_{11}^2} \right)^2 \right] + \left( \frac{\beta a^2}{p'_{11}^2} \right)^2 \left( 1 - \frac{1}{p'^2} \right) \right\}}$$

$$= 10,985 \checkmark$$

The unloaded  $Q$  due to dielectric loss is

$$Q_d = \frac{1}{\tan \delta} = 2,000 \checkmark$$

Then the total  $Q$  is,

$$Q = \frac{1}{\frac{1}{Q_d} + \frac{1}{Q_c}} = 1,692 \checkmark$$

(results checked with FORTRAN program CIRCAVITY.FOR)

6.15

Choose coordinate system so that  $b < a < d$ .

Then the dominant resonant mode is the  $TE_{101}$  mode:

$$f_{101} = \frac{c}{2} \sqrt{\left(\frac{1}{a}\right)^2 + \left(\frac{1}{d}\right)^2} = 5.2 \text{ GHz}$$

$$\text{or, } \frac{1}{a^2} + \frac{1}{d^2} = \left(\frac{2f_{101}}{c}\right)^2 = (34.7)^2$$

The next two higher modes must be either the  $TM_{110}$ ,  $TE_{102}$ , or  $TE_{011}$  modes:

$$\left(\frac{2f_{110}}{c}\right)^2 = \frac{1}{a^2} + \frac{1}{b^2} = (34.7)^2 + \frac{1}{b^2} - \frac{1}{d^2}$$

$$\left(\frac{2f_{102}}{c}\right)^2 = \frac{1}{a^2} + \frac{4}{d^2} = (34.7)^2 + \frac{3}{d^2}$$

$$\left(\frac{2f_{011}}{c}\right)^2 = \frac{1}{b^2} + \frac{1}{d^2}$$

Since  $d > a$ ,  $f_{011} < f_{110}$

Try  $f_{011} = 6.5 \text{ GHz}$ ;  $f_{110} = 7.2 \text{ GHz}$

Then we have,  $\frac{1}{b^2} - \frac{1}{d^2} = 1100$ .

$$\frac{1}{b^2} + \frac{1}{d^2} = 1878.$$

Solving gives,

$$b = 2.60 \text{ cm } \checkmark$$


$$d = 5.00 \text{ cm } \checkmark$$

$$a = 3.53 \text{ cm } \checkmark$$

CHECK:

$$b < a < d \quad \text{OK } \checkmark$$

$$f_{102} = 7.35 \text{ GHz} > f_{110} = 7.2 \text{ GHz } \checkmark$$

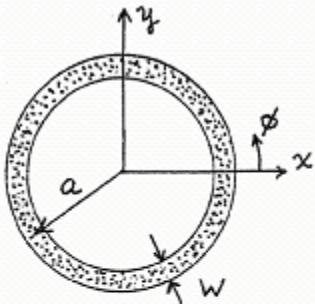**6.16**

$$e^{\pm j \beta a \phi} = e^{\pm j n \phi}, \quad n=1, 2, 3, \dots$$

FOR PERIODICITY

$$\text{So, } \beta a = \frac{2\pi a}{\lambda_g} = \frac{2\pi a \sqrt{\epsilon_r} f}{c} = n$$

$$f = \frac{n c}{2\pi a \sqrt{\epsilon_r}}; \quad n=1, 2, 3, \dots$$

(The ring circumference is  $2\pi a = n \lambda_g$ )

The above result assumes  $a \gg w$ , so that curvature effects can be neglected. This type of resonator is most often coupled using a gap feed to a microstripline.

**6.17**

For  $TM_{nmo}$  modes we have  $H_z=0$  and  $\frac{\partial H_\phi}{\partial z}=0$ . The wave equation for  $E_z$  is,

$$\left( \frac{\partial^2}{\partial p^2} + \frac{1}{p} \frac{\partial}{\partial p} + \frac{1}{p^2} \frac{\partial^2}{\partial \phi^2} + k^2 \right) E_z = 0 \quad (\text{from 3.134})$$

The general solution is,

$$E_z = (A_n \cos n\phi + B_n \sin n\phi) J_n(kp) \quad (\text{finite at } p=0)$$

Since the choice of  $\sin n\phi$  or  $\cos n\phi$  (or any combination) depends only on the choice of the  $\phi=0$  reference, we can let  $B_n=0$ .

Then,

$$E_z = A_n \cos n\phi J_n(kp)$$

We can find  $H_\phi$  from (3.110d):

$$H_\phi = -j \frac{w \epsilon_r}{k^2} \frac{\partial E_z}{\partial p} = -j \frac{w \epsilon_r}{k} A_n \cos n\phi J'_n(kp)$$

For  $H_\phi=0$  at  $p=a$  we require  $J'_n(ka)=0$ , or  $ka = \varphi'_{nm}$ . So the resonant frequency is,

$$f_{nmo} = \frac{c k}{2\pi \sqrt{\epsilon_r}} = \frac{c \varphi'_{nm}}{2\pi a \sqrt{\epsilon_r}}$$

and,

$$f_{110} = \frac{c \varphi'_{111}}{2\pi a \sqrt{\epsilon_r}} = \frac{1.841c}{2\pi a \sqrt{\epsilon_r}} \quad \checkmark$$

This solution neglects the effect of fringing fields.

**6.18**

From (6.70),  $\tan \beta L/2 = \alpha/\beta$ ,  
 with  $\alpha = \sqrt{\left(\frac{2.405}{a}\right)^2 - k_0^2}$

$$\beta = \sqrt{\epsilon_r k_0^2 - (2.405/a)^2}$$

The value of  $k_0$  at resonance must lie between  
 $k_0 = \frac{2.405}{a} = 602$ , and  $k_0 = \frac{2.405}{a\sqrt{\epsilon_r}} = 100$ .

We carry out a trial-and-error numerical search  
 as follows:

$k_0$	$\alpha$	$\beta$	$\tan \beta L/2 - \alpha/\beta$
110	592	275	-1.8
120	590	399	-1.02
150	583	672	.008
145	584	631	-.12
→ 149	583	664	-.0018

Thus, the resonant frequency is,

$$f_0 = \frac{ck_0}{2\pi} = 7.11 \text{ GHz } \checkmark$$

(measured value is 7.8 GHz)

6.19

Following the analysis of Section 6.5, for TE<sub>018</sub> mode:

$$H_z = H_0 J_0(k_c p) e^{\pm j \beta z}$$

$$E_\phi = \frac{j \omega \mu_0 H_0}{k_c} J_0'(k_c p) e^{\pm j \beta z} = A J_0'(k_c p) e^{\pm j \beta z}$$

$$H_p = \frac{\mp j \beta H_0}{k_c} J_0'(k_c p) e^{\pm j \beta z} = \frac{\mp A}{z_{TE}} J_0'(k_c p) e^{\pm j \beta z}$$

$$\text{for } |z| < L/2, \quad \beta = \sqrt{\epsilon_r k_c^2 - k_0^2} = \sqrt{\epsilon_r k_c^2 - (k_0/a)^2} \quad ; \quad z_{TE} = \frac{\omega \mu_0}{\beta} = z_d$$

$$\text{for } |z| > L/2, \quad j\beta = \alpha = \sqrt{k_c^2 - k_0^2} = \sqrt{(k_0/a)^2 - k_0^2} \quad ; \quad z_{TE} = \frac{j\omega \mu_0}{\alpha} = z_a$$

So the standing wave fields can be written as,

$$E_\phi = \begin{cases} A J_0'(k_c p) [e^{j\beta z} - e^{-j\beta z}] = -2j A J_0'(k_c p) \sin \beta z & \text{for } |z| < L/2 \\ B J_0'(k_c p) e^{-\alpha z} & \text{for } z > L/2 \end{cases}$$

$$H_p = \begin{cases} \frac{A}{z_d} J_0'(k_c p) [e^{j\beta z} + e^{-j\beta z}] = \frac{2A}{z_d} J_0'(k_c p) \cos \beta z & \text{for } |z| < L/2 \\ \frac{B}{z_a} J_0'(k_c p) e^{-\alpha z} & \text{for } z > L/2 \end{cases}$$

Continuity of  $E_\phi$  and  $H_p$  at  $z=L/2$  gives:

$$E_\phi: -2j A \sin \beta L/2 = B e^{-\alpha L/2}$$

$$H_p: \frac{2A}{z_d} \cos \beta L/2 = \frac{B}{z_a} e^{-\alpha L/2}$$

dividing gives:

$$-j z_d \tan \beta L/2 = z_a$$

$$\frac{-j}{\beta} \tan \beta L/2 = j/\alpha$$

$$\tan \beta L/2 + \beta/\alpha = 0 \quad \checkmark$$

6.20

assume  $a > b$ 

Because of the magnetic wall boundary conditions on the sidewalls, a rectangular dielectric waveguide along the  $z$ -axis would support TE modes with an  $H_z$  field of the form,

$$H_z = H_0 \sin \frac{m\pi x}{a} \sin \frac{n\pi y}{b},$$

so the lowest order TE mode would be the  $TE_{11}$  mode. But  $H_z \equiv 0$  for TM modes, so the lowest order TM mode would have,

$$H_x = H_0 \sin \frac{\pi x}{a}, \quad H_y = 0 \quad (\text{if } a > b)$$

So the dominant mode of this resonator must be the  $TM_{108}$  mode. Thus we can write,


$$E_y = E_0 \sin \frac{\pi x}{a} e^{\pm j\beta z}$$

$$H_x = \frac{\pm E_0}{Z_{TM}} \sin \frac{\pi x}{a} e^{\pm j\beta z},$$

where,

$$\beta = \sqrt{\epsilon_r k_0^2 - (\pi/a)^2} \quad \text{for } |z| < c/2$$
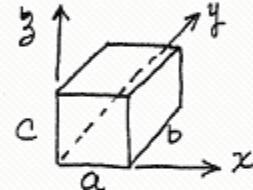
$$j\beta = \alpha = \sqrt{(\pi/a)^2 - k_0^2} \quad \text{for } z > c/2,$$



$$\text{and } Z_{TM} = Z_d = \beta n/k = \beta n_0/\epsilon_r k_0 \quad \text{for } |z| < c/2,$$

$$Z_{TM} = Z_a = j\alpha n_0/k_0. \quad \text{for } z > c/2$$

Then the standing wave fields can be written as,

$$E_y = \begin{cases} A \sin \frac{\pi x}{a} [e^{j\beta z} + e^{-j\beta z}] = 2A \sin \frac{\pi x}{a} \cos \beta z & \text{for } |z| < c/2 \\ B \sin \frac{\pi x}{a} e^{-\alpha z} & \text{for } z > c/2 \end{cases}$$

$$H_x = \begin{cases} \frac{A}{Z_d} \sin \frac{\pi x}{a} [-e^{-j\beta z} + e^{j\beta z}] = \frac{2jA}{Z_d} \sin \frac{\pi x}{a} \sin \beta z & \text{for } |z| < c/2 \\ -\frac{B}{Z_a} \sin \frac{\pi x}{a} e^{-\alpha z} & \text{for } z > c/2 \end{cases}$$

Continuity of  $E_y, H_x$  at  $z = c/2$ :

$$2A \cos \beta c/2 = B e^{-\alpha c/2}$$

$$\frac{2jA}{Z_d} \sin \beta c/2 = -\frac{B}{Z_a} e^{-\alpha c/2}$$

divide to get:

$$\alpha \epsilon_r \tan \beta c/2 + \beta = 0$$

6.21

a)  $d = \ell \lambda_0 / 2 = \frac{\ell}{2} \frac{c}{f_0} \Rightarrow f_0 = \frac{\ell c}{2d} \quad \checkmark$

b)  $E_x = E_0 \sin k_0 z$

$$H_y = j \frac{E_0}{\eta_0} \cos k_0 z$$

$$W_e = \frac{\epsilon_0}{4} \int_{z=0}^d |E_x|^2 dz = \frac{\epsilon_0 |E_0|^2}{4} \int_{z=0}^d \sin^2 \frac{\ell \pi z}{d} dz = \frac{\epsilon_0 |E_0|^2 d}{8}$$

$$W_m = \frac{\mu_0}{4} \int_{z=0}^d |H_y|^2 dz = \frac{\mu_0 |E_0|^2}{4 \eta_0^2} \int_{z=0}^d \cos^2 \frac{\ell \pi z}{d} dz = \frac{\mu_0 |E_0|^2 d}{8 \eta_0^2} = \frac{\epsilon_0 |E_0|^2 d}{8}$$

Thus  $W_e = W_m$  at resonance  $\checkmark$

$$P_c = 2 \left( \frac{R_s}{2} \right) |H_y(z=0)|^2 = \frac{R_s |E_0|^2}{\eta_0^2}, \quad R_s = \sqrt{\frac{\omega \mu_0}{2 \sigma}}$$


$$Q_C = \omega (W_e + W_m) / P_c = \frac{\omega \epsilon_0 d \eta_0^2}{4 R_s} = \frac{C \pi \ell \epsilon_0 \eta_0^2}{4 R_s} = \frac{\pi \ell \eta_0}{4 R_s}$$

c)  $f_0 = \frac{(25)(3 \times 10^8)}{2(.04)} = 93,8 \text{ GHz}$

$$R_s = 0.08 \Omega$$

$$Q_C = \frac{\pi (25)(377)}{4 (.08)} = 92,500$$

6.22

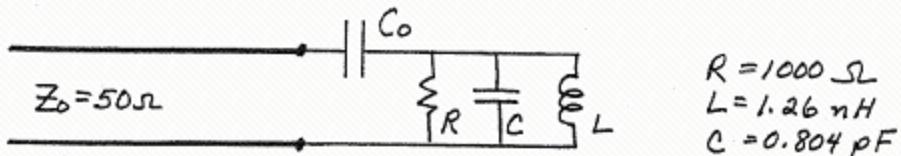

The simplest way to solve this problem is graphically, with a Smith chart. The admittance of the resonator at frequencies near resonance is,

$$Y_R = \frac{1}{R} + j \frac{2Q\Delta\omega}{R\omega_0},$$

$$\text{where } \omega_0 = \frac{1}{\sqrt{LC}} = 3.142 \times 10^6 \text{ RPS}; \quad f_0 = \frac{\omega_0}{2\pi} = 5.00 \text{ GHz}$$

$$Q = \frac{R}{\omega_0 L} = 25.3$$

Normalized to  $Z_0$ , we have  $Y_R = Z_0 Y_r = 0.05 + j 2.53 \frac{\Delta\omega}{\omega_0}$ . We can plot  $Y_R$  on a Smith chart, versus  $\Delta\omega/\omega_0$ . For  $\Delta\omega=0$ ,  $Y_R=0.05$ . For  $\Delta\omega=\pm 0.1\omega_0$ ,  $Y_R=0.05 \pm j 0.253$ .

Next, convert this locus to  $Z_R$ , an impedance locus. Then we see that a series capacitive reactance of  $-jX_{C_0} = -j4.2$  will yield an input impedance of  $Z_{in}=1$ . This corresponds to a resonator admittance

$Y_R = 0.05 - j 0.22$ . So the resonant frequency will be,

$$\Delta\omega = \frac{-0.22\omega_0}{2.53} = -0.0869\omega_0$$

$$\omega_r = \omega_0 + \Delta\omega = (1 - 0.0869)\omega_0 = 0.913\omega_0$$

$$\text{so, } f_r = \frac{\omega_r}{2\pi} = 4.566 \text{ GHz} \quad (\text{note lowering from } f_0)$$


The coupling capacitor value is,

$$C_0 = \frac{1}{4.2Z_0\omega_r} = 0.166 \text{ pF.}$$

CHECK: at 4.566 GHz,  $Y_R = (1 - j 4.39) \times 10^{-3} \text{ S}$

$$Z_R = 49.2 + j 216.5 \Omega \approx 50 + j X_{C_0}$$

$$\frac{1}{j\omega C_0} = -j 210.$$

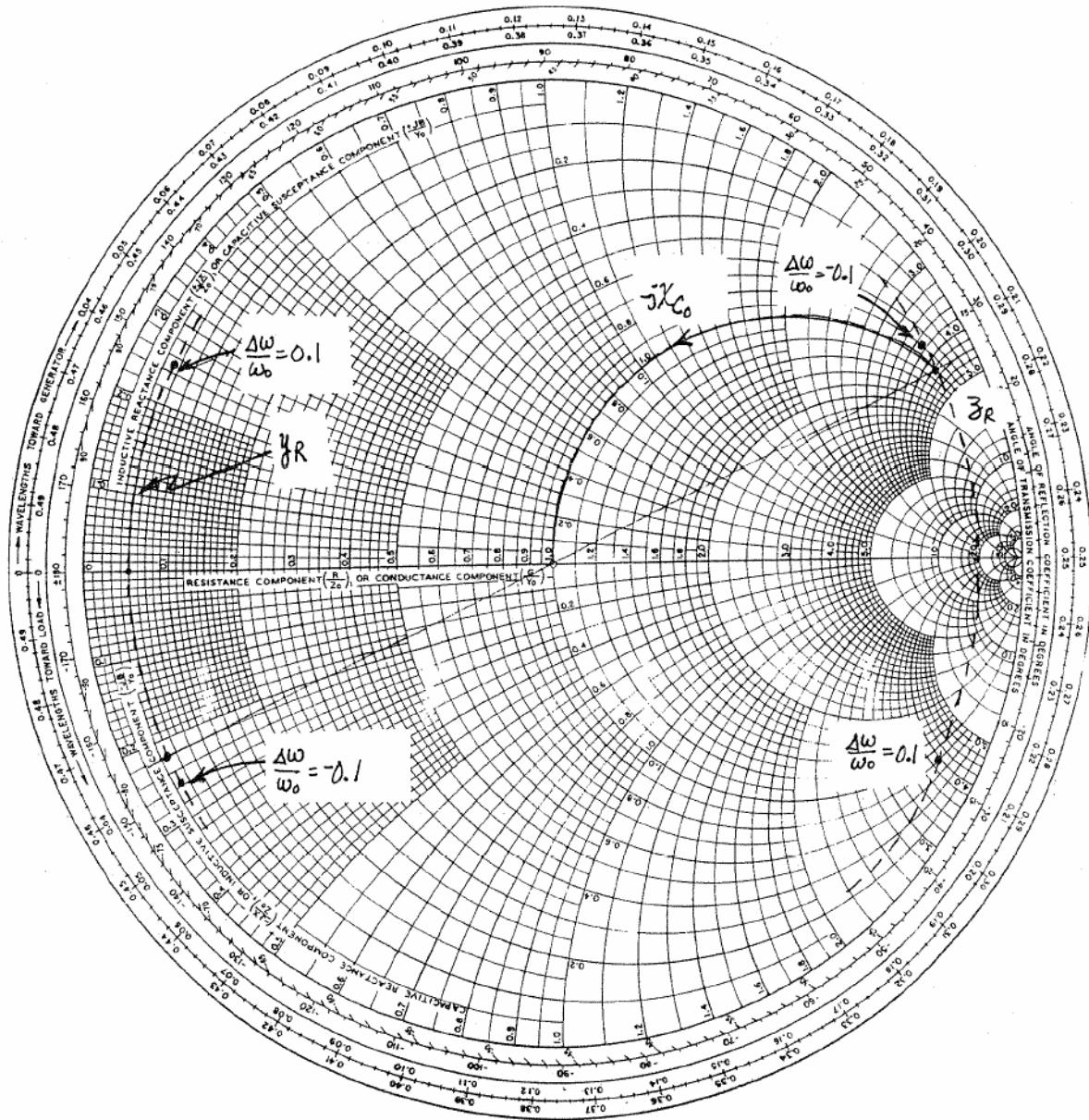

**6.23** Assume  $TE_{101}$  mode, as in Section 6.6.

At 9 GHz,  $k_0 = 188. m^{-1}$ ;  $\beta_0 = 140.5 m^{-1}$ ;  $l = \frac{\lambda_0}{2} = \frac{\pi}{\beta_0} = 2.24 \text{ cm}$ .

$\frac{\omega_0}{2\pi} = f_0 = 9 \text{ GHz}$  is the resonant frequency of the closed cavity, and does not include the effect of the coupling aperture. For a high-Q cavity, the actual resonant frequency,  $\omega_1$ , will be close to  $\omega_0$ . So we can approximately compute  $\chi_L$  using  $\omega_0$ . From (6.89),

$$\chi_L = \sqrt{\frac{\pi k_0 \omega_1}{2 Q \beta^2 C}} = 0.016 = \frac{\omega L}{Z_0} \Rightarrow \frac{L}{Z_0} = 2.83 \times 10^{-13}$$


Then solve (6.85) for  $\omega$ :

$$\tan \beta l + \chi_L = 0$$

Numerical trial-and-error:

$f$	$\beta$	$\chi_L$	$\tan \beta l + \chi_L$
9	140.	.0160	.01
8.9	137.7	.0158	-.04
8.97	139.65	.0159	.0025

Thus,  $f_1 = 8.97 \text{ GHz}$

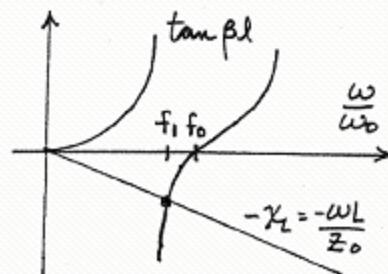

**6.24**


$$f_1 = 2.9985 \text{ GHz}$$

$$f_2 = 3.0015 \text{ GHz}$$

so  $f_0 = 3.0000 \text{ GHz}$ ,  $BW = 0.1\%$ ,  $Q_L = \frac{1}{BW} = 1000$ .

at resonance,  $RL = 14 \text{ dB} \Rightarrow \Gamma = 0.200 \Rightarrow r = \frac{1+\Gamma}{1-\Gamma} = 1.5$

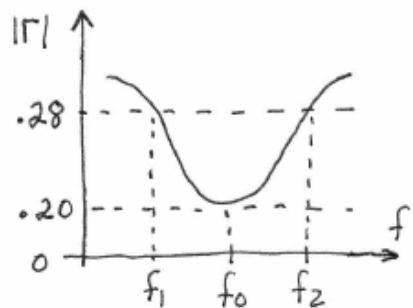at  $f_1$  or  $f_2$ ,  $RL = 11 \text{ dB} \Rightarrow \Gamma = 0.282$



assuming a series resonance,  
from (6.91),  $g = \frac{Z_0}{R} = \frac{1}{r} = 0.667$

$$Q_0 = (1+g)Q_L = \underline{\underline{1667}}$$

assuming parallel resonator :  $g = \frac{R}{Z_0} = r = 1.5$

$$Q_0 = (1+g)Q_L = \underline{\underline{2500}}$$

**6.25**

$f(\text{GHz})$	$ IL(\text{dB}) $	$ S_{21} (\text{dB})$	$ S_{21} $
3.0000	1.94	-1.94	0.800
2.9925	4.95	-4.95	
3.0075	4.95	-4.95	

$$Q_L = \frac{3}{.015} = 200 , g = \frac{S}{1-S} = \frac{.8}{1-.8} = 4.0$$

From (6.91)  $Q_0 = Q_L(1+g) = 1000 \checkmark$

## Chapter 7

### 7.1

From (7.17) an ideal symmetric coupler has

$$[S] = \begin{bmatrix} 0 & \alpha & j\beta & 0 \\ \alpha & 0 & 0 & j\beta \\ j\beta & 0 & 0 & \alpha \\ 0 & j\beta & \alpha & 0 \end{bmatrix}$$

a non-ideal matched symmetric coupler has


$$[S] = \begin{bmatrix} 0 & Y_L & j/c & Y_I \\ Y_L & 0 & Y_I & j/c \\ j/c & Y_I & 0 & Y_L \\ Y_I & j/c & Y_L & 0 \end{bmatrix}$$

From (7.18) an ideal anti-symmetric coupler has

$$[S] = \begin{bmatrix} 0 & \alpha & \beta & 0 \\ \alpha & 0 & 0 & -\beta \\ \beta & 0 & 0 & \alpha \\ 0 & -\beta & \alpha & 0 \end{bmatrix}$$

a non-ideal matched anti-symmetric coupler has

$$[S] = \begin{bmatrix} 0 & Y_L & Y_C & Y_I \\ Y_L & 0 & Y_I & -Y_C \\ Y_C & Y_I & 0 & Y_L \\ Y_I & -Y_C & Y_L & 0 \end{bmatrix}$$

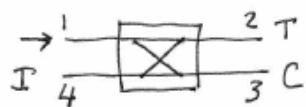**7.2**

$$P_{in} = 20 \text{ dBm}, C = 20 \text{ dB}, D = 35 \text{ dB}, L = 0.5 \text{ dB}, RL = \infty \text{ dB}.$$

$$C = 10 \log P_1/P_3, D = 10 \log P_3/P_4, I = 10 \log P_1/P_4, L = 10 \log P_1/P_2 \text{ in dB,}$$

$$\text{Through : } P_2 = P_1 - L = 20 - .5 = 19.5 \text{ dBm}$$

$$\text{Coupled : } P_3 = P_1 - C = 20 - 20 = 0 \text{ dBm}$$

$$\text{Isolated : } P_4 = P_3 - D = 0 - 35 = -35 \text{ dBm}$$

**7.3**

$$[S] = \begin{bmatrix} 0.1 \angle 40^\circ & 0.944 \angle 90^\circ & 0.178 \angle 180^\circ & 0.0056 \angle 90^\circ \\ 0.944 \angle 90^\circ & 0.1 \angle 40^\circ & 0.0056 \angle 90^\circ & 0.178 \angle 180^\circ \\ 0.178 \angle 180^\circ & 0.0056 \angle 90^\circ & 0.1 \angle 40^\circ & 0.944 \angle 90^\circ \\ 0.0056 \angle 90^\circ & 0.178 \angle 180^\circ & 0.944 \angle 90^\circ & 0.1 \angle 40^\circ \end{bmatrix}$$


$$RL = -20 \log |S_{11}| = -20 \log 0.1 = 20 \text{ dB}$$

$$C = -20 \log |S_{13}| = -20 \log 0.178 = 15 \text{ dB}$$

$$D = 20 \log \left| \frac{S_{13}}{S_{14}} \right| = 20 \log \left| \frac{.178}{.0056} \right| = 30 \text{ dB}$$

$$L = -20 \log |S_{12}| = -20 \log .944 = +0.5 \text{ dB}$$

7.4

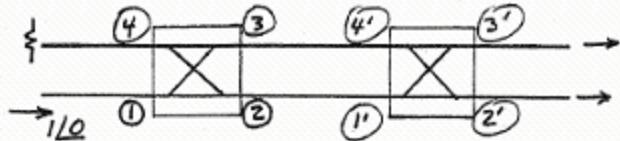

$$C = 8.34 \text{ dB} \Rightarrow \beta = |S_{13}| = 0.383$$

$$\alpha = \sqrt{1 - \beta^2} = 0.924$$

If  $V_1^+ = 1 \angle 0^\circ$ , then from (7.17),

$$V_3^- = j\beta V_1^+ = 0.383 \angle 90^\circ$$

$$V_2^- = \alpha V_1^+ = 0.924 \angle 0^\circ$$

Then the outputs of the second coupler are,

$$\begin{aligned} V_3'^- &= j\beta V_1'^+ + \alpha V_4'^+ = j\beta V_2^- + \alpha V_3^- \\ &= (0.383)(0.924) \angle 90^\circ + (0.924)(0.383) \angle 90^\circ = 0.707 \angle 90^\circ \quad \checkmark \end{aligned}$$

$$\begin{aligned} V_2'^- &= \alpha V_1'^+ + j\beta V_4'^+ = \alpha V_2^- + j\beta V_3^- \\ &= (0.924)(0.924) \angle 0^\circ - (0.383)(0.383) \angle 0^\circ = 0.707 \angle 0^\circ \quad \checkmark \end{aligned}$$

Thus the outputs are identical to those for a single 3dB hybrid.

7.5

This is a special case of a lossless reciprocal 3-port network; it was shown in general that such a network could not be matched at all ports (using the [S] matrix). Alternatively, we can argue as follows: If the input to each port is to be matched to its respective characteristic impedance, we must have,

$$\frac{1}{z_1} = \frac{1}{z_2} + \frac{1}{z_3} \quad (\text{port 1})$$


$$\frac{1}{z_2} = \frac{1}{z_1} + \frac{1}{z_3} \quad (\text{port 2})$$

$$\frac{1}{z_3} = \frac{1}{z_1} + \frac{1}{z_2} \quad (\text{port 3})$$

It is not possible to satisfy these three equations simultaneously:

$$\det \begin{bmatrix} 1 & -1 & -1 \\ 1 & 1 & 1 \\ 1 & 1 & -1 \end{bmatrix} = -4 \neq 0$$

7.6

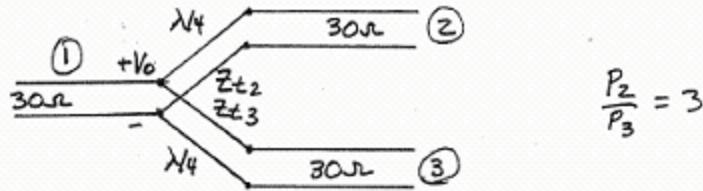

$$\frac{P_2}{P_3} = 3$$

$$P_1 = \frac{1}{2} \frac{V_0^2}{Z_0}$$

$$P_2 = \frac{1}{2} \frac{V_0^2}{Z_2} = \frac{3}{4} P_1 = \frac{1}{2} V_0^2 \left( \frac{3}{4 Z_0} \right)$$

$$P_3 = \frac{1}{2} \frac{V_0^2}{Z_3} = \frac{1}{4} P_1 = \frac{1}{2} V_0^2 \left( \frac{1}{4 Z_0} \right)$$

$$\text{So, } Z_2 = 4 Z_0 / 3 = 40 \Omega \quad \checkmark$$

$$Z_3 = 4 Z_0 = 120 \Omega \quad \checkmark$$

The  $\lambda/4$  matching transformers have impedances,

$$Z_{t2} = \sqrt{30(40)} = 34.6 \Omega \quad \checkmark$$

$$Z_{t3} = \sqrt{30(120)} = 60.0 \Omega \quad \checkmark$$

Then the S-parameters are, (phase ref. at  $30\omega$  ports)

$$S_{11} = \frac{30-30}{30+30} = 0$$

$$S_{22} = \frac{30||120 - 40}{30||120 + 40} = \frac{24-40}{24+40} = -0.25 \quad \checkmark$$

$$S_{33} = \frac{30||40 - 120}{30||40 + 120} = \frac{17.1-120}{17.1+120} = -0.75 \quad \checkmark$$

$$S_{21} = S_{12} = \sqrt{P_2/P_1} e^{j\theta} = \sqrt{3/4} \angle -90^\circ = 0.866 \angle -90^\circ \quad \checkmark$$

$$S_{31} = S_{13} = \sqrt{P_3/P_1} e^{j\theta} = \sqrt{1/4} \angle -90^\circ = 0.50 \angle -90^\circ \quad \checkmark$$

Since the network is lossless, we should have,

$$|S_{21}|^2 + |S_{22}|^2 + |S_{23}|^2 = 1$$

$$\text{Ans, } S_{23} = S_{32} = \sqrt{1-(.25)^2-(.866)^2} e^{-j\theta} = 0.433 \angle -180^\circ \quad \checkmark$$

7.7

T-NETWORK: From Table 4.1 the ABCD parameters are

$$A = 1 + R_1/R_2 \quad B = 2R_1 + R_1^2/R_2$$

$$C = 1/R_2 \quad D = 1 + R_1/R_2$$

Convert to S-parameters using Table 4.2:

$$S_{11} = \frac{A+B/Z_0 - C Z_0 - D}{A+B/Z_0 + C Z_0 + D} = 0 \Rightarrow 1 + \frac{R_1}{R_2} + \frac{2R_1}{Z_0} + \frac{R_1^2}{Z_0 R_2} - \frac{Z_0}{R_2} = 1 - \frac{R_1}{R_2} = 0$$

$$R_1^2 + 2R_1 R_2 - Z_0^2 = 0$$

$$R_2 = \frac{Z_0^2 - R_1^2}{2R_1}$$

$$S_{12} = \frac{2}{A+B/Z_0 + C Z_0 + D} = \alpha \Rightarrow 2 + \frac{2R_1}{R_2} + \frac{2R_1}{Z_0} + \frac{R_1^2}{Z_0 R_2} + \frac{Z_0}{R_2} = \frac{2}{\alpha}$$

$$2Z_0 R_2 + 2Z_0 R_1 + \underbrace{2R_1 R_2 + R_1^2 + Z_0^2}_{= Z_0^2} = \frac{2}{\alpha} Z_0 R_2$$

$$R_2 + R_1 + Z_0 = R_2/\alpha$$

$$(\frac{1}{\alpha} - 1)(Z_0 - R_1) = 2R_1$$

$$Z_0(\frac{1}{\alpha} - 1) = R_1(1 + \frac{1}{\alpha})$$

$$R_1 = Z_0 \frac{1 - \alpha}{1 + \alpha} \quad \checkmark$$

$$R_2 = \frac{2\alpha}{1 - \alpha^2} Z_0 \quad \checkmark$$

For  $Z_0 = 50 \Omega$ :

$\alpha$ (dB)	$\alpha$	$R_1(\Omega)$	$R_2(\Omega)$
3	.708	8.6	141.9
10	.316	26.0	35.1
20	.100	40.9	10.1

$\Pi$ -NETWORK: From Table 4.1 the ABCD parameters are,

$$A = 1 + R_2/R_1 \quad B = R_2$$

$$C = \frac{2}{R_1} + \frac{R_2}{R_1^2} \quad D = 1 + R_2/R_1$$

Convert to S-parameters using Table 4.2:

$$S_{11} = \frac{A + B/Z_0 - C Z_0 - D}{A + B/Z_0 + C Z_0 + D} = 0 \Rightarrow \frac{R_2}{Z_0} - \frac{2Z_0}{R_1} - \frac{R_2 Z_0}{R_1^2} = 0$$

$$R_2 R_1^2 - 2 Z_0^2 R_1 - R_2 Z_0^2 = 0$$

$$R_2 = \frac{2 Z_0^2 R_1}{R_1^2 - Z_0^2}$$

$$S_{12} = \frac{\alpha}{A + B/Z_0 + C Z_0 + D} = \alpha \Rightarrow \alpha + \frac{2 R_2}{R_1} + \frac{R_2}{Z_0} + \underbrace{\frac{2 Z_0}{R_1} + \frac{Z_0 R_2}{R_1^2}}_{= R_2/Z_0} = \frac{\alpha}{\alpha}$$

$$1 + \frac{R_2}{R_1} + \frac{R_2}{Z_0} = \frac{1}{\alpha}$$

$$R_1 Z_0 + R_2 (Z_0 + R_1) = \frac{1}{\alpha} Z_0 R_1$$

$$2 Z_0 R_1 = R_1 Z_0 (\frac{1}{\alpha} - 1)(R_1 - Z_0)$$

$$\frac{2 Z_0 \alpha}{1 - \alpha} = R_1 - Z_0$$


$$R_1 = Z_0 \left( 1 + \frac{2 \alpha}{1 - \alpha} \right) = \frac{1 + \alpha}{1 - \alpha} Z_0 \quad \checkmark$$

$$R_2 = \frac{1 - \alpha^2}{2 \alpha} Z_0 \quad \checkmark$$

For  $Z_0 = 50 \Omega$ :

$\alpha$ (dB)	$\alpha$	$R_1 (\Omega)$	$R_2 (\Omega)$
3	.708	292.5	17.6
10	.316	96.2	71.2
20	.100	61.1	247.5

7.8

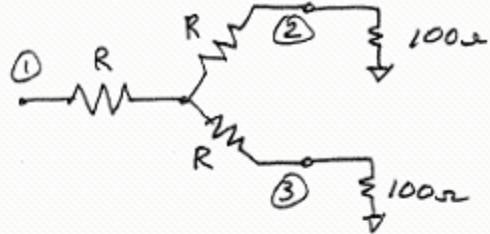

DESIGN:

$$Z_0 = 100 \Omega$$

$$R = 33.3 \Omega \quad \checkmark$$

$$[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$

CASE a) ports 2 & 3 matched to  $100 \Omega$  ( $V_2^+ = V_3^+ = 0$ ):

$$\text{If } V_1^+ = 1, \quad V_3^- = \frac{1}{2}[V_1^+ + V_2^+] = \frac{1}{2}$$

$$V_3 = V_3^+ + V_3^- = \frac{1}{2}$$

$$P_3 = V_3^2/Z_0 = 0.25/Z_0$$

CASE b) port 3 matched,  $\Gamma = 0.3$  at port 2 ( $V_3^+ = 0$ ):

$$\text{If } V_1^+ = 1, \quad V_2^- = \frac{1}{2}[V_1^+ + V_2^+] = \frac{1}{2}$$

$$V_2^+ = \Gamma V_2^- = (0.3)(\frac{1}{2}) = 0.15$$


$$V_3^- = \frac{1}{2}[V_1^+ + V_2^+] = \frac{1}{2}(1.15) = 0.575 \text{ V}$$

$$V_3 = V_3^+ + V_3^- = 0.575 \text{ V}$$

$$P_3 = V_3^2/Z_0 = 0.331/Z_0$$

$$\frac{P_3 (\text{PORT 2 MISMATCHED})}{P_3 (\text{PORT 2 MATCHED})} (\text{dB}) = 10 \log \left( \frac{0.331}{0.25} \right) = 1.2 \text{ dB}$$

7.9

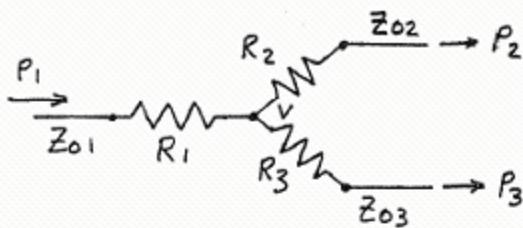

$$\alpha = \frac{P_2}{P_3}$$

$$\text{let } Z_1 = R_1 + Z_{01}$$

$$Z_2 = R_2 + Z_{02}$$

$$Z_3 = R_3 + Z_{03}$$

For  $\alpha = \frac{P_2}{P_3}$  we must have,

$$\frac{Z_{02} Z_3^2}{Z_2^2 Z_0} = \alpha \quad \dots (1)$$

For all three ports to be matched we must have,

$$Z_{01} = R_1 + \frac{Z_2 Z_3}{Z_2 + Z_3} \quad \dots (2)$$

$$Z_{02} = R_2 + \frac{Z_1 Z_3}{Z_1 + Z_3} \quad \dots (3)$$

$$Z_{03} = R_3 + \frac{Z_1 Z_2}{Z_1 + Z_2} \quad \dots (4)$$

We assume that  $Z_{01}$  and  $\alpha$  are given; then we have 5 unknowns ( $R_1, R_2, R_3, Z_{02}, Z_{03}$ ), and 4 equations. So we need one more equation: we will choose the condition that,

$$Z_{02} Z_{03} = Z_{01}^2 \quad \dots (5)$$

which will ensure that when  $\lambda/4$  transformers are used to match  $Z_{02}$  and  $Z_{03}$  to a final output impedance of  $Z_{01}$ , phase tracking will be maintained for ports 2 and 3. (See Problem 7.10). Now use (1) and (5) to eliminate  $Z_3$  and  $Z_{03}$  from (2), (3), (4). Then (2) reduces to,

$$R_1 = \frac{Z_{01} [Z_{02} + \sqrt{\alpha} (Z_{01} - Z_2)]}{Z_{02} + \sqrt{\alpha} Z_{01}}$$

$$Z_1 = \frac{Z_{01} [2Z_{02} + \sqrt{\alpha} (2Z_{01} - Z_2)]}{Z_{02} + \sqrt{\alpha} Z_{01}}$$

and (3) and (4) then reduce to,

$$Z_2[(Z_{02} + \sqrt{\alpha} Z_{01})^2 - \alpha Z_{01} Z_{02}] = 2Z_{02}^2 (Z_{02} + \sqrt{\alpha} Z_{01})$$

and,

$$Z_2[(Z_{02} + \sqrt{\alpha} Z_{01})^2 - Z_{01} Z_{02}] = 2Z_{01}^2 (Z_{02} + \sqrt{\alpha} Z_{01})$$

Then we obtain a quartic equation for  $Z_{02}$ :

$$Z_{02}^4 + Z_{01}(2\sqrt{\alpha} - 1)Z_{02}^3 + Z_{01}^2(\alpha - 1)Z_{02}^2 + Z_{01}^3(\alpha - 2\sqrt{\alpha})Z_{02} - \alpha Z_{01}^4 = 0$$

after finding  $Z_{02}$  (either numerically or using the formula for a quartic equation), the above equations can be used to find  $Z_{03}, R_2, R_3$ , and  $R_1$ .

EXAMPLE: let  $Z_{01} = 1, \alpha = 2$ ;

$$\text{Then, } Z_{02}^4 + 1.828Z_{02}^3 + Z_{02}^2 - 0.828Z_{02} - 2 = 0$$

The solution for  $Z_{02}$  was computed numerically using an HP-15C calculator to be,

$$Z_{02} = 0.8935$$

Then,

$$Z_2 = 1.041 ; R_2 = 0.1478$$

$$Z_3 = 1.6477 ; R_3 = 0.5285 ; Z_{03} = 1.1192 \\ R_1 = 0.3621$$

$$\text{CHECK: } Z_{in} = R_1 + Z_2 // Z_3 = 1,000 \checkmark$$

NOTE: There are other choices for the relation between  $Z_{02}$  and  $Z_{03}$ , or other pairs of variables. One possibility that may give a simpler solution would be to let  $Z_1 = \alpha^{1/3} Z_2$ .

**7.10**

From (7.37),  $K^2 = P_3/P_2 = 1/3 \Rightarrow K = 0.577$

$$Z_{03} = Z_0 \sqrt{\frac{1+K^2}{K^3}} = 131.7 \Omega \checkmark$$

$$Z_{02} = K^2 Z_{03} = 43.9 \Omega \checkmark$$


$$R = Z_0 (K + 1/K) = 115.5 \Omega \checkmark$$

The output impedances are,


$$R_2 = Z_0 K = 28.9 \Omega \checkmark$$

$$R_3 = Z_0 / K = 86.7 \Omega \checkmark$$

7.11

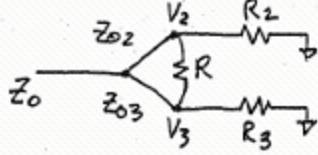

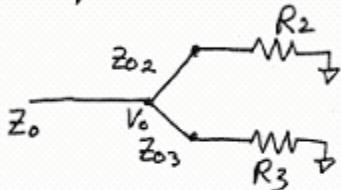assuming the output ports are matched, no power should be dissipated in resistor  $R$  (for lossless power division). Therefore  $V_2 = V_3$ , and the resistor  $R$  can be removed:



Input matching requires that,

$$\frac{1}{Z_0} = \frac{R_2}{Z_{02}^2} + \frac{R_3}{Z_{03}^2}$$

Power division requires that  $P_3 = K^2 P_2$ :

$$P_2 = \frac{1}{2} |V_0|^2 R_2 / Z_{02}^2$$

$$P_3 = \frac{1}{2} |V_0|^2 R_3 / Z_{03}^2 = K^2 P_2$$

Thus,

$$K^2 \frac{R_2}{Z_{02}^2} = \frac{R_3}{Z_{03}^2}$$

and,

$$Z_{02}^2 = Z_0 R_2 (1+K^2) \quad \dots (1)$$

$$Z_{03}^2 = Z_0 R_3 (1+1/K^2) \quad \dots (2)$$


For output matching,

PORt 2:

$$R_2 = R \parallel \frac{Z_{02}^2}{Z_0} = \frac{R R_2 (1+K^2)}{R+R_2(1+K^2)}$$


$$R_2 (1+K^2) = R K^2 \quad \dots (3)$$

PORt 3:

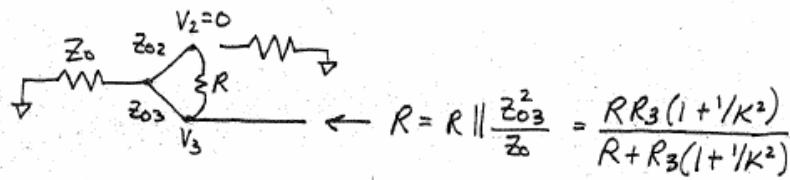

$$R_3(1 + K^2) = R \quad \dots (4)$$

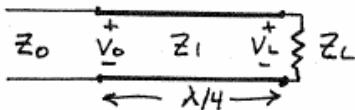
From (3) and (4) we have that  $R_2 = K^2 R_3$ . We need one more condition to obtain the design equations. This condition is that the output impedances  $R_2, R_3$  be chosen so that output matching transformers have the same transfer phase at both ports:



It is easy to show that,

$$\frac{V_L}{V_0} = -j \cdot \frac{1 + \Gamma}{1 - \Gamma}; \quad \Gamma = \frac{Z_L - Z_1}{Z_L + Z_1}$$

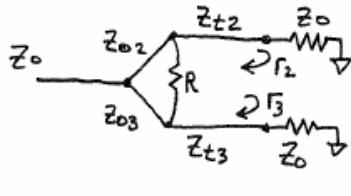So the phase of  $V_L/V_0$  does not change when  $\Gamma$  is replaced by  $-\Gamma$ , or when  $Z_L$  and  $Z_1$  are interchanged ( $Z_L, Z_1$  real).



$$\Gamma_2 = \frac{Z_0/Z_{t2} - 1}{Z_0/Z_{t2} + 1}$$

$$\Gamma_3 = \frac{Z_0/Z_{t3} - 1}{Z_0/Z_{t3} + 1}$$

So we choose  $Z_{t2} Z_{t3} = Z_0^2 = \sqrt{Z_0 R_2} \sqrt{Z_0 R_3} = K Z_0 R_3$ , which leads to the design equations,

$$R_2 = K Z_0 \quad \checkmark$$

$$Z_{02} = Z_0 \sqrt{K(1 + K^2)} \quad \checkmark$$

$$R_3 = Z_0/K \quad \checkmark$$

$$Z_{03} = Z_0 \sqrt{\frac{1 + K^2}{K^3}} \quad \checkmark$$

**7.12**Setting  $A_{10} = 0$  from (7.40b) :

$$\left(\epsilon_0 \alpha_e + \frac{4\mu_0 m}{Z_{10}^2}\right) \sin^2 \frac{\pi s}{a} - \frac{4\mu_0 \pi^2 \alpha_m}{\beta^2 a^2 Z_{10}^2} \cos^2 \frac{\pi s}{a} = 0$$

For a round aperture,  $\alpha_e = 2r_0^3/3$ ;  $\alpha_m = 4r_0^3/3$ :

$$\left(\epsilon_0 + \frac{2\mu_0}{Z_{10}^2}\right) \sin^2 \frac{\pi s}{a} - \frac{2\mu_0 \pi^2}{\beta^2 a^2 Z_{10}^2} \cos^2 \frac{\pi s}{a} = 0$$

Since  $Z_{10} = k_0 \eta_0 / \beta$ , this simplifies as follows:

$$(k_0^2 + 2\beta^2) \sin^2 \frac{\pi s}{a} - \frac{2\pi^2}{a^2} \cos^2 \frac{\pi s}{a} = 0$$

$$(3k_0^2 - \frac{2\pi^2}{a^2}) \sin^2 \frac{\pi s}{a} - \frac{2\pi^2}{a^2} (1 - \sin^2 \frac{\pi s}{a}) = 0$$

$$3k_0^2 \sin^2 \frac{\pi s}{a} = \frac{2\pi^2}{a^2}$$

$$\frac{6a^2}{\lambda_0^2} \sin^2 \frac{\pi s}{a} = 1, \text{ or } \sin \frac{\pi s}{a} = \frac{\lambda_0}{\sqrt{16a}} < 1 \text{ for } a > \lambda_0/2$$

**7.13**at  $f = 11 GHz$ ,  $k_0 = 230.4 m^{-1}$ ;  $\beta = 116.4 m^{-1}$ ;  $Z_{10} = k_0 \eta_0 / \beta = 746.2 \Omega$   
 $P_{10} = ab/Z_{10} = 1.67 \times 10^{-7} W$ 

From (7.41) the position of the coupling aperture is,

$$\sin \frac{\pi s}{a} = \pi \sqrt{\frac{2}{4\pi^2 - k_0^2 a^2}} = 0.867 \Rightarrow s = 0.334 a = 0.528 cm$$


Then,  $\sin^2 \frac{\pi s}{a} = 0.752$ ,  $\cos^2 \frac{\pi s}{a} = 0.248$ For  $C = 20 dB$ ,  $\left| \frac{A_{10}}{A} \right| = 0.1$ . From (7.40b) we have,

$$0.1 = \frac{W}{P_{10}} \left[ \frac{2}{3} \epsilon_0 \sin^2 \frac{\pi s}{a} + \frac{4\mu_0}{3 Z_{10}^2} \left( \sin^2 \frac{\pi s}{a} - \frac{\pi^2}{\beta^2 a^2} \cos^2 \frac{\pi s}{a} \right) \right] r_0^3$$

$$0.1 P_{10} = \left[ \frac{2}{3} \frac{k_0}{\eta_0} \sin^2 \frac{\pi s}{a} + \frac{4k_0 \eta_0}{3 Z_{10}^2} \left( \sin^2 \frac{\pi s}{a} - \frac{\pi^2}{\beta^2 a^2} \cos^2 \frac{\pi s}{a} \right) \right] r_0^3$$

$$1.67 \times 10^{-8} = 3.12 \times 10^{-1} r_0^3$$

$$r_0 = 3.77 mm$$

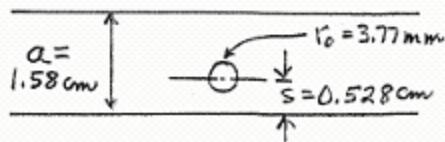

**7.14** at  $f = 17 \text{ GHz}$ ,  $k_0 = 356. \text{ m}^{-1}$ ,  $\beta = 295.3 \text{ m}^{-1}$ ,  
 $Z_{10} = k_0 \eta_0 / \beta = 454 \Omega$ ,  $P_{10} = ab / Z_{10} = 2.75 \times 10^{-7} \text{ W}$

From (7.44) the necessary skew angle is, for  $s = a/2$ ,  
 $\cos \theta = k_0^2 / 2\beta^2 = 0.728 \Rightarrow \theta = 43^\circ \checkmark$

From (7.45) the aperture radius is,

$$\left| \frac{A_{10}}{A} \right| = 0.0316 = \frac{4k_0^2 r_0^3}{3ab\beta} = 4.58 \times 10^6 r_0^3 \Rightarrow r_0 = 1.90 \text{ mm} \checkmark$$

**7.15**  $N=4$  (5-holes)

$$k_0 = 366.5 \text{ m}^{-1}, \beta = 307.9 \text{ m}^{-1}, Z_{10} = k_0 \eta_0 / \beta = 448.8 \Omega$$

$$P_{10} = ab / Z_{10} = 2.78 \times 10^{-7} \Omega$$

From (7.40a), with  $s = a/2$ ,

$$|K_f| = \frac{2k_0}{3\eta_0 P_{10}} \left| 1 - 2\beta^2/k_0^2 \right| = 9.59 \times 10^5$$

From (7.55),

$$C = 20 \text{ dB} = -20 \log |K_f| - 20 \log k - 20 \log \sum_{n=0}^N C_n^N$$

For  $N=4$ ,  $\sum_{n=0}^N C_n^N = 1+4+6+4+1 = 16$ , so

$$20 = -119.6 - 20 \log k - 24.1$$

$$k = 6.53 \times 10^{-9}$$

From (7.54) the aperture radii are,

$$r_0 = k^{1/3} = 1.87 \text{ mm} = r_4$$

$$r_1 = (4k)^{1/3} = 2.97 \text{ mm} = r_3$$

$$r_2 = (6k)^{1/3} = 3.97 \text{ mm}$$

The spacing between the apertures is  $\lambda g/4 = 5.1 \text{ mm}$ .  
(Smaller apertures would result if  $s = a/4$  were used.)

7.16

$N=4$  (5 hole)

$$k_0 = 366.5 \text{ m}^{-1}, \beta = 307.9 \text{ m}^{-1}, z_0 = 448.8 \text{ m}$$
$$P_{10} = 2.78 \times 10^{-7} \text{ W}$$

From (7.40a,b) with  $s=a/2$ ,

$$|K_f| = \frac{2k_0}{3\eta_0 P_{10}} \left| 1 - \frac{2\beta^2}{k_0^2} \right| = 9.59 \times 10^5$$

From (7.59),

$$30 \text{ dB} = D_{\min} = 20 \log T_4(\sec \theta_m)$$
$$T_4(\sec \theta_m) = \cosh [4 \cosh^{-1}(\sec \theta_m)] = 31.6$$
$$\sec \theta_m = 1.587$$

From (7.57),

$$C = 20 \text{ dB} = -20 \log |K_f| - 20 \log k - 30$$
$$k = 3.30 \times 10^{-9}$$

From (7.56) and (6.60d) :

$$2[r_0^3 \cos 4\theta + r_1^3 \cos 2\theta + r_2^3] = k[\sec^4 \theta_m (\cos 4\theta + 4 \cos 2\theta + 3) - 4 \sec^2 \theta_m (\cos 2\theta + 1) + 1]$$

Then,


$$2r_0^3 = k \sec^4 \theta_m \Rightarrow r_0 = r_4 = 2.19 \text{ mm}$$

$$2r_1^3 = k[4 \sec^4 \theta_m - 4 \sec^2 \theta_m] \Rightarrow r_1 = r_3 = 2.93 \text{ mm}$$

$$2r_2^3 = k[3 \sec^4 \theta_m - 4 \sec^2 \theta_m + 1] \Rightarrow r_2 = 2.54 \text{ mm.}$$

The spacing between the apertures is  $\lambda/4 = 5.1 \text{ mm.}$

7.17

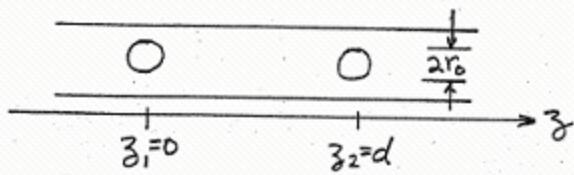

The incident TE<sub>10</sub> fields are, for  $x=0, y=b/2, z=z_n$ :

$$E_y = A \sin \frac{\pi x}{a} e^{-j\beta z} = 0$$

$$H_x = \frac{-A}{Z_0} \sin \frac{\pi x}{a} e^{-j\beta z} = 0$$

$$H_z = \frac{j\pi A}{\beta a Z_{10}} \cos \frac{\pi x}{a} e^{-j\beta z} = \frac{j\pi A}{\beta a Z_{10}} e^{-j\beta z_n}$$

$$P_{10} = ab/Z_{10}; \quad Z_{10} = k_0 \eta_0 / \beta.$$

From (4.124)-(4.125) the equivalent polarization currents are: ( $\hat{n} = \hat{x}$ )

$$\bar{P}_e = 0$$

$$\bar{P}_m = -\alpha_m H_z \delta(x) \delta(y - b/2) \delta(z - z_n) e^{-j\beta z_n}$$

Then the amplitudes of the forward and reverse coupled waves from a single aperture are,

$$A_{10}^+ = \frac{1}{P_{10}} \int_v \bar{H}_{10}^- \cdot j \omega \mu_0 \bar{P}_m dv = \frac{-j \omega \mu_0 \alpha_m}{P_{10}} \left( \frac{j\pi A}{\beta a Z_{10}} \right) e^{-j\beta z_n} H_3^- = \frac{j\pi^2 \alpha_m A}{P_{10} a^2 k_0 \eta_0}$$

$$A_{10}^- = \frac{1}{P_{10}} \int_v \bar{H}_{10}^+ \cdot j \omega \mu_0 \bar{P}_m dv = \frac{j\pi^2 \alpha_m A}{P_{10} a^2 k_0 \eta_0} e^{-2j\beta z_n}$$

Then the total forward and backward wave amplitudes from two apertures at  $z_1=0$  and  $z_2=d$  are,

$$A_{10}^+ = \frac{j\pi^2 \alpha_m A(2)}{P_{10} a^2 k_0 \eta_0} \quad A_{10}^- = \frac{j\pi^2 \alpha_m A}{P_{10} a^2 k_0 \eta_0} (1 + e^{-2j\beta d})$$


For  $A_{10}^- = 0$ , we must have  $(1 + e^{-2j\beta d}) = 0$ , or  $d = \lambda_g/4$ .

Then the coupling factor is,


$$C = 20 \log \left| \frac{A}{A_{10}} \right| = 20 \log \left| \frac{P_{10} a^2 k_0 \eta_0}{2\pi^2 \alpha_m} \right|$$

$$= 20 \log \left| \frac{3a^3 b \beta}{8\pi^2 r_0^3} \right| \text{ dB}$$


7.18

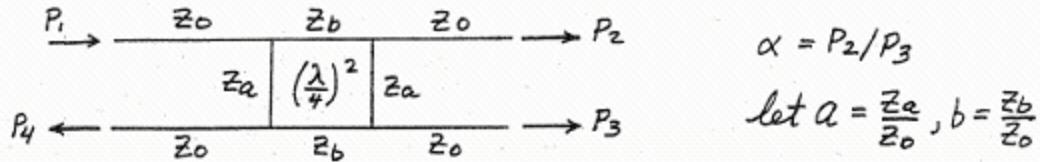

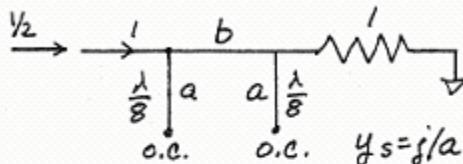Following the analysis of Section 7.5, the even and odd circuits are: (in normalized form)



EVEN MODE

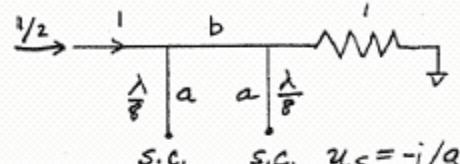

ODD MODE

The ABCD matrices are,

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e = \begin{bmatrix} 1 & 0 \\ j/a & 1 \end{bmatrix} \begin{bmatrix} 0 & jb \\ j/b & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ j/a & 1 \end{bmatrix} = \begin{bmatrix} -b/a & jb \\ j/b - jb/a^2 & -b/a \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_o = \begin{bmatrix} 1 & 0 \\ -j/a & 1 \end{bmatrix} \begin{bmatrix} 0 & jb \\ j/b & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ -j/a & 1 \end{bmatrix} = \begin{bmatrix} b/a & jb \\ j/b - jb/a^2 & b/a \end{bmatrix}$$

$$\Gamma_e = \frac{A+B-C-D}{A+B+C+D} = \frac{j(b-y_b+b/a^2)}{-2b/a+j(b+y_b-b/a^2)}$$

$$\Gamma_o = \frac{A+B-C-D}{A+B+C+D} = \frac{j(b-y_b+b/a^2)}{2b/a+j(b+y_b-b/a^2)}$$

The reflection at port 1 is then,

$$B_1 = \frac{1}{2}(\Gamma_e + \Gamma_o) = \frac{j}{2}(b - \frac{1}{b} + \frac{b}{a^2}) \frac{-2j(b + \frac{1}{b} - \frac{b}{a^2})}{(\frac{2b}{a})^2 + (b + \frac{1}{b} - \frac{b}{a^2})^2} = 0$$

Thus,  $b - \frac{1}{b} + \frac{b}{a^2} = 0$  (can't have  $b + \frac{1}{b} - \frac{b}{a^2} = 0$ , or else  $B_2 = B_3 = 0$ )

$$\text{So, } a = \frac{b}{\sqrt{1-b^2}} \quad \text{Then } \frac{b}{a^2} = \frac{1}{b} - b$$

Then,

$$\Gamma_e = \frac{2}{A+B+C+D} = \frac{2}{-2\frac{b}{a} + j(b + \frac{1}{b} - \frac{b}{a^2})} = \frac{1}{-\frac{b}{a} + jb}$$

$$T_0 = \frac{2}{A+B+C+D} = \frac{2}{\frac{2b}{a} + j(b + \frac{1}{b} - \frac{b}{a^2})} = \frac{1}{\frac{b}{a} + jb}$$

So the output wave amplitudes at ports 2 and 3 are,

$$B_2 = \frac{1}{2}(T_e + T_0) = \frac{1}{2} \left[ \frac{1}{-\frac{b}{a} + jb} + \frac{1}{\frac{b}{a} + jb} \right] = \frac{-j}{b(1 + \frac{1}{a^2})}$$

$$B_3 = \frac{1}{2}(T_e - T_0) = \frac{1}{2} \left[ \frac{1}{-\frac{b}{a} + jb} - \frac{1}{\frac{b}{a} + jb} \right] = \frac{-1/a}{b(1 + \frac{1}{a^2})}$$

This shows a  $90^\circ$  phase shift between ports 2 and 3.

For  $P_2/P_3 = \alpha$ ,

$$P_2 = \alpha P_3$$

$$|B_2|^2 = \alpha |B_3|^2$$

$$1 = \frac{\alpha}{a^2} \Rightarrow a = \sqrt{\alpha} \text{ or } Z_a = \sqrt{\alpha} Z_0 \checkmark$$

Then,  $b = \frac{a}{\sqrt{1+\alpha^2}} = \frac{\sqrt{\alpha}}{\sqrt{1+\alpha}} = \sqrt{\frac{\alpha}{1+\alpha}}$ , or  $Z_b = \sqrt{\frac{\alpha}{1+\alpha}} Z_0 \checkmark$

CHECK: When  $\alpha = 1$ ,  $Z_a = Z_0 \checkmark$ ,  $Z_b = Z_0/\sqrt{2} \checkmark$

at the isolated port,

$$B_4 = \frac{1}{2}(\Gamma_e - \Gamma_0) = \frac{j}{2} \left( b - \frac{1}{b} + \frac{b}{a^2} \right) (1) = 0$$

So there is isolation.

EXAMPLE:  $\alpha = 3$  (6dB),  $Z_0 = 50 \Omega$

$$\text{Then } Z_a = 87 \Omega \checkmark$$

$$Z_b = 43 \Omega \checkmark$$

**7.19**

$$b = 2.0 \text{ mm}, \quad \epsilon_r = 4.2$$

say  $s/b = 0.1, w/b = 0.3 \Rightarrow s = 0.2 \text{ mm}, w = 0.6 \text{ mm}$

Ansoft :  $z_{oe} = 80.0 \text{ r}, z_{oo} = 39.0 \text{ r}$

graph :  $\sqrt{\epsilon_r} z_{oe} = 168 \Rightarrow z_{oe} = 82.0 \text{ r}$   
(Fig 7.29)  $\sqrt{\epsilon_r} z_{oo} = 83 \Rightarrow z_{oo} = 40.5 \text{ r}$

**7.20**


$$d = 2.0 \text{ mm}, \quad \epsilon_r = 10 \quad (\text{to use graph of Fig 7.30})$$

say  $s/d = 0.4, w/d = 0.1 \Rightarrow s = 0.8 \text{ mm}, w = 0.2 \text{ mm.}$


Ansoft :  $z_{oe} = 133 \text{ r}, z_{oo} = 71.5 \text{ r}$

graph :  $z_{oe} = 138 \text{ r}, z_{oo} = 78 \text{ r}$

7.21

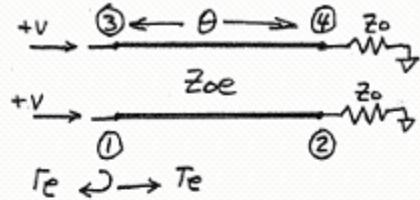

EVEN MODE

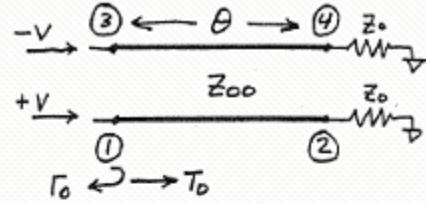

ODD MODE

For  $\theta = \pi/2$ ,

$$\Gamma_e = \frac{Z_{oe}^2/Z_0 - Z_0}{Z_{oe}^2/Z_0 + Z_0} = \frac{Z_{oe}^2 - Z_0^2}{Z_{oe}^2 + Z_0^2}$$

$$\Gamma_o = \frac{Z_{oo}^2/Z_0 - Z_0}{Z_{oo}^2/Z_0 + Z_0} = \frac{Z_{oo}^2 - Z_0^2}{Z_{oo}^2 + Z_0^2}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_e = \begin{bmatrix} \cos\theta & j Z_{oe} \sin\theta \\ j \frac{1}{Z_{oe}} \sin\theta & \cos\theta \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix}_o = \begin{bmatrix} \cos\theta & j Z_{oo} \sin\theta \\ j \frac{1}{Z_{oo}} \sin\theta & \cos\theta \end{bmatrix}$$

$$T_e = S_{21} = \frac{2}{2 \cos\theta + j \left( \frac{Z_{oe}}{Z_0} + \frac{Z_0}{Z_{oe}} \right) \sin\theta}$$

$$T_o = S_{21} = \frac{2}{2 \cos\theta + j \left( \frac{Z_{oo}}{Z_0} + \frac{Z_0}{Z_{oo}} \right) \sin\theta}$$

For a unit amplitude wave incident at port 1, the output wave amplitudes are,

$$B_1 = \frac{1}{2} (\Gamma_e + \Gamma_o)$$

$$B_2 = \frac{1}{2} (T_e + T_o)$$

$$B_3 = \frac{1}{2} (\Gamma_e - \Gamma_o)$$

$$B_4 = \frac{1}{2} (T_e - T_o)$$

so the reflection at port 1 is,

$$B_1 = \frac{1}{2} \left[ \frac{z_{0e}^2 - z_0^2}{z_{0e}^2 + z_0^2} + \frac{z_{00}^2 - z_0^2}{z_{00}^2 + z_0^2} \right] = \frac{z_{00}^2 z_{0e}^2 - z_0^4}{(z_0^2 + z_{0e}^2)(z_0^2 + z_{00}^2)} = 0$$

Thus,

$$\underline{z_0 = \sqrt{z_{0e} z_{00}}} \quad (\text{so all ports are matched})$$

Then,  $(\frac{z_{0e}}{z_0} + \frac{z_0}{z_{0e}}) = (\frac{z_0}{z_{00}} + \frac{z_{00}}{z_0})$

So,  $T_e = T_0$ , and  $\underline{B_4 = 0}$

The output waves at ports 2 and 3 are,

$$B_2 = \frac{2}{2 \cos \theta + j \left( \frac{z_{0e}}{z_0} + \frac{z_0}{z_{0e}} \right) \sin \theta} = \frac{1}{\cos \theta + j \frac{z_{0e} + z_{00}}{2 z_0} \sin \theta}$$

$$B_3 = \frac{1}{2} \left[ \frac{z_{0e} - z_{00}}{z_{0e} + z_{00}} - \frac{z_{00} - z_{0e}}{z_{00} + z_{0e}} \right] = \frac{z_{0e} - z_{00}}{z_{0e} + z_{00}}$$

Let  $C = B_3 = \frac{z_{0e} - z_{00}}{z_{0e} + z_{00}}$

Then  $\sqrt{1-C^2} = \frac{2 z_0}{z_{0e} + z_{00}}$ , and so,

$$B_2 = \frac{\sqrt{1-C^2}}{\sqrt{1-C^2} \cos \theta + j \sin \theta}$$

For  $\theta = \pi/2$ , the midband responses are,

$$B_3 = C$$

$$B_2 = -j \sqrt{1-C^2}$$

which agree with (7.85) - (7.86).

**7.22**

$$C = 10^{-19.1/20} = 0.1109 ; f = 8 \text{ GHz} ; Z_0 = 60 \Omega$$

From (7.87),

$$Z_{0e} = Z_0 \sqrt{\frac{1+c}{1-c}} = 67.1 \Omega \quad Z_{0o} = Z_0 \sqrt{\frac{1-c}{1+c}} = 53.7 \Omega$$

For a stripline with  $\epsilon_r = 2.2$ ,  $b = 0.32 \text{ cm}$ ,

$$\sqrt{\epsilon_r} Z_{0e} = 99.5 \Omega , \quad \sqrt{\epsilon_r} Z_{0o} = 79.7 \Omega$$

From Figure 7.29,

$$s/b = 0.36 \implies s = 1.15 \text{ mm}$$

$$w/b = 0.60 \implies w = 1.92 \text{ mm}$$

The line lengths are,

$$l = \frac{\lambda_g}{4} = \frac{c}{4\sqrt{\epsilon_r} f} = 6.32 \text{ mm}$$

**7.23**

$$C = 5 \text{ dB} = 10^{-5/20} = 0.562 ; f_o = 8 \text{ GHz} ; Z_0 = 60 \Omega$$

From (7.87),

$$Z_{0e} = Z_0 \sqrt{\frac{1+c}{1-c}} = 113.3 \Omega \quad Z_{0o} = Z_0 \sqrt{\frac{1-c}{1+c}} = 31.8 \Omega$$

$$\text{Then, } \sqrt{\epsilon_r} Z_{0e} = 168.1 \Omega \quad \sqrt{\epsilon_r} Z_{0o} = 47.2 \Omega \quad (\epsilon_r = 2.2)$$

From Figure 7.29,

$$s/b \approx 0.009 \implies s = 0.029 \text{ mm (!)}$$

$$w/b \approx 0.34 \implies w = 1.09 \text{ mm}$$

This design is probably not practical due to the extremely close spacing of the lines.

7.24

For  $V_{1e}$  or  $V_{1o}$  at port 1, we first find  $V_{2e}$  or  $V_{2o}$ :

$$V(z) = V^+ (e^{-j\beta z} + \Gamma_e e^{j\beta z})$$

$$\Gamma_e = \frac{Z_0 - Z_0e}{Z_0 + Z_0e}$$

$$1 + \Gamma_e = \frac{2Z_0}{Z_0 + Z_0e}$$

$$V_{1e} = V(-\theta) = V^+ (e^{j\theta} + \Gamma_e e^{-j\theta})$$

$$V_{2e} = V(0) = V^+ (1 + \Gamma_e)$$

So,

$$V_{2e} = \frac{V_{1e} (1 + \Gamma_e)}{e^{j\theta} + \Gamma_e e^{-j\theta}} = \frac{2Z_0 V_{1e}}{(Z_0 + Z_0e) e^{j\theta} + (Z_0 - Z_0e) e^{-j\theta}}$$

$$= \frac{Z_0 V_{1e}}{Z_0 \cos \theta + j Z_0e \sin \theta} = \frac{Z_0 V_{1e} \sec \theta}{Z_0 + j Z_0e \tan \theta}$$

Similarly,

$$V_{2o} = \frac{Z_0 V_{1o} \sec \theta}{Z_0 + j Z_0e \tan \theta}$$

Then using (7.74) and the results following (7.79) gives,

$$V_4 = V_{2e} - V_{2o} = \frac{Z_0 V \sec \theta}{2Z_0 + j(Z_0e + Z_0o) \tan \theta} \left[ \frac{Z_0 + j Z_0e \tan \theta}{Z_0 + j Z_0e \tan \theta} - \frac{Z_0 + j Z_0o \tan \theta}{Z_0 + j Z_0o \tan \theta} \right]$$

$$V_2 = V_{2e} + V_{2o} = \frac{2Z_0 V \sec \theta}{2Z_0 + j(Z_0e + Z_0o) \tan \theta} = \frac{\frac{2Z_0}{Z_0e + Z_0o} V}{\frac{2Z_0}{Z_0e + Z_0o} \cos \theta + j \sin \theta}$$

$$= \frac{V \sqrt{1 - C^2}}{\sqrt{1 - C^2} \cos \theta + j \sin \theta} \quad \text{since } \sqrt{1 - C^2} = \frac{2Z_0}{Z_0e + Z_0o}$$

**7.25**

$N = 3, C = 20 \text{ dB, maximally flat, } Z_0 = 50\Omega$

(a) From (7.90) and Example

$$C = \left| \frac{V_3}{V_1} \right| = 2 \sin \theta [C_1 \cos 2\theta + \frac{1}{2} C_2] \quad ; \quad C_3 = C_1 \\ = C_1 \sin 3\theta + (C_2 - C_1) \sin \theta \quad \text{for } \theta = \pi/2, \quad C = C_0 = C_2 - 2C_1$$

$$\frac{dC}{d\theta} = \left[ 3C_1 \cos 3\theta + (C_2 - C_1) \cos \theta \right] \Big|_{\pi/2} = 0$$

$$\frac{d^2C}{d\theta^2} = \left[ -9C_1 \sin 3\theta - (C_2 - C_1) \sin \theta \right] \Big|_{\pi/2} = 10C_1 - C_2 = 0$$

$$\text{at midband } (\theta = \pi/2), \quad C_0 = 10^{-20/20} = 0.1 = C_2 - 2C_1$$

$$\therefore C_1 = C_3 = 0.1/8 = 0.0125$$

$$C_2 = 10C_1 = 0.125$$

Using (7.87) gives  $Z_{0e}, Z_{0o}$ :

$$Z_{0e}^{(1)} = Z_{0e}^{(3)} = Z_0 \sqrt{\frac{1+C_1}{1-C_1}} = 50.63\Omega$$

$$Z_{0o}^{(1)} = Z_{0o}^{(3)} = Z_0 \sqrt{\frac{1-C_1}{1+C_1}} = 49.38\Omega$$

$$Z_{0e}^{(2)} = Z_0 \sqrt{\frac{1+C_2}{1-C_2}} = 56.69\Omega$$

$$Z_{0o}^{(2)} = Z_0 \sqrt{\frac{1-C_2}{1+C_2}} = 44.10\Omega$$



(b)  $\epsilon_r = 4.2, d = 0.158 \text{ cm}, \tan \delta = 0.02, \text{Cu, } 0.5 \text{ mil} = t$ .

From Serenade,

$$Z_{0e} = 50.63, Z_{0o} = 49.38 \Rightarrow W = 3.125 \text{ mm}, S = 9.94 \text{ mm}, l = 1.38 \text{ cm}$$

$$Z_{0e} = 56.69, Z_{0o} = 44.10 \Rightarrow W = 3.054 \text{ mm}, S = 1.60 \text{ mm}, l = 1.39 \text{ cm}$$

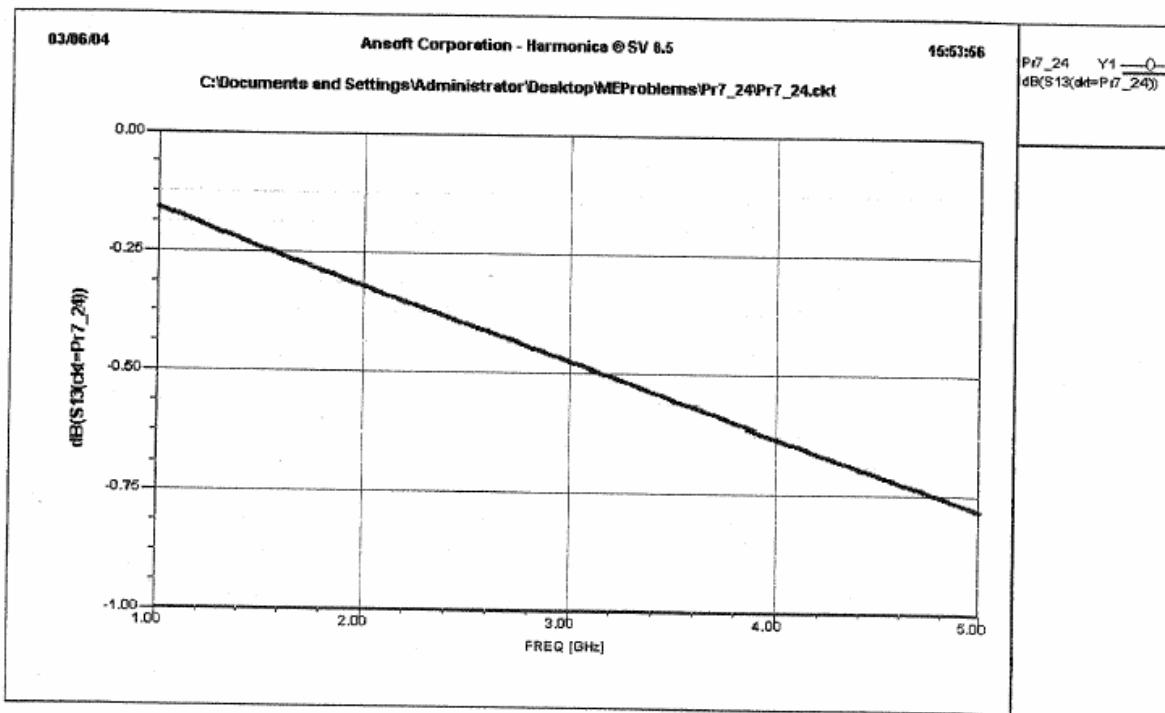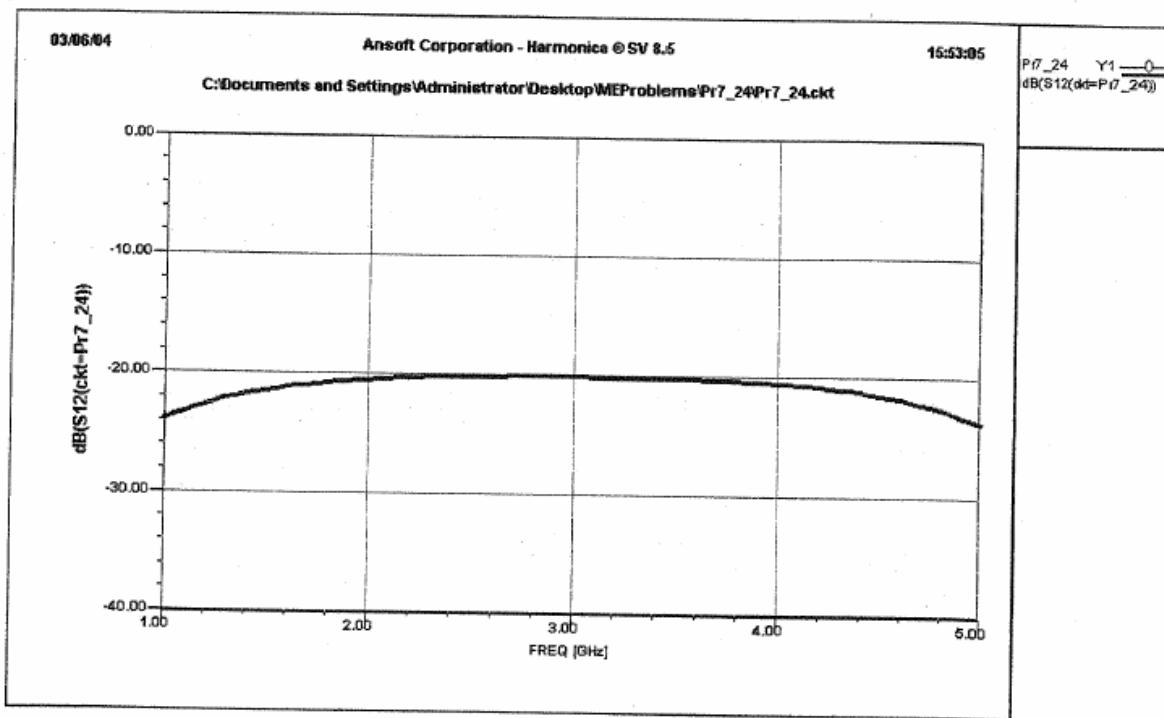The resulting coupling and insertion loss are plotted on the following page.




**7.26**  $C = 20 \text{ dB}$ , equal-ripple ( $1 \text{ dB}$ ),  $N = 3$ ,  $Z_1 = 50 \Omega$

(a) From (7.90) and Example 7.8:

$$C = \left| \frac{V_3}{V_1} \right| = 2 \sin \theta [C_1 \cos 2\theta + \frac{1}{2} C_2]$$

$$= C_1 \sin 3\theta + (C_2 - C_1) \sin \theta$$

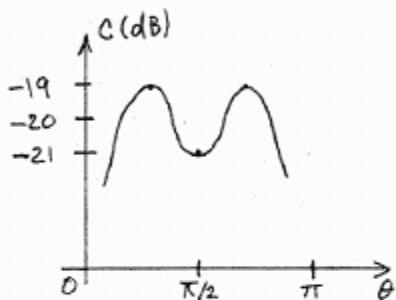We cannot equate this to a Chebyshev polynomial, since  $C$  is a polynomial in  $\sin \theta$ . The desired response is as shown:



$$\text{So at } \theta = \pi/2, C_0 = -21 \text{ dB} = 0.08913$$

$$= C_2 - 2C_1$$

$$C_{MAX} = -19 \text{ dB} = 0.1122$$

We can use trial-and-error to find  $C_1$ :

$$\text{Thus } C_1 = 0.035, C_2 = 0.1591$$

Then,

$$Z_{oe}^{(1)} = Z_{oo}^{(2)} = 51.78 \Omega$$

$$Z_{oe}^{(1)} = Z_{oo}^{(3)} = 48.28 \Omega$$

$$Z_{oe}^{(2)} = 58.70 \Omega$$

$$Z_{oo}^{(2)} = 42.59 \Omega$$



$C_1$	$C_{MAX}$
.05	.134
.06	.147
.03	.106
.035	.1125

(b) From Serenade,

$$Z_{oe} = 51.78, Z_{oo} = 48.28 \Rightarrow w = 3.121 \text{ mm}, s = 4.842 \text{ mm}, l = 1.38 \text{ cm}$$

$$Z_{oe} = 58.70, Z_{oo} = 42.59 \Rightarrow w = 3.002 \text{ mm}, s = 1.173 \text{ mm}, l = 1.39 \text{ cm}$$

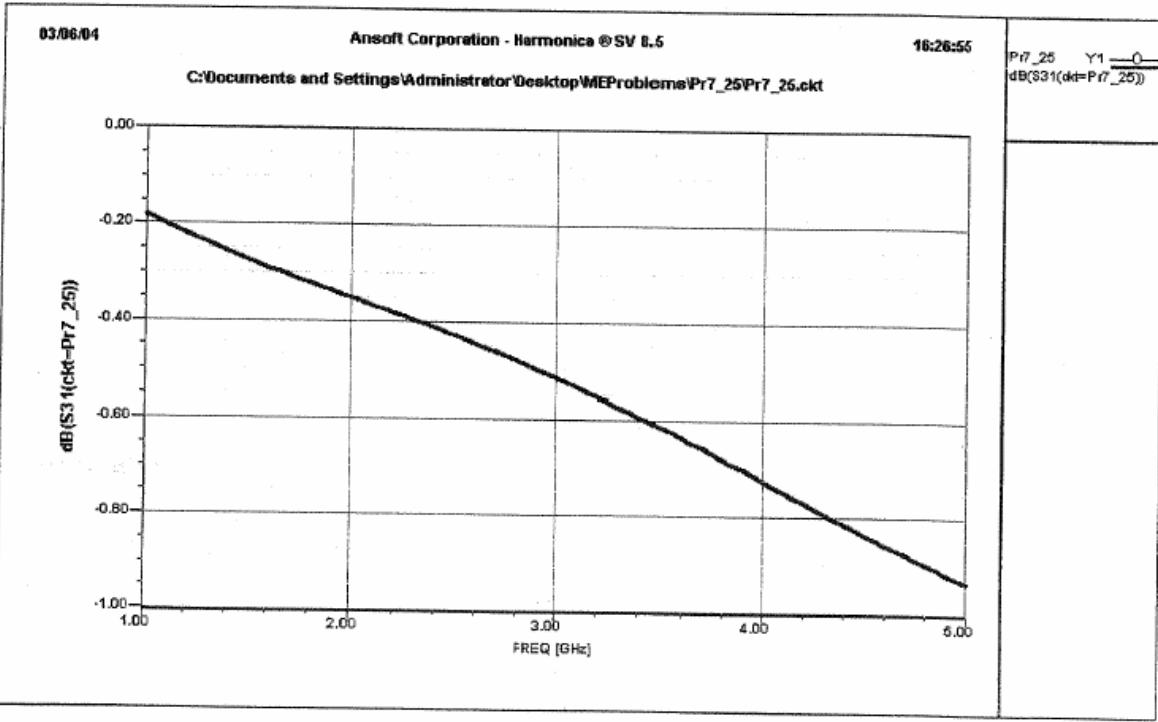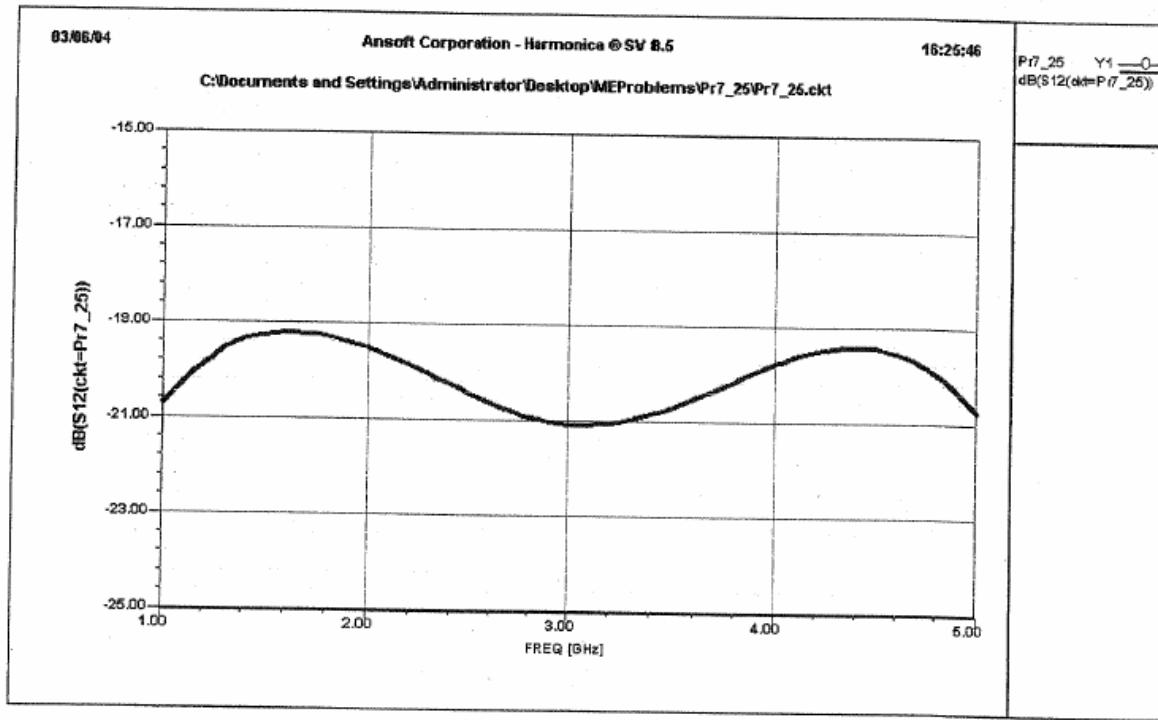The coupling and insertion loss are plotted on the following page.



7.27

From (7.98) and (7.99) we can show that,

$$Z_{e4} = Z_0 \sqrt{\frac{1+c}{1-c}}$$

Equating this to (7.97a) gives:

$$Z_0 \sqrt{\frac{1+c}{1-c}} = \frac{Z_{00} + Z_{oe}}{3Z_{00} + Z_{oe}} = \frac{1 + \frac{Z_{oe}}{Z_{00}}}{3 + \frac{Z_{oe}}{Z_{00}}} Z_{oe}$$

Now solve (7.99) for  $Z_{oe}$  in terms of  $Z_{00}$ :

$$3c(Z_{oe}^2 + Z_{00}^2) + 2cZ_{oe}Z_{00} = 3(Z_{oe}^2 - Z_{00}^2)$$

$$3(c-1)Z_{oe}^2 + 2cZ_{oe}Z_{00} + 3(c+1)Z_{00}^2 = 0$$

$$Z_{oe} = \frac{-2cZ_{00} \pm \sqrt{4c^2Z_{00}^2 - 36(c^2-1)Z_{00}^2}}{6(c-1)} = \frac{-c - \sqrt{9-8c^2}}{3(c-1)} Z_{00}$$

(choose negative root since  $Z_{oe}$  and  $Z_{00}$  are positive, and  $c < 1$ )  
Substituting for  $Z_{oe}/Z_{00}$  in the above expression gives,

$$Z_0 \sqrt{\frac{1+c}{1-c}} = \frac{2c-3-\sqrt{9-8c^2}}{8c-9-\sqrt{9-8c^2}} Z_{oe}$$

or

$$\begin{aligned} Z_{oe} &= Z_0 \sqrt{\frac{1+c}{1-c}} \frac{[8c-9-\sqrt{9-8c^2}][2c-3+\sqrt{9-8c^2}]}{(2c-3)^2 - (9-8c^2)} \\ &= Z_0 \sqrt{\frac{1+c}{1-c}} \frac{(24c^2 - 42c + 18) + 6(c-1)\sqrt{9-8c^2}}{12c(c-1)} \\ &= Z_0 \sqrt{\frac{1+c}{1-c}} \frac{4c-3+\sqrt{9-8c^2}}{2c} \quad \checkmark \end{aligned}$$

To find  $Z_{00}$ , simply replace  $c$  by  $-c$  (because of symmetry of (7.98) and (7.99)):

$$Z_{00} = Z_0 \sqrt{\frac{1-c}{1+c}} \frac{4c+3-\sqrt{9-8c^2}}{2c} \quad \checkmark$$

**7.28**

$$f = 56 \text{ GHz}, \epsilon_r = 10, d = 1 \text{ mm}$$

$$C = 10^{-3/20} = 0.708$$

assume  $Z_0 = 50 \Omega$  (not stated in problem!)

From (7.100) we have,

$$Z_{0e} = \frac{4C - 3 + \sqrt{9 - 8C^2}}{2C \sqrt{\frac{1-C}{1+C}}} Z_0 = 176.4 \Omega$$

$$Z_{0o} = \frac{4C + 3 - \sqrt{9 - 8C^2}}{2C \sqrt{\frac{1+C}{1-C}}} Z_0 = 52.5 \Omega$$

(These results are very approximate; SuperCompact gives  $Z_{0e} = 121 \Omega$  and  $Z_{0o} = 21 \Omega$  for this design)

From Figure 7.30,

$$s/d \approx 0.075 \Rightarrow s = 0.075 \text{ mm}$$

$$w/d \approx 0.07 \Rightarrow w = 0.07 \text{ mm}$$

(SuperCompact gives 0.071 mm and 0.075 mm for  $s$  and  $w$ , respectively, starting with the values calculated above for  $Z_{0e}$  and  $Z_{0o}$ . These are reasonably close to our values for  $s$  and  $w$ , even though  $Z_{0e}, Z_{0o}$  are not close to the SuperCompact values.)

**7.29**

From (7.101) the [s] matrix of a  $180^\circ$  (3dB) hybrid is,

$$[s] = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix}$$

For  $V_1$  at port 1 and  $V_4$  at port 4, the output voltages are (note: hybrid is matched, so  $V_1 = V_1^+$ ,  $V_4 = V_4^+$ )

$$\begin{bmatrix} V_1^- \\ V_2^- \\ V_3^- \\ V_4^- \end{bmatrix} = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix} \begin{bmatrix} V_1 \\ 0 \\ 0 \\ V_4 \end{bmatrix}$$

$$= \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 \\ V_1 - V_4 \\ V_1 + V_4 \\ 0 \end{bmatrix} \quad \begin{array}{l} \checkmark \\ \checkmark \\ \checkmark \\ \checkmark \end{array} \quad \begin{array}{l} \text{(difference)} \\ \text{(sum)} \end{array}$$

**7.30**

$$\alpha = \beta = \sqrt{2}/2 \text{ for } C = 3 \text{ dB}$$

$$\text{From (7.115a), } \beta = \frac{2\sqrt{k}}{k+1} \Rightarrow k = 0.1716 \checkmark$$

$$\text{From (7.115b), } \alpha = \frac{1-k}{1+k} \Rightarrow k = 0.1716 \checkmark$$

Then,


$$Z_{0e}(0) = Z_{0o}(0) = Z_0 = 50 \Omega$$

$$Z_{0e}(L) = Z_0/k = 291 \Omega$$


$$Z_{0o}(L) = k Z_0 = 8.6 \Omega$$

A Kloppenstein taper can be used for these taper variations.

7.31

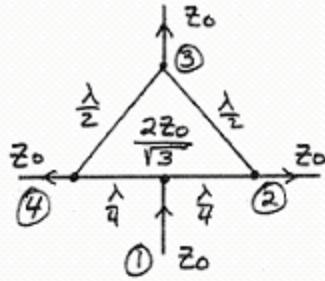

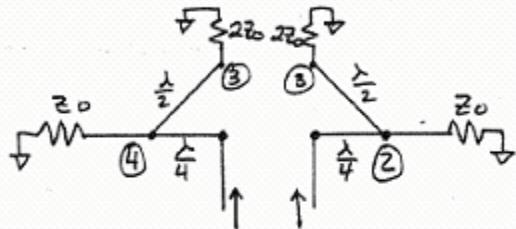First, let  $V_1^+ = 1v$  at port 1, with matched loads at other ports. Then we can bisect the network as follows:



The input impedance of one of these halves is,


$$\left(\frac{2Z_0}{\sqrt{3}}\right)^2 \frac{(Z_0 + 2Z_0)}{2Z_0} = 2Z_0, \text{ so } Z_{in}^{(1)} = Z_0, \text{ and } S_{11} = 0. \checkmark$$

Because of the  $\lambda/2$  line, the voltage magnitude at port 3 is equal to the voltage magnitude at port 4.

By power conservation,  $P_2 = P_4 = P_3 = P_{in}/3$ . Thus,

$$S_{41} = S_{21} = \frac{1}{\sqrt{3}} \angle -90^\circ, \quad S_{31} = \frac{1}{\sqrt{3}} \angle -270^\circ. \quad (|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 + |S_{41}|^2 = 1)$$

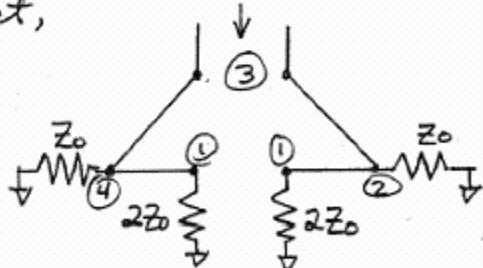Next, let  $V_3^+ = 1v$  at port 3, with other ports matched, and bisect,




The input impedance of one of these halves is

$$Z_0 \parallel \left(\frac{2Z_0}{\sqrt{3}}\right) \frac{1}{2Z_0} = Z_0 \parallel \frac{2Z_0}{3} = \frac{2Z_0}{5}, \text{ so } Z_{in}^{(3)} = Z_0/5, \text{ and } S_{33} = -2/3.$$

So the power delivered to each half is  $\frac{1}{2}P_{in}(1 - |S_{33}|^2) = 5/18 P_{in}$ . Of this,  $2/5$  goes to port 4 and  $3/5$  goes to port 1.

So,  $S_{43} = S_{23} = \frac{1}{3} \angle -180^\circ$ . The total power to port 1 is then  $\frac{1}{3}P_{in}$ , so  $S_{13} = \frac{1}{\sqrt{3}} \angle -270^\circ$ . (Then  $|S_{13}|^2 + |S_{23}|^2 + |S_{33}|^2 + |S_{43}|^2 = \frac{1}{3} + \frac{1}{9} + \frac{4}{9} + \frac{1}{9} = 1$ )

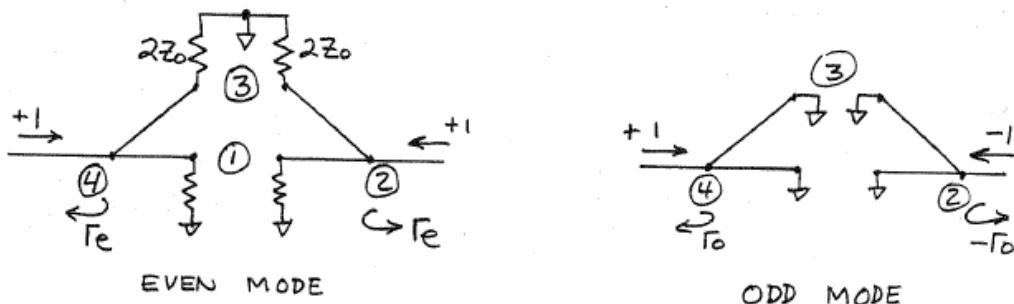Now drive ports 2 and 4 with even and odd excitations:



$$Z_{in}^e = 2Z_0 \parallel \frac{2Z_0}{3} = Z_0/2$$

$$\Gamma_e = \frac{\gamma_2 - 1}{\gamma_2 + 1} = -1/3$$

$$Z_{in}^o = 0$$

$$\Gamma_o = -1$$

$$\text{Then, } S_{22} = S_{44} = \frac{1}{2}(\Gamma_e + \Gamma_o) = \frac{1}{2}(-1/3 - 1) = -2/3$$

$$S_{24} = \frac{1}{2}(\Gamma_e - \Gamma_o) = \frac{1}{2}(-1/3 + 1) = 1/3$$

So the complete S-matrix is,

$$[S] = \begin{bmatrix} 0 & \sqrt{3} \angle -90^\circ & \sqrt{3} \angle -270^\circ & \sqrt{3} \angle 90^\circ \\ \sqrt{3} \angle -90^\circ & -2/3 & -1/3 & 1/3 \\ \sqrt{3} \angle -270^\circ & -1/3 & -2/3 & -1/3 \\ \sqrt{3} \angle 90^\circ & 1/3 & -1/3 & -2/3 \end{bmatrix}$$


This checks with an analysis using SuperCompact.

**7.32**

$$\text{Let } V_1^+ = 110$$

Bisecting the network places an effective short circuit at ports 3 and 4, due to the  $\lambda/4$  o.c. stubs. Thus  $S_{41} = S_{31} = 0$ . Then there is an effective open circuit in parallel with the  $Z_0$  loads at ports 2 and 5. So the input impedance of one of the halves is  $(\sqrt{2} Z_0)^2 / Z_0 = 2Z_0$ . The total input impedance at port 1 is then  $Z_0$ , so  $S_{11} = 0$ , and the input power divides evenly to ports 2 and 5. Thus,  $V_1^- = 0$ ;  $V_2^- = V_5^- = 0.707 \angle -90^\circ$ ;  $V_3^- = V_4^- = 0$ .

CHECK:  $|S_{11}|^2 + |S_{21}|^2 + |S_{31}|^2 + |S_{41}|^2 = 0 + \frac{1}{2} + 0 + \frac{1}{2} = 1$  ✓

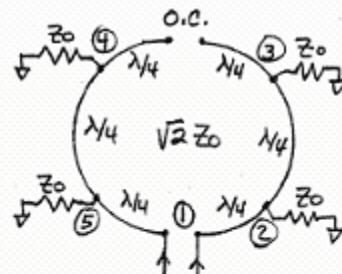

7.33

a) let  $b = \lambda/4$  at  $f_0 \Rightarrow \beta b = \pi/2$

Assume  $V_o^+$  incident at T-junction. Then,

$$V_1^+ = V_o^+ e^{-j\beta(b-a)} = e^{-j\pi/2} e^{j\beta a}$$

$$V_4^+ = V_o^+ e^{-j\beta a}$$

$$V_2^- = \frac{-V_o^+}{\sqrt{2}} (jV_1^+ + V_4^+) = \frac{-V_o^+}{\sqrt{2}} (e^{j\beta a} + e^{-j\beta a}) = -\sqrt{2} V_o^+ \cos \beta a$$

$$P_2 = \frac{1}{2} |V_2^-|^2 = |V_o^+|^2 \cos^2 \beta a$$


$$V_3^- = \frac{-V_o^+}{\sqrt{2}} (V_1^+ + jV_4^+) = \frac{-V_o^+}{\sqrt{2}} (-j e^{j\beta a} + j e^{-j\beta a}) = -\sqrt{2} V_o^+ \sin \beta a$$

$$P_3 = \frac{1}{2} |V_3^-|^2 = |V_o^+|^2 \sin^2 \beta a$$

$$\text{So } \frac{P_3}{P_2} = \tan^2 \beta a = \tan^2 \frac{\pi a}{2b} \checkmark \quad (\text{since } \beta = \frac{2\pi}{\lambda} = \frac{2\pi}{4b} = \frac{\pi}{2b})$$

b) For  $\frac{P_3}{P_2} = 0.5$ ,  $a = 0.098\lambda = 35.3^\circ$ ;  $(b-a) = 0.152\lambda = 54.7^\circ$

CIRCUIT:

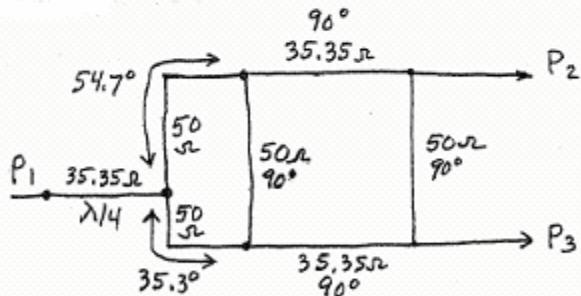

The S-parameters are plotted on the following page, for a center frequency of 1 GHz. Note that the power output ratios,

$$\frac{P_2}{P_1} = \frac{2}{3} = -1.76 \text{ dB} \quad \text{and} \quad \frac{P_3}{P_1} = \frac{1}{3} = -4.77 \text{ dB}$$

are verified.


$$[S] = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix} \text{ for hybrid}$$

03/06/04

Ansoft Corporation - Harmonica © SV 8.5

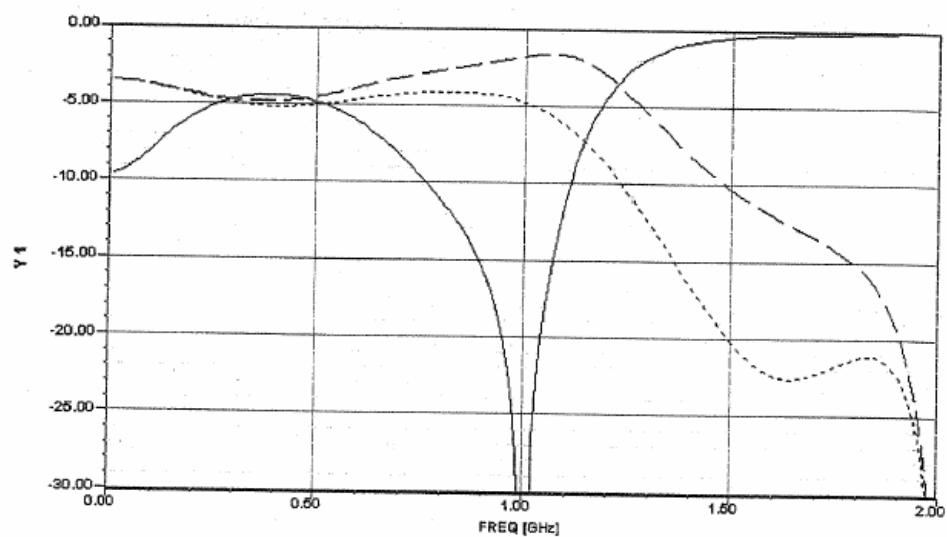17:00:45

C:\Documents and Settings\Administrator\Desktop\MEProblems\Pr7\_33.olt



bailey	$Y1 = 0$	$\text{dB}(S11(\text{ok}=\text{bailey}))$
bailey	$Y1 = +$	$\text{dB}(S12(\text{ok}=\text{bailey}))$
bailey	$Y1 = -$	$\text{dB}(S13(\text{ok}=\text{bailey}))$

## Chapter 8

8.1

$$Z_0 = 75 \Omega, L_0 = 1.25 \text{ mH}, d = 1.0 \text{ cm}$$


let  $\theta = k_0 d$ .

$$b = \frac{-Z_0}{\omega L_0} = \frac{-Z_0}{C k_0 L_0} = \frac{-200}{k_0}$$

Passband when  $|\cos pd| = |\cos \theta - \frac{b}{2} \sin \theta| \leq 1$


Stopband when  $\cosh \theta d = |\cos \theta - \frac{b}{2} \sin \theta| \geq 1$

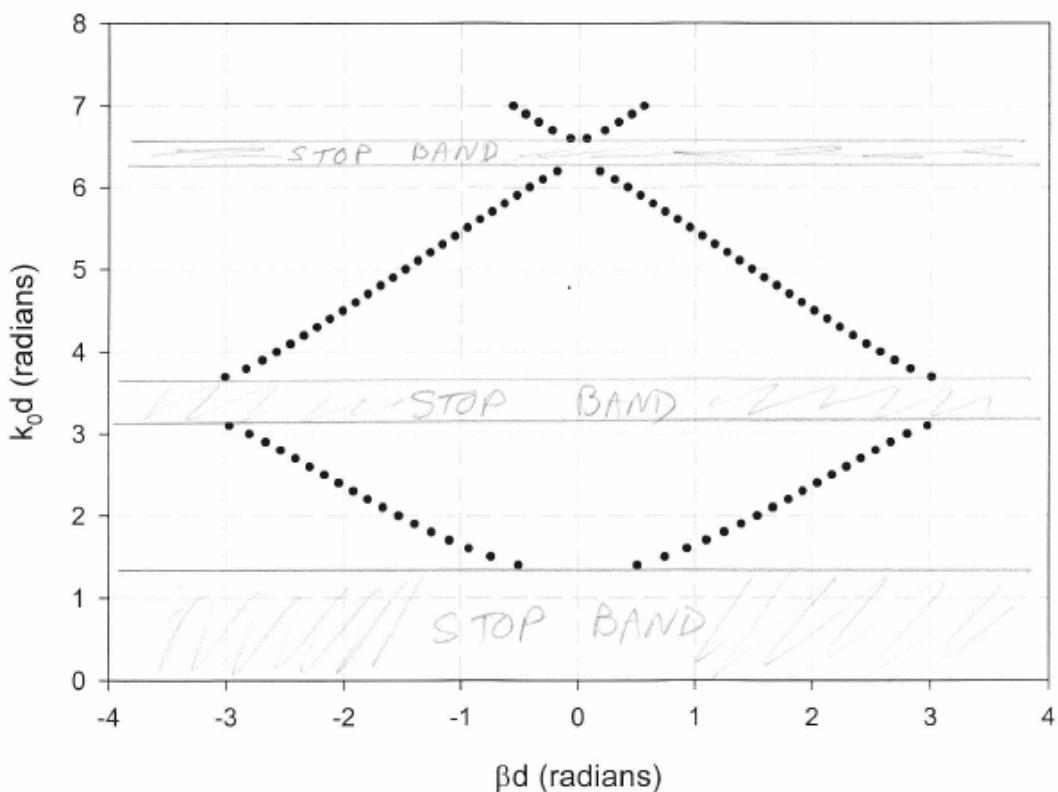a short program was used to compute  $pd$ , with results plotted below.



**8.2**  $Z_{i\pi}$  can easily be derived from  $Z_i = \sqrt{\frac{AB}{CD}} = \sqrt{\frac{B}{C}}$ .


Verify as follows:

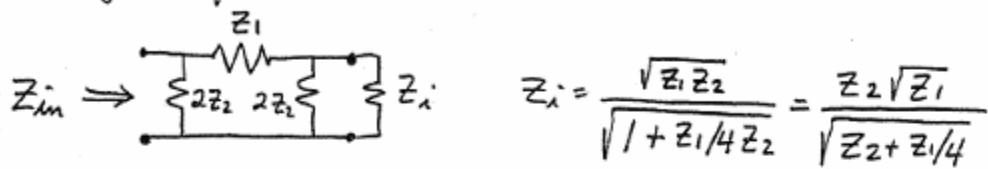

$$\text{let } z = z_2 \mid z_1 = \frac{\frac{2z_2^2\sqrt{z_1}}{\sqrt{z_2+z_1/4}}}{2z_2 + \frac{z_2\sqrt{z_1}}{\sqrt{z_2+z_1/4}}} = \frac{2z_2\sqrt{z_1}}{2\sqrt{z_2+z_1/4} + \sqrt{z_1}}$$

$$\begin{aligned}
 z_{\min} &= 2z_2 \left| \frac{4z_1 z_2 \sqrt{z_2+z_1/4} + 2z_2 \sqrt{z_1} (2z_2+z_1)}{2\sqrt{z_2+z_1/4} + \sqrt{z_1}} \right. \\
 &\quad \left. - 2z_2 + \frac{2z_1 \sqrt{z_2+z_1/4} + \sqrt{z_1} (2z_2+z_1)}{2\sqrt{z_2+z_1/4} + \sqrt{z_1}} \right| \\
 &= \frac{4z_1 z_2 \sqrt{z_2+z_1/4} + z_2 \sqrt{z_1} (2z_2+z_1) (2)}{4z_2 \sqrt{z_2+z_1/4} + 2z_2 \sqrt{z_1} + 2z_1 \sqrt{z_2+z_1/4} + \sqrt{z_1} (2z_2+z_1)} \\
 &= \frac{z_2 [\sqrt{z_1} (2z_2+z_1) + 2z_1 \sqrt{z_2+z_1/4}]}{2\sqrt{z_1} (z_2+z_1/4) + z_1 \sqrt{z_2+z_1/4} + 2z_2 \sqrt{z_2+z_1/4}} \\
 &= \frac{z_2 \sqrt{z_1}}{\sqrt{z_2+z_1/4}} = z_i \quad \checkmark
 \end{aligned}$$

8.3

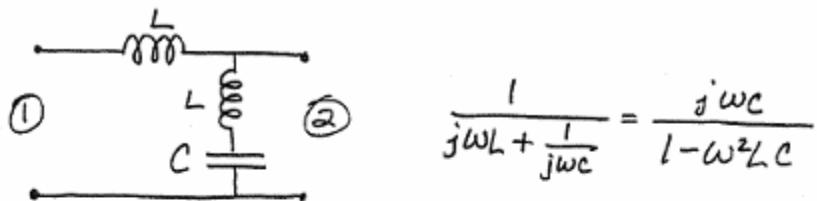

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & j\omega L \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{j\omega C}{1 - \omega^2 LC} & 1 \end{bmatrix} = \begin{bmatrix} \frac{1 - 2\omega^2 LC}{1 - \omega^2 LC} & j\omega L \\ \frac{j\omega C}{1 - \omega^2 LC} & 1 \end{bmatrix} \quad \checkmark$$

From (8.27),

$$Z_{i1} = \sqrt{\frac{AB}{CD}} = \sqrt{\frac{j\omega L(1 - 2\omega^2 LC)}{j\omega C}} = \sqrt{\frac{L}{C}(1 - 2\omega^2 LC)} \quad \checkmark$$

$$Z_{i2} = \sqrt{\frac{BD}{AC}} = \frac{1}{1 - \omega^2 LC} \sqrt{\frac{j\omega L}{j\omega C(1 - 2\omega^2 LC)}} = \frac{1}{1 - \omega^2 LC} \sqrt{\frac{L}{C(1 - 2\omega^2 LC)}}$$


From (8.31),  $\cosh \delta = \sqrt{AD} = \sqrt{\frac{1 - 2\omega^2 LC}{1 - \omega^2 LC}}$

**8.4**

$R_o = 50\Omega$ ,  $f_c = 50 \text{ MHz}$ ,  $f_{oo} = 52 \text{ MHz}$ , LOW-PASS

Design equations from Table 8.2:


CONSTANT-K SECTION:

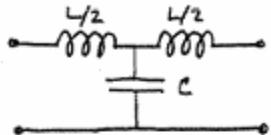

$$L = 2R_o/\omega_c = 3.18 \times 10^{-7} \text{ H}; L/2 = 159 \text{ nH} \quad \checkmark$$

$$C = 2/\omega_c R_o = 127 \text{ pF} \quad \checkmark$$

m-DERIVED SECTION:

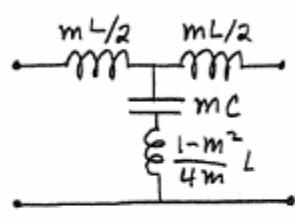


$$m = \sqrt{1 - (f_c/f_{oo})^2} = 0.275 \quad \checkmark$$

$$\frac{mL}{2} = 43.7 \text{ nH} \quad \checkmark$$

$$mc = 34.9 \text{ pF} \quad \checkmark$$

$$\frac{1-m^2}{4m} L = 267 \text{ nH} \quad \checkmark$$

MATCHING SECTIONS: ( $m_u = 0.6$ )

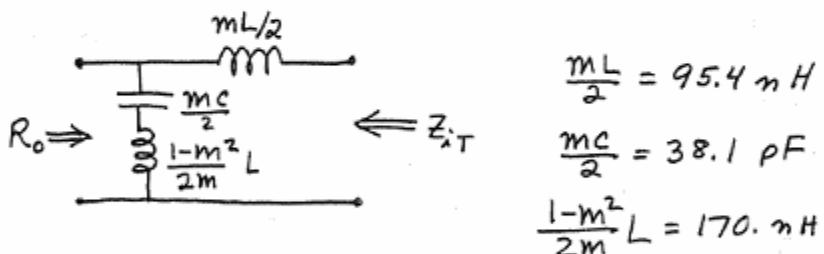


$$\frac{mL}{2} = 95.4 \text{ nH} \quad \checkmark$$

$$\frac{mc}{2} = 38.1 \text{ pF} \quad \checkmark$$


$$\frac{1-m^2}{2m} L = 170 \text{ nH} \quad \checkmark$$

COMPLETE FILTER:

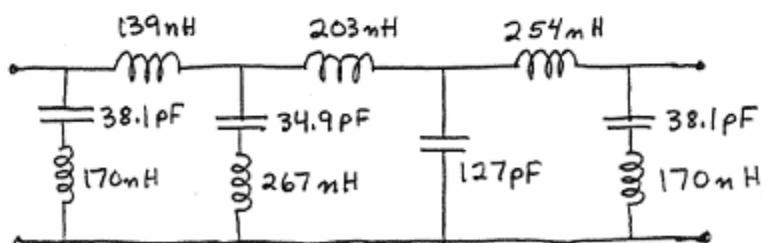


The calculated response is shown on the following page.

▽ MS12 [dB] FILTER

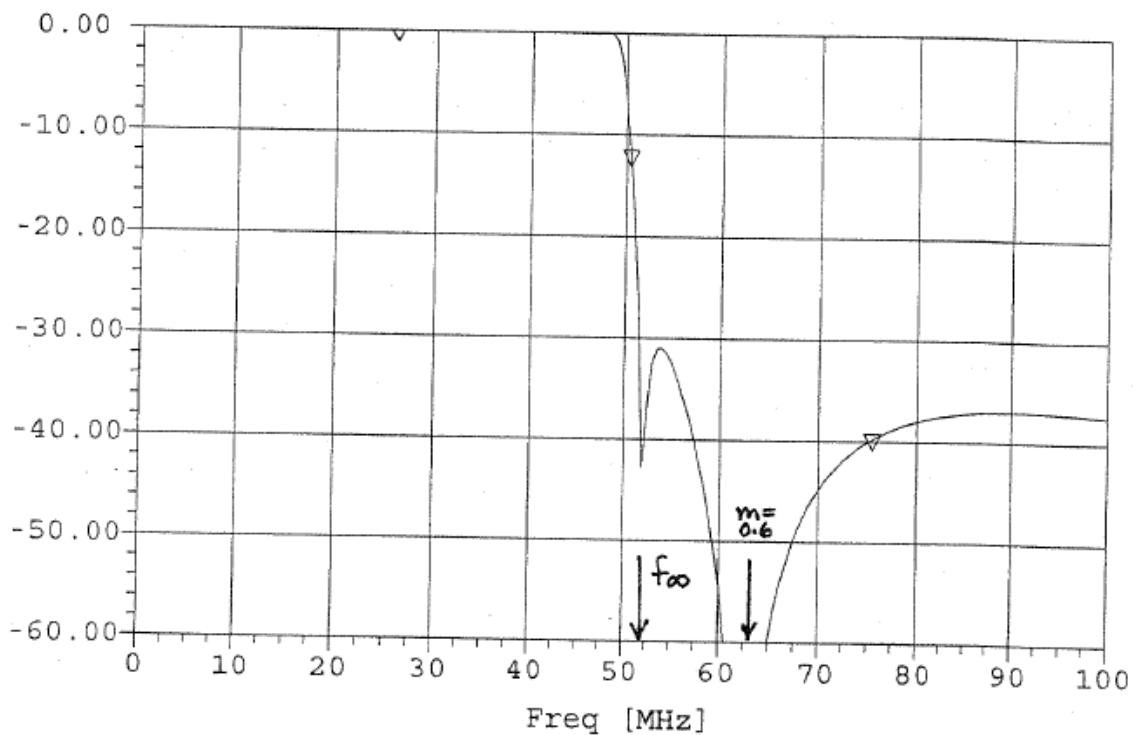

**8.5**

$R_o = 75 \Omega$ ,  $f_c = 50 \text{ MHz}$ ,  $f_{oo} = 48 \text{ MHz}$ , HIGH-PASS  
 Design equations are given in Table 8.2

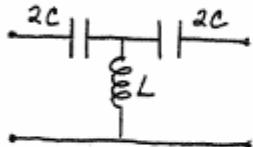
CONSTANT -  $R$  SECTION:

$$L = R_o / 2\omega_C = 119. \text{ nH} \quad \checkmark$$

$$C = 1 / 2R_o\omega_b = 21.2 \text{ pF} \quad \checkmark$$

$$2C = 42.4 \text{ pF} \quad \checkmark$$

M - DERIVED SECTION:

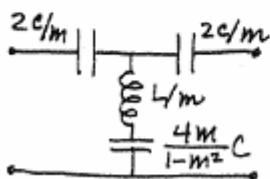


$$m = \sqrt{1 - (f_{oo}/f_c)^2} = 0.280 \quad \checkmark$$

$$\frac{2C}{m} = 151. \text{ pF} \quad \checkmark$$

$$L/m = 425. \text{ nH} \quad \checkmark$$

$$\frac{4mC}{1-m^2} = 25.8 \text{ pF} \quad \checkmark$$

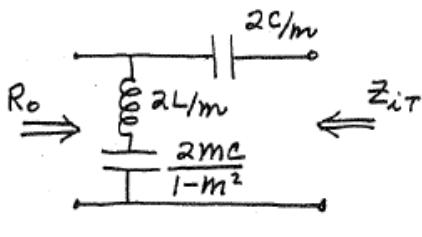
MATCHING SECTION: ( $m = 0.6$ )

$$\frac{2C}{m} = 70.7 \text{ pF} \quad \checkmark$$

$$\frac{2L}{m} = 397. \text{ nH.} \quad \checkmark$$


$$\frac{2mC}{1-m^2} = 39.8 \text{ pF} \quad \checkmark$$

COMPLETE FILTER:

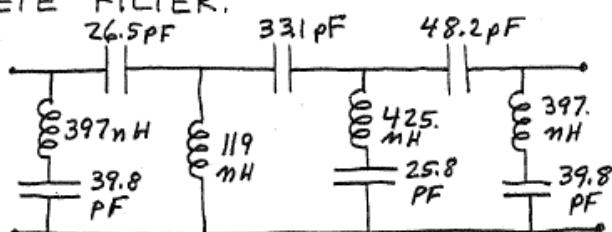

The calculated filter response is shown below.


▽ MS12 [dB] FILTER

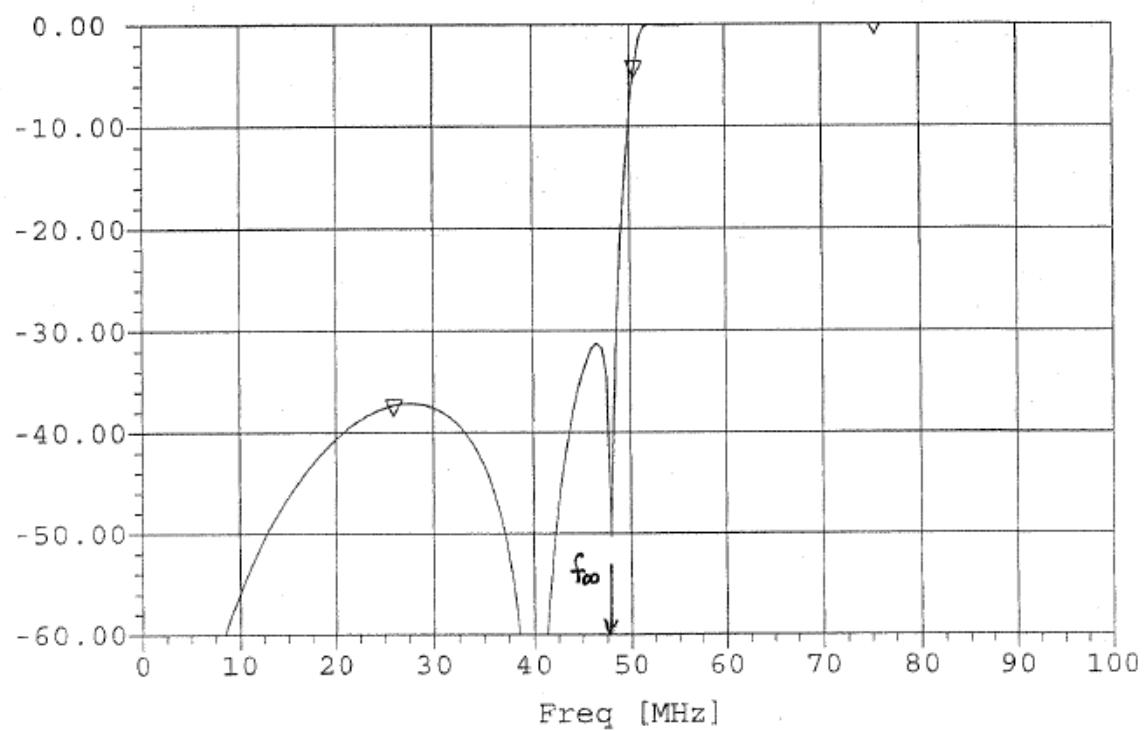

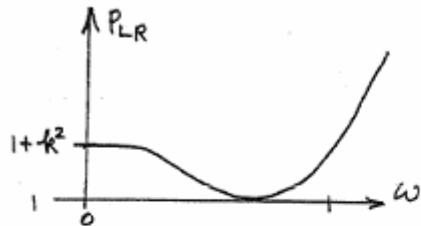**8.6**

From (8.61),

$$P_{LR} = 1 + k^2 T_N^2(\omega) = 1 + k^2 (2\omega^2 - 1)^2 \quad \text{for } N=2$$



$$P_{LR} = 1 = 0 \text{ dB}$$

$$P_{LR} = 1 + k^2 = 1 \text{ dB} = 1.0259$$

$$\text{so } k = \pm 0.509$$

(We must choose  $k = -0.509$ , otherwise  $L, C$  are not real.)

Then from (8.63),

$$R = 1 + 2k^2 - 2k\sqrt{1+k^2} = 2.66 \quad \checkmark$$

We also have that,

$$4k^2 = \frac{1}{4R} L^2 C^2 R^2 \implies L = \frac{-4k}{C\sqrt{R}}$$

$$-4k^2 = \frac{1}{4R} (R^2 C^2 + L^2 - 2LCR^2)$$

$$-16k^2 R = R^2 C^2 + \frac{16k^2}{C^2 R} + 8kR\sqrt{R}$$

$$R^2 C^4 + (16k^2 R + 8kR\sqrt{R})C^2 + \frac{16k^2}{R} = 0$$

$$7.08C^4 - 6.64C^2 + 1.56 = 0$$

Thus,

$$C = 0.685 \quad \checkmark$$

$$L = 1.822 \quad \checkmark$$

( $R, L, C$  check with results given in Matthai, Young, and Jones.)

**8.7** maximally flat, 0-2 GHz,  $\alpha > 20$  dB at 3.4 GHz  
 $Z_0 = 50 \Omega$

$$\left| \frac{\omega}{\omega_c} \right| - 1 = \frac{3.4}{2} - 1 = 0.7 \quad \text{From Fig 8.26, } N=5$$

From Table 8.3


$$g_1 = 0.6180$$

$$g_2 = 1.6180$$

$$g_3 = 2.000$$

$$g_4 = 1.6180$$

$$g_5 = 0.6180$$

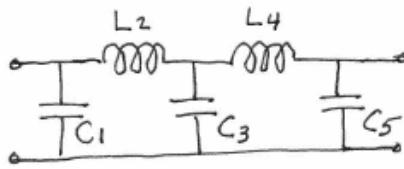

Using (8.67),

$$C_1 = \frac{g_1}{R_0 \omega_c} = 0.984 \mu F$$


$$L_2 = \frac{R_0 g_2}{\omega_c} = 6.44 \text{ nH}$$

$$C_3 = \frac{g_3}{R_0 \omega_c} = 3.183 \text{ pF}$$

$$L_4 = \frac{R_0 g_4}{\omega_c} = 6.44 \text{ nH}$$

$$C_5 = \frac{g_5}{R_0 \omega_0} = 0.984 \text{ pF}$$

filter response is plotted below.

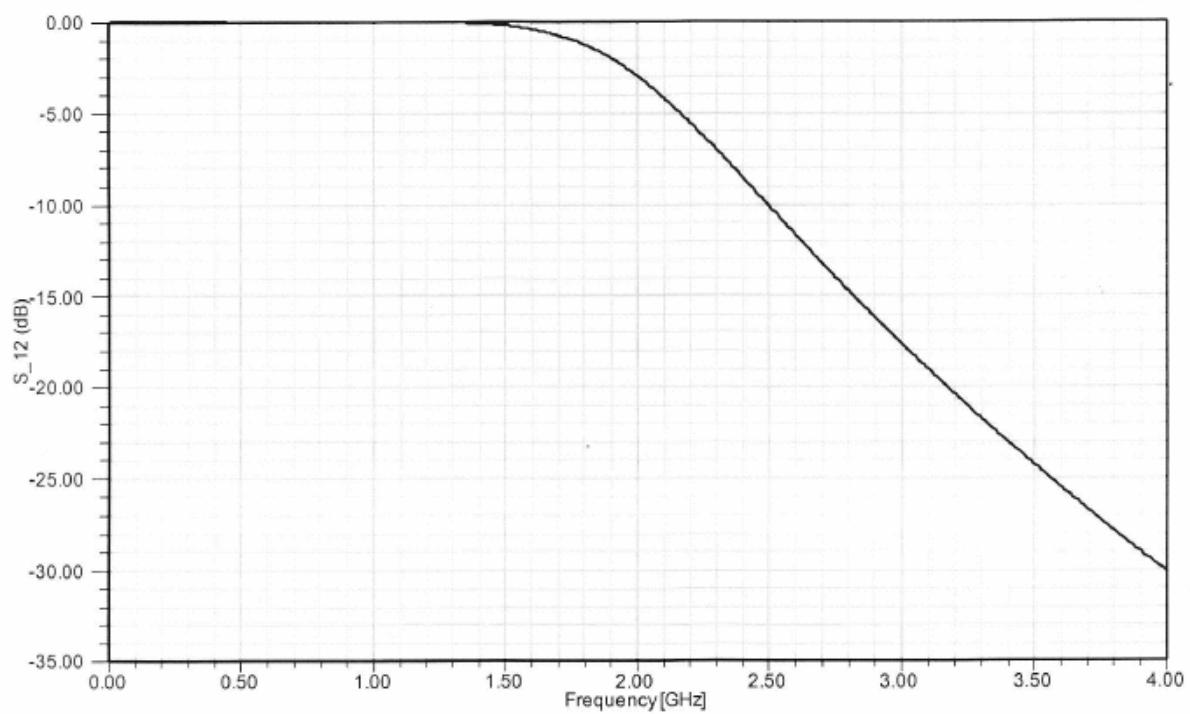

**8.8**

high-pass, 3dB equal-ripple,  $f_c = 3\text{GHz}$ ,  
 $\alpha > 30\text{dB}$  at  $2.0\text{GHz}$ ,  $Z_0 = 75\Omega$

$$\text{at } 2.0\text{GHz}, \left| \frac{\omega_c}{\omega} \right| - 1 = \frac{3}{2} - 1 = 0.5 \Rightarrow N=5$$

From Table 8.4,


$$g_1 = 3.4817$$

$$g_2 = 0.7618$$

$$g_3 = 4.4381$$

$$g_4 = 0.7618$$

$$g_5 = 3.4817$$

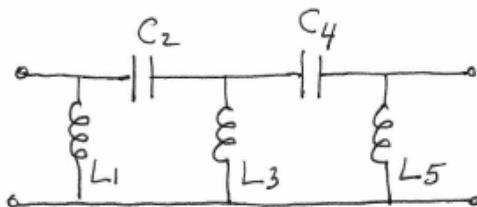

Using (8.70),

$$L_1 = \frac{Z_0}{\omega_c g_1} = 1.143 \mu\text{H}$$


$$C_2 = \frac{1}{Z_0 \omega_c g_2} = 0.928 \mu\text{F}$$

$$L_3 = \frac{Z_0}{\omega_c g_3} = 0.877 \mu\text{H}$$

$$C_4 = \frac{1}{Z_0 \omega_c g_4} = 0.928 \mu\text{F}$$

$$L_5 = \frac{Z_0}{\omega_c g_5} = 1.143 \mu\text{H}$$

filter response is shown below.

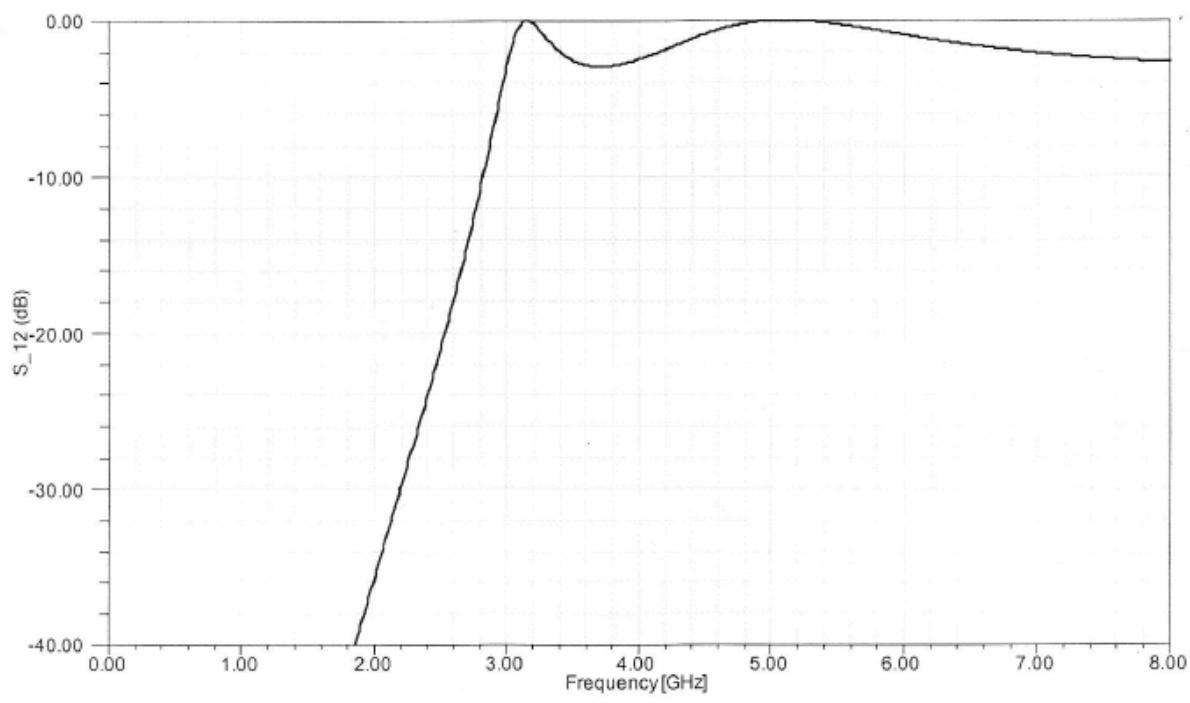

8.9

$$f_0 = 2 \text{ GHz}, \text{ B.P., M.F.G.D.}, \Delta = 0.05, N = 4, Z_0 = 50 \Omega$$


From Table 8.5 the prototype element values are,

$$g_1 = 1.0598$$

$$g_2 = 0.5116$$

$$g_3 = 0.3181$$

$$g_4 = 0.1104$$

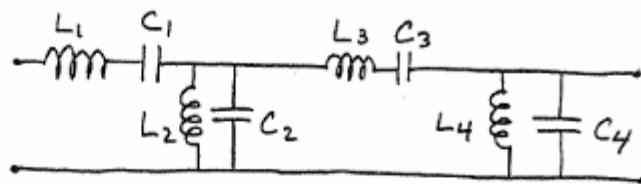

From Table 8.6 and (8.64) the scaled element values are

$$L_1 = \frac{g_1 Z_0}{\omega_0 \Delta} = 84.3 \text{ nH} \quad \checkmark \quad C_1 = \frac{\Delta}{\omega_0 g_1 Z_0} = 0.075 \text{ pF} \quad \checkmark$$


$$L_2 = \frac{\Delta Z_0}{\omega_0 g_2} = 0.388 \text{ nH} \quad \checkmark \quad C_2 = \frac{g_2}{\omega_0 \Delta Z_0} = 16.3 \text{ pF} \quad \checkmark$$

$$L_3 = \frac{g_3 Z_0}{\omega_0 \Delta} = 25.3 \text{ nH} \quad \checkmark \quad C_3 = \frac{\Delta}{\omega_0 g_3 Z_0} = 0.25 \text{ pF} \quad \checkmark$$

$$L_4 = \frac{\Delta Z_0}{\omega_0 g_4} = 1.80 \text{ nH} \quad \checkmark \quad C_4 = \frac{g_4}{\omega_0 \Delta Z_0} = 3.51 \text{ pF} \quad \checkmark$$

The calculated filter response is shown below.

▽ MS12 [dB] FILTER

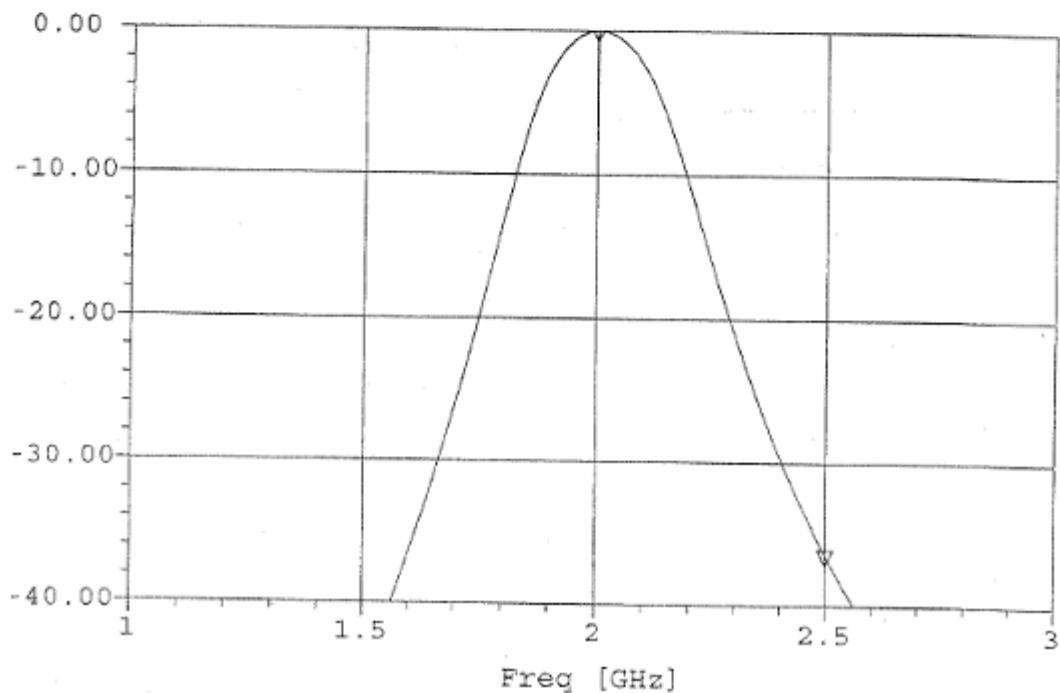

**8.10**  $f_0 = 3 \text{ GHz}$ ,  $Z_0 = 75 \Omega$ ,  $N = 3$ , B.S.,  $0.5 \text{ dB E.R.}$

First use (8.75) to transform  $3.1 \text{ GHz}$  to a L.P. prototype response frequency:


$$\omega \leftarrow \Delta \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)^{-1} = 0.1 \left( \frac{3.1}{3} - \frac{3}{3.1} \right)^{-1} = 1.52$$

So,  $\left| \frac{\omega}{\omega_c} \right| - 1 = 0.52$ , and Figure 8.27a gives an attenuation of  $11 \text{ dB}$  for  $N = 3$ . From Table 8.4, the prototype values are,

$$g_1 = 1.5963$$

$$g_2 = 1.0967$$

$$g_3 = 1.5963$$

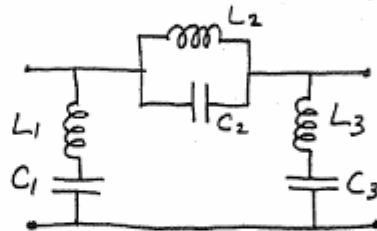

From Table 8.6 and (8.64) the scaled element values are,


$$L_1 = \frac{Z_0}{\omega_0 g_1 \Delta} = 24.9 \text{ nH } \checkmark \quad C_1 = \frac{g_1 \Delta}{\omega_0 Z_0} = 0.113 \text{ pF } \checkmark$$

$$L_2 = \frac{g_2 \Delta Z_0}{\omega_0} = 0.436 \text{ nH } \checkmark \quad C_2 = \frac{1}{Z_0 \omega_0 g_2 \Delta} = 6.45 \text{ pF } \checkmark$$


$$L_3 = \frac{Z_0}{\omega_0 g_3 \Delta} = 24.9 \text{ nH } \checkmark \quad C_3 = \frac{g_3 \Delta}{\omega_0 Z_0} = 0.113 \text{ pF } \checkmark$$

The calculated response for this filter is shown on the following page. Note that the insertion loss at  $3.1 \text{ GHz}$  is about  $10 \text{ dB}$ .

▽ MS12 [dB] FILTER

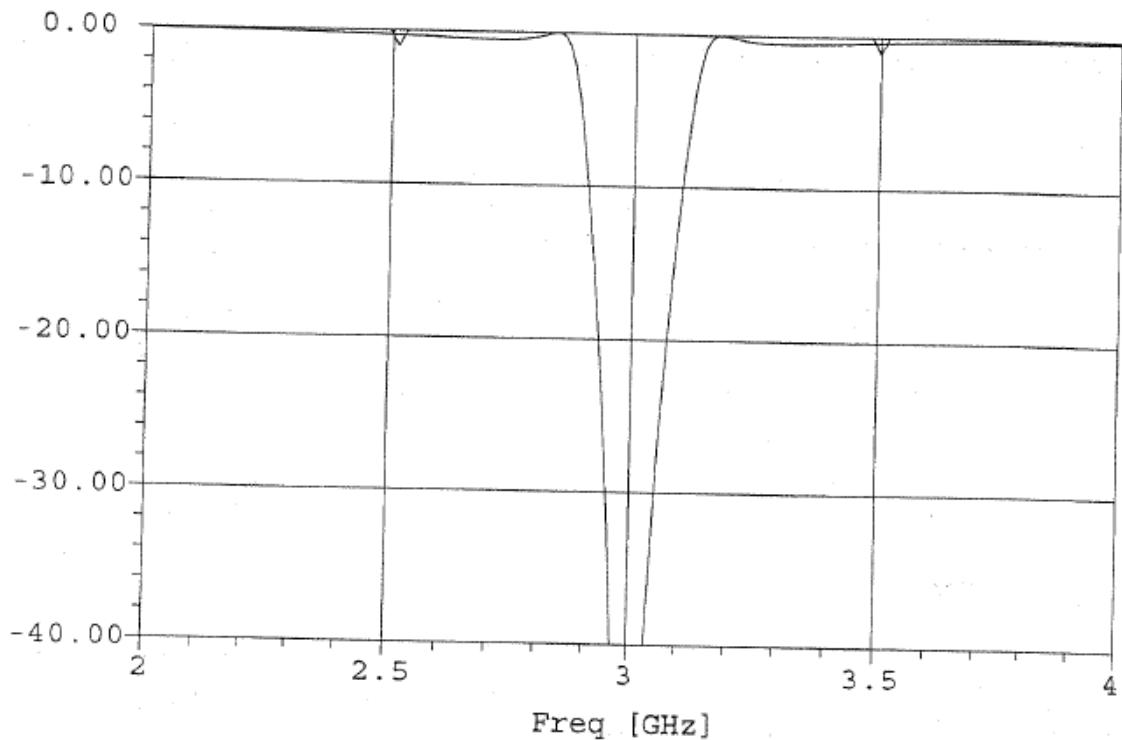


8.11

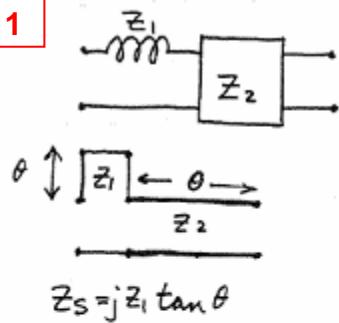

$$\theta \uparrow \boxed{z_1} \leftarrow \theta \rightarrow z_2$$

$$Z_S = j z_1 \tan \theta$$

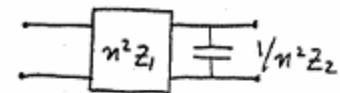

$$n^2 z_1 \xleftarrow{\theta} \begin{array}{c} \uparrow \\ \downarrow \end{array} \theta \xrightarrow{\theta} n^2 z_2$$

$$Y_S = \frac{j}{n^2 z_2} \tan \theta$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & j z_1 \tan \theta \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \cos \theta & j z_2 \sin \theta \\ \frac{j}{z_2} \sin \theta & \cos \theta \end{bmatrix} \quad \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \theta & j n^2 z_2 \sin \theta \\ j \sin \theta & \cos \theta \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{j \tan \theta}{n^2 z_2} & 1 \end{bmatrix}$$

$$= \begin{bmatrix} \cos \theta - \frac{z_1}{z_2} \frac{\sin^2 \theta}{\cos \theta} & j(z_1 + z_2) \sin \theta \\ \frac{j}{z_2} \sin \theta & \cos \theta \end{bmatrix} \quad = \begin{bmatrix} \cos \theta - \frac{z_1}{z_2} \frac{\sin^2 \theta}{\cos \theta} & j n^2 z_1 \sin \theta \\ \frac{j}{n^2} \left( \frac{1}{z_1} + \frac{1}{z_2} \right) \sin \theta & \cos \theta \end{bmatrix}$$


So these two matrices are equal if,

$$z_1 + z_2 = n^2 z_1$$


$$\text{or, } n^2 = 1 + z_2/z_1 \quad \checkmark$$

**8.12**  $f_0 = 6 \text{ GHz}, N=3, M.F., Z_0 = 50\Omega$


From Table 8.3 the L.P. prototype is,

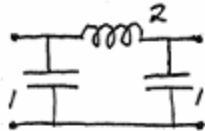

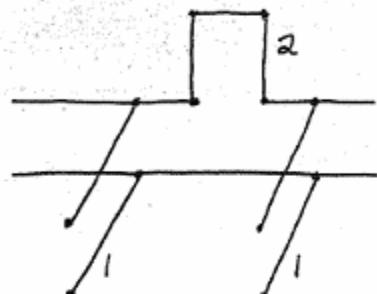(choosing a  $\pi$ -circuit simplifies the problem)  
Richards' transform:




Add unit elements at ends:

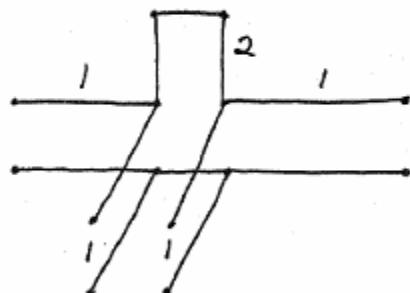


Apply first Kuroda identity (twice):
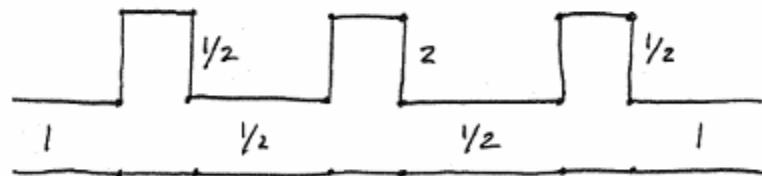
$$\begin{aligned} Z_1 &= 1 \\ Z_2 &= 1 \\ n^2 &= 1 + \frac{Z_2}{Z_1} \\ &= 2 \end{aligned}$$




Scale to  $50\Omega$ :

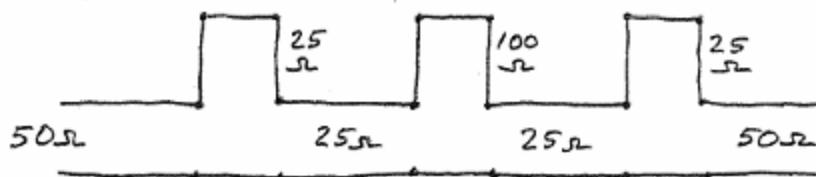


All line lengths and stub lengths are  $\lambda/8$  long at 6 GHz. The calculated filter response is shown below.

▽ MS12 [dB] FILTER

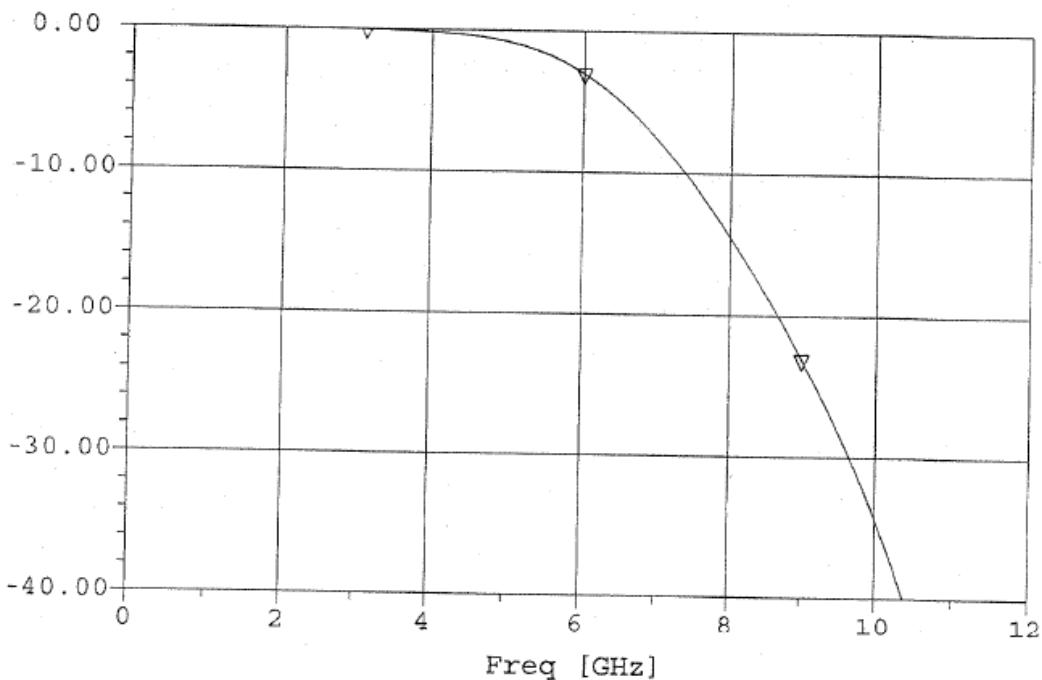


**8.13**  $f_0 = 8 \text{ GHz}$ ,  $N=4$ , L.P., M.F.,  $Z_0 = 50 \Omega$


From Table 8.3 the L.P. prototype is,

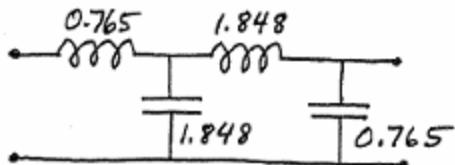


Applying Richards transform:

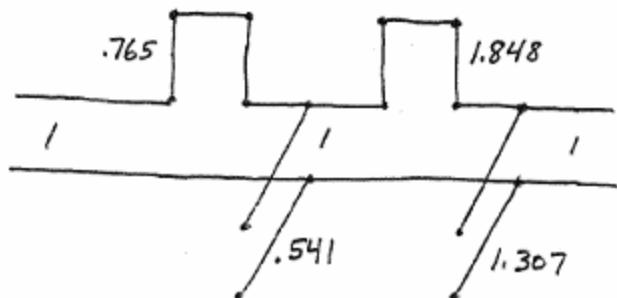


Add unit elements:

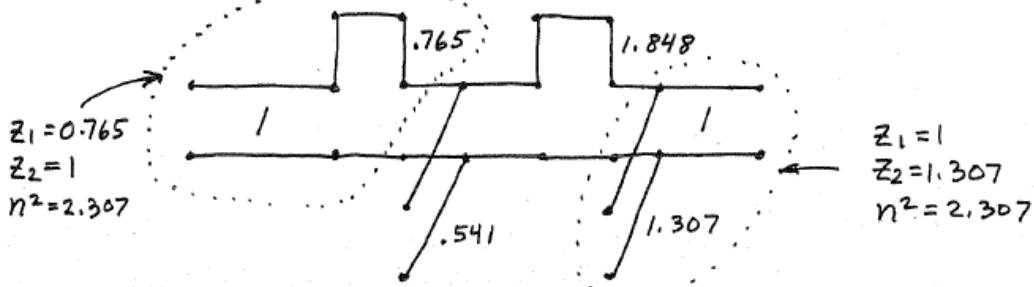

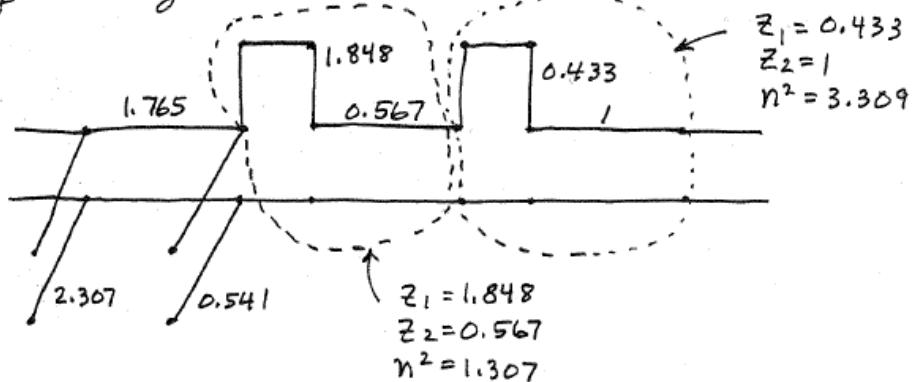
Use the second Kuroda identity on left; first Kuroda identity on right:



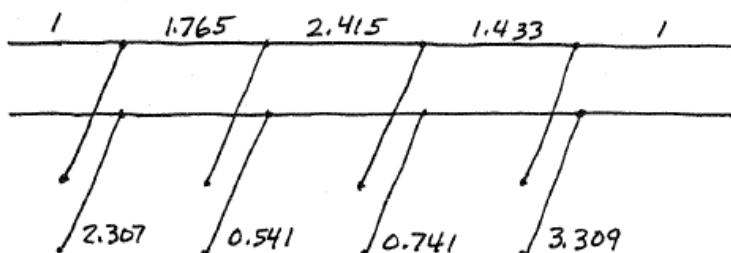Now use the second Kuroda identity twice:




Scale to  $50\Omega$ :

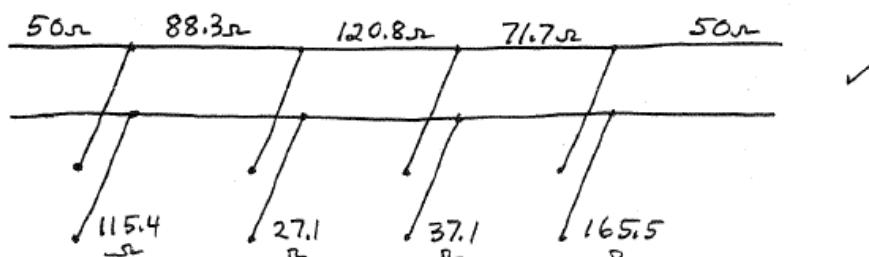


all lines are  $\lambda/8$  long at 8GHz. The calculated filter response is shown on the following page.

▽ MS12 [dB] FILTER

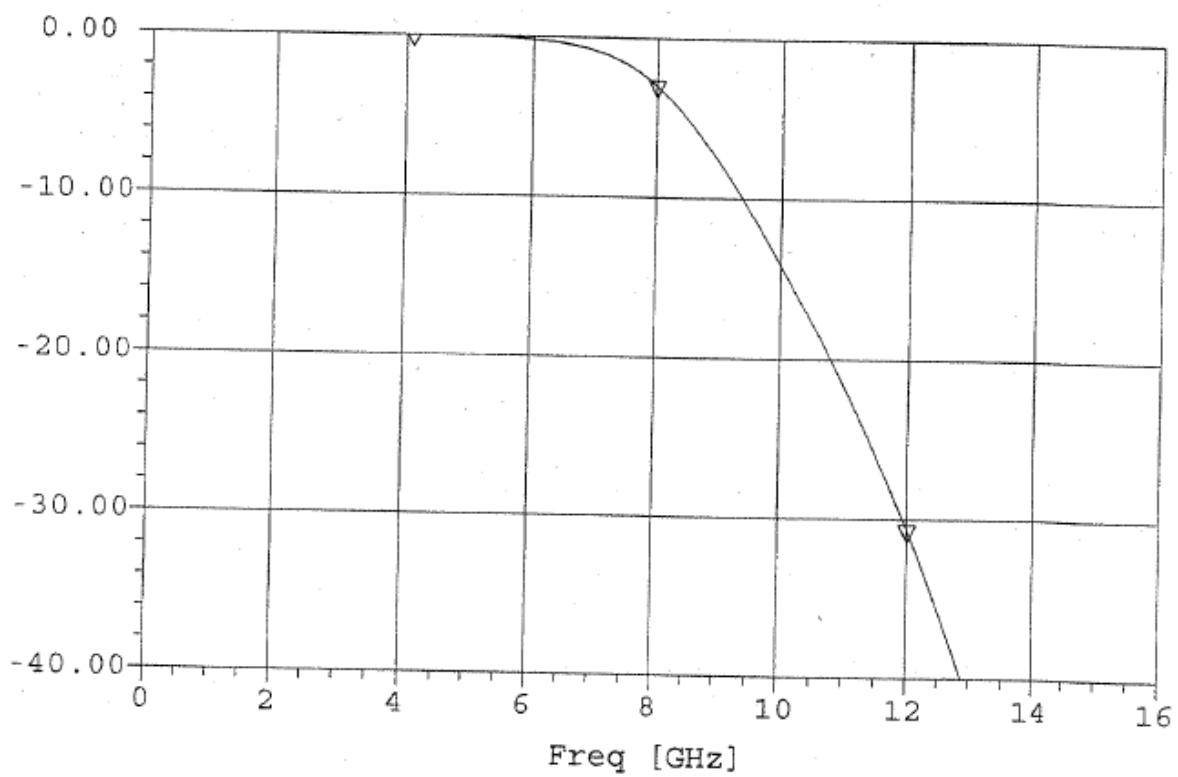


8.14

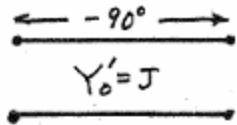Quarter-wave line ( $-\lambda/4$  long, since  $\theta < 0$ )

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 0 & -j/J \\ -j\bar{J} & 0 \end{bmatrix}$$

ADMITTANCE INVERTER:

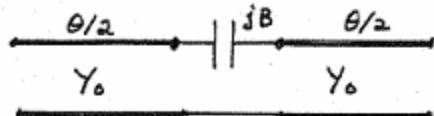

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} \cos \theta/2 & j/Y_0 \sin \theta/2 \\ jY_0 \sin \theta/2 & \cos \theta/2 \end{bmatrix} \begin{bmatrix} 1 & -j/B \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \cos \theta/2 & j/Y_0 \sin \theta/2 \\ jY_0 \sin \theta/2 & \cos \theta/2 \end{bmatrix}$$

$$= \begin{bmatrix} (\cos \theta + \frac{Y_0}{2B} \sin \theta) & j(\frac{1}{Y_0} \sin \theta - \frac{1}{B} \cos^2 \frac{\theta}{2}) \\ jY_0(\sin \theta + \frac{Y_0}{B} \sin^2 \frac{\theta}{2}) & (\cos \theta + \frac{Y_0}{2B} \sin \theta) \end{bmatrix} \checkmark$$

Equivalence requires the following conditions:

$$A, D: \cos \theta + \frac{Y_0}{2B} \sin \theta = 0 \Rightarrow \theta = -\tan^{-1}\left(\frac{2B}{Y_0}\right) < 0 \quad \checkmark$$

$$B: \frac{Y_0}{J} = -\sin \theta + \frac{Y_0}{B} \cos^2 \theta/2$$

$$C: \frac{J}{Y_0} = -\sin \theta - \frac{Y_0}{B} \sin^2 \theta/2$$

$$\therefore \frac{Y_0}{J} - \frac{J}{Y_0} = \frac{Y_0}{B}$$

$$\text{or, } B = \frac{Y_0}{\frac{Y_0}{J} - \frac{J}{Y_0}} = \frac{J}{1 - (J/Y_0)^2} \quad \checkmark$$

also,


$$\tan |\theta| = \frac{2B}{Y_0} = \frac{2(J/Y_0)}{1 - (J/Y_0)^2} = \frac{2 \tan |\frac{\theta}{2}|}{1 - \tan^2 |\frac{\theta}{2}|}$$

so,

$$\tan |\frac{\theta}{2}| = J/Y_0 \quad \checkmark$$

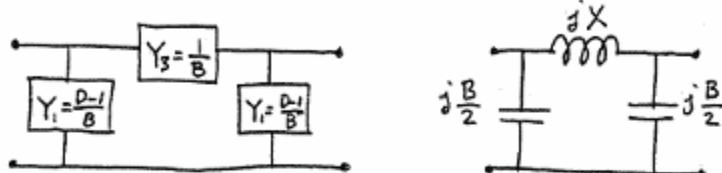**8.15**

The easiest way to do this problem is to use the  $\pi$ -network of Table 4.1, with the shunt and series element values given in terms of the ABCD parameters:



Then using the ABCD parameters for a transmission line gives the equivalent circuit elements as,

$$jX = B = jZ_0 \sin \beta l$$

$$j\frac{B}{2} = \frac{D-1}{B} = \frac{\cos \beta l - 1}{jZ_0 \sin \beta l} = \frac{j}{Z_0} \tan \beta l / 2$$

For  $\beta l < \pi/4$  and large  $Z_0$ , these results reduce to :

$$X \approx Z_0 \beta l \quad \checkmark$$

$$\frac{B}{2} \approx 0 \quad \checkmark$$

$$\xrightarrow[X_L = Z_0 \beta l]{\text{---}} \quad \checkmark$$

For  $\beta l < \pi/4$  and small  $Z_0$ , these results reduce to :

$$X \approx 0$$

$$\frac{B}{2} \approx \frac{\beta l}{2Z_0}$$

$$\xrightarrow[B_c = Y_0 \beta l]{\text{---}} \quad \checkmark$$

(NOTE : This problem can also be done using  $y$ -parameters, but a sign change for  $y_{12}$  will be required because of the reference direction for  $I_2$  for the ABCD parameters.)

**8.16**  $f_0 = 3 \text{ GHz}$ ,  $N=5$ ,  $0.5 \text{ dB}$  equal ripple,  $Z_0 = 50\Omega$ ,  $Z_L = 15\Omega$ ,  $Z_h = 120\Omega$

a) From Table 8.4 and (8.86):

$$g_1 = 1.7058 = C_1 \Rightarrow \beta l_1 = g_1 Z_0 / Z_0 = 29.3^\circ$$

$$g_2 = 1.2296 = L_2 \Rightarrow \beta l_2 = g_2 Z_0 / Z_h = 29.4^\circ$$

$$g_3 = 2.5408 = C_3 \Rightarrow \beta l_3 = g_3 Z_L / Z_0 = 43.7^\circ$$

$$g_4 = 1.2296 = L_4 \Rightarrow \beta l_4 = g_4 Z_0 / Z_h = 29.4^\circ$$

$$g_5 = 1.7058 = C_5 \Rightarrow \beta l_5 = g_5 Z_L / Z_0 = 29.3^\circ$$


Observe that  $\beta l_i < 45^\circ$  for all lines

b)  $\epsilon_r = 4.2$ ,  $d = 0.079 \text{ cm}$ ,  $\tan \delta = 0.02$ , Cu,  $t = 0.5 \text{ mil}$

$$W(15\Omega) = 7.98 \text{ mm} ; l_1 = 0.42 \text{ cm} ; l_3 = 0.63 \text{ cm} ; l_5 = 0.42 \text{ cm}$$

$$W(120\Omega) = 0.213 \text{ mm} ; l_2 = 0.48 \text{ cm} ; l_4 = 0.48 \text{ cm}$$

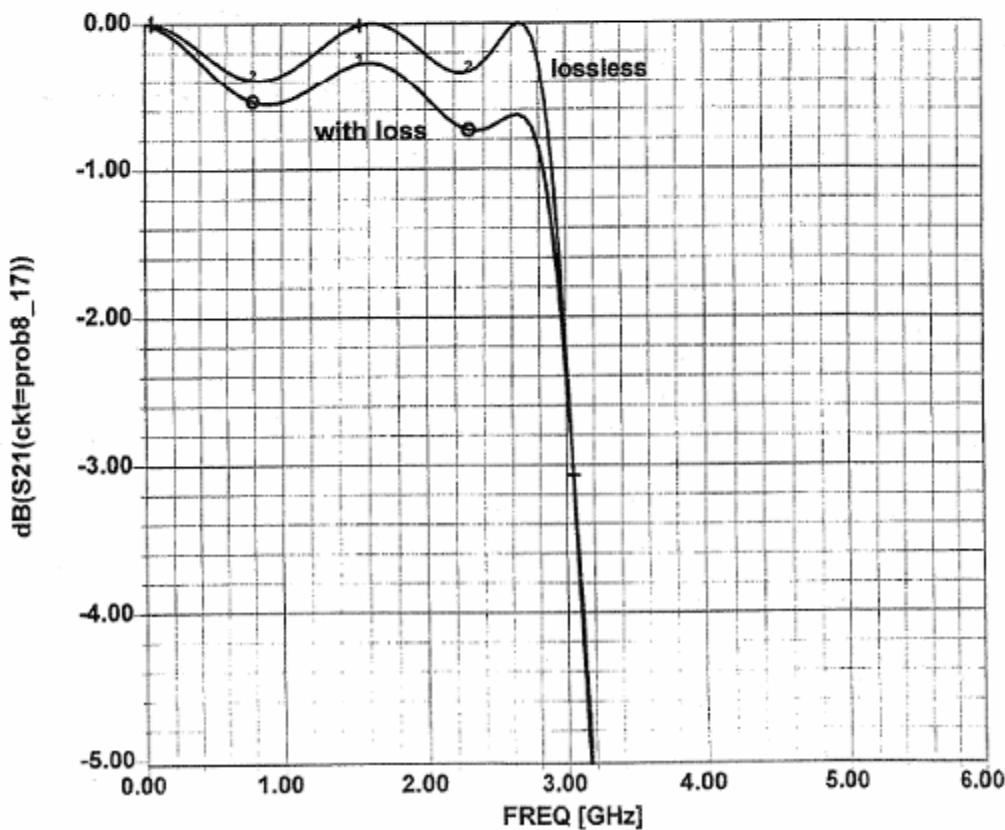
The response, with and without loss, is shown below.



8.17


$$f_0 = 2 \text{ GHz}, \text{ L.P., M.F., } Z_0 = 50 \Omega$$

From Table 8.3 the LP prototype is,

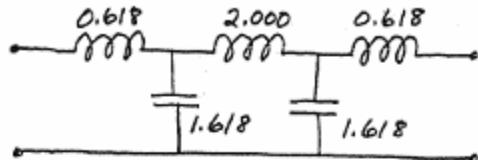

The shunt capacitors can be implemented with a length of  $Z_L$  line. Using (8.83b) gives,

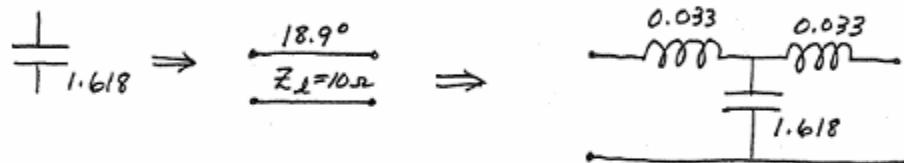
$$B = \frac{1.618}{Z_0} = \frac{\sin \beta l}{Z_L} \Rightarrow \beta l = 18.9^\circ$$




The model for this line (see Figure 8.39) shows inductors on either side, with values given by (8.83a):

$$\frac{X}{2Z_0} = \frac{Z_L}{Z_0} \tan \beta l/2 = 0.033$$

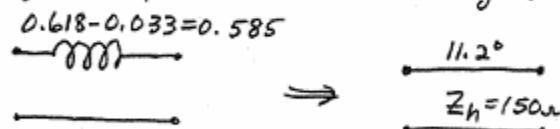
Then the end inductors of value 0.618 can be implemented as lengths of  $Z_h$  line. Using (8.83a) gives,



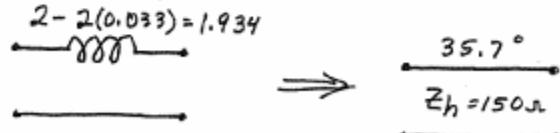
and the middle inductor of value 2.000 can be implemented as,




The final filter:

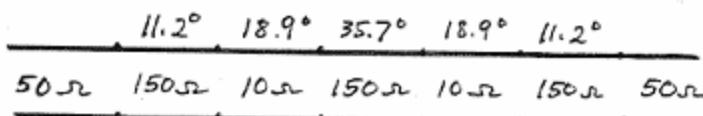

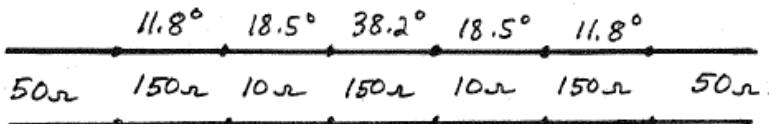For comparison, the design using the approximations of (8.84) and (8.85) is,



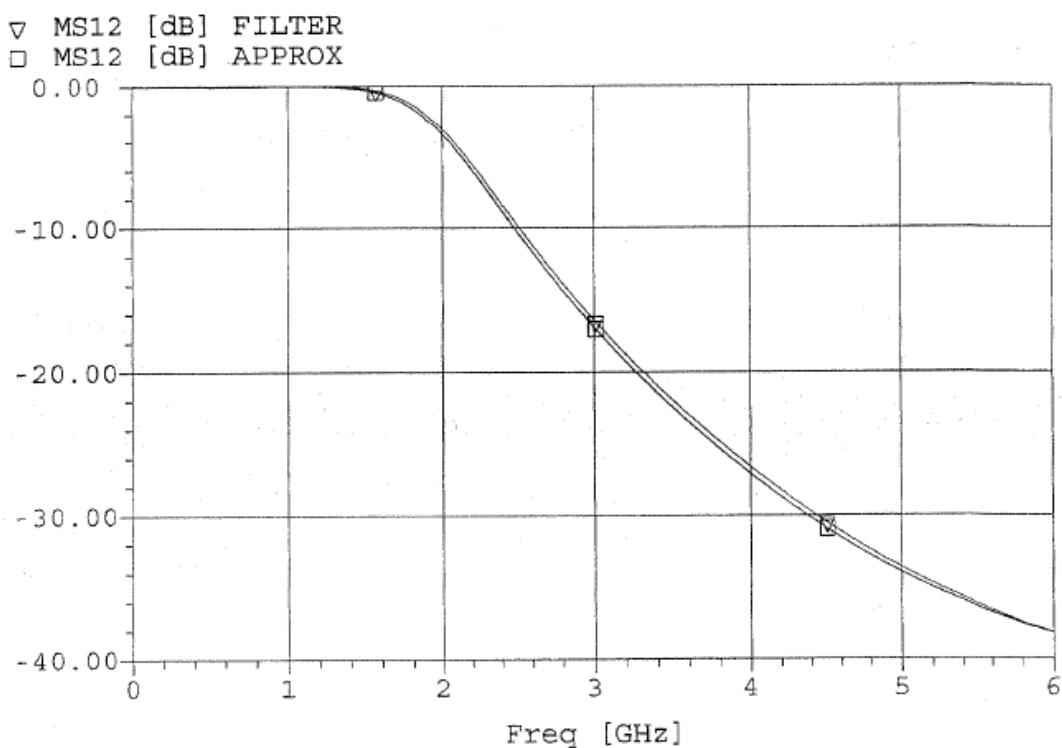Note that only the middle section differs very much in these two designs. The calculated filter response is shown below for both designs. Note that there is very little difference.



**8.18**  $f_0 = 2.45 \text{ GHz}$ ,  $\text{BW} = 10\%$ , EQUAL-RIPPLE ( $0.5 \text{ dB}$ ),  $N=3$ ,  $Z_0 = 50 \Omega$

a) Use (8.71) to transform  $2.1 \text{ GHz}$  to normalized L.P. form:

$$\omega \leftarrow \frac{1}{\Delta} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{0.1} \left( \frac{2.1}{2.45} - \frac{2.45}{2.1} \right) = -3.09$$


Then,  $\left| \frac{\omega}{\omega_0} \right| - 1 = 2.09 \Rightarrow$  Fig 8.27 gives  $\alpha \approx 30 \text{ dB}$

The L.P. prototype values are given in Table 8.4

$Z_{0Jn}$  is found from (8.121), and  $Z_{0e}, Z_{0o}$  from (8.108):

$n$	$g_n$	$Z_{0Jn}$	$Z_{0e}(n)$	$Z_{0o}(n)$
1	1.5963	0.3137	70.6	39.2
2	1.0967	0.1187	56.6	44.8
3	1.5963	0.1187	56.6	44.8
4	1.0000	0.3137	70.6	39.2

$Z_0 = 50 \Omega$

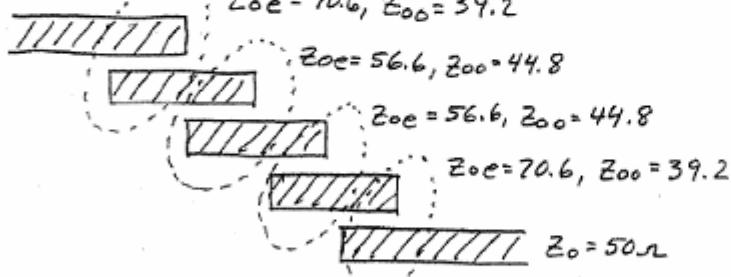


b)  $d = 0.158 \text{ cm}$ ,  $\epsilon_r = 4.2$ ,  $\tan \delta = 0.01$ ,  $Cu$ ,  $t = 0.5 \text{ mil}$

From Serenade,

$$Z_{0e} = 70.6, Z_{0o} = 39.2 \Rightarrow W = 2.484 \text{ mm}, S = 0.415 \text{ mm}, l = 1.74 \text{ cm}$$

$$Z_{0e} = 56.6, Z_{0o} = 44.8 \Rightarrow W = 3.026 \text{ mm}, S = 1.723 \text{ mm}, l = 1.71 \text{ cm}$$

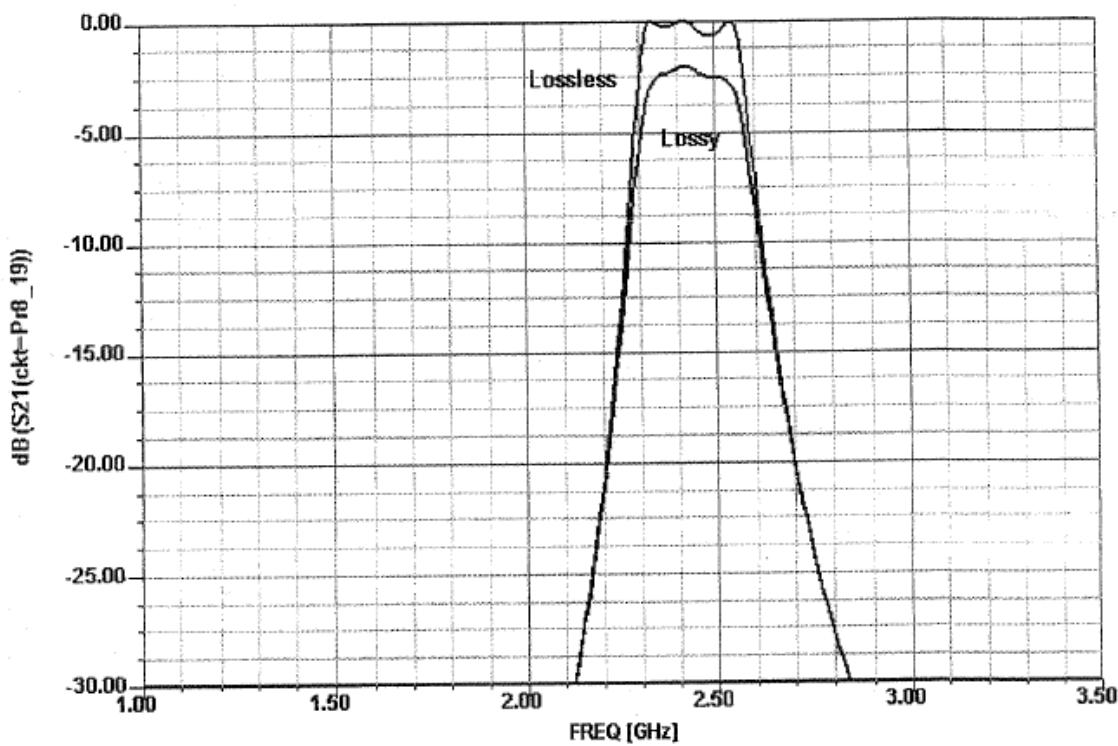
The calculated response, from Serenade, is shown on the following page.



8.19
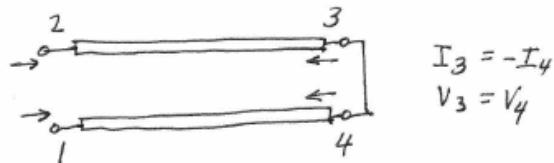
## Schiffman Phase Shifter (see MTT April 1958)

First consider the shorted coupled line section:



$$V_1 = Z_{11} I_1 + Z_{12} I_2 + Z_{13} I_3 + Z_{14} I_4$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 + Z_{23} I_3 + Z_{24} I_4$$

$$V_3 = Z_{31} I_1 + Z_{32} I_2 + Z_{33} I_3 + Z_{34} I_4$$

$$V_4 = Z_{41} I_1 + Z_{42} I_2 + Z_{43} I_3 + Z_{44} I_4$$

Using the terminal conditions that  $I_3 = -I_4$ ,  $V_3 = V_4$ , allow this to be reduced to

$$V_1 = \left[ Z_{11} - \frac{(Z_{13} - Z_{14})^2}{2(Z_{11} - Z_{12})} \right] I_1 + \left[ Z_{12} + \frac{(Z_{13} - Z_{14})^2}{2(Z_{11} - Z_{12})} \right] I_2$$

$$V_2 = \left[ Z_{12} + \frac{(Z_{14} - Z_{13})^2}{2(Z_{11} - Z_{12})} \right] I_1 + \left[ Z_{11} - \frac{(Z_{14} - Z_{13})^2}{2(Z_{11} - Z_{12})} \right] I_2$$

where we have used symmetry and relations such as

$Z_{11} = Z_{22} = Z_{33} = Z_{44}$ . From (8.99), the  $Z_{ij}$  are given for the coupled line. For a 2-port, the image impedance is,

$$Z_i = \sqrt{Z_1 Z_2} \sqrt{1 + \frac{Z_1}{4 Z_2}} = \sqrt{2 Z_{12} (Z_{11} - Z_{12})} \sqrt{1 + \frac{2(Z_{11} - Z_{12})}{4 Z_{12}}}$$

$$= \sqrt{(Z_{11} - Z_{12})(Z_{11} + Z_{12})} \quad (Z_{11}, Z_{12} \text{ are the equiv. 2-port } Z \text{ params})$$

we can show that

$$Z_{11} - Z_{12} = -j Z_0 \cot \theta + j Z_0 \sec \theta \csc \theta$$

$$Z_{11} + Z_{12} = -j Z_0 e \cot \theta$$



Then  $Z_i = \sqrt{Z_0 e Z_0} \checkmark$  (agrees w/ result in Table 8.8)

The propagation constant is,

$$\begin{aligned} e^{\gamma} &= 1 + Z_1 / 2Z_2 + \sqrt{Z_1 / Z_2 + Z_1^2 / 4Z_2^2} \\ &= \frac{Z_{11}}{Z_{12}} + \frac{1}{Z_{12}} \sqrt{(Z_{11} + Z_{12})(Z_{11} - Z_{12})} = \frac{Z_0}{Z_{12}} + \frac{1}{Z_{12}} Z_i \\ &= \frac{Z_0 e \cot \theta - Z_0 e \tan \theta + 2j \sqrt{Z_0 e Z_0}}{Z_0 e \cot \theta + Z_0 e \tan \theta} = (\cos \beta + j \sin \beta) e^{\alpha} \end{aligned}$$

$$\text{so, } \cos \beta = \frac{Z_0 e \cot \theta - Z_0 e \tan \theta}{Z_0 e \cot \theta + Z_0 e \tan \theta} = \frac{Z_0 e - Z_0 e \tan^2 \theta}{Z_0 e + Z_0 e \tan^2 \theta} \checkmark$$

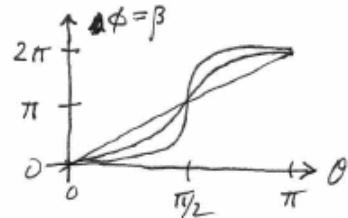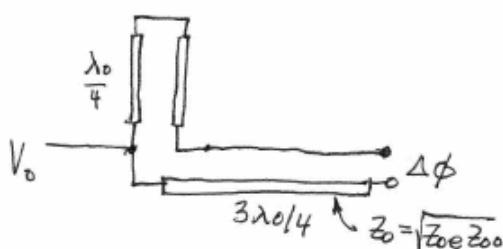at midband,  $\theta = \pi/2$ ,  $\cos \beta = -1$ ,  $\beta = 180^\circ \checkmark$




$$\text{let } \phi = \cos^{-1} \frac{Z_0 e - Z_0 e \tan^2 \theta}{Z_0 e + Z_0 e \tan^2 \theta}, \text{ let } p = \frac{Z_0 e}{Z_0}$$

$$\text{Then } \Delta \phi = \phi - \beta \theta$$

Using  $p = 2.7$  gives BW from  $61.2^\circ$  to  $118.8^\circ$   
for  $\Delta \phi = 90^\circ \pm 2.5^\circ$ , or 1.93:1.

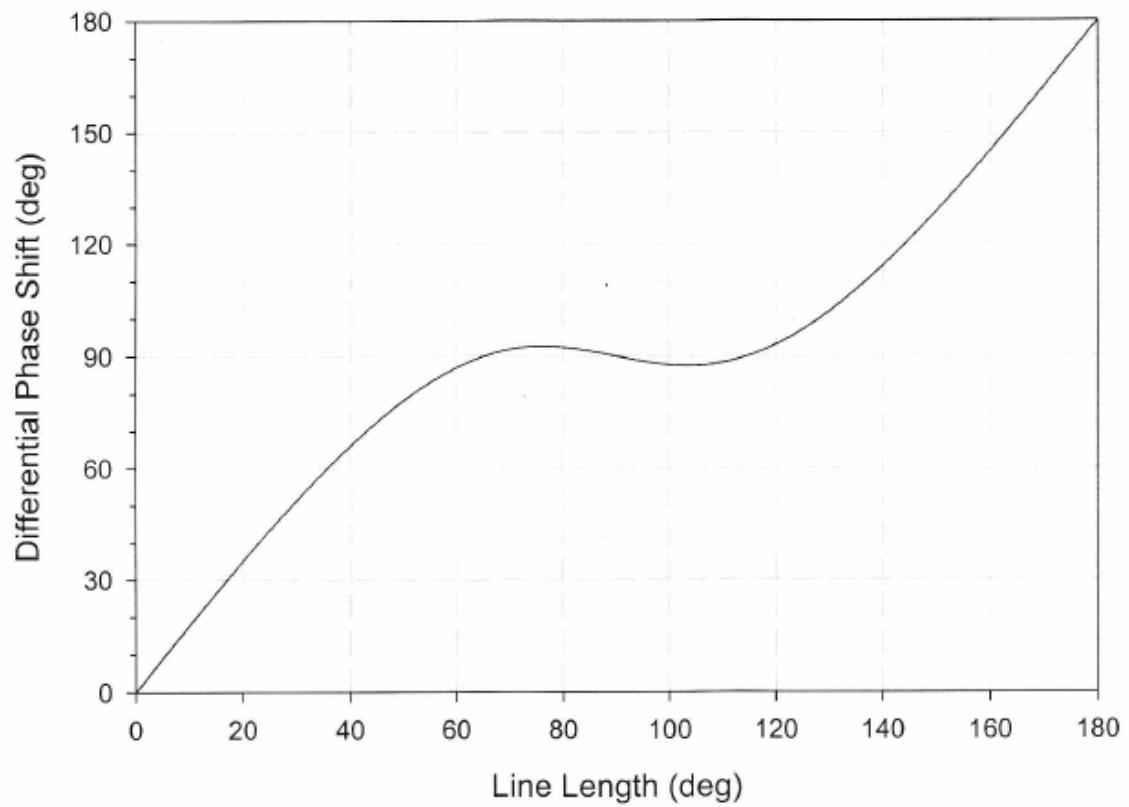$\Delta \phi$  is plotted vs  $\theta$  below.




**8.20**

$$f_0 = 3 \text{ GHz}, \text{ B.S., M.F.}, N=4, \Delta=0.15, Z_0 = 40\Omega.$$

We find the  $g_n$  values from Table 8.3. Then the  $\lambda/4$  o.c. stub characteristic impedances can be found from (8.130) :


$n$	$g_n$	$Z_{on}(\Omega)$
1	0.765	444.
2	1.848	184.
3	1.848	184.
4	0.765	444.

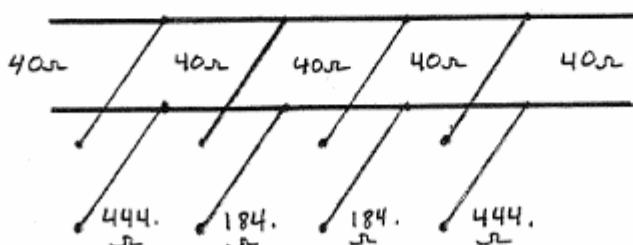( $Z_{o1}$  and  $Z_{o4}$  may be too high to be practical)  
The final filter is shown below:



all lines and stubs are  $\lambda/4$  long at 3 GHz. The calculated filter response is shown below:


▽ MS12 [dB] FILTER

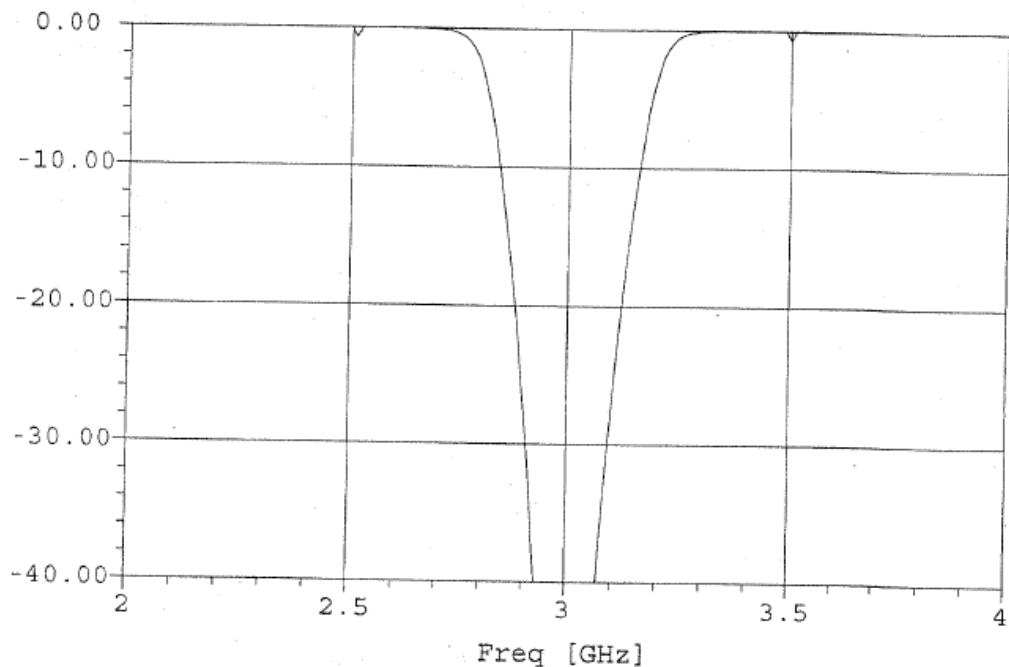

**8.21** BANDPASS,  $N=3$ , EQUAL RIPPLE (0.5 dB),  $\lambda/4$  S.C. stubs,  $f_0=3\text{GHz}$ , 20% BW

a) Find  $g_n$  from Table 8.4. Then the  $\lambda/4$  short-circuited stub characteristic impedances can be found as,

$n$	$g_n$	$Z_{on}(\omega)$	
1	1.5963	9.8	$\Delta = 0.20$
2	1.0967	14.3	$Z_{on} = \frac{\pi Z_c A}{4 g_n}$
3	1.5963	9.8	

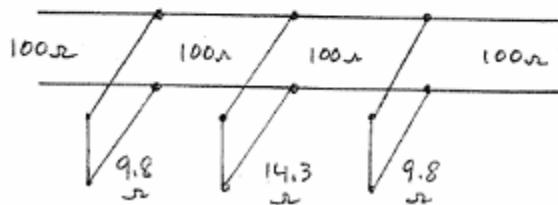


b) FR-4,  $\epsilon_r=4.2$ ,  $d=0.079\text{cm}$ ,  $\tan \delta=0.02$ , Cu,  $t=0.5\text{mil}$

$$W(9.8) = 1.307\text{ cm}, \quad 90^\circ = 1.27\text{ cm}$$

$$W(14.3) = 0.845\text{ cm}, \quad 90^\circ = 1.29\text{ cm}$$
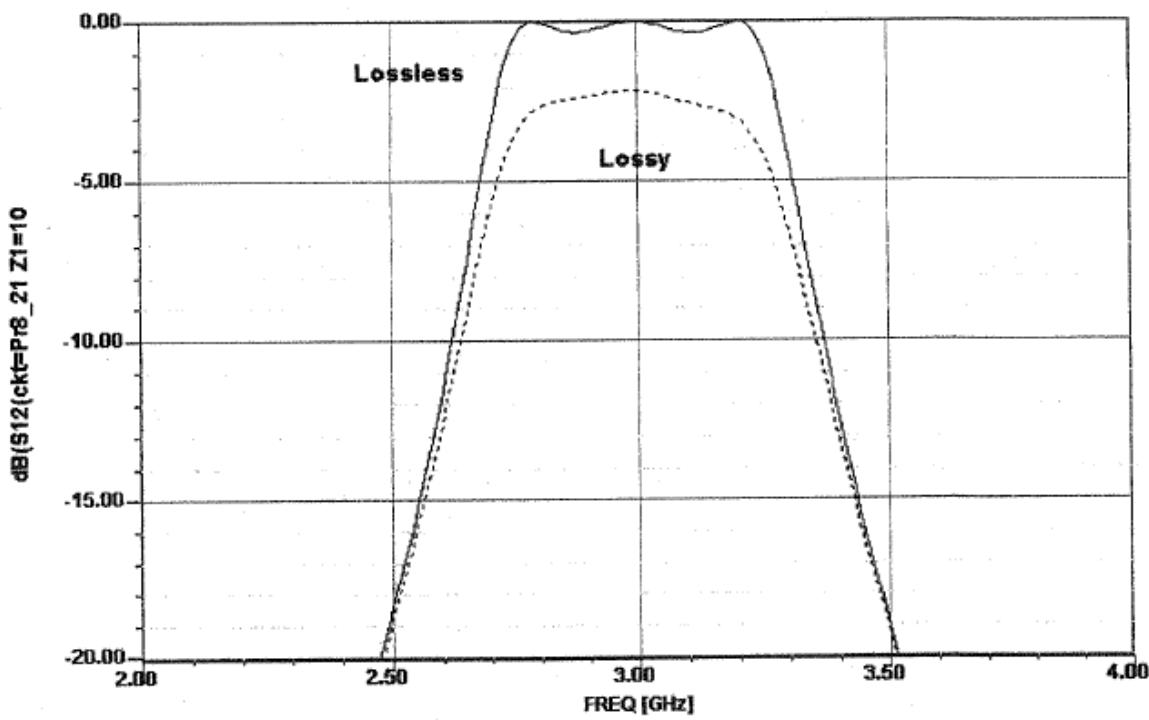
$$W(100) = 0.367\text{ mm}, \quad 90^\circ = 1.46\text{ cm}$$



**8.22** The bandpass  $\lambda/4$  resonator filter uses short-circuited stubs, which have an input admittance of,

$$Y = -jY_{on} \cot \theta, \text{ where } \theta = \pi/2 \text{ for } \omega = \omega_0.$$

Let  $\omega = \omega_0 + \Delta\omega$ . Then  $\theta = \pi/2 (1 + \Delta\omega/\omega_0)$ , and


$Y = jY_{on} \tan \frac{\pi \Delta\omega}{2\omega_0} \approx \frac{j\pi Y_{on} (\omega - \omega_0)}{2\omega_0}$ . Now the admittance of a parallel LC resonator is, from Table 6.1,

$$Y \approx 2jC_n(\omega - \omega_0).$$

So the characteristic impedance of the stub is,

$$Z_{0n} = \frac{1}{Y_{0n}} = \frac{\pi}{4\omega_0 C_n}$$

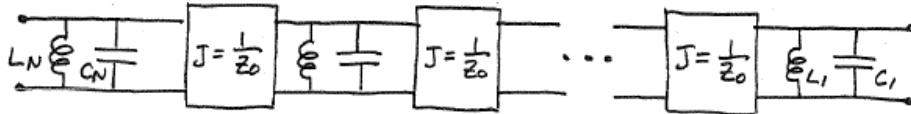The filter circuit can be redrawn as follows :



This is the same as the circuit in part (e) of Figure 8.45, for coupled line bandpass filters (with  $Z_0 J_n = 1$ ). Correspondence with the lumped-element bandpass filter requires that,

$$\sqrt{\frac{C_1}{L_1}} = \sqrt{\frac{C'_1}{L'_1}}$$

$$Z_0^2 \sqrt{\frac{C_2}{L_2}} = \sqrt{\frac{L'_2}{C'_2}}$$

where  $C'_n$  and  $L'_n$  are the lumped element filter values, and  $L_n C_n = L'_n C'_n = 1/\omega_0^2$ . Solving for  $C_n$  gives,

$$C_1 = C'_1$$

$$C_2 = \frac{1}{\omega_0^2 Z_0^2 C'_2}$$

Using Table 8.6 to transform back to LP prototype values gives,

$$C_1 = C'_1 = \frac{g_1}{\Delta \omega_0 Z_0}$$

$$C_2 = \frac{1}{\omega_0^2 Z_0^2} \left( \frac{\omega_0 g_2 Z_0}{\Delta} \right) = \frac{g_2}{\Delta \omega_0 Z_0}$$

So the characteristic impedances are,

$$Z_{0n} = \frac{\pi}{4\omega_0} \left( \frac{\Delta \omega_0 Z_0}{g_1} \right) = \frac{\pi \Delta Z_0}{4 g_1} \quad \checkmark$$

which agrees with (8.131).

**8.23**

$$f_0 = 4 \text{ GHz}, \Delta = 0.12, \text{B.P., M.F.}, Z_0 = 50\Omega$$

First transform 3.6 GHz to L.P. prototype form:

$$\omega \leftarrow \frac{1}{\Delta} \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) = \frac{1}{0.12} \left( \frac{3.6}{4} - \frac{4}{3.6} \right) = -1.76$$

Then,


$$\left| \frac{\omega}{\omega_c} \right| - 1 = 0.76$$

So from Figure 8.26 we see that  $N=3$  is required to achieve  $\alpha > 12 \text{ dB}$  at 3.6 GHz. (or, analytically,  $P_{LR} = 1 + (\omega/\omega_c)^{2N} = 14.9 \text{ dB}$  for  $N=3$ )


The prototype values are given in Table 8.3. Then  $Z_0 J_n$  can be found from (8.121). Then,  $Z_0 B_n = \frac{J_n Z_0}{1 - (J_n Z_0)^2}$ , and  $\theta_n = \pi - \frac{1}{2} [\tan^{-1}(2Z_0 B_n) + \tan^{-1}(2Z_0 B_{n+1})]$ . Also,  $C_n = B_n / \omega_0$ .

$n$	$g_n$	$Z_0 J_n$	$Z_0 B_n$	$C_n(\text{PF})$	$\theta_n @ 4 \text{ GHz}$
1	1.000	0.434	0.535	0.43	$149^\circ$
2	2.000	0.133	0.135	0.11	$165^\circ$
3	1.000	0.133	0.135	0.11	$149^\circ$
4	1.000	0.434	0.535	0.43	—

The filter circuit is shown below:

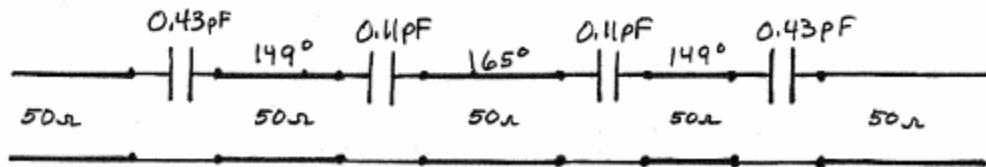

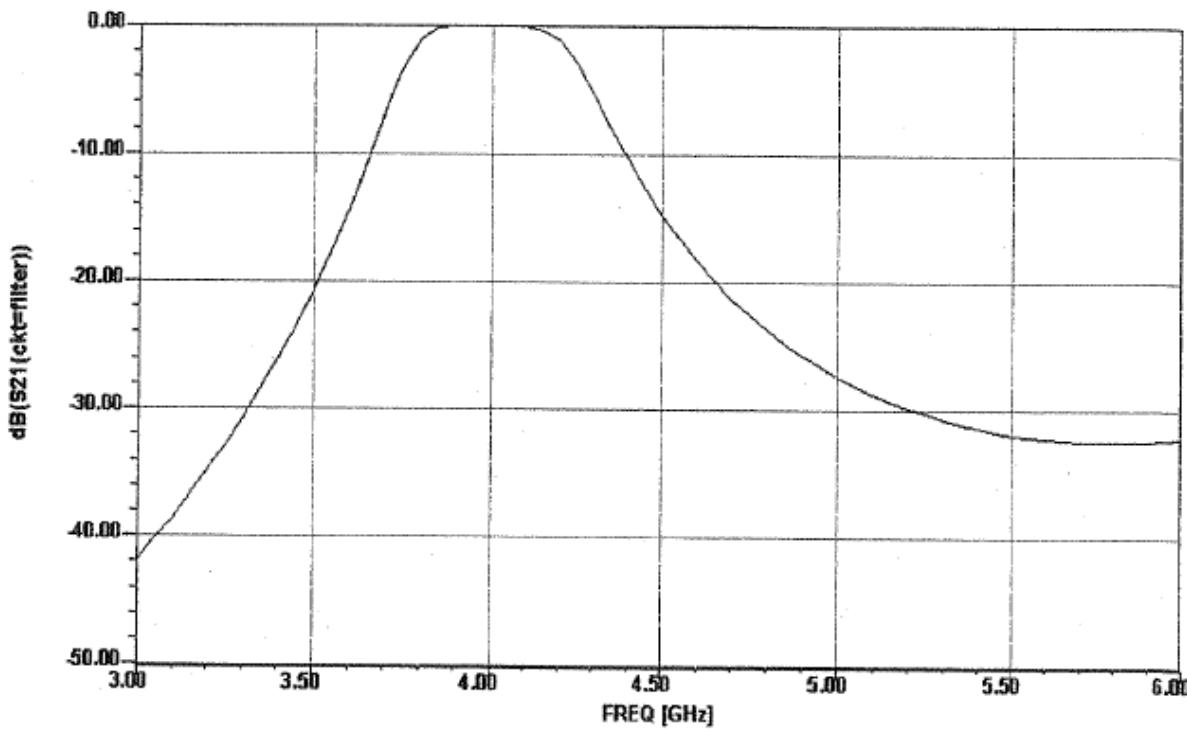The calculated filter response is shown on the following page.



**8.24**  $f_0 = 836.5 \text{ MHz}$ ,  $A = 0.03$ , BANDPASS, 1.0dB EQUAL RIPPLE,  $Z_0 = 50\Omega$

Use 0.5dB ripple design to allow for approximation errors. Use (8.136)-(8.137) to find inverter constants and coupling capacitor values:


$n$	$g_n$	$Z_0 J_{n-1,n}$	$C_{n-1,n} (\text{pF})$
1	1.6703	0.1188	0.455
2	1.1926	0.0167	0.063
3	2.3661	0.0140	0.053
4	0.8419	0.0167	0.063
5	1.9841	0.1188	0.455

Then use (8.138) and (8.141) to find the resonator lengths:


$$C'_n = C_n + \Delta C_n$$

$n$	$\Delta C_n (\text{pF})$	$l_n (\lambda)$	$l^\circ$
1	-0.518	0.228	82.1
2	-0.116	0.245	88.2
3	-0.116	0.245	88.2
4	-0.518	0.228	82.1

Final filter circuit:

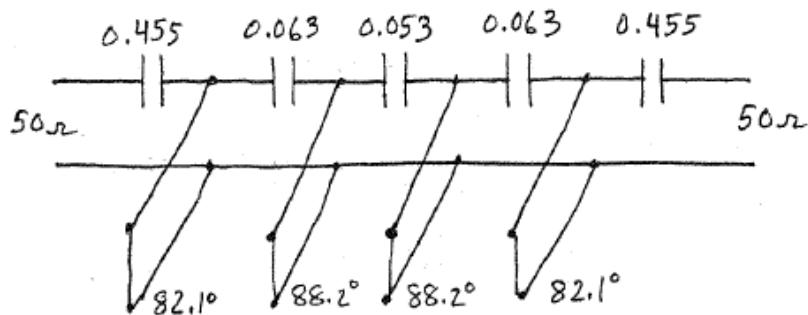

The resulting response is shown below.

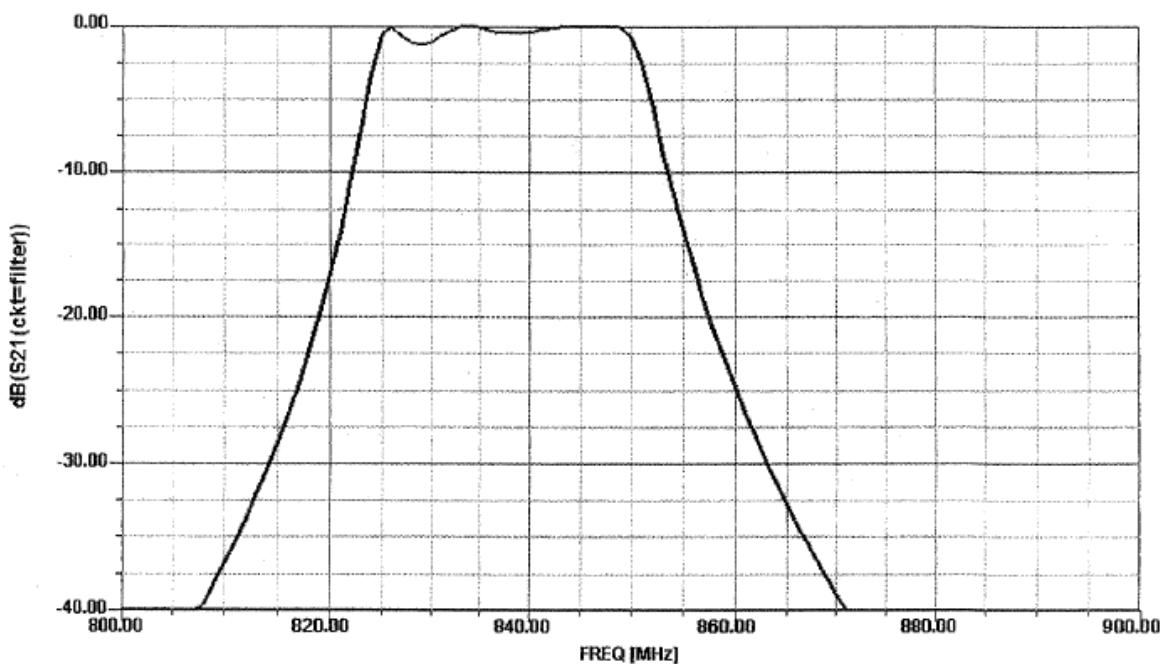


**8.25** From Matthai, Young & Jones, P.482, we have the general results that

$$J_1 = \sqrt{\frac{G_A b_1 \Delta}{g_0 g_1 \omega_1}}, \quad J_n = \frac{\Delta}{\omega_1} \sqrt{\frac{b_n b_{n+1}}{g_n g_{n+1}}}, \quad J_N = \sqrt{\frac{G_B b_N \Delta}{\omega_1 g_N g_{N+1}}}$$

with  $G_A = G_B = 1/Z_0$ ,  $\omega_1 = 1$ ,  $g_0 = 1$ , and where

$b_j = \frac{\omega_0}{2} \left. \frac{dB_j}{d\omega} \right|_{\omega=\omega_0} = \frac{\pi}{4Z_0}$  is the admittance slope parameter for the S.C. stub resonator:

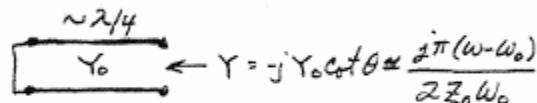


Then,

$$Z_0 J_1 = \sqrt{\frac{\pi \Delta}{4 g_1}} \quad \checkmark$$

$$Z_0 J_n = \frac{\pi \Delta}{4 \sqrt{g_n g_{n+1}}} \quad \checkmark$$

$$Z_0 J_N = \sqrt{\frac{\pi \Delta}{4 g_N g_{N+1}}} \quad \checkmark$$


The end inverters are modeled as

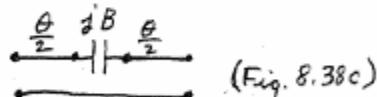

for which  $C_{i,i+1} = \frac{B}{\omega} = \frac{J_{i,i+1}}{\omega_0 \sqrt{1 - (Z_0 J_{i,i+1})^2}}$  for  $C_{01}, J_{01}$  and  $C_{N,N+1}, J_{N,N+1}$ .

The middle inverters are modeled as
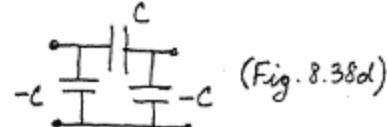
$$\text{for which } C_{n,n+1} = \frac{J_{n,n+1}}{\omega} \quad \checkmark$$



## Chapter 9

**9.1**

$$\hat{H} = (0.5 \hat{x} + j 0.5 \hat{y}), 4\pi M_s = 900 G$$

a)  $H_0 = M_s = 0$ . So  $\omega_0 = \omega_m = 0 \Rightarrow \mu = \mu_0, \kappa = 0$

$$\hat{B} = [\mu] \hat{H} = \begin{bmatrix} \mu_0 & 0 & 0 \\ 0 & \mu_0 & 0 \\ 0 & 0 & \mu_0 \end{bmatrix} \begin{bmatrix} 0.5 \\ 0.5j \\ 0 \end{bmatrix} = \begin{bmatrix} 0.5 \\ 0.5j \\ 0 \end{bmatrix} \mu_0$$

(isotropic, non-magnetic)

b)  $H_0 = 8000 e$ .  $f_0 = 2.8 \frac{M_{H2}}{Oe} (8000 e) = 2.24 GHz$

$$f_m = 2.8 \frac{M_{H2}}{Oe} (900 G) = 2.52 GHz$$

$$\mu = \mu_0 \left( 1 + \frac{f_0 f_m}{f_0^2 - f^2} \right) = 6.55 \mu_0$$

$$\kappa = \mu_0 \frac{f f_m}{f_0^2 - f^2} = 4.95 \mu_0$$

$$\hat{B} = [\mu] \hat{H} = \mu_0 \begin{bmatrix} 6.55 & j4.95 & 0 \\ -j4.95 & 6.55 & 0 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} 0.5 \\ 0.5j \\ 0 \end{bmatrix}$$

$$= (3.275 - 2.475) \mu_0 \hat{x} + (-j2.475 + j3.275) \mu_0 \hat{y}$$

$$= 0.8 \mu_0 \hat{x} + j0.8 \mu_0 \hat{y}$$

check: since LHCP,  $M_e = \mu - \kappa = 1.6$ ,  $1.6 \times 0.5 = 0.8 \checkmark$

**9.2**

$$B_x = \mu H_x + j \times H_y$$

$$B_y = -j \times H_x + \mu H_y$$

$$B_z = \mu_0 H_z$$

Then,

$$\begin{aligned} B^+ &= \frac{1}{2}(B_x + j B_y) = \frac{1}{2}[\mu H_x + j \times H_y + \kappa H_x + j \mu H_y] \\ &= \frac{1}{2}(\mu + \kappa)(H_x + j H_y) = (\mu + \kappa) H^+ \end{aligned}$$

$$\begin{aligned} B^- &= \frac{1}{2}(B_x - j B_y) = \frac{1}{2}[\mu H_x + j \times H_y - \kappa H_x - j \mu H_y] \\ &= \frac{1}{2}(\mu - \kappa)(H_x - j H_y) = (\mu - \kappa) H^- \end{aligned}$$

Thus,

$$\begin{bmatrix} B^+ \\ B^- \\ B_z \end{bmatrix} = \begin{bmatrix} (\mu + \kappa) & 0 & 0 \\ 0 & (\mu - \kappa) & 0 \\ 0 & 0 & \mu_0 \end{bmatrix} \begin{bmatrix} H^+ \\ H^- \\ H_z \end{bmatrix} \checkmark$$

**9.3**

$$4\pi M_s = 1780 G$$

internal field =  $\bar{H} = \bar{H}_e - N \bar{M}$

From Table 9.1 the demagnetization factors for a sphere are  $N_x = N_y = N_z = \frac{1}{3}$ , so

$$H_{ez} = H_z = N_z M_z = 700 + \frac{1}{3}(1780) = \underline{1293 Oe}$$

**9.4**

$$4\pi M_s = 800 \text{ G}$$

From Table 9.1 the demagnetization factors for a thin rod are  $N_x = N_y = \frac{1}{2}$ ,  $N_z = 0$ . Eq. (9.46) gives the gyromagnetic resonance frequency as

$$\begin{aligned}\omega_r &= \mu_0 \gamma \sqrt{(H_a + \frac{1}{2}M_s)(H_a + \frac{1}{2}M_s)} \\ &= \mu_0 \gamma (H_a + \frac{1}{2}M_s)\end{aligned}$$

$$\begin{aligned}H_a &= \frac{\omega_r}{\mu_0 \gamma} - \frac{1}{2}M_s = f_r \left( \frac{10 \text{ e}}{2.8 \text{ MHz}} \right) - \frac{M_s}{2} \\ &= 2520 \left( \frac{10 \text{ e}}{2.8} \right) - \frac{800}{2} = \underline{500 \text{ Oe}}\end{aligned}$$

9.5

$$4\pi M_s = 1200 \text{ G}, \quad \epsilon_r = 10, \quad H_0 = 500 \text{ Oe}, \quad f = 8 \text{ GHz}$$

(FARADAY ROTATION)

$$f_0 = (2.8 \frac{\text{MHz}}{\text{Oe}})(500 \text{ Oe}) = 1.4 \text{ GHz}$$

$$f_m = (2.8 \frac{\text{MHz}}{\text{Oe}})(1200 \text{ G}) = 3.36 \text{ GHz}$$

$$k_0 = 167.6 \text{ m}^{-1}$$

Then from (9.25),

$$\mu = \mu_0 \left(1 + \frac{f_0 f_m}{f_0^2 - f^2}\right) = 0.924 \mu_0 \quad \checkmark$$

$$\kappa = \mu_0 \frac{f f_m}{f_0^2 - f^2} = -0.433 \mu_0 \quad \checkmark$$

From (9.52) the propagation constants of the CP waves are,

$$\text{RHCP: } \beta_+ = \omega \sqrt{\epsilon(\mu + \kappa)} = k_0 \sqrt{\epsilon_r} \sqrt{0.924 - 0.433} = 371.4 \text{ m}^{-1} \quad \checkmark$$

$$\text{LHCP: } \beta_- = \omega \sqrt{\epsilon(\mu - \kappa)} = k_0 \sqrt{\epsilon_r} \sqrt{0.924 + 0.433} = 617.4 \text{ m}^{-1} \quad \checkmark$$

$$\text{Then, } \Delta \beta = \beta_+ - \beta_- = -246.0 \text{ m}^{-1}$$

From (9.57) the polarization rotation of an LP wave is,

$$\phi = -(\beta_+ - \beta_-) z / 2$$

so,

$$z = \frac{2\phi}{\beta_- - \beta_+} = \frac{2(\pi/2)}{246 \text{ rad/m}} = 12.8 \text{ mm} \quad \checkmark$$

**9.6**

$$4\pi M_s = 1780 \text{ G}, \quad \epsilon_r = 13, \quad H_0 = 2000 \text{ Oe}, \quad f = 5 \text{ GHz}$$

$$f_0 = (2.8 \text{ MHz/Oe})(2000 \text{ Oe}) = 5.60 \text{ GHz}$$

$$f_m = (2.8 \text{ MHz/Oe})(1780 \text{ Oe}) = 4.98 \text{ GHz}$$

$$k_0 = 2\pi f/c = 104.7 \text{ m}^{-1}$$

From (9.25),

$$\mu = \mu_0 \left( 1 + \frac{f_0 f_m}{f_0^2 - f^2} \right) = 5.385 \mu_0$$

$$k = \mu_0 \frac{f f_m}{f_0^2 - f^2} = 3.915 \mu_0$$

The  $\hat{x}$ -polarized wave has  $\vec{H} = \hat{y} H_0 \hat{y}$ , and is the extraordinary wave. From (9.64)-(9.65),

$$\mu_e = \frac{\mu^2 - k^2}{\mu} = 2.539 \mu_0$$

$$\beta_e = \omega / \sqrt{\epsilon_r \mu_e} = k_0 \sqrt{\epsilon_r \mu_e / \mu_0} = 601.5 \text{ m}^{-1}$$


The  $\hat{y}$ -polarized wave has  $\vec{H} = \hat{x} H_0 \hat{x}$ , and is the ordinary wave. Thus,

$$\beta_o = \sqrt{\epsilon_r} k_0 = 377.5 \text{ m}^{-1}$$

So the distance required for a differential phase shift of  $180^\circ$  is,

$$L = \frac{\pi}{\beta_e - \beta_o} = \underline{\underline{1.403 \text{ cm}}}$$

9.7

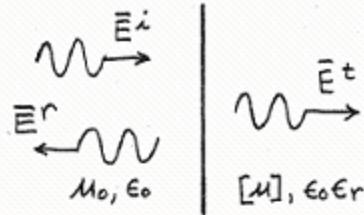

The incident, reflected, and transmitted fields for a RHCW wave can be written as,

$$\vec{E}^i = E_0 (\hat{x} - j\hat{y}) e^{-j\beta_0 z}$$

$$\vec{H}^i = \frac{E_0}{\eta_0} (\hat{y} + j\hat{x}) e^{-j\beta_0 z}$$

$$\vec{E}^r = \Gamma^+ E_0 (\hat{x} - j\hat{y}) e^{j\beta_0 z}$$

$$\vec{H}^r = -\frac{E_0}{\eta_0} \Gamma^+ (\hat{y} + j\hat{x}) e^{j\beta_0 z}$$

$$\vec{E}^t = T^+ E_0 (\hat{x} - j\hat{y}) e^{-j\beta_0 z}$$

$$\vec{H}^t = \frac{E_0}{\eta_0} T^+ (\hat{y} + j\hat{x}) e^{-j\beta_0 z}$$

where,

$$\beta_0 = \omega \sqrt{\mu_0 \epsilon_0}, \quad \beta_+ = \omega \sqrt{\epsilon(\mu + \kappa)}, \quad \eta_+ = \frac{1}{Y_+} = \sqrt{\frac{\mu + \kappa}{\epsilon}}$$

matching fields at  $z=0$  gives (for both  $\hat{x}$  and  $\hat{y}$  components)

$$1 + \Gamma^+ = T^+$$

$$\eta_+ (1 - \Gamma^+) = \eta_0 T^+$$

Solving gives,

$$\Gamma^+ = \frac{\eta_+ - \eta_0}{\eta_+ + \eta_0}, \quad T^+ = \frac{2\eta_+}{\eta_+ + \eta_0} \quad \checkmark$$

Similarly, for a LHCW wave we obtain,

$$\Gamma^- = \frac{\eta_- - \eta_0}{\eta_- + \eta_0}, \quad T^- = \frac{2\eta_-}{\eta_- + \eta_0} \quad \checkmark$$

where,

$$\eta_- = \frac{1}{Y_-} = \sqrt{\frac{\mu - \kappa}{\epsilon}}.$$

**9.8**

$$4\pi Ms = 1200 G, \bar{H}_o = \hat{x} H_o, f = 4 \text{ GHz}, \bar{E} = \hat{x} E_o$$

$$f_m = (2.8 \text{ MHz/Oe})(1200 \text{ G}) = 3.36 \text{ GHz}$$

This is a case of birefringence. From (9.64)-(9.65),

$$\beta_e = \omega \sqrt{\mu_e \epsilon}$$

$$\mu_e = \frac{\mu^2 - k^2}{\mu}$$

The wave will be cutoff when  $\mu_e \leq 0$ :

$$\frac{\mu^2 - k^2}{\mu} < 0$$

$$\frac{\left(1 + \frac{f_0 f_m}{f_0^2 - f^2}\right)^2 - \left(\frac{f f_m}{f_0^2 - f^2}\right)^2}{1 + \frac{f_0 f_m}{f_0^2 - f^2}} < 0$$

$$\frac{(f_0^2 - f^2)^2 + 2f_0 f_m (f_0^2 - f^2) + f_m^2 (f_0^2 - f^2)}{(f_0^2 - f^2)[(f_0^2 - f^2) + f_0 f_m]} < 0$$

$$\frac{(f_0^2 - f^2) + 2f_0 f_m + f_m^2}{f_0^2 - f^2 + f_0 f_m} < 0$$

If  $f_0^2 - f^2 + f_0 f_m > 0$ , then  $(f_0 + f_m)^2 - f^2 < 0$

$$f_0 + f_m < f$$

$$f_0 < f - f_m = 4.0 - 3.36 = 0.64 \text{ GHz} \Rightarrow H_o = 229 \text{ Oe} \quad \checkmark$$


If  $f_0^2 - f^2 + f_0 f_m < 0$ , then  $(f_0 + f_m)^2 - f^2 > 0$

$$f_0 = \frac{-f_m \pm \sqrt{f_m^2 + 4f^2}}{2} = -1.68 \pm 4.34 = 2.66 \text{ GHz}$$

$$H_o = 950 \text{ Oe} \quad \checkmark$$


So the cutoff range is between 229 Oe and 950 Oe.

9.9

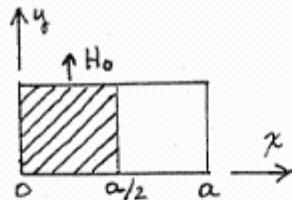


$$\begin{aligned} a &= 1.0 \text{ cm} & (c = 0, t = a/2) \\ f &= 10 \text{ GHz} \\ 4\pi M_s &= 1700 \text{ G} \\ \epsilon_r &= 13 \end{aligned}$$

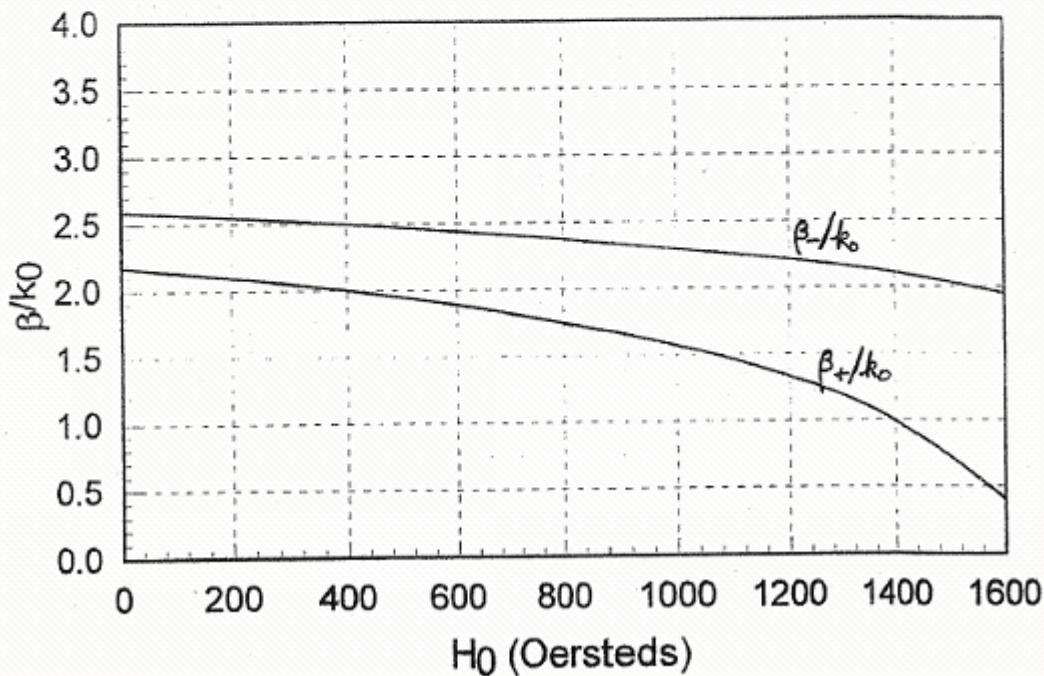The propagation constants are found by solving (9.79) numerically. This was done using the FORTRAN program FLW1S.FOR, with the results shown below:



**9.10**

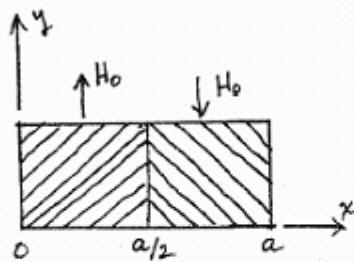


$$a = 1.0 \text{ cm} \quad (c=0, t=a/2)$$

$$f = 10 \text{ GHz}$$


$$4\pi M_s = 1700 \text{ G}$$

$$\epsilon_r = 13$$

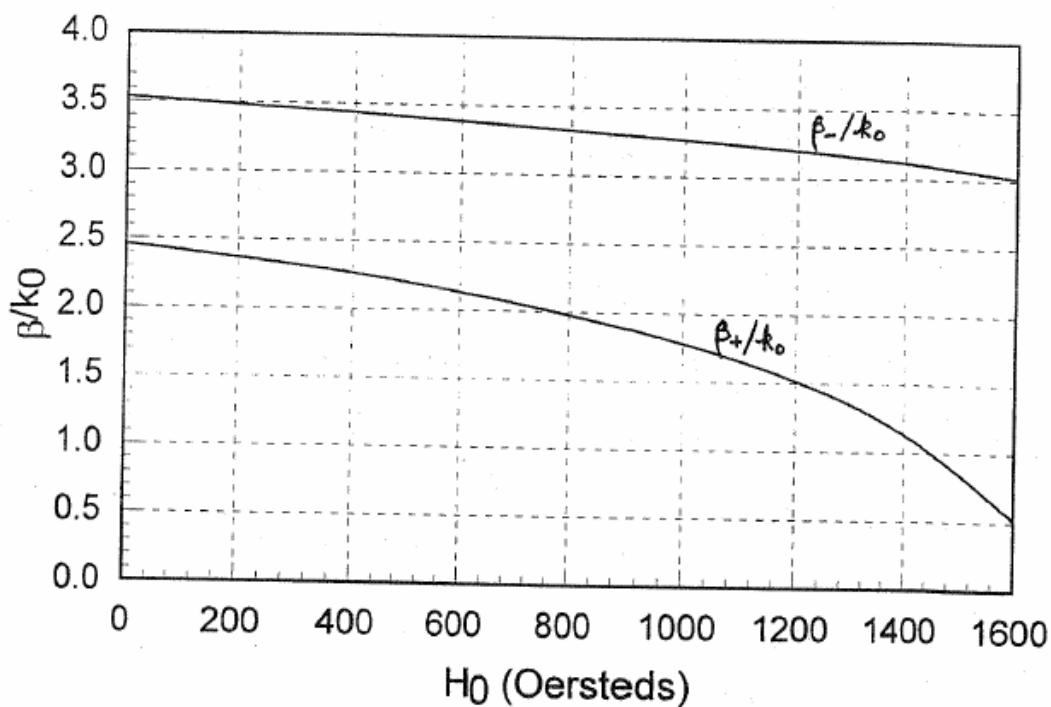The propagation constants are found by solving (9.84) numerically. This was done using the FORTRAN program FLW2S.FOR, with the results shown below.



9.11

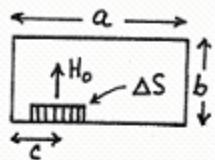

$$f = 10 \text{ GHz}, \quad a = 2.286 \text{ cm}, \quad b = 1.016 \text{ cm}$$

$$4\pi M_s = 1700 \text{ G}, \quad C = a/4, \quad \Delta S = 2 \text{ mm}^2$$


$$k_0 = 209.4 \text{ m}^{-1}, \quad S = 232.3 \text{ mm}^2, \quad f_m = 4.76 \text{ GHz}$$

From (9.80) the differential phase shift is,


$$(\beta_+ - \beta_-)/k_0 = -2 \frac{k_0}{k_0} \frac{\chi}{M} \frac{\Delta S}{S} \sin 2k_0 c = -0.0113 \frac{\chi}{M}$$

$H_0$ (Oe)	$f_0$ (GHz)	$\chi/M_0$	$M/M_0$	$(\beta_+ - \beta_-)/k_0$
0	0	-0.476	1.000	0.0054 ✓
200	0.56	-0.477	0.973	0.0055
400	1.12	-0.482	0.946	0.0058
600	1.68	-0.489	0.918	0.0060
800	2.24	-0.501	0.891	0.0064
1000	2.80	-0.516	0.855	0.0068
1200	3.36	-0.537	0.820	0.0074 ✓

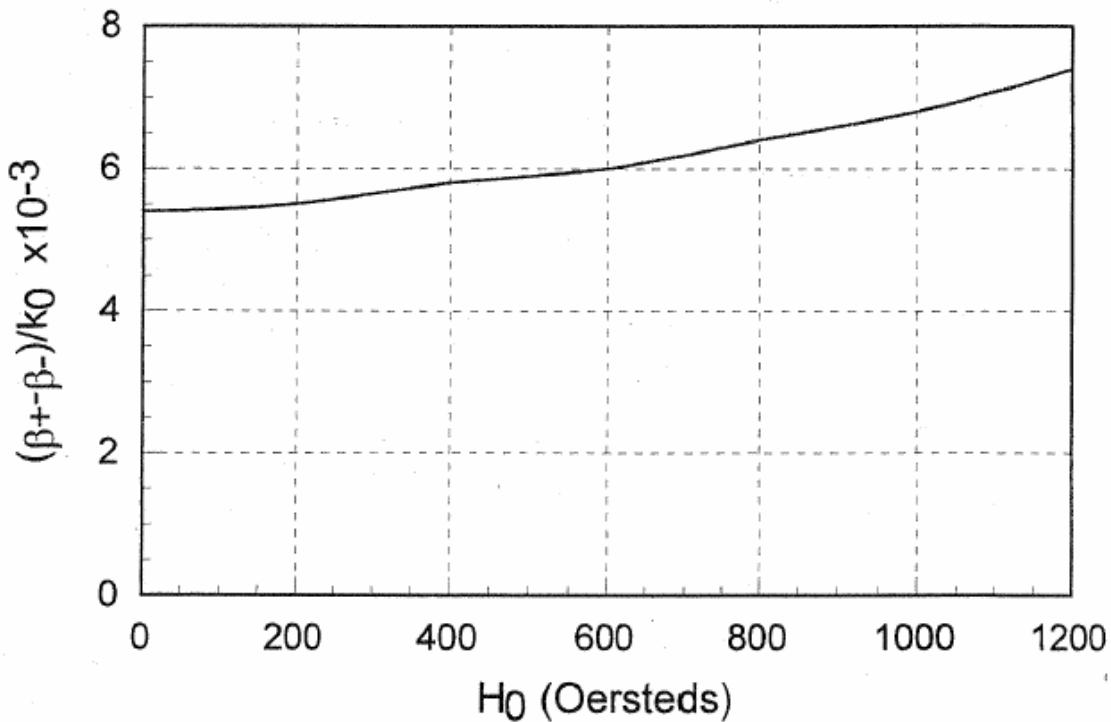This data is plotted on the following page



9.12

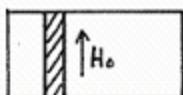


$$f = 8 \text{ GHz}, 4\pi M_s = 1500 \text{ G}, f_m = 4.2 \text{ GHz}$$

Gyromagnetic resonance for this geometry is given approximately by (9.87): ( $N_x = 1, N_y = N_z = 0$ )

$$f = \sqrt{f_0(f_0 + f_m)}$$

Solve for  $f_0$ :  $f_0^2 + 4.2f_0 - 64 = 0 \Rightarrow f_0 = -2.1 \pm 8.27 = 6.17 \text{ GHz}$

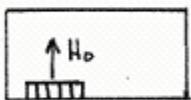Thus,  $H_0 = \frac{6170 \text{ MHz}}{2.8 \text{ MHz/Oe}} = 2204 \text{ Oe. } \checkmark$



Gyromagnetic resonance for this geometry is given by the condition,


$$f_0 = f = 8 \text{ GHz} \quad (N_x = N_z = 0, N_y = 1)$$

Thus,

$$H_0 = \frac{8000 \text{ MHz}}{2.8 \text{ MHz/Oe}} = 2857. \text{ Oe } \checkmark$$

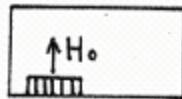9.13

$$f = 10 \text{ GHz}, 4\pi M_s = 1700 \text{ G}, \Delta H = 2000 \text{ e}$$



$$\frac{\Delta S}{S} = 0.01$$

Gyromagnetic resonance is given by the condition,

$$f_0 = f = 10 \text{ GHz} \quad (\text{since } N_x = N_z = 0, N_y = 1)$$

$$H_0 = \frac{10,000 \text{ MHz}}{2.8 \text{ MHz/Oe}} = 3571.0 \text{ Oe}$$

The position of the ferrite slab is given by (9.86), since the RF magnetic fields,  $H_x$  and  $H_z$ , have demagnetization factors of zero. Thus,

$$\tan k_c x = \pm \frac{k_c}{\beta_0}$$

$$k_0 = 209.4 \text{ m}^{-1}$$

$$k_c = \pi/a = 137.4 \text{ m}^{-1}$$

$$S = x = \frac{1}{k_c} \tan^{-1} \frac{k_c}{\beta_0} = 0.521 \text{ cm}$$

$$\beta_0 = \sqrt{k_0^2 - k_c^2} = 158. \text{ m}^{-1}$$

The perturbation result of (9.81) must be used to find the attenuation constants, since this geometry cannot be analyzed exactly:

$$\alpha \pm = \frac{\Delta S}{S \beta_0} \left( f_0^2 \chi''_{xx} \sin^2 k_c x + k_c^2 \chi''_{zz} \cos^2 k_c x \mp \chi''_{xy} k_c f_0 \sin 2k_c x \right)$$

where the susceptibilities are given by (9.39):

$$f_0 = f = 10 \text{ GHz}$$

$$f_m = 1700(2.8) = 4.76 \text{ GHz}$$

$$\alpha = \frac{\Delta H}{2\omega_0 \mu_0 Y} = \frac{(200)(2.8 \text{ MHz})}{2(19,000 \text{ MHz})} = 0.028$$

$$\chi''_{xx} = \frac{\alpha f f_m [f_0^2 + f^2(1+\alpha^2)]}{[f_0^2 - f^2(1+\alpha^2)]^2 + 4f_0^2 f^2 \alpha^2} = 8.50$$

$$\chi''_{zz} = \chi''_{xx} = 8.50$$

$$\chi''_{xy} = \frac{2f_0 f_m f^2 \alpha}{[f_0^2 - f^2(1+\alpha^2)]^2 + 4f_0^2 f^2 \alpha^2} = 8.49$$

Then,  $\alpha_{\pm} = 6.3 \times 10^{-5} (9.139 \times 10^4 + 9.136 \times 10^4 \mp 1.825 \times 10^5)$

$$\alpha_+ = 0.0158 \text{ neper/m} = 0.137 \text{ dB/m}$$

$$\alpha_- = 23.0 \text{ neper/m} = 200 \text{ dB/m}$$

For 30 dB reverse attenuation, the required length is,

$$L = \frac{30 \text{ dB}}{200 \text{ dB/m}} = 0.15 \text{ m} = 15 \text{ cm}$$

Then the forward insertion loss is,

$$IL = (0.137)(0.15) = 0.02 \text{ dB}$$

Note: the calculation of  $\alpha_{\pm}$  is numerically sensitive.

**9.14** The magnetic fields for the TE<sub>10</sub> waveguide mode can be written as,

$$H_x = \frac{j\beta A}{k_c} \sin k_c x e^{-j\beta z}$$


$$H_z = A \cos k_c x e^{-j\beta z}$$

with  $k_c = \pi/a$ ,  $\beta = \sqrt{k_0^2 - k_c^2}$ . Circular polarization occurs when,

$$\frac{H_x}{H_z} = \pm j = \frac{j\beta}{k_c} \tan k_c x, \text{ or } \tan k_c x = \pm \frac{k_c}{\beta} \quad (9.86)$$

$k_0/k_c$	$\beta/k_c$	$x_1/a$	$x_2/a$
1.0	0	0.500	0.500
1.2	0.663	0.314	0.686
1.4	0.980	0.253	0.747
1.6	1.249	0.215	0.785
1.8	1.497	0.187	0.813
2.0	1.732	0.167	0.833

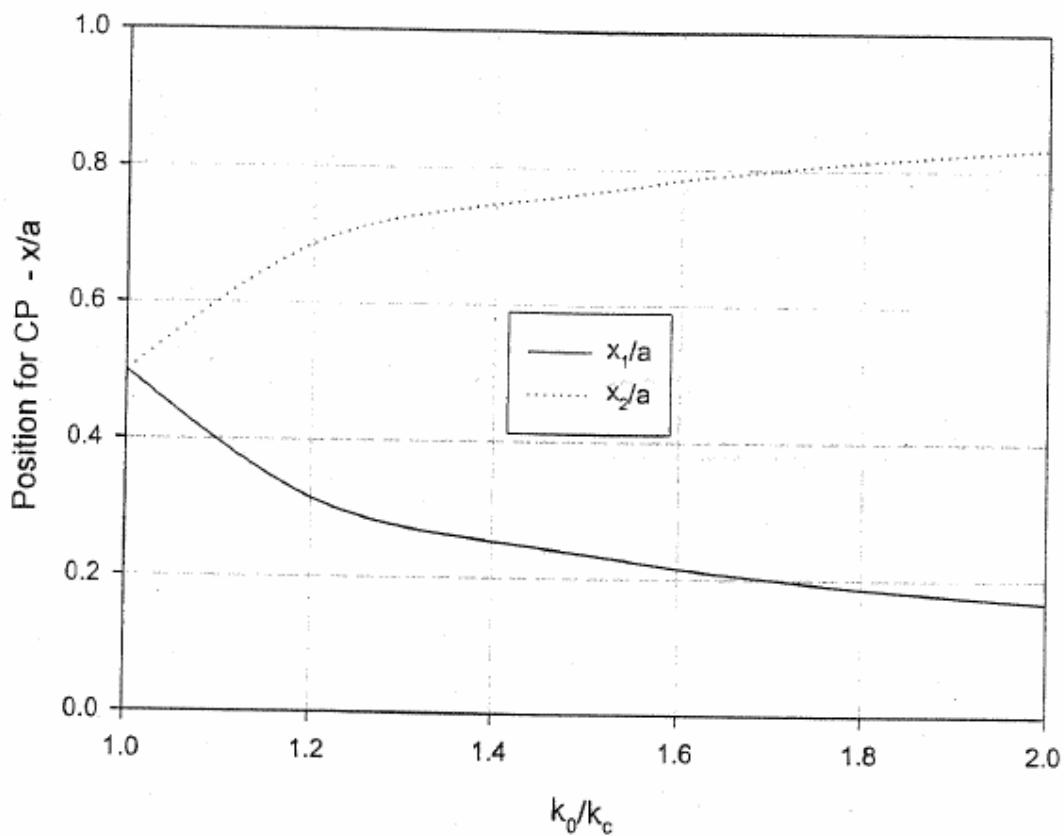These results are plotted on the following page.



**9.15**

$$f = 10 \text{ GHz}, \epsilon_r = 12, 4\pi M_r = 1500. \Delta\phi = 90^\circ$$

$$f_m = (2.8 \text{ MHz/0e})(1500 \text{ 0e}) = 4.2 \text{ GHz}$$

$$k_0 = 2\pi f/c = 209.44 \text{ m}^{-1}$$

In the remanent state,  $H_0 = f_0 = 0$ . Then,

$$\mu = M_0, K = -\frac{f_m}{f} M_0 = -0.420 M_0, M_e = \frac{\mu^2 - K^2}{\mu} = 0.824 M_0$$


State #1:  $\bar{M} = M_r \hat{x}$  and  $\bar{H} = \hat{y} H_y$ , so this is an extraordinary wave:  $\beta_e = k_0 \sqrt{\epsilon_r M_e / M_0} = 658.6 \text{ m}^{-1}$

State #2:  $\bar{M} = M_r \hat{y}$  and  $\bar{H} = \hat{y} H_y$ , so this is an ordinary wave:  $\beta_o = \sqrt{\epsilon_r k_0} = 725.5 \text{ m}^{-1}$

Differential phase shift is

$$\Delta\phi = (\beta_o - \beta_e) L = 90^\circ$$

$$L = \frac{90^\circ (\pi/180^\circ)}{\beta_o - \beta_e} = \underline{23.5 \text{ mm}}$$

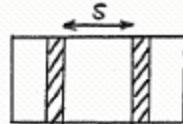**9.16**

$$S = 2 \text{ mm}, f = 10 \text{ GHz}, 4\pi Mr = 1000 \text{ G}$$

From Figure 9.17, maximum differential phase shift for  $S = 2 \text{ mm}$  occurs for  $t/a \approx 0.112$ , so  $t = 0.112a = 2.6 \text{ mm}$  ✓.


Then  $(\beta_+ - \beta_-)/k_0 = 0.24$ , for  $4\pi Mr = 1786 \text{ G}$ . If we assume  $(\beta_+ - \beta_-)$  is proportional to  $X$  (and so  $Mr$ ), then for  $4\pi Mr = 1000 \text{ G}$  we have  $\frac{(\beta_+ - \beta_-)}{k_0} = 0.24 \left( \frac{1000}{1786} \right) = 0.134$ ,

$$\text{so, } (\beta_+ - \beta_-) = 0.134 k_0 = 16.1^\circ/\text{cm} \quad \checkmark$$

Then the slab lengths for  $180^\circ$  and  $90^\circ$  sections are,

$$L = \frac{180^\circ}{16.1^\circ/\text{cm}} = 11.2 \text{ cm} \quad \checkmark$$

$$L = \frac{90^\circ}{16.1^\circ/\text{cm}} = 5.6 \text{ cm} \quad \checkmark$$

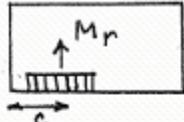**9.17**

$$a = 2.286 \text{ cm}, b = 1.016 \text{ cm}, f = 9 \text{ GHz}$$

$$4\pi Mr = 1200 \text{ G}, c = a/4, \Delta S = 2 \text{ mm}^2$$

From (9.80) the (approximate) differential phase shift is,

$$\beta_+ - \beta_- = \frac{-2\pi}{a} \frac{X}{\mu} \frac{\Delta S}{S} \sin \frac{2\pi c}{a}$$

Now for  $H_0 = 0$ ,

$$\frac{X}{\mu} = -\frac{fm}{f} = \frac{-2.8(1200)}{9000} = -0.373$$

and,

$$S = ab = 232.3 \text{ mm}^2, \text{ so}$$

$$\beta_+ - \beta_- = 0.883 \text{ rad/m} = 0.506^\circ/\text{cm} \quad \checkmark$$

So the required length is,

$$L = \frac{22.5^\circ}{0.506^\circ/\text{cm}} = 44.5 \text{ cm} \quad \checkmark$$

(a bit long!)

**9.18**

$$f = 9 \text{ GHz}, 4\pi M_s = 1700 \text{ G}, \Delta S = 6 \text{ mm}^2$$

$$a = 2.286 \text{ cm}, b = 1.016 \text{ cm}, H_a = 4000 \text{ oe}$$

From (9.41) the internal bias field is ( $N_3 = 1$ )

$$H_0 = H_a - NM_s = 4000 - 1700 = \underline{2300 \text{ oe}}$$

From (9.80) the (approximate) differential phase shift is,

$$\beta_+ - \beta_- = \frac{-2\pi}{a} \frac{x}{S} \sin \frac{2\pi c}{a}$$

Maximum phase shift will occur for  $c = a/4 = \underline{0.572 \text{ cm}}$ .

$$\text{Then, } f_m = 2.8(1700) = 4.76 \text{ GHz}, f_0 = 2.8(2300) = 6.44 \text{ GHz}.$$

So,

$$\mu = \mu_0 \left( 1 + \frac{f_0 f_m}{f_0^2 - f^2} \right) = 0.224 \mu_0$$

$$\chi = \mu_0 \frac{f f_m}{f_0^2 - f^2} = -1.08 \mu_0$$

Thus,


$$\beta_+ - \beta_- = 0.342 \text{ rad/cm} = 19.6^\circ/\text{cm}$$

So the required length for a  $180^\circ$  phase shift is,


$$L = \frac{180^\circ}{19.6^\circ/\text{cm}} = \underline{9.2 \text{ cm}}$$

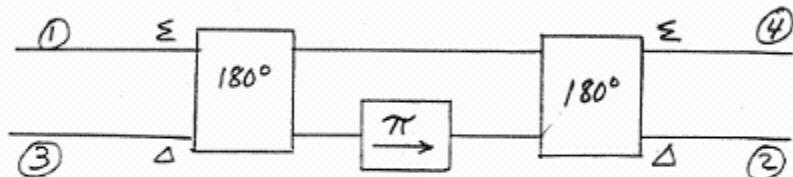**9.19**

a four-port circulator can be made using a gyrator and two  $180^\circ$  hybrid couplers :



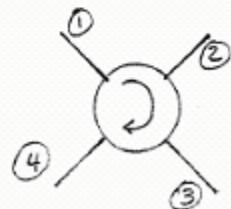A three port circulator can be obtained by shorting any one of the ports.



**9.20**

$$RL = 10 \text{ dB}, 20 \text{ dB}.$$

From (9.92) the scattering matrix of a mismatched circulator is,

$$[S] = \begin{bmatrix} \Gamma & \beta & \alpha \\ \alpha & \Gamma & \beta \\ \beta & \alpha & \Gamma \end{bmatrix}$$

Then  $|\beta| \approx |\Gamma|$

$$|\alpha| \approx 1 - |\Gamma|^2$$

For  $RL = 10 \text{ dB}$ ,  $|I| = |\beta| = 10 \text{ dB}$

For  $RL = 20 \text{ dB}$ ,  $|I| = |\beta| = 20 \text{ dB}$

## Chapter 10

10.1

$$ENR = 22 \text{ dB } (T_1) , \quad T_2 = 77 \text{ K} , \quad Y = 15.83 \text{ dB}$$

$$ENR = 10 \log \frac{T_1 - T_0}{T_0} \Rightarrow \frac{T_1 - T_0}{T_0} = 10^{\frac{22}{10}} = 158.5$$

$$T_1 = T_0 (1 + 158.5) = 4.63 \times 10^4 \text{ K}$$

$$Y = 10^{\frac{15.83}{10}} = 38.28$$

$$T_e = \frac{T_1 - YT_2}{Y-1} = 1.163 \times 10^3 \text{ K}$$

$$F = 1 + \frac{T_e}{T_0} = 5.01 = \underline{7.0 \text{ dB}} \quad \checkmark$$

**10.2**

$$T_e = \frac{T_1 - YT_2}{Y-1}$$

$$T_e + \Delta T_e = \frac{T_1 - (Y + \Delta Y)T_2}{(Y + \Delta Y) - 1}$$

$$\Delta T_e = \frac{T_1 - (Y + \Delta Y)T_2}{(Y + \Delta Y) - 1} - \frac{T_1 - YT_2}{Y-1}$$

$$= \frac{T_1 - (Y + \Delta Y)T_2}{(Y-1)\left(1 + \frac{\Delta Y}{Y-1}\right)} - \frac{T_1 - YT_2}{Y-1}$$

$$\simeq \frac{[T_1 - (Y + \Delta Y)T_2]\left[1 - \frac{\Delta Y}{Y-1}\right] - (T_1 - YT_2)}{Y-1}$$

$$\simeq \frac{-\frac{T_1}{Y-1} + \frac{YT_2}{Y-1} - T_2}{Y-1} \Delta Y = \frac{(T_2 - T_1)}{(Y-1)^2} \Delta Y$$

$$\frac{\Delta T_e}{T_e} = \frac{(T_2 - T_1)Y}{(Y-1)^2 T_e} \frac{\Delta Y}{Y} = \frac{(T_1 + T_e)(T_2 + T_e)}{T_e(T_2 - T_1)} \frac{\Delta Y}{Y}$$

minimize with respect to  $T_e$ :

$$\frac{d}{dT_e} \left[ \frac{\Delta T_e}{T_e} \right] = \frac{\left(\frac{T_1}{T_e} + 1\right)\left(\frac{T_2}{T_e} + 1\right) + T_e \left(\frac{-T_1}{T_e^2}\right)\left(\frac{T_2}{T_e} + 1\right) + T_e \left(\frac{T_1}{T_e} + 1\right)\left(\frac{-T_2}{T_e^2}\right)}{T_2 - T_1} = 0$$

Thus,

$$T_e = \sqrt{T_1 T_2} \quad \checkmark$$

**10.3**


$$T = 0 \text{ to } 1000 \text{ K}, F_0 = 1 \text{ dB}, 3 \text{ dB}.$$


From (10.16)  $F = 1 + (L-1) T/T_0$

When  $F_0 = 1 \text{ dB}$ ,  $L = 1 \text{ dB} = 1.259$

$F_0 = 3 \text{ dB}$ ,  $L = 3 \text{ dB} = 2.00$

$T (\text{K})$	$F (F_0 = 1 \text{ dB})$	$F (F_0 = 3 \text{ dB})$
0	0	0
250	0.88	2.70
500	1.60	4.35
750	2.23	5.55
1000	2.77	6.48

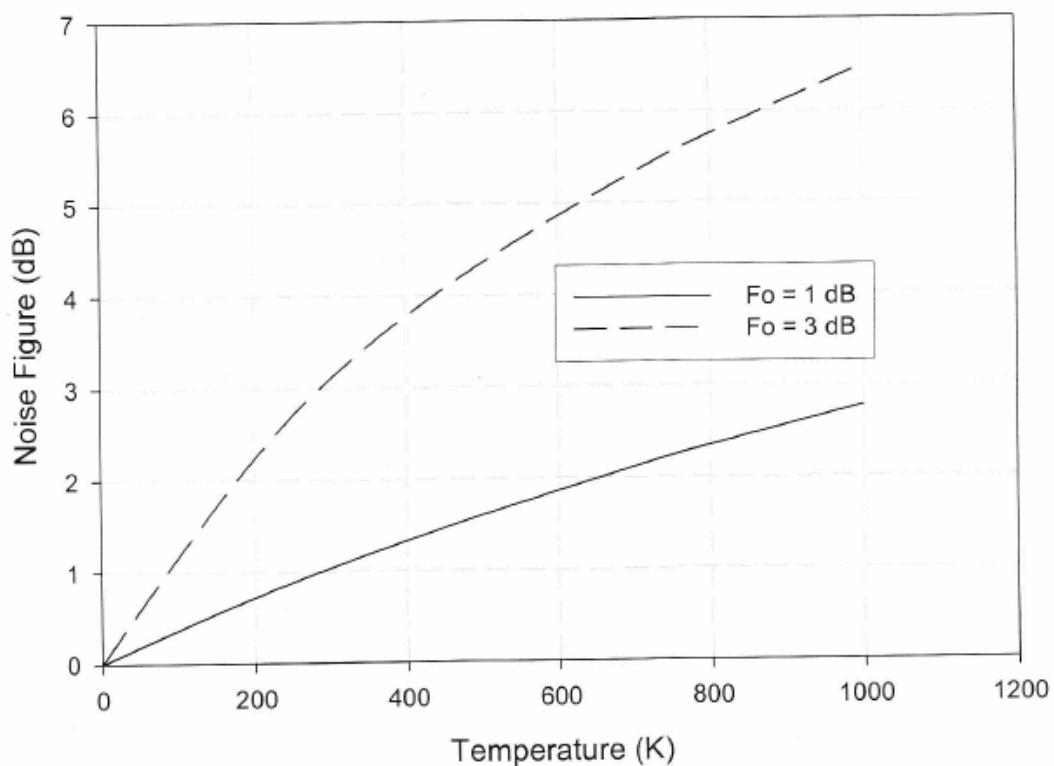

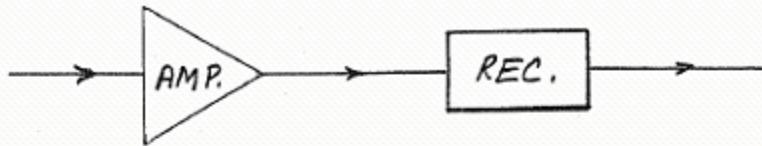**10.4**

$$G = 12 \text{ dB} = 15.8$$

$$\text{BW} = 150 \text{ MHz}$$

$$F = 4 \text{ dB} = 2.51$$

$$T_e = 900 \text{ K}$$

The noise figure of the receiver is, from (10.11),

$$F_2 = 1 + \frac{T_e}{T_0} = 1 + \frac{900}{290} = 4.10$$

Then the noise figure of the cascade is, from (10.21),

$$F_{\text{cas}} = F_1 + \frac{1}{G_1} (F_2 - 1) = 2.51 + \frac{4.10 - 1}{15.8} = 2.71 = 4.3 \text{ dB } \checkmark$$

**10.5**

$$a) T_e = \frac{P}{k_B} = \frac{(0.001) \times 10^{-9.5}}{(1.38 \times 10^{-23})(75 \times 10^6)} = 305.5 \text{ K } \checkmark$$

$$b) F_L = 1 + (L-1) \frac{T}{T_0} = 1 + (1.413 - 1) \frac{300}{290} = 1.43, F_a = 1 + \frac{T_e}{T_0} = 1.62 = 2.1 \text{ dB}$$


$$c) F_C = F_L + \frac{F_a - 1}{G_L} = 1.43 + \frac{1.62 - 1}{1.413} = 2.30 = 3.6 \text{ dB } \checkmark$$

$$T_C = (F_C - 1) T_0 = (2.30 - 1) (290) = 378 \text{ K } \checkmark$$

$$d) N_o = k(T_C + T_s) B G = (1.38 \times 10^{-23})(378 + 305.5)(75 \times 10^6) \left( \frac{15.8}{1.413} \right)$$

$$= 7.9 \times 10^{-12} \text{ W} = 7.9 \times 10^{-9} \text{ mW} = -81.0 \text{ dBm } \checkmark$$

10.6

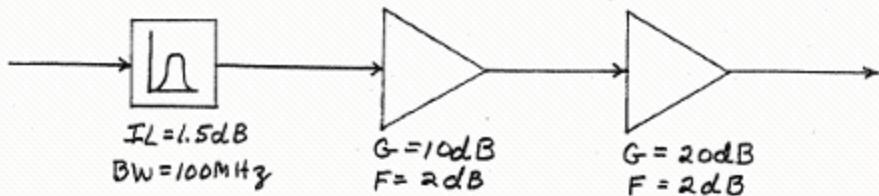

From (10.23) the noise figure of the cascade is ( $F_1 = IL = 1.5 \text{ dB}$ )


$$F_{\text{CAS}} = F_1 + \frac{F_2 - 1}{G_1} + \frac{F_3 - 1}{G_1 G_2} = 1.41 + (1.41)(1.58 - 1) + \frac{1.41}{10}(1.58 - 1)$$
$$= 2.31 = 3.64 \text{ dB}$$

If  $P_{\text{in}} = -90 \text{ dBm}$ , then  $P_{\text{out}} = -90 \text{ dBm} - 1.5 \text{ dB} + 10 \text{ dB} + 20 \text{ dB} = -61.5 \text{ dBm}$   
The noise power output is then,

$$P_n = G_{\text{cas}} k T_{\text{cas}} B = k (F_{\text{cas}} - 1) T_0 B G_{\text{cas}}$$
$$= (1.38 \times 10^{-23}) (2.31 - 1) (290) (10^8) (10^{28.5/10}) = 3.71 \times 10^{-10} \text{ W}$$
$$= -64.3 \text{ dBm}$$

Thus,  $\frac{S_o}{N_o} = -61.5 + 64.3 = 2.8 \text{ dB}$

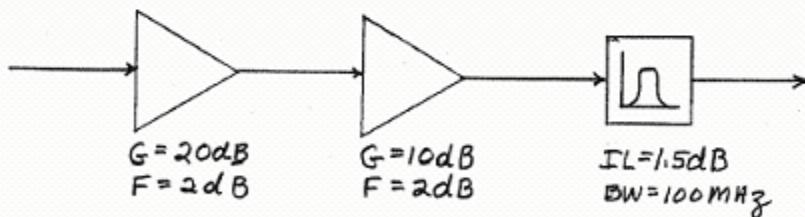The best noise figure would be achieved with the arrangement shown below:




Then,

$$F_{\text{CAS}} = 1.58 + \frac{(1.58 - 1)}{100} + \frac{(1.41 - 1)}{1000} = 1.586 = 2.0 \text{ dB}$$

(In practice, however, the initial filter may serve to prevent overload of the amplifier, and may not be allowed to be moved.)

**10.7**

a) RESISTIVE DIVIDER

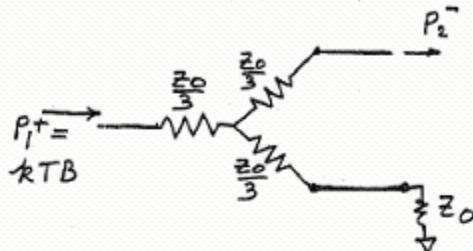

$$[S] = \frac{1}{2} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 0 \end{bmatrix}$$

When the input noise power at port 1 is  $kTB$ , and the divider is at temperature  $T$ , the system is in thermodynamic equilibrium. Thus the output noise power at port 2 must be  $kTB$ . We can also express this as due to the attenuated input noise power and noise power added by the network (ref. at input). Thus,

$$P_2^- = kTB = \frac{kTB}{4} + \frac{N_{\text{added}}}{4}$$

$$\therefore N_{\text{added}} = 3kTB$$

The equivalent noise temperature is then,


$$T_e = \frac{N_{\text{added}}}{k_B} = 3T$$

and the noise figure is,

$$F = 1 + \frac{T_e}{T_0} = 1 + \frac{3T}{T_0}$$

at room temperature,  $T = T_0$ , so  $F = 4 = 6dB$ ,  
(this result checks with that obtained using the available gain method)

b) WILKINSON DIVIDER

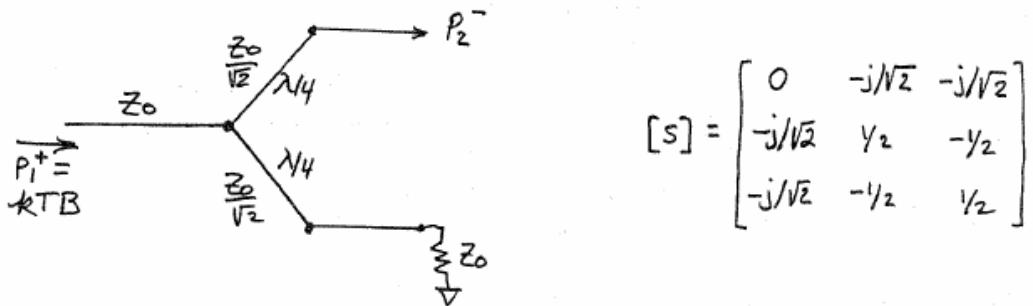

$$[S] = \begin{bmatrix} 0 & -j/\sqrt{2} & -j/\sqrt{2} \\ -j/\sqrt{2} & y_2 & -y_2 \\ -j/\sqrt{2} & -y_2 & y_2 \end{bmatrix}$$

In this case, if the input noise power is  $kTB$ , and the system is in thermodynamic equilibrium, the net output power at port 2 is  $\frac{3}{4}kTB$ , because of the mismatch of the output ports ( $\frac{1}{4}$  of output power is reflected). Then we have,

$$P_2^- = \frac{3}{4}kTB = \frac{kTB}{2} + \frac{N_{\text{added}}}{2} \quad (\text{N}_{\text{added}} \text{ ref. at input})$$

$$\therefore N_{\text{added}} = \frac{1}{2}kTB$$


$$T_e = \frac{N_{\text{added}}}{k_B T_0} = \frac{I}{2}$$

$$F = 1 + \frac{T_e}{T_0} = 1 + \frac{T}{2T_0}$$

$$\text{If } T = T_0, \quad F = \frac{3}{2} = 1.76 \text{ dB.}$$

(Result verified with HP-MDS, calculations using available gain, and direct measurement)

c) QUADRATURE HYBRID

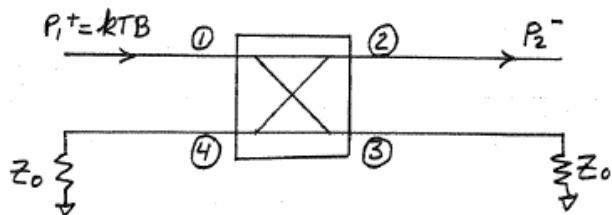

$$[S] = \frac{-1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$

Using the same thermodynamic arguments as above, the output noise power is  $kTB$  (outputs are matched). Thus,

$$P_2^- = kTB = \frac{kTB}{2} + \frac{N_{\text{added}}}{2}$$

$$\therefore N_{\text{added}} = kTB$$

$$T_e = \frac{N_{\text{added}}}{k_B} = T$$

$$F = 1 + \frac{T_e}{T_0} = 1 + \frac{T}{T_0}$$

If  $T = T_0$ , we have

$$F = 2 = 3 \text{dB}$$

**10.8** From (10.33),  $T_e = \frac{(L-1)(L+|\Gamma_s|^2)}{L(1-|\Gamma_s|^2)} T$

let  $x^2 = |\Gamma_s|^2$ ;  $C = (L-1)T/L$ . Then  $T_e = C \frac{L+x^2}{1-x^2}$

$$\frac{d T_e}{d x} = C \frac{(1-x^2)(2x) + (2x)(L+x^2)}{(1-x^2)^2} = \frac{2x(1+L)}{(1-x^2)^2} = 0$$

Thus  $x=0$ , so  $|\Gamma_s|=0$  minimizes  $T_e$  ✓


**10.9**

$$|\Gamma| = 0 \text{ to } 0.9, F = 1 \text{ dB}, 3 \text{ dB}, 10 \text{ dB}.$$

From (10.36)

$$F_m = 1 + \frac{F-1}{1-|\Gamma|^2}$$

$ \Gamma $	$F=1 \text{ dB}$	$F=3 \text{ dB}$	$F=10 \text{ dB}$
0	1.00	3.00	10.0
0.3	1.09	3.22	10.4
0.6	1.48	4.09	11.8
0.9	3.74	7.97	16.8

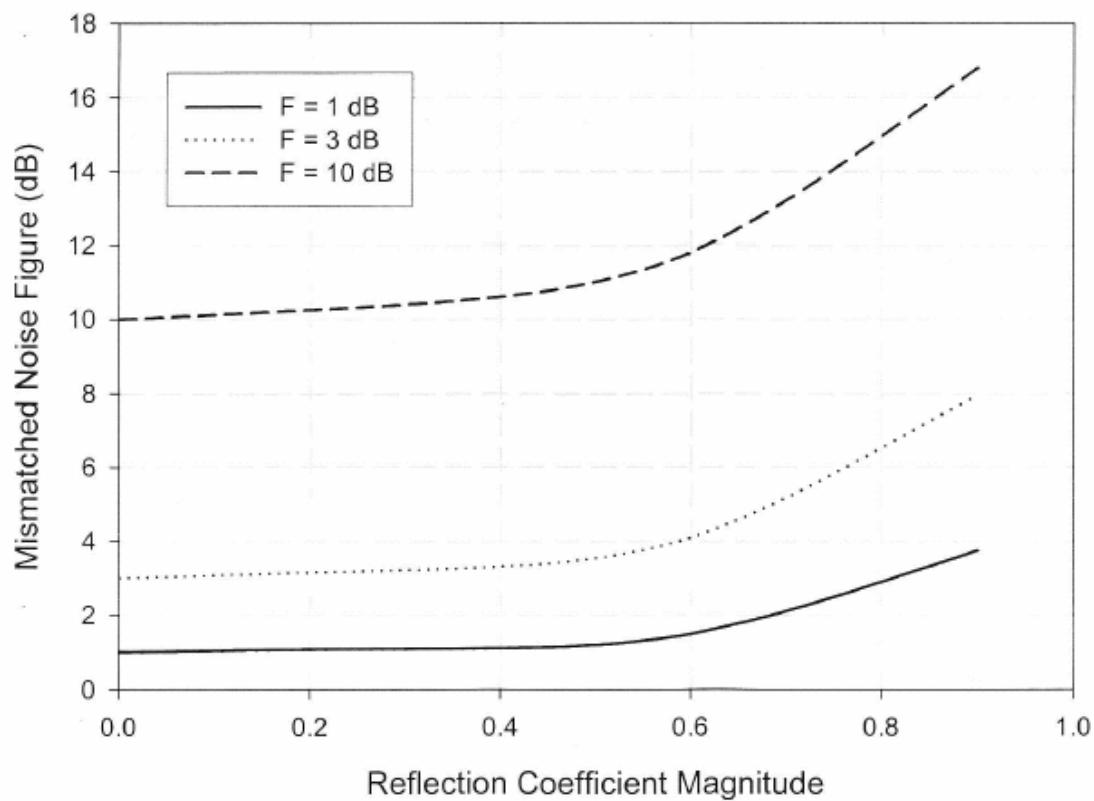

10.10



Solution using noise temperature:

$$\text{Let } N_i = kT_0 B$$

$$\text{Then } N_o = \underbrace{\frac{kT_0 BG}{L} (1 - |\Gamma|^2)}_{\text{INPUT NOISE}} + \underbrace{\frac{(L-1)}{L} kTB(1 - |\Gamma|^2) G}_{\text{NOISE ADDED BY LINE}} + \underbrace{kT_0(F-1)GB}_{\text{NOISE ADDED BY AMP}}$$

also,

$$S_o = \frac{G(1 - |\Gamma|^2)}{L} S_i$$

$$\text{So, } F_{\text{CAS}} = \frac{S_o N_o}{S_o N_i} = \frac{L}{G(1 - |\Gamma|^2)} \cdot \frac{\cancel{kT_0 BG}(1 - |\Gamma|^2) + \cancel{(L-1)} \cancel{kTB(1 - |\Gamma|^2)} + \cancel{kT_0(F-1)GB}}{\cancel{kT_0 B}}$$

$$= 1 + (L-1) \frac{T}{T_0} + \frac{L(F-1)}{1 - |\Gamma|^2} \quad \checkmark$$

Solution using cascade formula:

$$T_e(\text{LINE}) = (L-1)T$$

$$F(\text{LINE}) = 1 + (L-1) \frac{T}{T_0}$$


$$G(\text{LINE}) = \frac{1}{L} (1 - |\Gamma|^2)$$

$$F_{\text{CAS}} = F_{(\text{LINE})} + \frac{F_{\text{AMP-1}}}{G_{(\text{LINE})}} = 1 + (L-1) \frac{T}{T_0} + \frac{L}{1 - |\Gamma|^2} (F-1) \quad \checkmark$$

$$\text{CHECK: IF } \Gamma=0, \quad F_{\text{CAS}} = 1 + (L-1) \frac{T}{T_0} + L(F-1) \quad \checkmark$$

$$\text{IF } \Gamma=0 \text{ AND } T=T_0, \quad F_{\text{CAS}} = 1 + (L-1) + L(F-1) = LF \quad \checkmark$$


NUMERICAL CHECK:

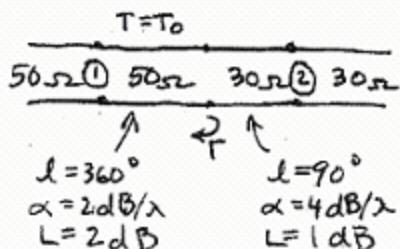

$$\Gamma = \frac{30 - 50}{30 + 50} = -\frac{1}{4}$$

$$F_{\text{CAS}} = 3.06 \text{ dB} - \text{AGREES WITH SERENADE.}$$

10.11

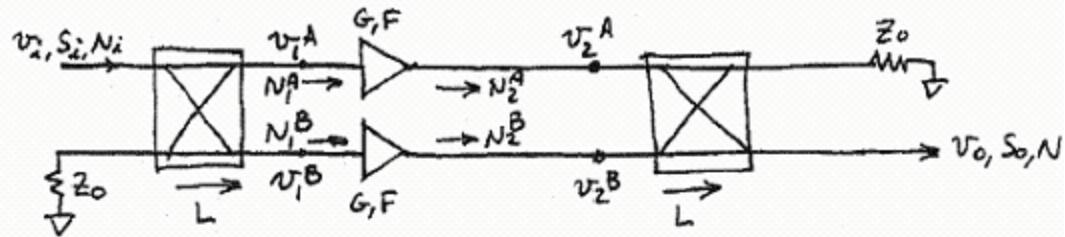

$$S_i = v_i^2 / 2$$

$$v_i^A = \frac{v_i}{\sqrt{2L}}$$

$$v_i^B = -j \frac{v_i}{\sqrt{2L}}$$

$$v_2^A = \frac{v_i \sqrt{G}}{\sqrt{2L}}$$

$$v_2^B = -j \frac{v_i \sqrt{G}}{\sqrt{2L}}$$

$$v_o = -j \frac{v_2^A}{\sqrt{2L}} + \frac{v_2^B}{\sqrt{2L}} = -j \frac{v_i \sqrt{G}}{2L} - j \frac{v_i \sqrt{G}}{2L} = -j \frac{v_i \sqrt{G}}{L}$$

$$S_o = \frac{v_o^2}{2} = \frac{v_i^2 G}{2L^2} = \frac{G S_i}{L^2} \quad \checkmark$$

$$N_i^A = N_i^B = kT_o B$$


$$N_2^A = N_2^B = kT_o BG + kT_e BG = kT_o BG(1+F-1) = kT_o BG F$$

$$\begin{aligned} N_o &= \frac{N_2^A}{2L} + \frac{N_2^B}{2L} + \frac{N_{ADDED}}{2L} = \frac{kT_o BG}{L} F + \underbrace{\frac{kT_o B}{2L} (2L-2)}_{\text{SEE BELOW}} \\ &= \frac{kT_o BG}{L} F + kT_o B(L-1) \end{aligned}$$

$$F_{TOT} = \frac{S_o N_o}{S_o N_i} = \frac{L^2}{G} \left[ \frac{GF}{L} + \left( L - \frac{1}{L} \right) \right] = LF + \frac{L}{G}(L-1) \quad \checkmark$$

CHECK: IF  $L=1$ ,  $F_{TOT} = F \quad \checkmark$

$N_{ADDED}$  FOR HYBRID :

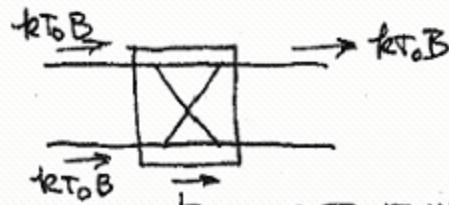

$$N_o = \frac{kT_o B}{2L} + \frac{kT_o B}{2L} + \frac{N_{ADDED}}{2L} \xrightarrow{\text{REF. AT INPUT}} = kT_o B$$

$$\therefore N_{ADDED} = 2kT_o B(L-1) \quad (\text{REF. AT INPUT})$$


**10.12**

The ratio  $\frac{OIP_3 - P_{w_1}^0}{IIP_3 - P_{w_1}^i} = 1$  defines the slope


of the fundamental (1st order response)

The ratio  $\frac{OIP_3 - P_{2w_1-w_2}^0}{IIP_3 - P_{2w_1-w_2}^i} = 3$  defines the slope

of the third order response.

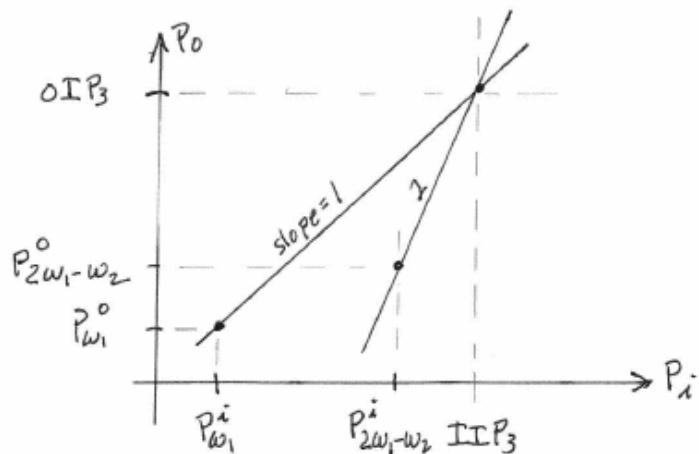

10.13

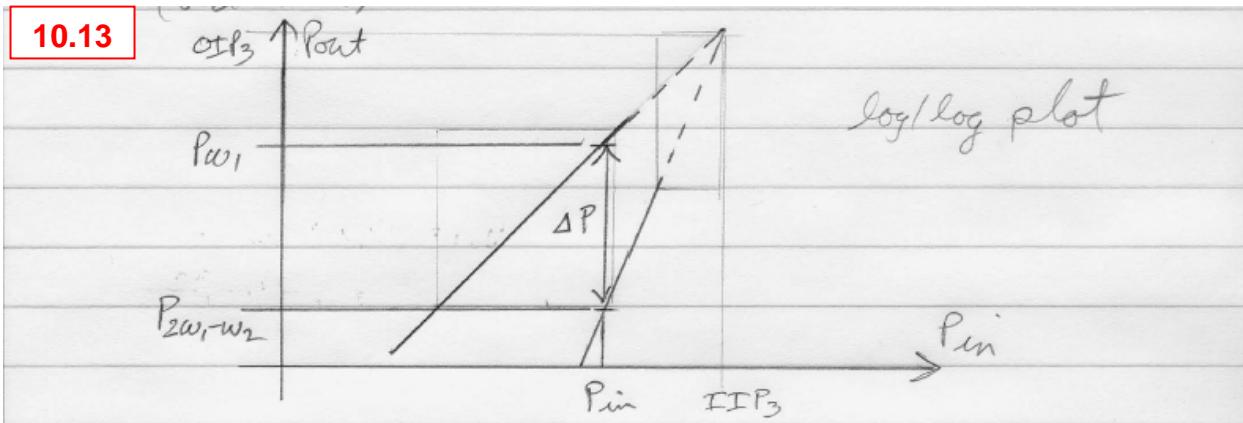

$$P_{w_1} = P_{in} + b_1 \quad (\text{eq. of line, slope } = 1)$$

$$P_{2w_1-w_2} = 3P_{in} + b_2 \quad (\text{eq. of line, slope } = 3)$$

subtract:

$$\Delta P = P_{w_1} - P_{2w_1-w_2} = -2P_{in} + b_1 - b_2$$

Now,

$$IIP_3 = P_{in} \text{ when } \Delta P = 0, \text{ so}$$

$$\Delta P = -2P_{in} + b_1 - b_2$$

$$0 = -2(IIP_3) + b_1 - b_2$$

$$\text{so } \Delta P = -2P_{in} + 2(IIP_3)$$

or,

$$\text{in dB} \quad \begin{cases} IIP_3 = P_{in} + \Delta P/2 & (\text{ref. at input}) \\ OIP_3 = P_{w_1} + \Delta P/2 & (\text{ref. at output}) \end{cases}$$

Example:  $P_{w_1} = 5 \text{ dBm}$ ,  $P_{2w_1-w_2} = -27 \text{ dBm}$ ,  $P_{in} = -4 \text{ dBm}$  (Egony, p. 100)

$$\text{Then } \Delta P = 32 \text{ dB}$$

$$IIP_3 = -4 + 32/2 = 12 \text{ dBm}$$

$$OIP_3 = 5 + 32/2 = 21 \text{ dBm}$$

$$\text{check: } G = P_{w_1}/P_{in} = 5/4 = 9 \text{ dB}$$

$$OIP_3 = G(IIP_3) = 9 + 12 = 21 \text{ dBm} \checkmark$$

**10.14**

Retaining only the terms that give rise to the third order intermodulation products:

$$v_o \sim k(v_1 \cos \omega_1 t + v_2 \cos \omega_2 t)^3$$

$$\sim k(v_1^2 v_2 \cos^2 \omega_1 t \cos \omega_2 t + v_1 v_2^2 \cos \omega_1 t \cos^2 \omega_2 t)$$

$$\sim k(v_1^2 v_2 \cos 2\omega_1 t \cos \omega_2 t + v_1 v_2^2 \cos \omega_1 t \cos 2\omega_2 t)$$

$$\sim \frac{k}{2} [v_1^2 v_2 \cos(2\omega_1 - \omega_2)t + v_1 v_2^2 \cos(2\omega_2 - \omega_1)t]$$

So the ratio of the powers in the two outputs is,

$$\left(\frac{v_1^2 v_2}{v_1 v_2}\right)^2 = \left(\frac{v_1}{v_2}\right)^2 = 6 \text{ dB}$$

Note that the individual output powers vary as  $P_{in}^3$ .

**10.15**

Moving the reference for  $OIP_3'$  to the output of the mixer gives

$$OIP_3' = 13 \text{ dBm} - 6 \text{ dB} = 7 \text{ dBm}$$

numerical values:

$$OIP_3'' = 22 \text{ dBm} = 158 \text{ mW} \quad (\text{AMP})$$

$$OIP_3' = 7 \text{ dBm} = 5 \text{ mW} \quad (\text{MIXER})$$

$$G_2 = 20 \text{ dB} = 100 \quad (\text{AMP})$$

Assuming coherent products, using (10.53),

$$\begin{aligned} OIP_3 &= \left( \frac{1}{G_2(OIP_3')} + \frac{1}{OIP_3''} \right)^{-1} = \left( \frac{1}{(100)(5)} + \frac{1}{158} \right)^{-1} = 120 \text{ mW} \\ &= \underline{20.8 \text{ dBm}} \quad \checkmark \end{aligned}$$

Assuming non-coherent products, using (10.54),

$$\begin{aligned} OIP_3 &= \left[ \frac{1}{G_2^2 (OIP_3')^2} + \frac{1}{(OIP_3'')^2} \right]^{-\frac{1}{2}} = \left[ \frac{1}{(100)^2 (5)^2} + \frac{1}{(158)^2} \right]^{-\frac{1}{2}} \\ &= 150.7 \text{ mW} = \underline{21.8 \text{ dBm}} \end{aligned}$$

**10.16**

$$\text{For } v_i = V_0 \cos \omega_0 t$$

$$V_{\omega_0} = a_1 V_0 + \frac{3}{4} a_3 V_0^3 \quad (10.40)$$

$$V_{3\omega_0} = \frac{1}{4} a_3 V_0^3$$

$$\text{For } v_i = V_0 (\cos \omega_1 t + \cos \omega_2 t)$$

$$V_{2\omega_1 - \omega_2} = \frac{3}{4} a_3 V_0^3 \quad (10.43)$$

Assume  $a_3$  is of opposite sign to  $a_1$  (for compression).

Now let  $V_0$  be input voltage where 3rd order term reduces 1st order term by 1 dB:

$$\frac{|a_1|V_0 - \frac{3}{4}|a_3|V_0^3}{|a_1|V_0} = 1 - \frac{3}{4} \left| \frac{a_3}{a_1} \right| V_0^2 = 10^{-1/20} = 0.8913$$

$$\frac{3}{4} \left| \frac{a_3}{a_1} \right| V_0^2 = 0.10875$$

From (10.44) the input voltage at IP<sub>3</sub> is

$$V_{IP}^2 = \frac{4a_1}{3a_3} \text{ so } \frac{V_0^2}{V_{IP}^2} = 0.10875 = \frac{IP_{1dB}}{IIP_3} = -9.64 \text{ dB}$$

$$\text{Then, } OP_{1dB} = G + IP_{1dB} - 1 \text{ dB} = G + IIP_3 - 1 \text{ dB} - 9.64 \text{ dB}$$

$$= OIP_3 - 10.64 \text{ dB} \quad (\text{see Egan, P.103})$$

**10.17**

$$OP_{1dB} = 5 \text{ dBm}, \quad G = 15 \text{ dB}, \quad B = 1 \text{ GHz}, \quad T_e = 250 \text{ K}$$

$$N_i = kT_e B = (1.38 \times 10^{-23})(250)(10^9) = 3.5 \times 10^{-12} \text{ W} = -84.5 \text{ dBm}$$

$$N_o = G N_i = 15 \text{ dB} + (-84.5 \text{ dBm}) = -69.5 \text{ dBm}$$

From (10.55),  $LDR = OP_{1dB} - N_o = 5 - (-69.5) = \underline{74.5 \text{ dB}}$

(Note: using input levels will result in a value 1dB higher,  
but LDR is usually defined as output levels)

**10.18**

$$F = 6 \text{ dB} = 4, \quad G = 30 \text{ dB} = 10^3, \quad B = 20 \text{ MHz},$$

$$OIP_3 = 33 \text{ dBm}, \quad OP_{1dB} = 21 \text{ dBm}, \quad SNR = 8 \text{ dB}.$$

$$N_i = -105 \text{ dBm} = 3.16 \times 10^{-14} \text{ W}$$

$$T_e = (F-1)T_0 = 3(290) = 870 \text{ K} \quad \checkmark$$

$$N_o = G(N_i + kT_e B)$$

$$= 10^3 [3.16 \times 10^{-14} + (1.38 \times 10^{-23})(870)(20 \times 10^6)]$$

$$= 2.72 \times 10^{-10} \text{ W} = -65.7 \text{ dBm} \quad \checkmark$$

From (10.55)  $LDR = OP_{1dB} - N_o = 21 - (-65.7) = \underline{86.7 \text{ dB}} \quad \checkmark$

From (10.60)  $SFDR = \frac{2}{3}(OIP_3 - N_o) - SNR$

$$= \frac{2}{3}(33 + 65.7) - 8 = \underline{57.8 \text{ dB}}$$

## Chapter 11

11.1


$$C_J = 0.38 \text{ pF}, \quad R_S = 4 \Omega, \quad I_S = 0.3 \mu A$$

$I_0 (\mu A)$	$R_J (\Omega)$	$\beta_v (V/mW)$
0	$8.3 \times 10^4$	8.7
20	$1.23 \times 10^3$	6.4
50	$4.97 \times 10^2$	4.6

11.2

INFINEON BA592 PIN :  $R_f = 0.36 \Omega$ ,  $C_j = 1.4 \mu F$   
assume  $R_r = 0.5 \Omega$ ,  $L_i = 0.5 mH$


SWITCH ON (diode OFF)

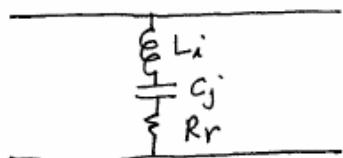

$$Z_d = 0.5 - j15.8 \Omega$$

$$Y_d = 1.98 + j63.01 mS$$

SWITCH OFF (diode ON)

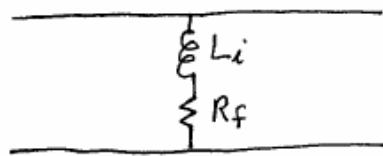

$$Z_d = 0.36 + j12.6 \Omega$$

$$Y_d = 2.28 - j79.5 mS$$

Use stub with  $Y_s = -j0.06301 = -j3.15/Z_0 \Rightarrow l_s = 0.30\lambda$ .


$$\text{ON: } Z = 1/0.0198 = 505.1 \Omega$$

$$IL(\text{ON}) = -20 \log \left| \frac{2Z}{2Z+Z_0} \right| = 0.42 \text{ dB} \quad \checkmark$$

$$\text{OFF: } Z = 0.112 + j7.01$$

$$IL(\text{OFF}) = -20 \log \left| \frac{2Z}{2Z+Z_0} \right| = 11.4 \text{ dB} \quad \checkmark$$



11.3

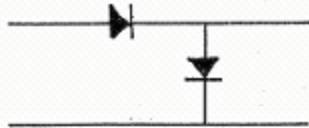



$$\omega L_i = 15 \Omega$$

$$1/\omega C_j = 265 \Omega$$

SWITCH ON:

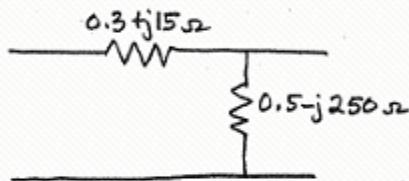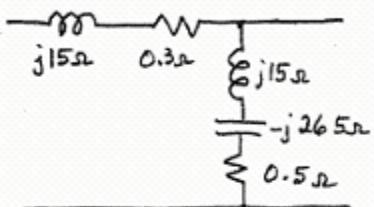


SWITCH OFF:

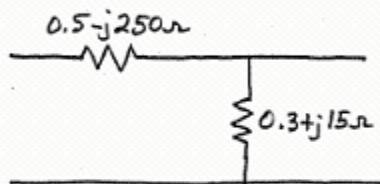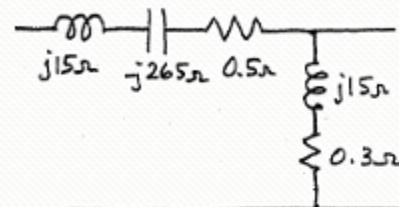

ABCD matrix:
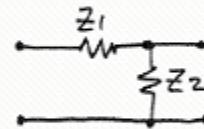
$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} 1 & Z_1 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1/Z_2 & 1 \end{bmatrix} = \begin{bmatrix} 1 + Z_1/Z_2 & Z_1 \\ 1/Z_2 & 1 \end{bmatrix}$$



Convert to S<sub>21</sub>:

$$S_{21} = \frac{2}{A+B/Z_0+CZ_0+D} = \frac{2}{1 + Z_1/Z_2 + Z_1/Z_0 + Z_0/Z_2 + 1} = \frac{2}{2 + \frac{Z_1}{Z_2} + \frac{Z_1}{Z_0} + \frac{Z_0}{Z_2}}$$

ON STATE:  $Z_1 = 0.3 + j15 \Omega$ ,  $Z_2 = 0.5 - j250 \Omega$

$$S_{21} = 0.995 \angle -14^\circ$$


$$IL = 0.044 \text{ dB}$$

OFF STATE:  $Z_1 = 0.5 - j250 \Omega$ ,  $Z_2 = 0.3 + j15 \Omega$

$$S_{21} = 0.118 \angle 149^\circ$$

$$IL = 18.6 \text{ dB}$$

11.4

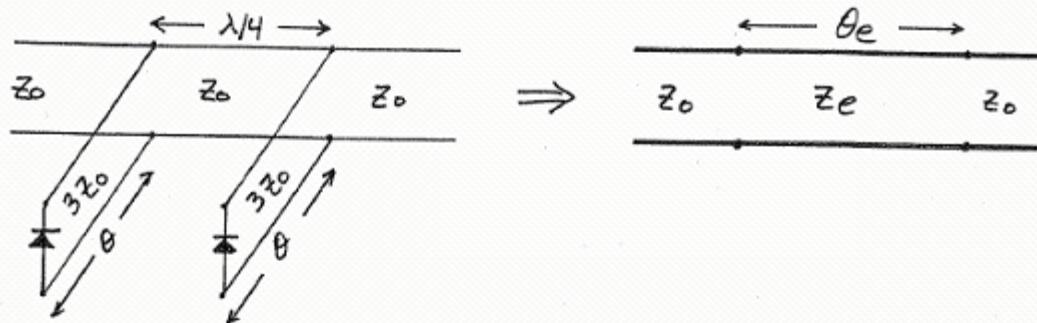

From (10.74),  $\cos \theta_i = -b$

$$Z_i = Z_0 / \sqrt{1 - b^2}$$

where  $b$  is the normalized stub susceptance.

For diodes ON,  $b = -\frac{1}{3} \cot \theta$

$$\cos \theta_i = \frac{1}{3} \cot \theta$$

For diodes OFF,  $b = \frac{1}{3} \tan \theta$

$$\cos \theta_i = -\frac{1}{3} \tan \theta$$

$$\text{So } \Delta\phi = 45^\circ = \cos^{-1}\left(\frac{1}{3} \cot \theta\right) - \cos^{-1}\left(-\frac{1}{3} \tan \theta\right) \quad (\text{ON-OFF})$$

Solving this equation numerically:

$\theta$	$\Delta\phi$
$110^\circ$	$73^\circ$
$120^\circ$	$46^\circ$
$130^\circ$	$40^\circ$
$122^\circ$	$44.3^\circ$
$121^\circ$	$45.2^\circ$

So we choose  $\theta = 121^\circ$ . (Using  $\theta = 31^\circ$  gives  $\Delta\phi = -45^\circ$ )

Insertion loss for  $\theta = 121^\circ$ :

Using (10.73),  $b = B Z_0$

$$S_{21} = \frac{2}{A + B/Z_0 + C Z_0 + D} = \frac{2}{-B Z_0 + j(1 - B^2 Z_0^2) - B Z_0} = \frac{2}{-2b + j(2 - b^2)}$$

$$|S_{21}|^2 = \frac{4}{4b^2 + (2-b^2)^2}$$

DIODES ON:  $b = -\frac{1}{3} \cot \theta = 0.20$

$$|S_{21}|^2 = 0.9996$$

$$IL = 0.0017 \text{ dB } \sim 0 \text{ dB } \checkmark$$

DIODES OFF:  $b = \frac{1}{3} \tan \theta = -0.555$


$$|S_{21}|^2 = 0.977$$

$$IL = 0.102 \text{ dB } \checkmark$$

(SuperCompact analysis gives  $IL_{ON} = 0 \text{ dB}$ ,  $\phi_{ON} = -101.5^\circ$ ,  $IL_{OFF} = 0.10 \text{ dB}$ ,  $\phi_{OFF} = -56.7^\circ$ , thus  $\Delta\phi = 44.8^\circ$ )

### 11.5

Unilateral bipolar transistor model:

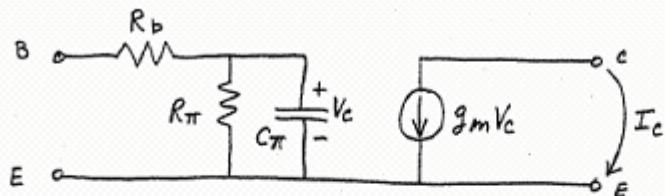

From (10.77) the short-circuit current gain is,

$$\begin{aligned} G_i^{sc} &= \left| \frac{I_c}{I_b} \right| \Big|_{V_{ce}=0} = \frac{g_m V_c}{I_b} = \frac{g_m I_b |R_\pi / i\omega C_\pi|}{I_b} \\ &= g_m \frac{R_\pi}{|1 + j\omega R_\pi C_\pi|} = \frac{g_m}{|\frac{1}{R_\pi} + j\omega C_\pi|} \approx \frac{g_m}{\omega C_\pi} \quad \text{since } R_\pi \gg 1/\omega C_\pi \end{aligned}$$

(e.g., if  $R_\pi = 110 \Omega$ ,  $C_\pi = 18 \mu F$ ,  $f = 1 \text{ GHz}$ , then  $1/\omega C_\pi = 9 \Omega$ )

11.6

First find  $z_{ij}$ , then convert to  $s_{ij}$ :

$$z_{11} = R_i - j/wCgs$$

$$z_{22} = \left( \frac{1}{R_{ds}} + jwC_{ds} \right)^{-1}$$

$$z_{12} = 0$$

$$z_{21} = -g_m z_{22}/jwCgs = jg_m z_{22}/wCgs$$

$$s_{11} = \frac{(z_{11} - z_0)(z_{22} + z_0)}{\Delta z}, \quad \Delta z = (z_{11} + z_0)(z_{22} + z_0)$$

$$= \frac{z_{11} - z_0}{z_{11} + z_0} \quad \checkmark$$

$$s_{12} = 0$$

$$s_{21} = \frac{2z_{12}z_0}{\Delta z} = \frac{2jz_0 g_m z_{22}/wCgs}{(z_{11} + z_0)(z_{22} + z_0)}$$

$$s_{22} = \frac{(z_{11} + z_0)(z_{22} - z_0)}{\Delta z} = \frac{z_{22} - z_0}{z_{22} + z_0} \quad \checkmark$$

11.7

From 11.6,

$$Z_{11} = Z_0 \frac{1+S_{11}}{1-S_{11}} = R_i - j/\omega C_{gs}$$

$$R_i = \operatorname{Re}\{Z_{11}\}, \quad C_{gs} = -1/\omega \operatorname{Im}\{Z_{11}\}$$

$$Z_{22} = Z_0 \frac{1+S_{22}}{1-S_{22}} = \left( \frac{1}{R_{ds}} + j\omega C_{ds} \right)^{-1}$$

$$R_{ds} = 1/\operatorname{Re}\{Z_{22}\}, \quad C_{ds} = \operatorname{Im}\{1/Z_{22}\}/\omega$$

$$g_m = -j\omega C_{gs} Z_{21}/Z_{22}, \quad Z_{21} = \frac{S_{21} Z_0}{2Z_0} = \frac{S_{21}(Z_i + Z_0)(Z_{22} + Z_0)}{2Z_0}$$

From Table 11.7, MESFET @ 2GHz :

$$S_{11} = 0.9 \angle -55^\circ$$

$$S_{21} = 3.56 \angle 129^\circ$$

$$S_{12} = 0.08 \angle 54^\circ \approx 0$$

$$S_{22} = 0.65 \angle -37^\circ$$

Then,

$$R_i = 12.2 \Omega, \quad C_{gs} = 0.84 \text{ pF}$$

$$R_{ds} = 213 \Omega, \quad C_{ds} = 0.51 \text{ pF}$$

$$g_m = 54 \text{ mS.}$$

## Chapter 12

**12.1**

The [S] matrix for a 3-dB matched attenuator is,

$$[S] = \begin{bmatrix} 0 & 0.707 \\ 0.707 & 0 \end{bmatrix}$$

FOR  $Z_L = 50\Omega$ :  $\Gamma_L = \Gamma_{in} = 0, \Gamma_S = 0, \Gamma_{out} = 0$

Then from (11.12), (11.13), and (11.8) we have

$$G_A = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{|(1 - S_{11}\Gamma_S|^2)(1 - |\Gamma_{out}|^2)} = |S_{21}|^2 = 0.5 \checkmark$$

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)(1 - |\Gamma_L|^2)}{|(1 - \Gamma_S \Gamma_{in})^2 |(1 - S_{22}\Gamma_L)|^2} = |S_{21}|^2 = 0.5 \checkmark$$

$$G = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2)|(1 - S_{22}\Gamma_L)|^2} = |S_{21}|^2 = 0.5 \checkmark$$

FOR  $Z_L = 25\Omega$ :  $\Gamma_L = -1/3, \Gamma_S = \Gamma_{out} = 0, \Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L} = -1/6$

$$G_A = |S_{21}|^2 = 0.5 \checkmark$$

$$G_T = |S_{21}|^2 (1 - |\Gamma_L|^2) = 0.444 \checkmark$$

$$G = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2)} = 0.457 \checkmark$$

FOR  $Z_S = 25\Omega, Z_L = 50\Omega$ :  $\Gamma_L = \Gamma_{in} = 0, \Gamma_S = -1/3, \Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1 - S_{11}\Gamma_S} = -1/6$

$$G_A = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{(1 - |\Gamma_{out}|^2)} = 0.457$$

$$G_T = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)}{1} = 0.444$$

$$G = |S_{21}|^2 = 0.5$$

**12.2**

Envision BFP Si-Ge HBT at 1GHz

$$(a) \quad \Gamma_s = \Gamma_L = 0, \text{ so } \Gamma_{in} = S_{11}, \Gamma_{out} = S_{22}$$

$$(12.8) \quad G = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{(1 - |\Gamma_{in}|^2)(1 - |S_{22}\Gamma_L|^2)} = \frac{|S_{21}|^2}{(1 - |S_{11}|^2)} = \frac{(3.92)^2}{1 - (.91)^2} = 89.4 \checkmark$$

$$(12.12) \quad G_A = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)}{(1 - |\Gamma_{out}|^2)(1 - |S_{11}\Gamma_s|^2)} = \frac{|S_{21}|^2}{(1 - |S_{22}|^2)} = \frac{(3.92)^2}{1 - (.93)^2} = 113.7 \checkmark$$

$$(12.13) \quad G_T = \frac{|S_{21}|^2 (1 - |\Gamma_s|^2)(1 - |\Gamma_L|^2)}{|1 - \Gamma_s \Gamma_{in}|^2 (1 - |S_{22}\Gamma_L|^2)} = |S_{21}|^2 = (3.92)^2 = 15.4 \checkmark$$

(b) for  $G$ , let  $\Gamma_L = S_{22}^*$ ,  $\Gamma_s = 0$  ( $G$  does not depend on  $\Gamma_s$ )  
 Then, for  $S_{12} = 0$ ,  $\Gamma_{in} = S_{11}$

$$G = \frac{|S_{21}|^2}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)} = 661.7 \checkmark$$

for  $G_A$ , let  $\Gamma_s = S_{11}^*$ ,  $\Gamma_L = 0$  ( $G_A$  does not depend on  $\Gamma_L$ )  
 Then, with  $S_{12} = 0$ ,  $\Gamma_{out} = S_{22}$

$$G_A = \frac{|S_{21}|^2}{(1 - |S_{22}|^2)(1 - |S_{11}|^2)} = 661.7 \checkmark$$

For  $G_T$ , let  $\Gamma_s = S_{11}^*$ ,  $\Gamma_L = S_{22}^*$ .

Then, with  $S_{12} = 0$ ,  $\Gamma_{in} = S_{11}$ ,  $\Gamma_{out} = S_{22}$ .

$$G_T = \frac{|S_{21}|^2}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)} = 661.7 \checkmark$$

**12.3**

$$S_{11} = 0.61 \angle -170^\circ, S_{12} = 0.06 \angle 70^\circ, S_{21} = 2.3 \angle 80^\circ, S_{22} = 0.72 \angle -25^\circ$$

$$Z_S = 25 \Omega, Z_L = 100 \Omega, V_S = 2V.$$

a)  $\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1-S_{22}\Gamma_L} = 0.641 \angle -174^\circ \quad \checkmark$

$$\Gamma_{out} = S_{22} + \frac{S_{12}S_{21}\Gamma_S}{1-S_{11}\Gamma_S} = 0.777 \angle -25^\circ \quad \checkmark$$

$$G = 12.8 = 11.1 \text{ dB} \quad \checkmark$$


$$G_A = 18.4 = 12.6 \text{ dB} \quad \checkmark$$

$$G_T = 10.8 = 10.3 \text{ dB} \quad \checkmark$$

$$G_{TU} = \frac{|S_{21}|^2 (1 - |\Gamma_S|^2)(1 - |\Gamma_L|^2)}{|1 - S_{11}\Gamma_S|^2 |1 - S_{22}\Gamma_L|^2} = 10.4 = 10.2 \text{ dB} \quad \checkmark$$

(verified with Serenade)

b)

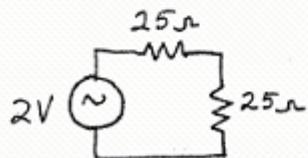

$$P_{AVS} = \frac{1}{2} \left( \frac{2}{2} \right)^2 \frac{1}{25} = 0.02 \text{ W}$$


$$P_L = G_T P_{AVS} = (10.8)(0.02) = 0.216 \text{ W}$$

**12.4**

$$S_{11} = 0.880 \angle -115^\circ, S_{12} = 0.029 \angle 31^\circ, S_{21} = 9.4 \angle 110^\circ, S_{22} = 0.328 \angle -67^\circ$$

$$C_L = 4.0 \angle 96^\circ, R_L = 3.60, C_S = 1.16 \angle 119^\circ, R_S = 0.367$$

$$K = 0.275$$

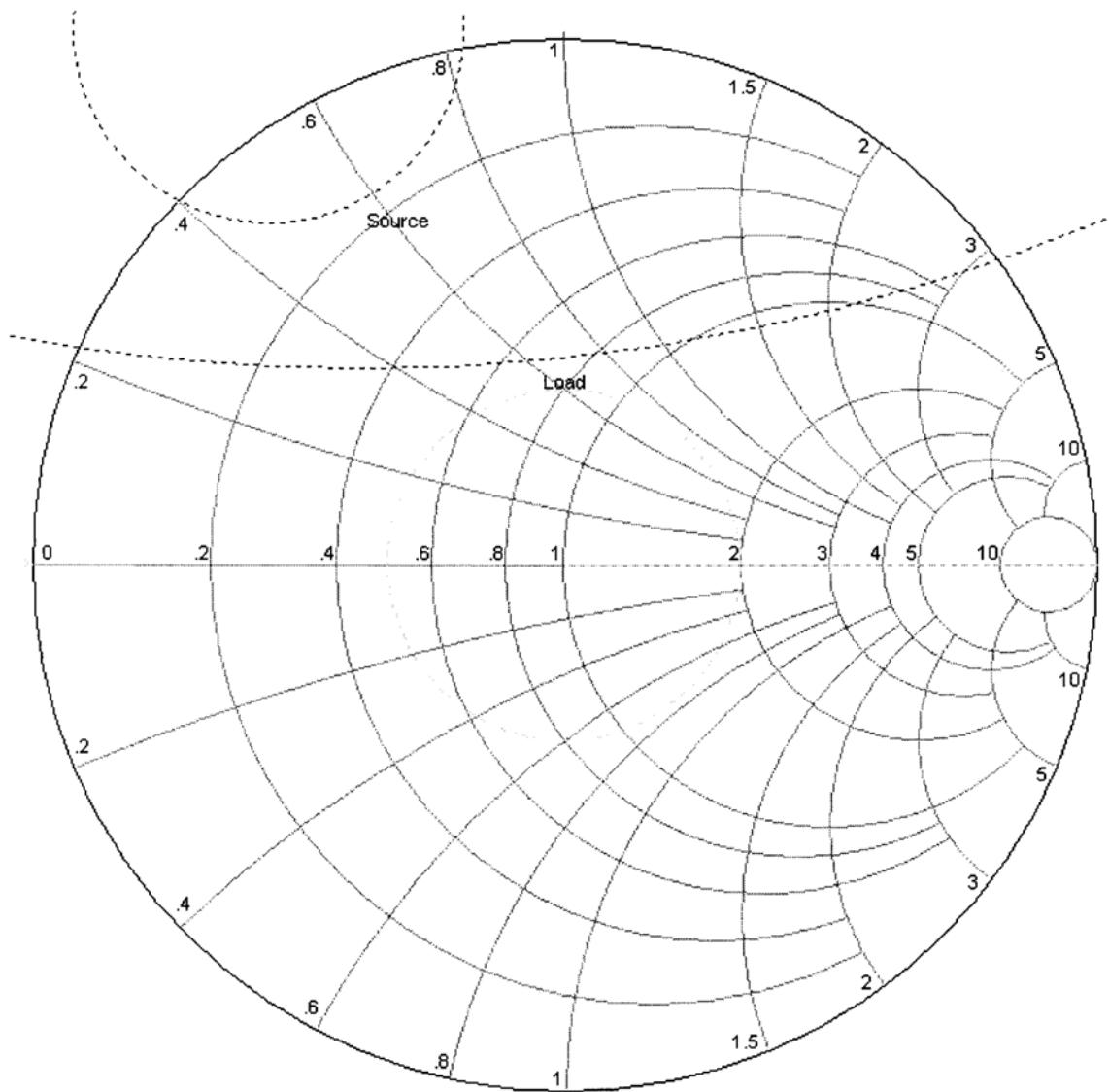

**12.5**

## GaN HEMT

S-parameters from Table 11.8

$f(6\text{Hz})$	K	$\Delta$	STABILITY
0.5	0.604	0.686	pot. unstable
1.0	0.452	0.725	pot. unstable
2.0	1.030	0.705	uncond. stable
4.0	3.262	0.770	uncond. stable

**12.6**Using (12.30) to compute  $M$ :

DEVICE	$S_{11}$	$S_{12}$	$S_{21}$	$S_{22}$	$M$	
A	$0.34 \angle -70^\circ$	$0.06 \angle 70^\circ$	$4.3 \angle 80^\circ$	$0.45 \angle -25^\circ$	1.193	UNC. STABLE
B	$0.75 \angle -60^\circ$	$0.2 \angle 70^\circ$	$5.0 \angle 90^\circ$	$0.5 \angle 60^\circ$	0.283	POT. UNSTABLE
C	$0.65 \angle -140^\circ$	$0.04 \angle 60^\circ$	$2.4 \angle 50^\circ$	$0.7 \angle -65^\circ$	1.057	UNC. STABLE

Device A has the best stability.

**12.7**

From (11.30) the  $\mu$ -parameter test is,

$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - S_{11}^* \Delta| + |S_{21} S_{12}|} > 1$$

If  $S_{12} = 0$  (unilateral) then we have,

$$\Delta = S_{11} S_{22}$$

So,

$$\mu = \frac{1 - |S_{11}|^2}{|S_{22} - |S_{11}|^2 S_{22}|} = \frac{1 - |S_{11}|^2}{|S_{22}| |1 - |S_{11}|^2|} > 1$$

Since the denominator is positive and  $\mu$  is positive, the numerator must also be positive, thus  $|S_{11}| < 1$ . Then the above reduces to,

$$\mu = \frac{1}{|S_{22}|} > 1 ,$$

So,

$$|S_{22}| < 1 .$$

**12.8**

From the definition of (11.41),

$$B_1 = 1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2 , \quad C_1 = S_{11} - \Delta S_{22}^* .$$

Similar to the expansion used after (11.35), it can be verified by direct expansion that,

$$|C_1|^2 = |S_{11} - \Delta S_{22}^*|^2 = |S_{12} S_{21}|^2 + (1 - |S_{22}|^2)(|S_{11}|^2 - |\Delta|^2)$$

$$(1 + |S_{11}|^2 - |S_{22}|^2 - |\Delta|^2)^2 > 4 |S_{12} S_{21}|^2 + 4(1 - |S_{22}|^2)(|S_{11}|^2 - |\Delta|^2)$$

$$\begin{aligned} & 1 + 2|S_{11}|^2 - 2|S_{22}|^2 - 2|\Delta|^2 + |S_{11}|^4 - 2|S_{11}|^2 |S_{22}|^2 - 2|S_{11}|^2 |\Delta|^2 + |S_{22}|^4 \\ & + 2|\Delta|^2 |S_{22}|^2 + |\Delta|^4 > 4 |S_{12} S_{21}|^2 + 4(|S_{11}|^2 - |\Delta|^2 - |S_{11}|^2 |S_{22}|^2 + |\Delta|^2 |S_{22}|^2) \end{aligned}$$

$$\begin{aligned} & 1 - 2|S_{11}|^2 - 2|S_{22}|^2 + 2|\Delta|^2 + |S_{11}|^4 + 2|S_{11}|^2 |S_{22}|^2 - 2|S_{11}|^2 |\Delta|^2 + |S_{22}|^4 \\ & - 2|\Delta|^2 |S_{22}|^2 + |\Delta|^4 > 4 |S_{12} S_{21}|^2 \end{aligned}$$

$$(1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2)^2 > 4 |S_{12} S_{21}|^2$$

Or,

$$K^2 = \frac{(1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2)^2}{4 |S_{12} S_{21}|^2} > 1 \quad \checkmark$$

12.9


Data from Table 11.7 GaAs MESFET

conjugate matching for maximum gain (at 8 GHz):


$$\Gamma_s = \Gamma_{in}^* = 0.883 \angle -172^\circ$$

$$\Gamma_L = \Gamma_{out}^* = 0.859 \angle 139^\circ$$


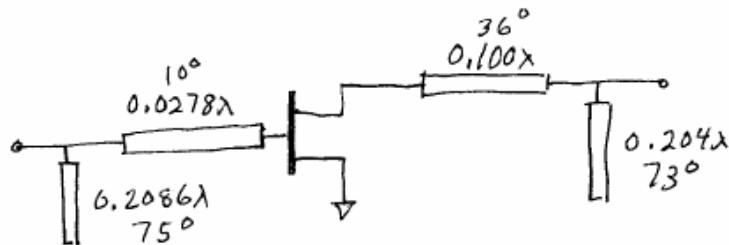
$$G_s = 4.53, G_o = 4.00, G_L = 0.623 \Rightarrow G_T = 11.29 = 10.53 \text{ dB}$$



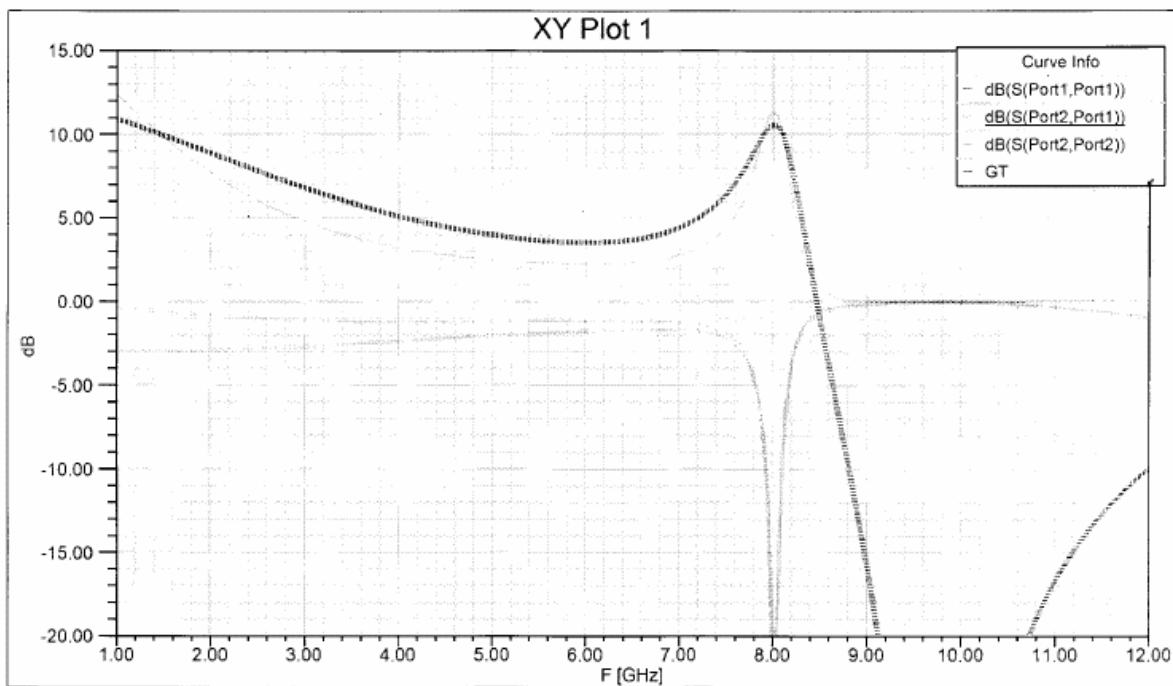CAD modeling gives gain = 10.5 dB; no stability problems from 1-12 GHz. Gain is plotted below.



12.10

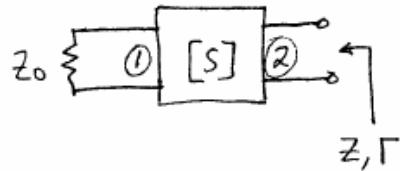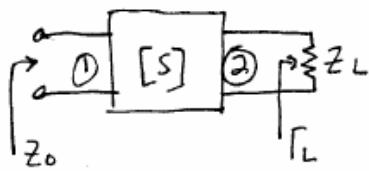

Assuming a lossless reciprocal network,

$$S_{12} = S_{21}, \quad |S_{11}|^2 + |S_{12}|^2 = |S_{22}|^2 + |S_{12}|^2 = 1$$

$$S_{11} S_{12}^* + S_{12} S_{22}^* = 0$$

For the second circuit,  $\Gamma = S_{22} + \frac{S_{12} S_{21} \Gamma_s}{1 - S_{11} \Gamma_s} = S_{22}$  since  $\Gamma_s = 0$ .

For the first circuit, at port 1,  $\Gamma_L = \Gamma^* = S_{22}^*$ , so

$$\begin{aligned} \Gamma_{in} &= S_{11} + \frac{S_{12} S_{21} \Gamma_L}{1 - S_{22} \Gamma_L} = S_{11} + \frac{S_{12}^2 S_{22}^*}{1 - |S_{22}|^2} \\ &= S_{11} + \frac{S_{12}^2 S_{22}^*}{|S_{12}|^2} = \frac{S_{12} (S_{11} S_{12}^* + S_{12} S_{22}^*)}{|S_{12}|^2} = 0 \quad \checkmark \end{aligned}$$

**12.11**  $S_{11} = 0.61 \angle -770^\circ$ ,  $S_{21} = 2.24 \angle 32^\circ$ ,  $S_{12} = 0$ ,  $S_{22} = 0.72 \angle -83^\circ$


The transistor is unconditionally stable since  $K=\infty$  and  $|A| < 1$ . Since the transistor is unilateral,

$$\Gamma_S = S_{11}^* = 0.61 \angle 170^\circ \quad , \quad \Gamma_L = S_{22}^* = 0.72 \angle 83^\circ$$

and the maximum gain is, from (11.45),

$$G_{TU\max} = \frac{1}{1-|S_{11}|^2} |S_{21}|^2 \frac{1}{1-|S_{22}|^2} = 16.6 = 12.2 \text{ dB}$$

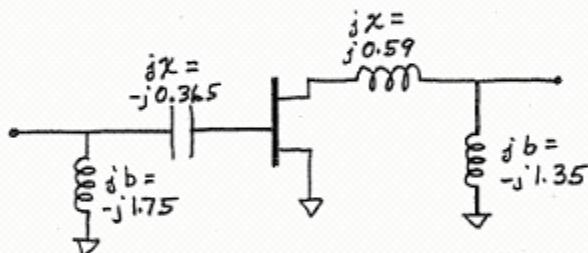Matching was done with a Smith chart. The final circuit is:



The matching element values are, at 6 GHz,

$$C = \frac{-1}{\omega Z_0 X_0} = 1.45 \text{ pF} \quad L = \frac{Z_0 K_L}{\omega} = 0.78 \text{ mH}$$

$$L = \frac{-Z_0}{\omega b_L} = 0.76 \text{ mH} \quad L = \frac{-Z_0}{\omega b_L} = 0.98 \text{ mH}$$

SuperCompact analysis gives  $|S_{11}| = 0.035$ ,  $|S_{22}| = 0.008$ , and  $G = 12.2 \text{ dB}$

**12.12**

$$S_{11} = 0.61 \angle -170^\circ, S_{21} = 2.24 \angle 32^\circ; S_{12} = 0, S_{22} = 0.72 \angle -83^\circ$$

$$G = 10 \text{ dB}, G_s = 1 \text{ dB}, G_L = 2 \text{ dB}$$

Since  $K = \infty$  and  $|A| < 1$ , the transistor is unconditionally stable. From (11.45), we have

$$G_{S_{MAX}} = \frac{1}{1 - |S_{11}|^2} = 1.59 \checkmark, \quad G_{L_{MAX}} = \frac{1}{1 - |S_{22}|^2} = 2.08 \checkmark$$

So for  $G_s = 1 \text{ dB} = 1.26$ , and  $G_L = 2 \text{ dB} = 1.58$ , we have from (11.46),


$$g_s = \frac{G_s}{G_{S_{MAX}}} = 0.792, \quad g_L = \frac{G_L}{G_{L_{MAX}}} = 0.760$$

Then the centers and radii of the constant gain circles can be found from (11.49)-(11.50) :


$$C_s = 0.524 \angle 170^\circ \checkmark \quad C_L = 0.625 \angle 83^\circ \checkmark$$

$$R_s = 0.310 \checkmark \quad R_L = 0.269 \checkmark$$

Since  $G_0 = 10 \log |S_{21}|^2 = 7.0 \text{ dB}$ , using the  $G_s = 1 \text{ dB}$  and the  $G_L = 2 \text{ dB}$  gain circles will give an overall gain of  $10 \text{ dB}$ . We plot these circles on the Smith chart, and choose  $\Gamma_s = 0.215 \angle 170^\circ \checkmark$  and  $\Gamma_L = 0.361 \angle 83^\circ \checkmark$  to minimize the magnitude of these values. After matching, we have the following amplifier circuit:

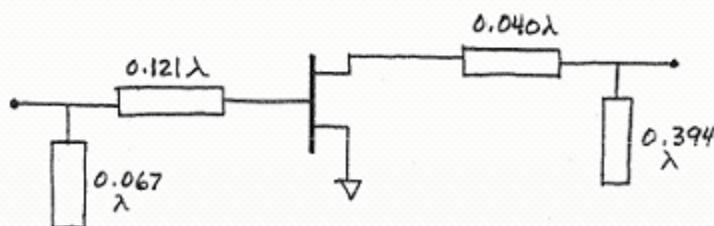

Supercompact analysis gives  $|S_{11}| = 0.45$ ,  $|S_{22}| = 0.48$ ,  $G = 10.05 \text{ dB} \checkmark$  (reflections at input and output serve to reduce the gain to  $10 \text{ dB}$ ). Smith chart shown on following page.

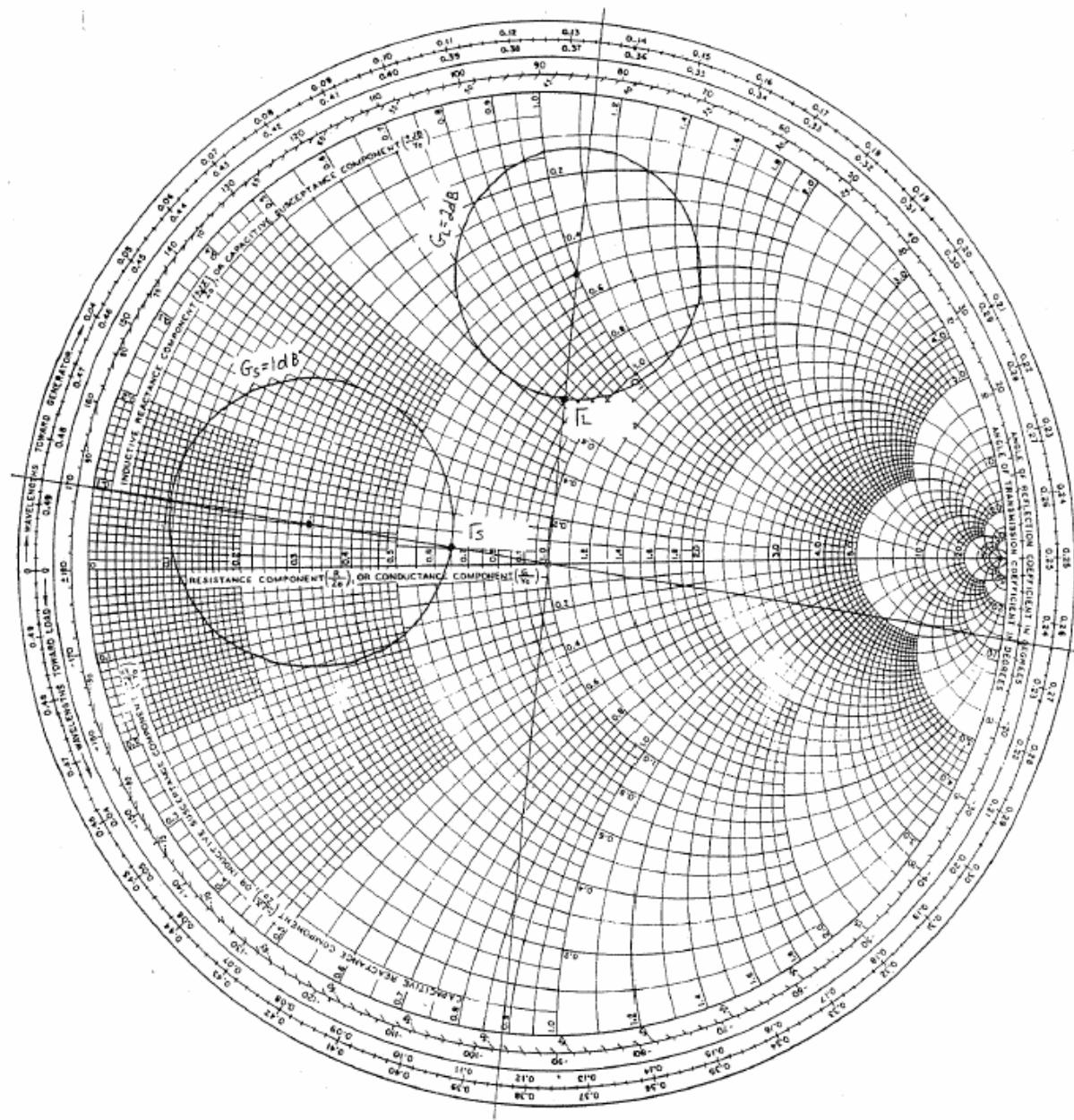

**12.13**

$$S_{11} = .88 \angle -115^\circ, S_{12} = .029 \angle 131^\circ, S_{21} = 9.40 \angle 110^\circ, S_{22} = .328 \angle -67^\circ$$

From (12.46) the unilateral figure of merit is

$$U = \frac{|S_{12}| |S_{21}| |S_{11}| |S_{22}|}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)} = \frac{(.029)(9.4)(.88)(.328)}{[1 - (.88)^2][1 - (.328)^2]} = 0.391$$

From (12.45) this bounds the error in  $G_T/G_{Tu}$  by

$$.517 = \frac{1}{(1+U)^2} < \frac{G_T}{G_{Tu}} < \frac{1}{(1-U)^2} = 2.70$$

$$\text{in dB, } -2.9 \text{ dB} < G_T(\text{dB}) - G_{Tu}(\text{dB}) < 4.3 \text{ dB}$$

An assumption that the device is unilateral is not justified in this case.

**12.14** From (11.48) and (11.47), when  $G_S = 1$  we have,

$$g_S = \frac{1}{G_{S_{MAX}}} = 1 - |S_{11}|^2 , \quad 1 - g_S = |S_{11}|^2$$

so (11.51) reduces to,

$$C_S = \frac{(1 - |S_{11}|^2) S_{11}^*}{1 - |S_{11}|^4} = \frac{S_{11}^*}{1 + |S_{11}|^2}$$

$$R_S = \frac{|S_{11}|(1 - |S_{11}|^2)}{1 - |S_{11}|^4} = \frac{|S_{11}|}{1 + |S_{11}|^2}$$

So the equation of the constant gain circle becomes,

$$\left| r_S - \frac{S_{11}^*}{1 + |S_{11}|^2} \right| = \frac{|S_{11}|}{1 + |S_{11}|^2}$$

one solution to this equation occurs for  $r_S = 0$ , so the circle must pass through the center of the Smith chart.

12.15

$$S_{11} = 0.7 \angle 110^\circ, S_{12} = 0.02 \angle 60^\circ, S_{21} = 3.5 \angle 60^\circ, S_{22} = 0.8 \angle -70^\circ$$

$$F_{\text{MIN}} = 2.5 \text{ dB}, \Gamma_{\text{OPT}} = 0.7 \angle 120^\circ, R_N = 15 \Omega$$

First check stability:  $K = 1.07, |\Delta| = 0.53$

Since  $K > 1$  and  $|\Delta| < 1$  the device is unconditionally stable.

Minimum noise figure occurs for  $\Gamma_s = \Gamma_{\text{OPT}} = 0.7 \angle 120^\circ$ . Then we maximize gain by conjugate matching the output.

From (11.41b),


$$\Gamma_L = \left( S_{22} + \frac{S_{12}S_{21}\Gamma_s^*}{1 - S_{11}\Gamma_s} \right)^* = 0.873 \angle 74^\circ \checkmark$$

So the noise figure will be  $F = F_{\text{min}} = 2.5 \text{ dB}$ , and the gain will be,

$$G_T = \frac{1 - |\Gamma_s|^2}{|1 - S_{11}\Gamma_s|^2} |S_{21}|^2 \frac{1 - |S_{22}|^2}{|1 - S_{22}\Gamma_L|^2}$$

$$= (1.85)(12.25)(3.81) = 86.3 = 19.4 \text{ dB}$$

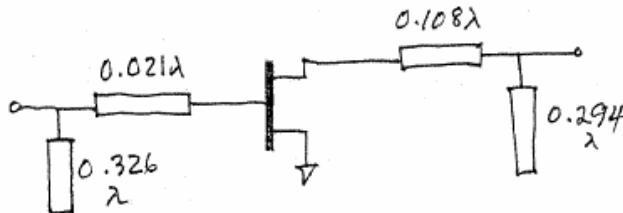Impedance matching is done with a Smith chart; the final amplifier circuit is shown below.



Serenade analysis of this amplifier gives

$$|S_{11}| = 0.33, |S_{22}| = 0.13,$$

$$G = 19.7 \text{ dB}, F = 2.5 \text{ dB} \checkmark.$$

The solution is simpler if  $S_{12}$  is set to zero, resulting in  $G = 18 \text{ dB}$ .

12.16

$$S_{11} = 0.6 \angle -60^\circ, S_{21} = 2.181^\circ, S_{12} = 0, S_{22} = 0.7 \angle -60^\circ$$

$$F_{\min} = 2.0 \text{ dB}, \Gamma_{\text{opt}} = 0.62 \angle 100^\circ, R_N = 20 \Omega$$

Since  $S_{12} = 0$  and  $|S_{11}| |S_{22}| < 1$ , the device is unconditionally stable. The overall gain is,  $G_{\text{TO}} = G_S G_o G_L$ , where  $G_o = |S_{21}|^2 = 4 = 6 \text{ dB}$ . ✓ So  $G_S + G_L = 0 \text{ dB}$ .

Plot noise figure circles for  $F = 2.0, 2.05, 2.2$ , and  $3.0 \text{ dB}$ :

$F(\text{dB})$	$N$	$C_F$	$R_F$
2.05	0.0134	$0.61 \angle 100^\circ$	0.09
2.20	0.055	$0.59 \angle 100^\circ$	0.18
3.00	0.30	$0.48 \angle 100^\circ$	0.40
2.00	0.	$0.62 \angle 100^\circ$	0

Now plot constant gain circles for  $G_S = G_L = 0 \text{ dB}$ :

$$G_{S_{\text{MAX}}} = 1.56 \checkmark$$

$$G_{L_{\text{MAX}}} = 1.96 \checkmark$$

$$g_S = 0.641$$

$$g_L = 0.510$$


$$C_S = 0.44 \angle 60^\circ$$

$$C_L = 0.47 \angle 60^\circ$$


$$R_S = 0.44$$

$$R_L = 0.47$$

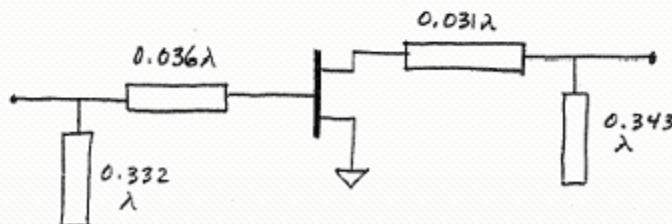These two circles are close together near the  $F = 2 \text{ dB}$  point. We choose  $\Gamma_L = 0.66 \angle 105^\circ$ ,  $\Gamma_S = 0.62 \angle 105^\circ$ . Then we should obtain  $F \approx 2.04 \text{ dB}$ . The final AC amplifier circuit is:



Super Compact analysis gives  $|S_{11}| = 0.62$ ,  $|S_{22}| = 0.67$ ,  $G = 6.1 \text{ dB}$ , and  $F = 2.04 \text{ dB}$  ✓ The gain and noise circles are shown below.

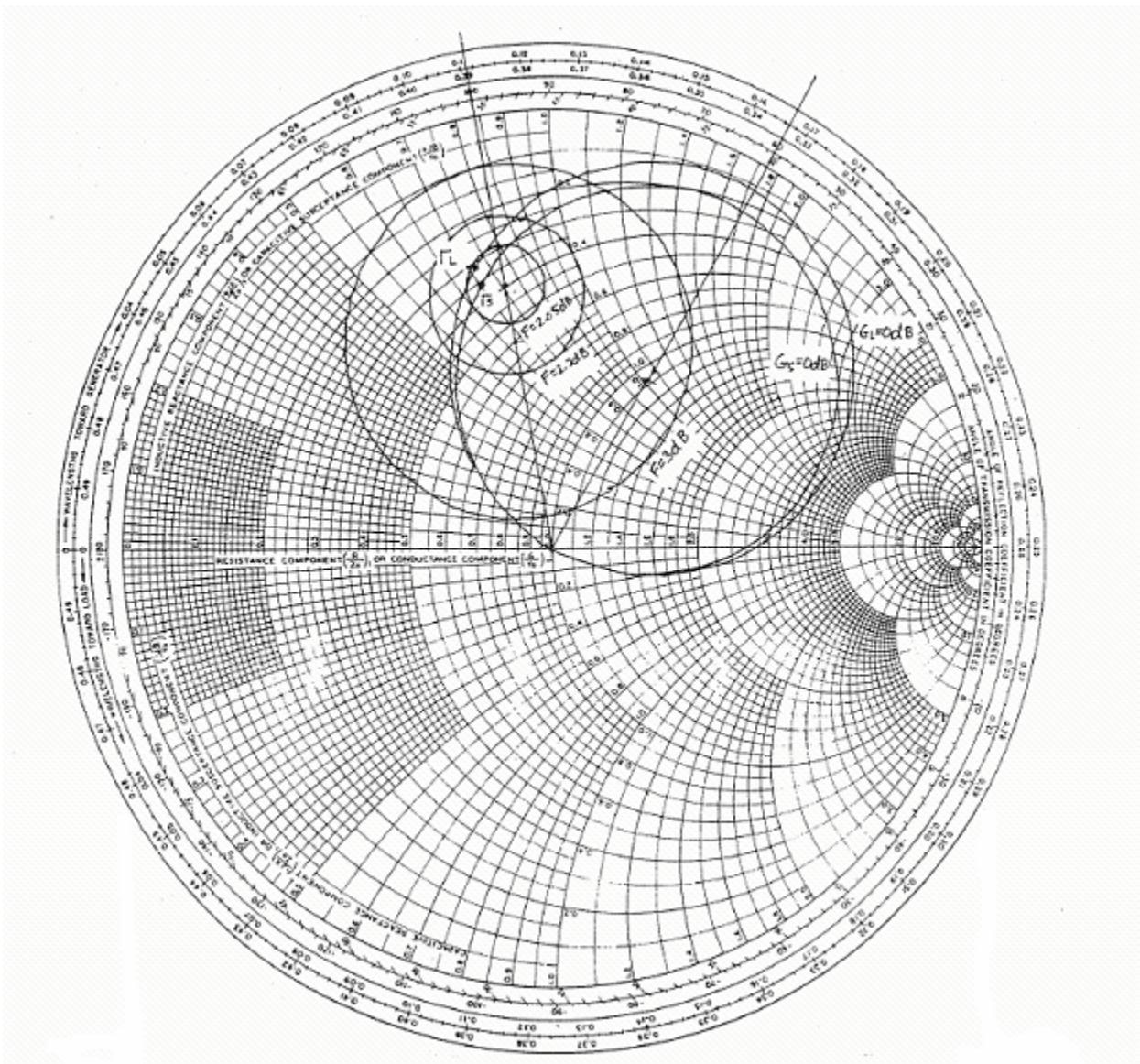

**12.17**

S-parameters and noise parameters of Problem 11.14

Plot the  $F = 2.5 \text{ dB}$  constant noise figure circle:


$$N = 0.141, \quad C_F = 0.543 \angle 100^\circ, \quad R_F = 0.286$$

$$\text{Now, } G_{S\text{MAX}} = 1.56 = 1.93 \text{ dB}, \quad G_{L\text{MAX}} = 1.96 = 2.92 \text{ dB}$$


But these points  $(S_{11}^*, S_{22}^*)$  do not lie on the  $F = 2.5 \text{ dB}$  circle. We can plot some gain circles to just give intersections with the  $F = 2.5 \text{ dB}$  noise circle:

$G_S = 1.5 \text{ dB}$	$g_S = 0.905$	$C_S = 0.56 \angle 60^\circ$	$R_S = 0.204$
$G_L = 2.5 \text{ dB}$	$g_L = 0.907$	$C_L = 0.67 \angle 60^\circ$	$R_L = 0.163$
$G_S = 1.7 \text{ dB}$	$g_S = 0.948$	$C_S = 0.58 \angle 60^\circ$	$R_S = 0.149$
$G_S = 1.8 \text{ dB}$	$g_S = 0.970$	$C_S = 0.59 \angle 60^\circ$	$R_S = 0.112$

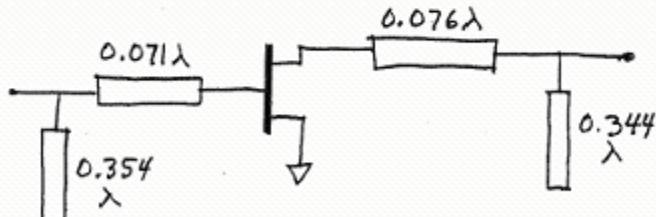The  $G_S = 1.8 \text{ dB}$  and  $G_L = 2.5 \text{ dB}$  circles are close to optimum (the  $F = 2.5 \text{ dB}$  noise circle). Thus we have  $f_S = 0.545 \angle 70^\circ$ ,  $f_L = 0.59 \angle 72^\circ$ , which will yield a gain of  $G_T = 1.8 + 2.5 + 6 = 10.3 \text{ dB}$ . The final AC amplifier circuit is shown below:



SuperCompact analysis of this circuit gives  $|S_{11}| = 0.20$ ,  $|S_{22}| = 0.28$ ,  $G = 10.3 \text{ dB}$ , and  $F = 2.4 \text{ dB}$ . The noise and gain circles are shown on the following page.

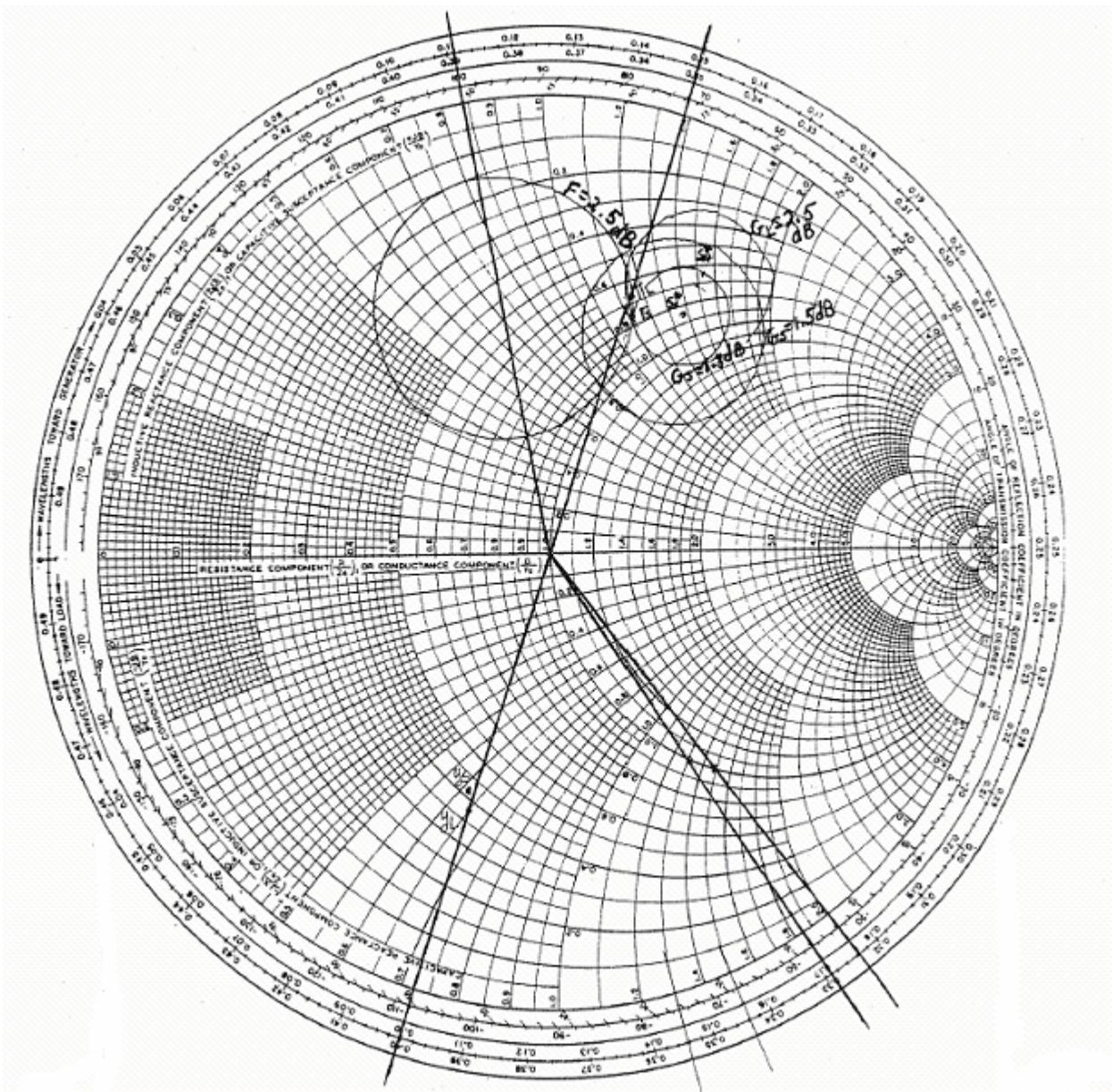


12.18

FOR THE COUPLED LINE COUPLERS:

$$C = 10^{-3/20} = 0.708$$



$$Z_{oe} = 50 \sqrt{\frac{1+c}{1-c}} = 121 \Omega$$
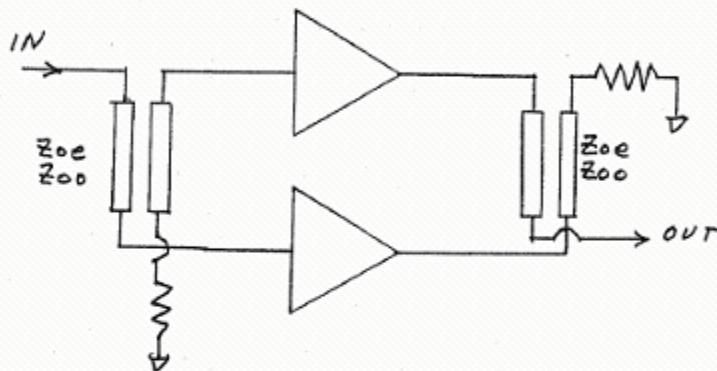
$$Z_{oo} = 50 \sqrt{\frac{1-c}{1+c}} = 21 \Omega$$




The amplifier circuit of Example 11.4 was used for both amplifiers here. As in Example 11.6, the amplifier matching networks were optimized using SuperCompact to give a flat 10dB gain response, with good input matching. Results of the optimization are given below, including the line and stub lengths before and after optimization, the SuperCompact data file, and the calculated gain and input return loss of the balanced amplifier before and after optimization. Results seem to be a bit better than those of Example 11.6.

PARAMETER	BEFORE OPT.	AFTER OPT.
INPUT SECTION STUB LENGTH	0.100λ	0.125λ
INPUT SECTION LINE LENGTH	0.179λ	0.119λ
OUTPUT SECTION LINE LENGTH	0.045λ	0.089λ
OUTPUT SECTION LINE LENGTH	0.432λ	0.458λ

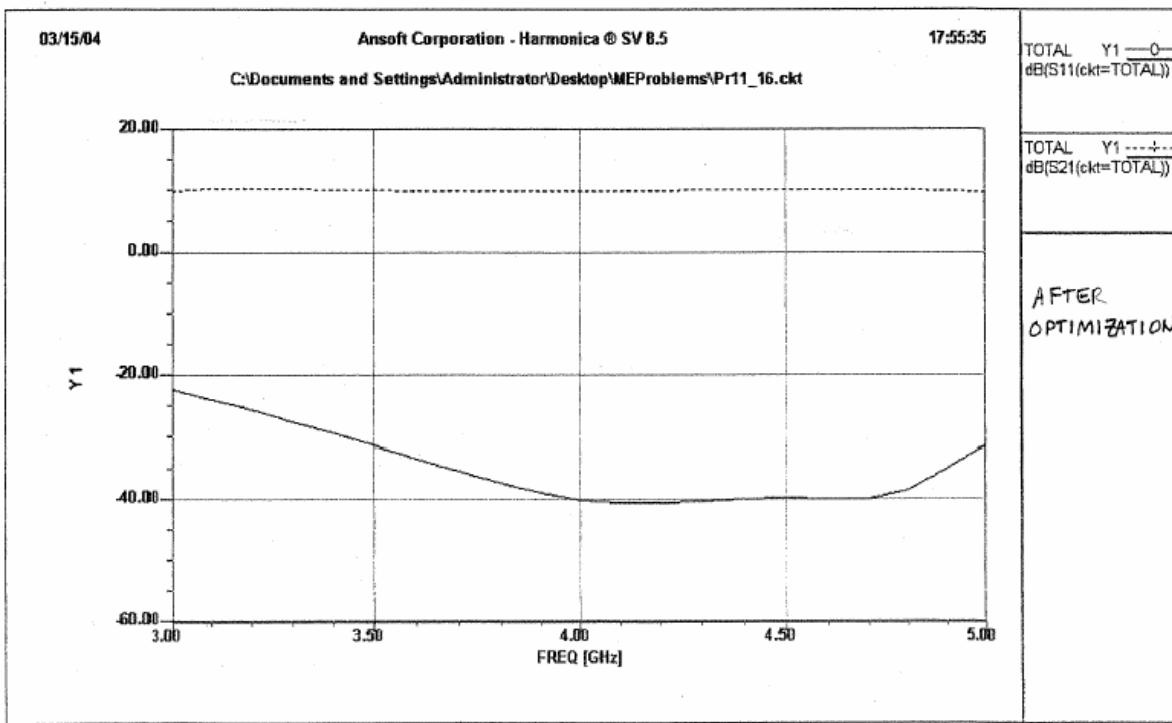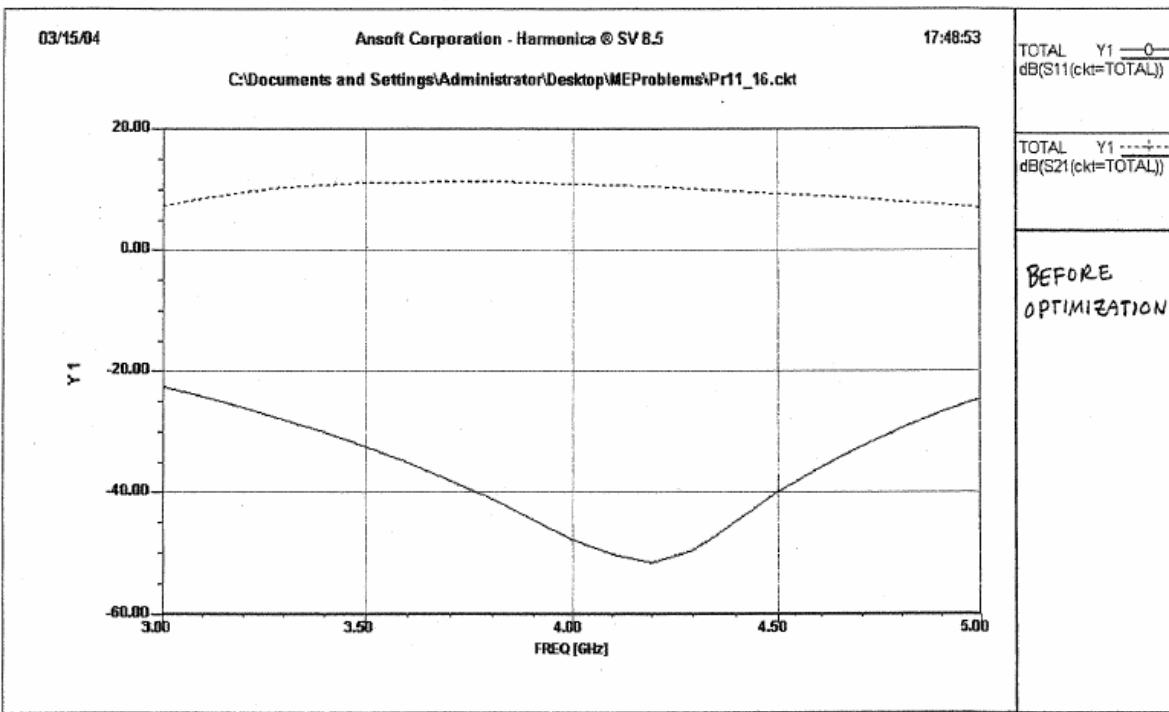

12.19

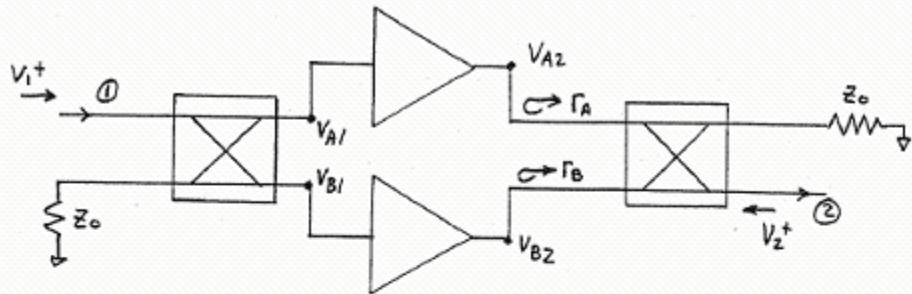

The analysis for  $S_{22}$  is identical to that for  $S_{11}$  in eqs (11.61) - (11.65), but with input  $V_2^+$  at port 2.

Thus, if the input at port 2 is  $V_2^+$ , then the voltages incident at the amplifiers are,

$$V_{A2}^- = \frac{1}{\sqrt{2}} V_2^+$$

$$V_{B2}^- = \frac{-j}{\sqrt{2}} V_2^+$$

Then the reflected output voltage at port 2 is,

$$\begin{aligned} V_2^- &= \frac{1}{\sqrt{2}} V_{A2}^+ + \frac{-j}{\sqrt{2}} V_{B2}^+ = \frac{1}{\sqrt{2}} \Gamma_A V_{A2}^- + \frac{-j}{\sqrt{2}} \Gamma_B V_{B2}^- \\ &= \frac{1}{2} V_2^+ (\Gamma_A - \Gamma_B) \end{aligned}$$

Thus,

$$S_{22} = \left. \frac{V_2^-}{V_2^+} \right|_{V_2^+=0} = \frac{1}{2} (\Gamma_A - \Gamma_B) \quad \checkmark$$

**12.20**

$$\text{From (11.77), } G = \frac{g_m^2 z_d Z_d}{4} \frac{(e^{-N\alpha_d l_d} - e^{-N\alpha_d l_d})^2}{(e^{-\alpha_d l_d} - e^{-\alpha_d l_d})^2}$$

differentiating with respect to  $N$  and setting to zero gives,

$$\alpha_d l_d e^{-N\alpha_d l_d} - \alpha_d l_d e^{-N\alpha_d l_d} = 0$$

$$\ln \alpha_d l_d - N\alpha_d l_d = \ln \alpha_d l_d - N\alpha_d l_d$$

$$\ln \frac{\alpha_d l_d}{\alpha_d l_d} = N(\alpha_d l_d - \alpha_d l_d)$$

$$N = \frac{\ln (\alpha_d l_d / \alpha_d l_d)}{\alpha_d l_d - \alpha_d l_d} \quad \checkmark$$


12.21

$R_i = 5 \Omega$ ,  $R_{DS} = 200 \Omega$ ,  $C_{GS} = 0.3 \text{ pF}$ ,  $g_m = 40 \text{ mS}$   
 $f = 0 - 20 \text{ GHz}$ , opt  $G$  at  $16 \text{ GHz}$ .  $N = 4, 8, 16$ .

at  $f = 16 \text{ GHz}$ ,  $\alpha_{g\text{lg}} = 0.1137$   
 $\alpha_{d\text{ld}} = 0.125$

$$N_{opt} = \frac{\ln \alpha_{g\text{lg}} / \alpha_{d\text{ld}}}{(\alpha_{g\text{lg}} - \alpha_{d\text{ld}})} = 8.4$$

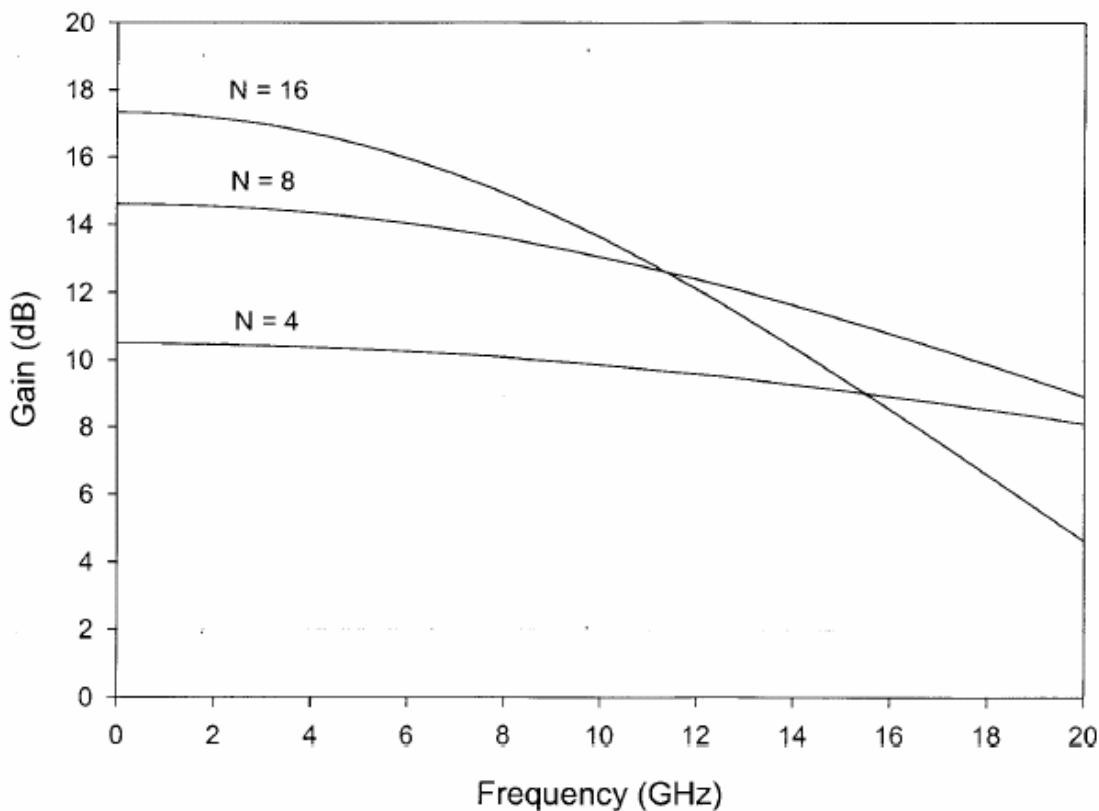gain vs. frequency is plotted below for  $N = 4, 8, 16$ .  
graph shows  $N_{opt} \approx 8$  at  $16 \text{ GHz}$  ✓



**12.22**

$$S_{11} = 0.76 \angle 169^\circ, S_{12} = 3.08 \angle 69^\circ, S_{21} = 0.079 \angle 53^\circ, S_{22} = 0.36 \angle -169^\circ$$

$$\Gamma_{SP} = 0.797 \angle -187^\circ, \Gamma_{LP} = 0.491 \angle 185^\circ, G_p = 10 \text{ dB}, f = 1 \text{ GHz}.$$

Check stability using small-signal S-parameters:

$$\Delta = S_{11}S_{22} - S_{12}S_{21} = 0.452 \angle -27^\circ$$


$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2|S_{12}S_{21}|} = 1.02$$

Since  $|\Delta| < 1$  and  $K > 1$ , the device is unconditionally stable at this frequency.

Using the given large-signal source and load reflection coefficients gives,

$$\Gamma_s = 0.797 \angle 187^\circ, \Gamma_{LP} = 0.491 \angle 185^\circ$$

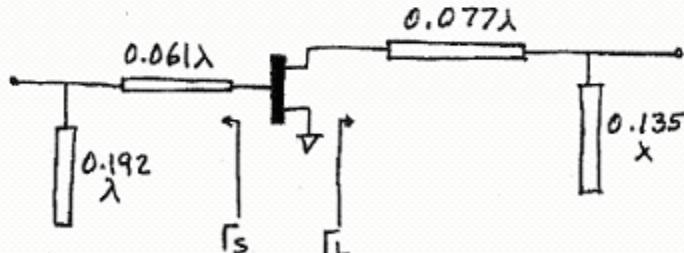Then the matching circuits can be designed, resulting in the following AC circuit:




Since the gain with this  $\Gamma_s, \Gamma_p$  is 10 dB, the input power for a 1W output is,

$$P_{in} = P_{out} - G_p = 30 \text{ dBm} - 10 = 20 \text{ dBm} = 100 \text{ mW.}$$

## Chapter 13

13.1

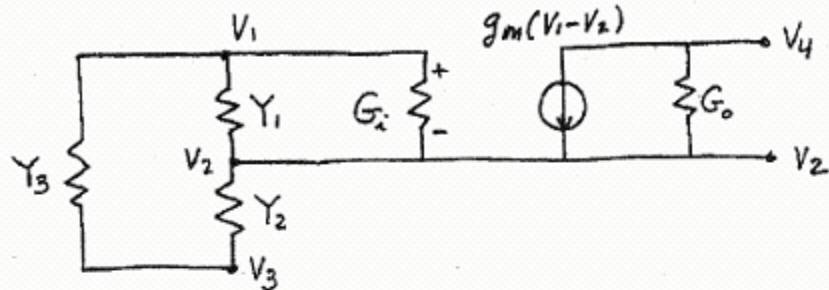

Writing KCL for nodes  $V_1, V_2, V_3, V_4$ :

$$V_1: (V_3 - V_1)Y_3 + (V_2 - V_1)Y_1 + (V_2 - V_1)G_i = 0$$

$$V_2: (V_1 - V_2)Y_1 + (V_3 - V_2)Y_2 + (V_1 - V_2)G_i + g_m(V_1 - V_2) + (V_4 - V_2)G_o = 0$$

$$V_3: (V_1 - V_3)Y_3 + (V_2 - V_3)Y_2 = 0$$

$$V_4: (V_2 - V_4)G_o - g_m(V_1 - V_2) = 0$$

Rearranging:

$$V_1(Y_1 + Y_3 + G_i) + V_2(-Y_1 - G_i) + V_3(-Y_3) + V_4(0) = 0$$

$$V_1(-Y_1 - G_i - g_m) + V_2(Y_1 + Y_2 + G_i + G_o + g_m) + V_3(-Y_2) + V_4(-G_o) = 0$$

$$V_1(-Y_3) + V_2(-Y_2) + V_3(Y_2 + Y_3) + V_4(0) = 0$$

$$V_1(g_m) + V_2(-G_o - g_m) + V_3(0) + V_4 G_o = 0$$

which agrees with the matrix of (12.3).

**13.2**

From (13.4),

$$\det \begin{bmatrix} (Y_1 + Y_3 + G_i) & -Y_3 \\ (g_m - Y_3) & (Y_2 + Y_3) \end{bmatrix} = 0 \quad \text{for oscillation.}$$

For a Colpitts oscillator, let  $Y_1 = j\omega C_1$ ,  $Y_2 = j\omega C_2$ ,  $Z_3 = R + j\omega L_3$ .

Then,

$$\det [ \cdot ] = \left( j\omega C_1 + \frac{1}{R + j\omega L_3} + G_i \right) \left( j\omega C_2 + \frac{1}{R + j\omega L_3} \right) + \left( \frac{1}{R + j\omega L_3} \right) g_m - \frac{1}{R + j\omega L_3} = 0$$

$$[1 + (G_i + j\omega C_1)(R + j\omega L_3)][1 + j\omega C_2(R + j\omega L_3)] + g_m(R + j\omega L_3) - 1 = 0$$

$$1 + j\omega C_2 \cancel{(R + j\omega L_3)} + (G_i + j\omega C_1)(R + j\omega L_3) + j\omega C_2(G_i + j\omega C_1)(R + j\omega L_3)^* + g_m(R + j\omega L_3) - 1 = 0$$

$$j\omega C_2 + G_i + j\omega C_1 + j\omega C_2(G_i + j\omega C_1)(R + j\omega L_3) + g_m = 0$$

$$\text{Re: } G_i + g_m - \omega^2 L_3 G_i C_2 - \omega^2 C_1 C_2 R = 0$$

$$\text{Im: } \omega C_2 + \omega C_1 + \omega C_2 G_i R - \omega^3 C_1 C_2 L_3 = 0$$

$$C_1 + C_2 + C_2 G_i R - \omega^2 C_1 C_2 L_3 = 0$$

$$\omega = \sqrt{\frac{C_1 + C_2 + C_2 G_i R}{C_1 C_2 L_3}} = \sqrt{\frac{1}{L_3} \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{G_i R}{C_1} \right)} \quad \checkmark$$

13.3

$$\text{From (13.4) : } \begin{vmatrix} (Y_1 + Y_2 + g_m + G_o) & - (Y_2 + G_o) \\ - (G_o + g_m + Y_2) & (Y_2 + Y_3 + G_o) \end{vmatrix} = 0$$

$$(Y_1 + Y_2 + g_m + G_o)(Y_2 + Y_3 + G_o) - (Y_2 + G_o)(G_o + g_m + Y_2) = 0$$

Simplifying gives

$$Y_1 Y_2 + Y_1 Y_3 + Y_1 G_o + Y_2 Y_3 + g_m Y_3 + G_o Y_3 = 0$$

$$\frac{1}{Y_3} + \frac{1}{Y_2} + \frac{G_o}{Y_2 Y_3} + \frac{g_m}{Y_1 Y_2} + \frac{G_o}{Y_1 Y_2} = 0$$

For Colpitts, let  $\frac{1}{Y_3} = Z_3 = R + j\omega L$ ;  $\frac{1}{Y_1} = 1/j\omega C_1$ ;  $\frac{1}{Y_2} = 1/j\omega C_2$ .

$$R + j\omega L_3 - \frac{j}{\omega C_2} + G_o(R + j\omega L_3)\left(\frac{1}{j\omega C_2}\right) - \frac{j}{\omega C_1} - \frac{(g_m + G_o)}{\omega^2 C_1 C_2} = 0$$

$$\text{Re: } R + G_o L_3 / C_2 - \frac{(g_m + G_o)}{\omega^2 C_1 C_2} = 0 \quad \checkmark$$

$$\text{Im: } \omega L_3 - \frac{1}{\omega C_2} - G_o R / \omega C_2 - 1/\omega C_1 = 0$$

$$\omega L_3 = \frac{1}{\omega} \left( \frac{1}{C_2} + \frac{G_o R}{C_2} + \frac{1}{C_1} \right)$$

$$\omega = \sqrt{L_3 \left( \frac{1}{C_1} + \frac{1}{C_2} + \frac{G_o R}{C_2} \right)} \quad \checkmark$$

Design:  $f = 200 \text{ MHz}$  common gate FET,  $g_m = 20 \text{ mS}$ ,  
 $R_o = 1/G_o = 200 \Omega$ ,  $L_3 = 15 \text{ nH}$ ,  $Q = 50$ .

$$\text{Then, } \frac{1}{\omega^2 L_3} = \frac{C_1 C_2'}{C_1 + C_2'} = 42.2 \text{ pF} \quad , \quad C_2' = \frac{C_2}{1 + G_o R}$$

$$R = \frac{\omega_0 L_3}{Q} = 0.38 \Omega$$

Assume  $C_1 = C'_2$ , then  $C_1 = 84.4 \text{ pF} = C'_2$

$$C_2 = C'_2(1 + G_0 R) = 84.4 \text{ pF}$$

$$R < \frac{g_m + G_0}{\omega^2 C_1 C_2} - \frac{G_0 L_3}{C_2} = 1.33 \Omega$$

$$Q_{MIN} = \frac{\omega_0 L_3}{R_{MAX}} = \underline{14.}$$

**13.4**

Let  $z = R + jX$ ,  $R > 0$  (POSITIVE RESISTANCE)

Then  $\bar{z} = z/z_0 = r + jx$ ,  $r > 0$

$$\Gamma = \frac{\bar{z} - 1}{\bar{z} + 1} = \frac{(r-1) + jx}{(r+1) + jx}$$

Now let  $z = -R + jX$ ,  $R > 0$  (NEGATIVE RESISTANCE)

$\bar{z} = -r + jx$ ,  $r > 0$

$$\text{Then, } \Gamma = \frac{\bar{z} - 1}{\bar{z} + 1} = \frac{-(r+1) + jx}{(-r+1) + jx} = \frac{(r+1) - jx}{(r-1) - jx}$$

So,


$$\frac{1}{\Gamma^*} = \frac{(r-1) + jx}{(r+1) + jx}$$

which has the same form as  $\Gamma$  for positive resistance. So we can read the resistance circles as negative, and interpret the "reflection coefficient" read from the Smith chart as  $1/\Gamma^*$ .

13.5

 $f = 1.9 \text{ GHz}, \text{ Si BJT}$ 

$$S_{11} = .72 \angle 157^\circ, S_{12} = .15 \angle 56^\circ, S_{21} = 1.9 \angle 52^\circ, S_{22} = .63 \angle -63^\circ$$

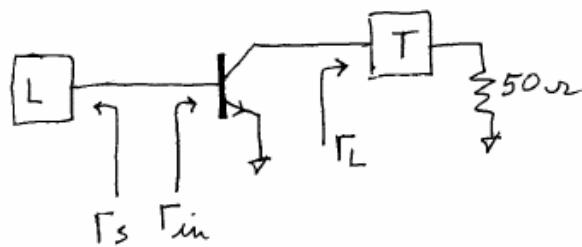


From 13.3a,  $\Gamma_{in} = S_{11} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{22}\Gamma_L}$

Choose  $\Gamma_L$  so that  $|\Gamma_L| < 1$  and  $|\Gamma_{in}|$  is large.


By trial and error,

$\Gamma_L$	$\Gamma_{in}$	$Z_{in}$
.6 \angle 60	.99 \angle 160	.2 + j .9
.8 \angle 60	1.17 \angle 160	-4.2 + j 8.7
.9 \angle 50	1.26 \angle 150	-6.2 + j 12.9
.9 \angle 60	1.31 \angle 160	-6.8 + j 8.6

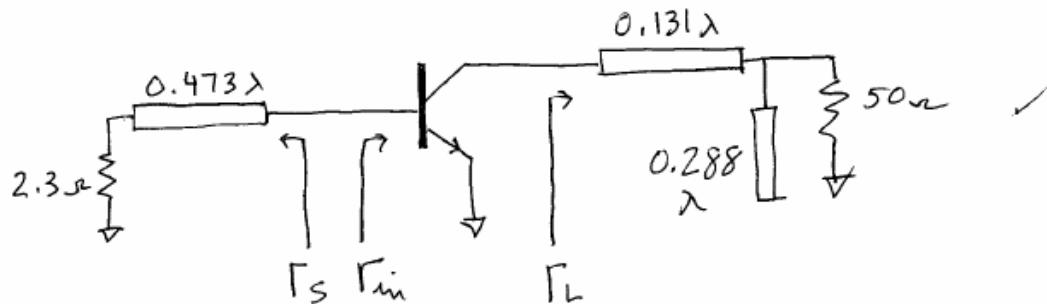Select  $\Gamma_L = 0.9 \angle 60^\circ$ . Then  $\Gamma_{in} = 1.31 \angle 160^\circ$ ,  $Z_{in} = -6.8 + j 8.6 \Omega$   
Let  $Z_s = -R_{in}/3 - j X_{in} = 2.3 - j 8.6 \Omega$ . Stub matching circuits were designed as shown below.



13.6

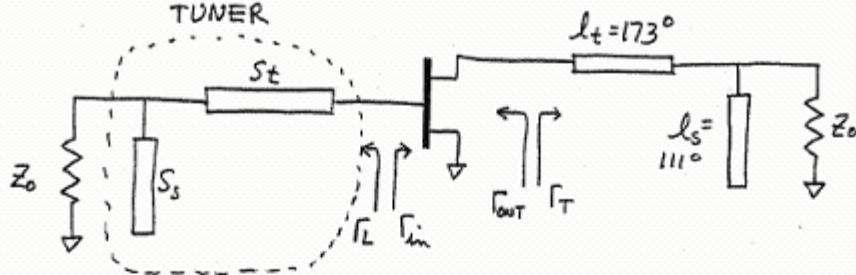


As in Example 12.4, choose  $\Gamma_L = 0.6 \angle -130^\circ$ . The  $\Gamma_{out}$ ,  $Z_{out}$ ,  $Z_T$ ,  $l_t$ , and  $l_S$  are unchanged. Then we have the simple matching problem of using the stub tuner to match  $50\Omega$  to  $\Gamma_L$ . The stub susceptance is  $j b_s = +j1.56$ , or a stub length of  $S_s = 0.158\lambda$ . The line length is  $S_t = 0.18 - 0.176 = 0.004\lambda$ .

We then analyze the above circuit to compute  $|\Gamma_{out}|$  versus frequency:

$f$ (GHz)	$\Delta f/f_0$	$ \Gamma_{out} $
2.10	-0.125	5.0
2.18	-0.092	7.2
2.20	-0.083	9.1
2.26	-0.058	11.9
2.30	-0.042	15.4
2.34	-0.025	16.5
2.38	-0.008	13.6
2.40	0	11.8
2.42	0.008	10.2
2.46	0.025	7.9
2.50	0.042	6.3
2.60	0.083	4.1
2.66	0.110	3.4
2.70	0.125	3.0

The maximum of  $|\Gamma_{out}|$  does not occur at  $\Delta f = 0$  because the tuner is not resonant at  $f_0$ . The "Q" is much lower than in Example 12.4. This problem shows the advantage of using a high-Q resonator for the oscillator.  $|\Gamma_{out}|$  vs  $f$  is plotted on the following page.

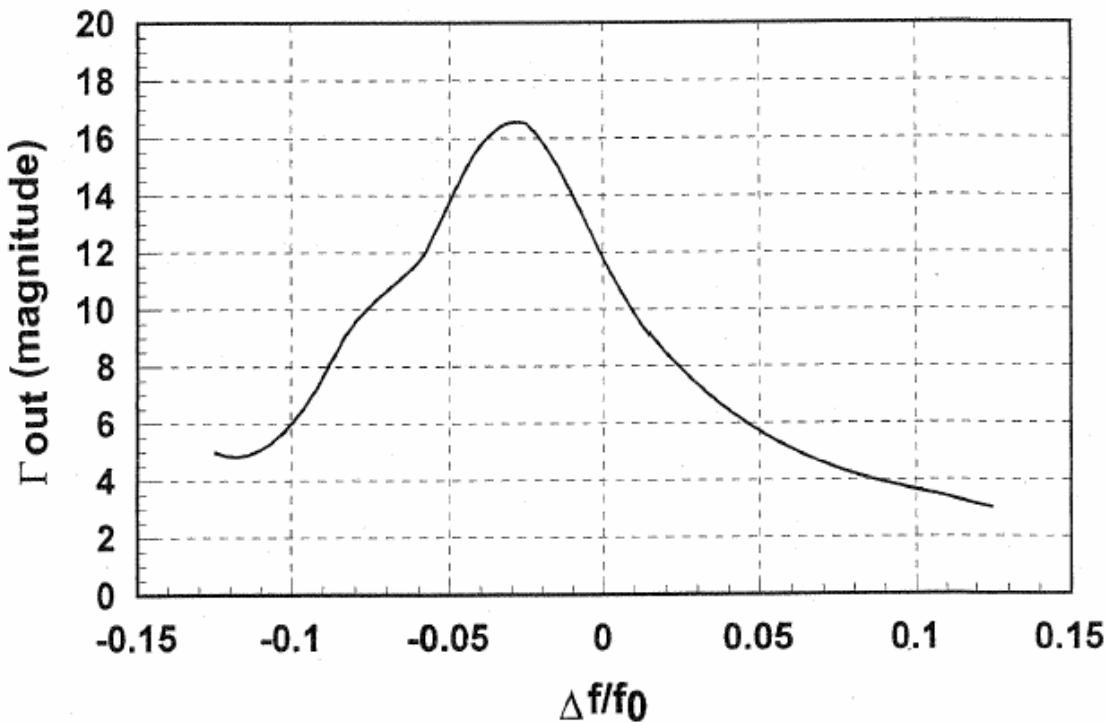

**13.7**

$$S_{11} = 1.2 \angle 150^\circ, S_{12} = 0.2 \angle 120^\circ, S_{21} = 3.7 \angle -72^\circ, S_{22} = 1.3 \angle -67^\circ$$

as in Example 12.4, maximize  $|\Gamma_{\text{out}}|$  by choosing  $S_{11}\Gamma_L \approx 1$ , since

$$\Gamma_{\text{out}} = S_{22} + \frac{S_{12}S_{21}\Gamma_L}{1 - S_{11}\Gamma_L}$$

Thus let  $\Gamma_L = 0.8 \angle -150^\circ$ . Then  $\Gamma_{\text{out}} = 15.88 \angle -99.3^\circ$ , and

$$Z_{\text{out}} = Z_0 \frac{1 + \Gamma_{\text{out}}}{1 - \Gamma_{\text{out}}} = -7.6 + j1.9 \Omega$$


$$Z_T = \frac{-R_{\text{out}}}{3} - jX_{\text{out}} = 2.53 - j1.9 \Omega \quad (Z_T = 0.0506 - j0.038)$$

Matching  $Z_T$  to the load impedance gives  $l_t = 0.031\lambda$  with a required stub susceptance of  $+j4$ . Thus  $l_s = 0.21\lambda$ .

at the dielectric resonator,  $\Gamma'_L = \Gamma_L e^{j\beta l_r} = (0.8 \angle -150^\circ) e^{j\beta l_r} = 0.8 \angle 180^\circ$ . Thus  $l_r = 0.4583\lambda$ .


$$z_L' = z_0 \frac{1 + \Gamma_L'}{1 - \Gamma_L'} = 5.55 R = N^2 R$$

$|\Gamma_{\text{out}}|$  vs  $f$  was calculated with SuperCompact, and is plotted below:

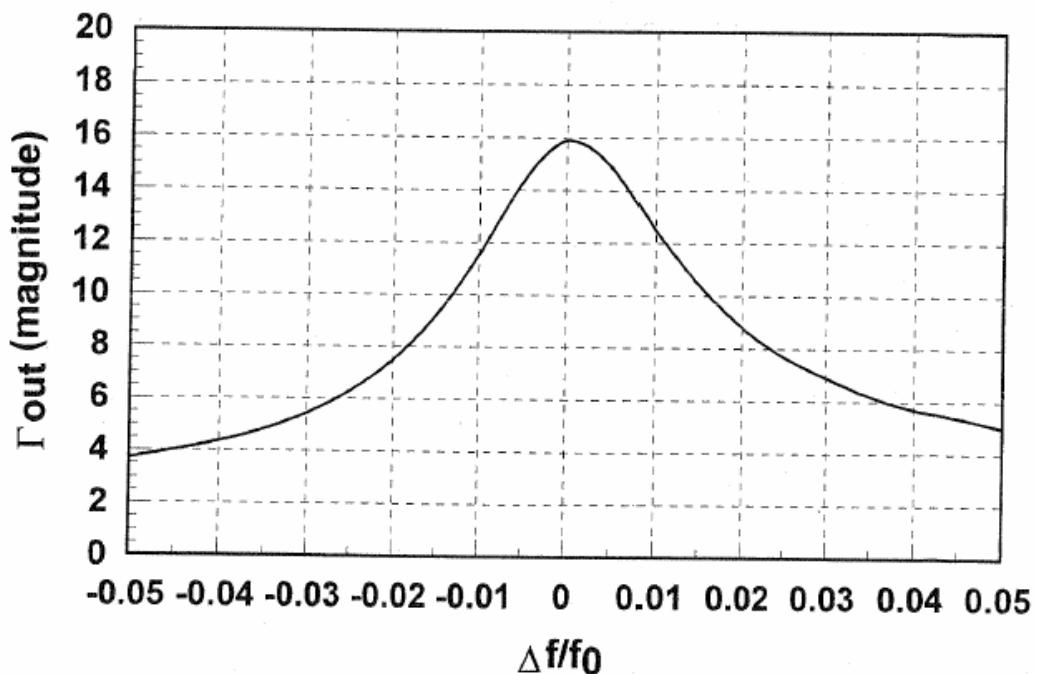

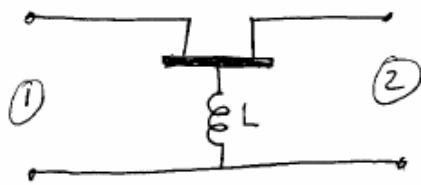**13.8**

common gate:  $S_{11} = .46 \angle 78^\circ$ ,  $S_{12} = .045 \angle 73^\circ$ ,  
 $S_{21} = 1.41 \angle -19^\circ$ ,  $S_{22} = 1.02 \angle -12^\circ$



Find L to minimize  $M$ ,  
using CAD.

$L (mH)$	$M$
0	.922
1	.088
2	-.928
3	-.927
5	-.89
1.5	-.88
2.5	-.931

13.9

From (12.49),

$$S_\phi = \frac{kT_0F}{P_0} \left( \frac{K\omega_\alpha\omega_h^2}{\Delta\omega^3} + \frac{\omega_h^2}{\Delta\omega^2} + \frac{K\omega_\alpha}{\Delta\omega} + 1 \right)$$


$$\mathcal{L}(f) = S_\phi/2.$$

For  $F=6\text{dB}=4$ ,  $f_0=100\text{MHz}$ ,  $Q=500$ ,  $P_0=10\text{dBm}=10\text{mW}$ ,  $K=1$ ,  
 $\omega_\alpha=50\text{kHz}$ ,  $\omega_h=f_0/2Q=100\text{kHz}$ ,  $\Delta f=f-f_0$ .

a short computer program was written to compute data for the plot shown below.


(a)  $\Delta f=1\text{MHz}$ ,  $S_\phi=-178\text{dBm}$ ,  $\mathcal{L}(1\text{MHz})=-181\text{dBc/Hz}$

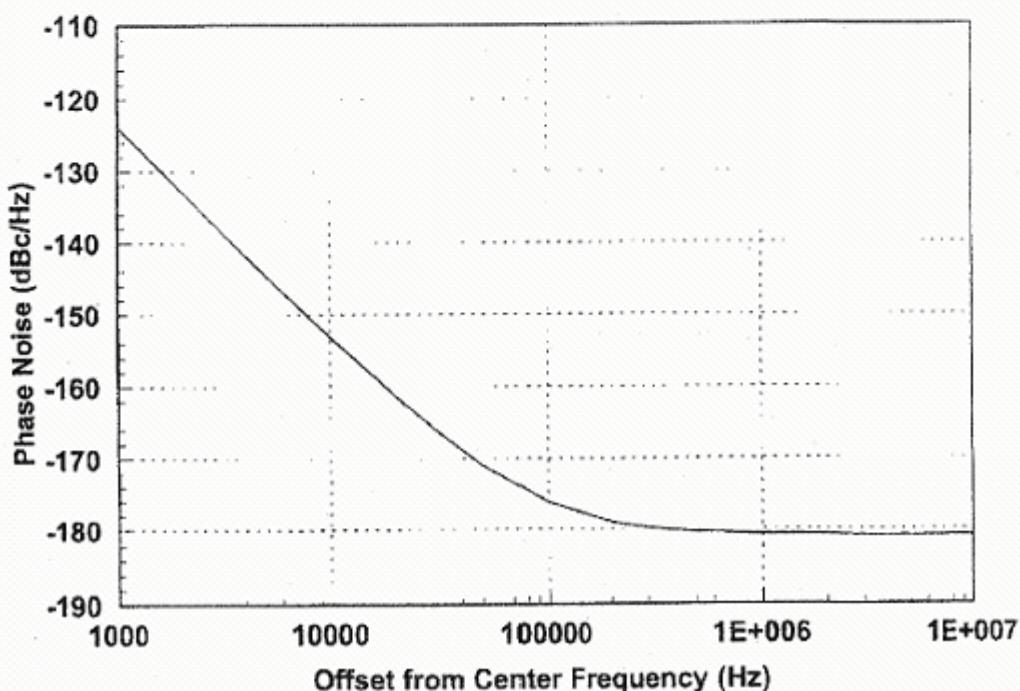(b)  $\Delta f=10\text{kHz}$ ,  $S_\phi=-150\text{dBm}$ ,  $\mathcal{L}(10\text{kHz})=-153\text{dBc/Hz}$



**13.10** This calculation is similar to that of Problem 13.9 , but with  $f_d = 200 \text{ kHz}$ . Plot shown below.

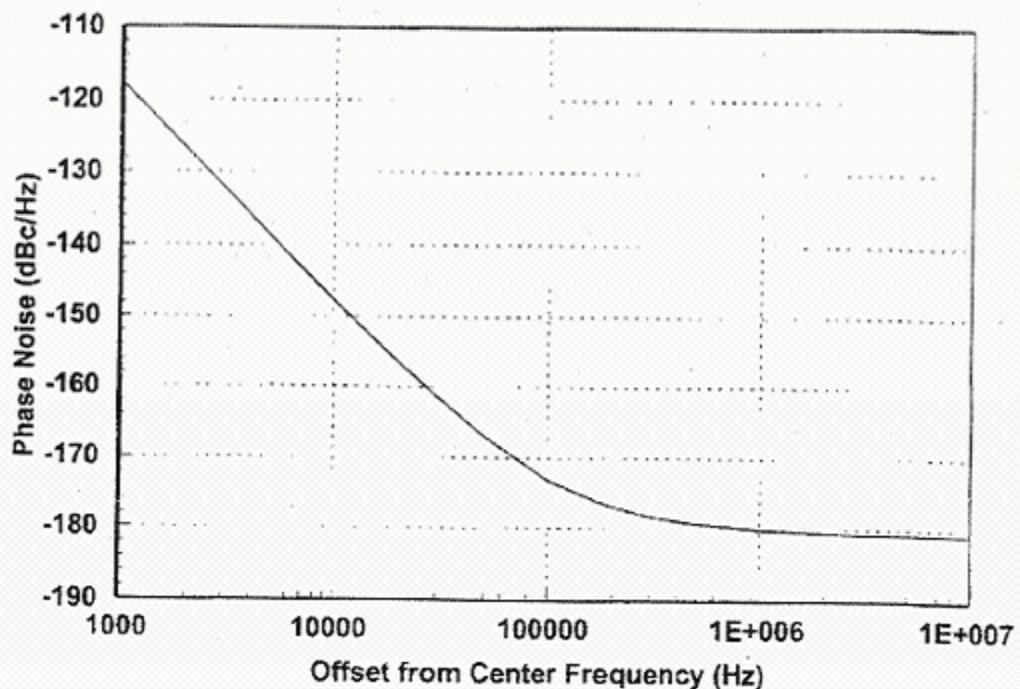- (a)  $\Delta f = 1 \text{ MHz} , S_\phi = -177 \text{ dBm} , \chi(1 \text{ MHz}) = -180 \text{ dBc/Hz}$
- (b)  $\Delta f = 10 \text{ kHz} , S_\phi = -144 \text{ dBm} , \chi(10 \text{ kHz}) = -147 \text{ dBc/Hz}$ .



**13.11**

If  $C$  is the desired signal level,  $I$  is the undesired signal level,  $S$  is the desired rejection ratio,  $\mathcal{L}(f)$  the phase noise, and  $B$  the filter bandwidth, then

$$S = \frac{C}{IB\mathcal{L}(f)}$$

In dB,

$$\mathcal{L}(f) = C(dBm) - I(dBm) - S(dB) - 10\log(B). \checkmark$$

**13.12**

$$B = 12 \text{ kHz}, \quad S = 80 \text{ dB}, \quad C = I$$

From (13.50),

$$\begin{aligned} \mathcal{L}(30 \text{ kHz}) &= C(dBm) - I(dBm) - S(dB) - 10\log(B) \\ &= -80 \text{ dB} - 10\log(12 \times 10^3) \\ &= -121 \text{ dBc/Hz}. \end{aligned}$$

**13.13**


Assume excitation at  $f_1, f_2$ ; o.c. at all other frequencies except  $f_3 = f_1 + f_2$ . Then all power terms are zero except for  $n = \pm 1, m = 0$ ;  $n = 0, m = \pm 1$ ; and  $n = m = \pm 1$ . So the Manley-Rowe relations give,

$$\frac{P_{10}}{\omega_1} + \frac{P_{11}}{\omega_1 + \omega_2} = 0$$

$$\frac{P_{01}}{\omega_2} + \frac{P_{11}}{\omega_1 + \omega_2} = 0$$

For sources at  $f_1, f_2$ , we have  $P_{10} > 0$  and  $P_{01} > 0$ . Then  $P_{11} < 0$ , representing power at  $f_3 = f_1 + f_2$  ( $m = n = 1$ ). Conversion gain is then,

$$G_C = -\frac{P_{11}}{P_{10}} = \frac{\omega_1 + \omega_2}{\omega_1} = 1 + \omega_2/\omega_1. \checkmark$$

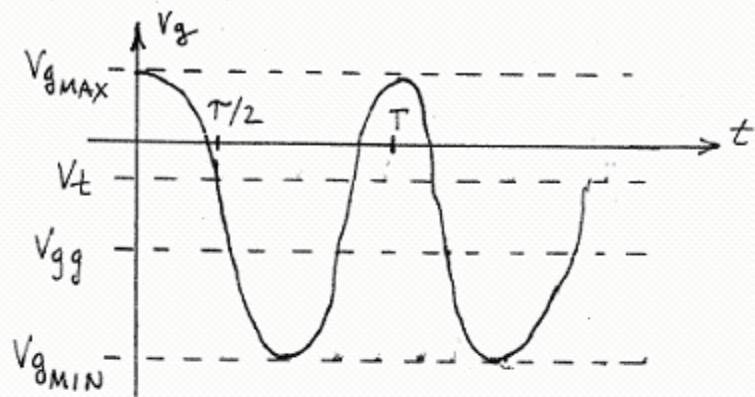**13.14**

$$V_g = V_{gg} + V_g \cos \frac{2\pi t}{T}$$

$$V_g = (V_{g\text{MAX}} - V_{g\text{MIN}})/2 \quad (\text{PEAK})$$

$$V_{gg} = (V_{g\text{MAX}} + V_{g\text{MIN}})/2 \quad (\text{AVG})$$

$$V_t = V_{gg} + V_g \cos \frac{\pi t}{T} \quad \text{solve for } \cos \frac{\pi t}{T}:$$

$$\cos \frac{\pi t}{T} = \frac{V_t - V_{gg}}{V_g} = \frac{2V_t - V_{g\text{MAX}} - V_{g\text{MIN}}}{V_{g\text{MAX}} - V_{g\text{MIN}}} \quad \checkmark$$

**13.15**

$$V_{RF}(t) = V_{RF} [\cos(\omega_{LO} - \omega_{IF})t + \cos(\omega_{LO} + \omega_{IF})t]$$

$$V_{LO}(t) = V_{LO} \cos \omega_{LO} t$$

After mixing and LPF:

$$V_{OUT}(t) = \frac{K V_{RF} V_{LO}}{2} [\cos \omega_{IF} t + \cos \omega_{IF} t] = K V_{RF} V_{LO} \cos \omega_{IF} t$$

(both sidebands convert to same IF)

13.16

$$i(t) = e^{3v(t)} - 1 \quad , \quad v(t) = 0.1 \cos \omega_1 t + 0.1 \cos \omega_2 t$$

$$i(t) = i|_{v=0} + \frac{di}{dv}|_{v=0} v + \frac{d^2 i}{dv^2}|_{v=0} \frac{v^2}{2} + \frac{d^3 i}{dv^3}|_{v=0} \frac{v^3}{6} + \dots$$

$$i|_{v=0} = 0 ; \quad \frac{di}{dv}|_{v=0} = 3 ; \quad \frac{d^2 i}{dv^2}|_{v=0} = 9 ; \quad \frac{d^3 i}{dv^3}|_{v=0} = 27.$$

So,

$$i(t) = 3v + 4.5v^2 + 4.5v^3 + \dots$$

$$v^2 = .01 [\cos^2 \omega_1 t + 2 \cos \omega_1 t \cos \omega_2 t + \cos^2 \omega_2 t]$$

$$= .01 [1 + \frac{1}{2} \cos^2 \omega_1 t + \frac{1}{2} \cos 2\omega_2 t + \cos(\omega_1 + \omega_2)t + \cos(\omega_1 - \omega_2)t]$$

$$v^3 = .001 [\cos^3 \omega_1 t + 3 \cos^2 \omega_1 t \cos \omega_2 t + 3 \cos \omega_1 t \cos^2 \omega_2 t + \cos^3 \omega_2 t]$$

$$= .001 [\frac{1}{4} \cos 3\omega_1 t + \frac{3}{4} \cos \omega_1 t + \frac{3}{2} \cos \omega_2 t + \frac{3}{4} \cos(2\omega_1 - \omega_2)t]$$

$$+ \frac{3}{4} \cos(2\omega_1 + \omega_2)t + \frac{3}{2} \cos \omega_1 t + \frac{3}{4} \cos(\omega_1 - 2\omega_2)t$$

$$+ \frac{3}{4} \cos(\omega_1 + 2\omega_2)t + \frac{3}{4} \cos 2\omega_2 t + \frac{3}{4} \cos 3\omega_2 t]$$

$\omega$	I	
0	(4.5)(.01)	= 0.045 ✓
$\omega_1, \omega_2$	$(3)(.1) + (4.5)(.001)(\frac{3}{2} + \frac{3}{4})$	= 0.3101 ✓
$2\omega_1, 2\omega_2$	$(4.5)(.01)(\frac{1}{2})$	= 0.0225 ✓
$3\omega_1, 3\omega_2$	$(4.5)(.001)(\frac{1}{4})$	= 0.00113 ✓
$\omega_1 + \omega_2$	$(4.5)(.01)(1)$	= 0.045 ✓
$\omega_1 - \omega_2$	$(4.5)(.01)(1)$	= 0.045 ✓
$2\omega_1 - \omega_2$	$(4.5)(.001)(\frac{3}{4})$	= 0.003375 ✓
$2\omega_1 + \omega_2$	$(4.5)(.001)(\frac{3}{4})$	= 0.003375 ✓
$\omega_1 - 2\omega_2$	$(4.5)(.001)(\frac{3}{4})$	= 0.003375 ✓
$\omega_1 + 2\omega_2$	$(4.5)(.001)(\frac{3}{4})$	= 0.003375 ✓

**13.17**

$$f_{RF} = 1800 \text{ MHz}, \quad f_{IF} = 87 \text{ MHz}$$

possible LO frequencies are

$$f_{LO} = f_{RF} \pm f_{IF} = 1887 \text{ MHz}, 1713 \text{ MHz}$$


image frequency for  $f_{LO} = 1887 \text{ MHz}$  is

$$f_{IM} = f_{LO} + f_{IF} = 1974 \text{ MHz}$$

image frequency for  $f_{LO} = 1713 \text{ MHz}$  is


$$f_{IM} = f_{LO} - f_{IF} = 1626 \text{ MHz}$$

13.18

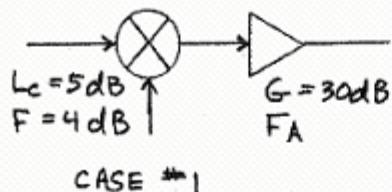

CASE #1

$$F_c = 2.51 + \frac{F_A - 1}{1/3.16}$$

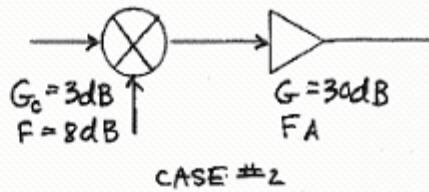

CASE #2

$$F_c = 6.31 + \frac{F_A - 1}{2.0}$$

$F_A (\text{dB})$	$F_c (\#1) \text{dB}$	$F_c (\#2) \text{dB}$
0	4.0	8.0
3	7.5	8.3
5	9.7	8.7
10	14.9	10.3


$$3 \text{ dB} = 2.0$$

$$4 \text{ dB} = 2.51$$

$$5 \text{ dB} = 3.16$$


$$8 \text{ dB} = 6.31$$

RESULTS ARE PLOTTED BELOW:

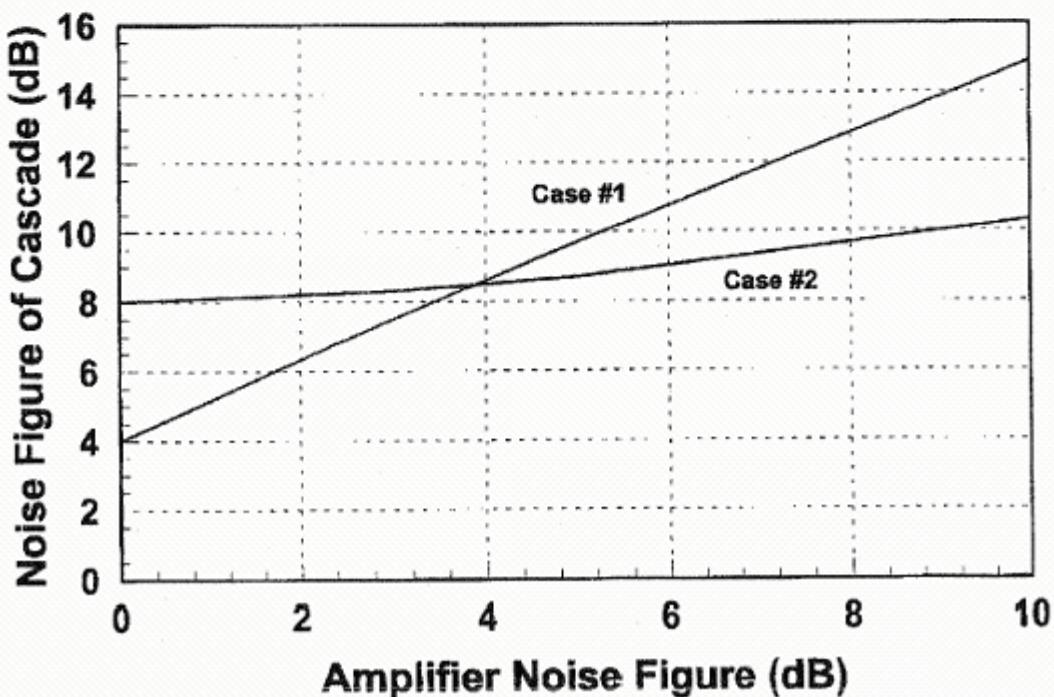


13.19

DSB

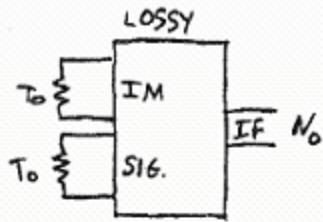

$$N_o = N_{\text{ADDED}} + \frac{kT_o B}{L} + \frac{kT_o B}{L}$$

(B is SSB)

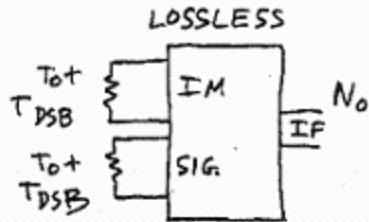


$$N_o = \frac{2kT_o B}{L} (T_o + T_{DSB})$$


$$\therefore N_{\text{ADDED}} = \frac{2kT_o B}{L} T_{DSB}$$

$$F_{DSB} = \frac{S_i N_o}{S_o N_i} = \frac{N_o L}{2kT_o B} = 1 + \frac{T_{DSB}}{T_o} \quad (\text{INPUT NOISE} - N_i = 2kT_o B)$$

SSB

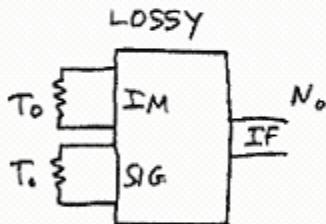
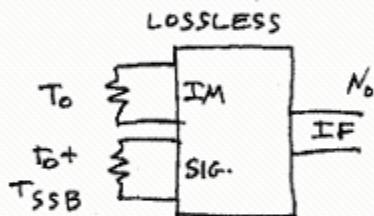
$$N_o = N_{\text{ADDED}} + \frac{2kT_o B}{L}$$



$$N_o = \frac{2kBT_o}{L} + \frac{kBT_{SSB}}{L}$$


$$\therefore T_{SSB} = \frac{L N_{\text{ADDED}}}{k B}$$

$$\underline{T_{SSB} = 2 T_{DSB}} \quad \checkmark$$

$$F_{SSB} = \frac{S_i N_o}{S_o N_i} = \frac{N_o L}{2kT_o B} = 2 + \frac{T_{SSB}}{T_o} = 2 \left( 1 + \frac{T_{DSB}}{T_o} \right) = 2 F_{DSB} \quad \checkmark$$

$$(\text{INPUT NOISE} - N_i = kT_o B)$$

13.20

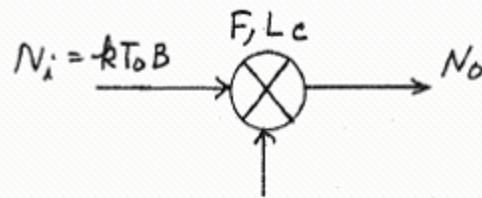

$$N_o = \underbrace{\frac{k T_0 B}{L_c}}_{\text{INPUT NOISE}} + \underbrace{\frac{k T_0 B(F-1)}{L_c}}_{\text{MIXER NOISE}} = \frac{k T_0 B F}{L_c} \quad \checkmark$$

13.21

$$v_1 = V_0 \cos \omega t \quad ; \quad v_2 = V_0 \cos(\omega t + \theta)$$

as in (12.112)-(12.113), the diode currents in a mixer using a quadrature hybrid will be,

$$\begin{aligned} i_1 &= k V_0^2 [\cos(\omega t - \pi/2) + \cos(\omega t + \theta - \pi)]^2 \\ &= k V_0^2 [\sin \omega t - \cos(\omega t + \theta)]^2 \end{aligned}$$

$$\begin{aligned} i_2 &= -k V_0^2 [\cos(\omega t - \pi) + \cos(\omega t + \theta - \pi/2)]^2 \\ &= -k V_0^2 [-\cos \omega t + \sin(\omega t + \theta)]^2 \end{aligned}$$

Low-pass filtering leaves the following DC components:

$$i_1 = k V_0^2 (1 + \frac{1}{2} \sin \theta)$$

$$i_2 = -k V_0^2 (1 - \frac{1}{2} \sin \theta)$$

so the output is  $i_1 + i_2 = k V_0^2 \sin \theta \quad \checkmark$

If a mixer with a  $180^\circ$  hybrid is used, the diode currents become,

$$i_1 = k V_0^2 [\cos \omega t + \cos(\omega t + \theta)]^2$$

$$i_2 = -k V_0^2 [\cos \omega t - \cos(\omega t + \theta)]^2$$


Then low-pass filtering leaves the following DC components:

$$i_1 = k V_0^2 (1 + \frac{1}{2} \cos \theta)$$

$$i_2 = -k V_0^2 (1 - \frac{1}{2} \cos \theta)$$

so the output is  $i_1 + i_2 = k V_0^2 \cos \theta \quad \checkmark$

13.22

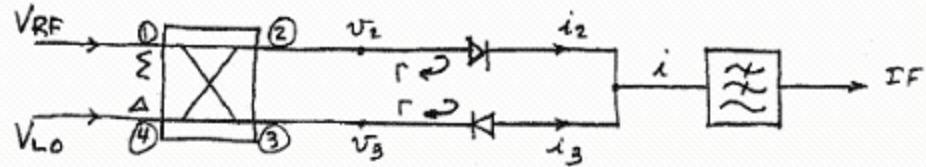

$$[S] = \frac{-j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 & 0 \\ 1 & 0 & 0 & -1 \\ 1 & 0 & 0 & 1 \\ 0 & -1 & 1 & 0 \end{bmatrix} \quad \text{let } v_{RF}(t) = V_{RF} \cos(\omega_{RF} t) = v_i(t) \\ v_{LO}(t) = V_{LO} \cos(\omega_{LO} t) = v_4(t)$$

Then the diode voltages are,

$$v_2(t) = \frac{1}{\sqrt{2}} V_{RF} \cos(\omega_{RF} t - 90^\circ) + \frac{1}{\sqrt{2}} V_{LO} \cos(\omega_{LO} t + 90^\circ)$$

$$v_3(t) = \frac{1}{\sqrt{2}} V_{RF} \cos(\omega_{RF} t - 90^\circ) + \frac{1}{\sqrt{2}} V_{LO} \cos(\omega_{LO} t - 90^\circ)$$

Assume  $i_2 = k v_2^2$ ,  $i_3 = -k v_3^2$ .  $\omega_{IF} = \omega_{RF} - \omega_{LO}$ .

Then, after LP filtering, the diode currents are,

$$i_2 = \frac{k}{4} V_{RF} V_{LO} \cos(\omega_{RF} t - 90^\circ - \omega_{LO} t - 90^\circ) = \frac{-k}{4} V_{RF} V_{LO} \cos \omega_{IF} t.$$

$$i_3 = -\frac{k}{4} V_{RF} V_{LO} \cos(\omega_{RF} t - 90^\circ - \omega_{LO} t + 90^\circ) = -\frac{k}{4} V_{RF} V_{LO} \cos \omega_{IF} t.$$

So the IF output current is  $i(t) = -\frac{k}{2} V_{RF} V_{LO} \cos \omega_{IF} t$  ✓

AT RF INPUT:

$$V_2^+ = \Gamma V_2^- = \frac{-j}{\sqrt{2}} \Gamma V_{RF}^+ ; V_3^+ = \Gamma V_3^- = \frac{-j}{\sqrt{2}} \Gamma V_{RF}^+$$

$$V_{RF}^{\Sigma} = V_i^- = V_2^+ (-j/\sqrt{2}) + V_3^+ (-j/\sqrt{2}) = -\underline{\Gamma V_{RF}^+} \quad \checkmark$$

$$V_{RF}^{\Delta} = V_4^- = V_2^+ (j/\sqrt{2}) + V_3^+ (-j/\sqrt{2}) = \underline{0} \quad \checkmark$$

AT LO INPUT:

$$V_2^+ = \Gamma V_2^- = \frac{j}{\sqrt{2}} \Gamma V_{LO}^+ ; V_3^+ = \Gamma V_3^- = \frac{j}{\sqrt{2}} \Gamma V_{LO}^+$$

$$V_{LO}^{\Sigma} = V_4^- = V_2^+ (j/\sqrt{2}) + V_3^+ (-j/\sqrt{2}) = \underline{0} \quad \checkmark$$

$$V_{LO}^{\Delta} = V_4^- = V_2^+ (j/\sqrt{2}) + V_3^+ (-j/\sqrt{2}) = -\underline{\Gamma V_{LO}^+} \quad \checkmark$$

Assume now that

$$v_{LO}(t) = V_{LO}^{(2)} \cos 2\omega_{LO} t.$$

Then after LPF,


$$V_2^2(t) = \frac{1}{\sqrt{2}} V_{RF} V_{L0}^{(2)} \cos(\omega_{RF} t + 2\omega_{L0} t + 90^\circ) + \frac{1}{\sqrt{2}} V_{RF} V_{L0}^{(2)} \cos(\omega_{RF} t - 2\omega_{L0} t + 90^\circ)$$

$$V_3^2(t) = \frac{1}{\sqrt{2}} V_{RF} V_{L0}^{(2)} \cos(\omega_{RF} t + 2\omega_{L0} t + 90^\circ) + \frac{1}{\sqrt{2}} V_{RF} V_{L0}^{(2)} \cos(\omega_{RF} t - 2\omega_{L0} t + 90^\circ)$$

Then forming

$$i(t) = k(V_2^2 - V_3^2) \Big|_{LPF} = 0 \text{ for } \omega_{RF} \pm 2\omega_{L0} \text{ frequencies.}$$

13.23

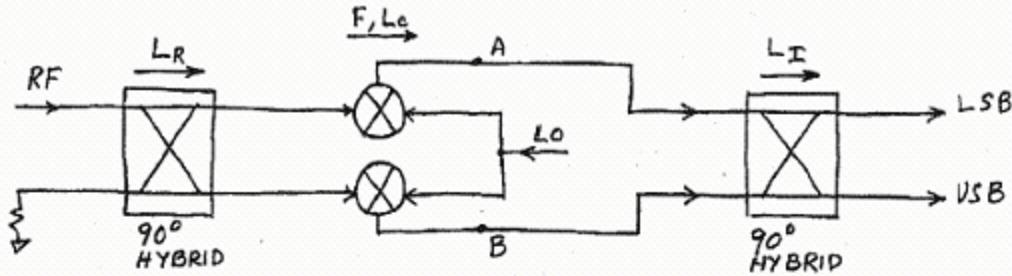


The noise power due to the RF hybrid and the mixer, ref. to IF output of mixer, is

$$N_A = N_B = \frac{kB}{L_c} [T_0 + (F-1) T_0] = \frac{kBT_0 F}{L_c},$$

since the noise power output of the matched hybrid is  $kT_0 B$ . The total noise power output is (at either LSB or USB),

$$N_o = \frac{N_A}{2L_I} + \frac{N_B}{2L_I} + \frac{N_{\text{added}}}{2L_I} = \frac{kBT_0 F}{L_I L_c} + \frac{N_{\text{added}}}{2L_I}$$

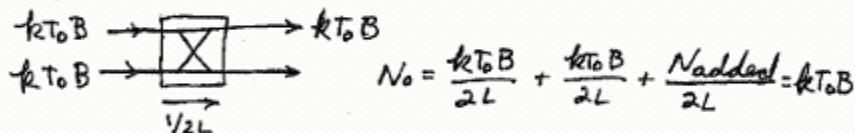$N_{\text{added}}$  is the output noise power of the IF hybrid when not terminated at second input port :



$$\text{Thus } N_{\text{added}} = 2kT_0 B(L-1)$$

$$\text{So, } N_o = \frac{kBT_0 F}{L_I L_c} + kT_0 B \left(1 - \frac{1}{L_I}\right); S_o = \frac{4S_i}{L_c} \frac{1}{4L_I L_R} = \frac{S_i}{L_c L_I L_R}$$

$$N_i = kT_0 B$$

And then,

$$F_{\text{TOT}} = \frac{S_i N_o}{S_o N_i} = \frac{L_c L_I L_R}{kT_0 B} \left[ \frac{kBF T_0}{L_I L_c} + kT_0 B \left(1 - \frac{1}{L_I}\right) \right] = \underline{\underline{FL_R + L_c L_R L_I - L_c L_R}}$$

CHECK: if  $L_R = L_I = 1$ ,  $F_{\text{TOT}} = F + 2L_c - 2L_c = F$  ✓ (mixer noise only)

CHECK: if  $F = L_c$  (passive mixer loss only),  $F_{\text{TOT}} = L_c L_I L_R$  ✓

(The cascade noise figure formula can be used to obtain the same result if we set  $F_R = L_R$ ,  $F_I = L_I$ .)

## Chapter 14

### 14.1

Data on satellite fading at L-band in various environments can be found in “Handbook of Propagation Effects for Vehicular and Personal Mobile Satellite Systems”, by J. Goldhirsh and W. Vogel, and in “Satellite Systems for Personal and Broadband Communications”, by E. Lutz, M. Werner, and A. Jahn, as well as from various other sources. Typically, one can expect fading levels of 15 to 20 dB for domestic and commercial buildings, for 95% link availability. For vehicles, the fading levels can be 20 dB or more. On the other hand, a line-of-sight system (as when the handset is used outdoors with little or no blockage to the satellite) would require a link margin of 0 dB in principal, although a few dB of margin would provide a more robust system. In view of this data, it is not clear why the Iridium system was designed with a link margin of 16 dB.

14.2

$$F_\theta(\theta, \phi) = A \sin^2 \theta \cos \phi$$



Main beam at  $\theta = 90^\circ, \phi = 0^\circ \text{ or } 180^\circ$

3 dB points at  $\theta = 90^\circ$  (az) plane :

$$\cos \phi = 0.707 \Rightarrow \phi = 45^\circ \text{ or } 135^\circ$$

$$\text{HPBW}_\phi = 135 - 45 = 90^\circ \quad \checkmark$$

3 dB points in  $\phi = 0^\circ$  (el) plane :

$$\sin^2 \theta = 0.707 \Rightarrow \theta = \sin^{-1} \sqrt{0.707} = 57.2^\circ, 122.8^\circ$$

$$\text{HPBW}_\theta = 122.8 - 57.2 = 65.6^\circ$$

$$\begin{aligned} \int_{\theta=0}^{\pi} \int_{\phi=0}^{2\pi} F^2(\theta, \phi) \sin \theta d\theta d\phi &= \int_{\theta=0}^{\pi} \int_{\phi=0}^{2\pi} \sin^5 \theta \cos^2 \phi d\theta d\phi \\ &= \left( \frac{16}{15} \right) \pi \end{aligned}$$

$$D = \frac{4\pi F_{\text{MAX}}^2}{\iint} = \frac{15}{4} = 3.75 = 5.74 \text{ dB}$$

linearly polarized in vertical direction.

**14.3**

$$F_\theta(\theta, \phi) = \begin{cases} A \sin \theta & \text{for } 0 \leq \theta \leq \pi/2 \\ 0 & \text{otherwise} \end{cases}$$

$$D = \frac{4\pi F_{MAX}^2}{\int_{\theta=0}^{\pi} \int_{\phi=0}^{2\pi} F_\theta^2(\theta, \phi) \sin \theta d\theta d\phi} = \frac{4\pi}{2\pi \int_{\theta=0}^{\pi/2} \sin^3 \theta d\theta} = \frac{4\pi}{2\pi (\frac{2}{3})}$$

$$= 3 = \underline{4.8 \text{ dB}} \quad (\text{verified with PCAAD})$$

**14.4**

$$f = 12.4 \text{ GHz}, \quad \text{Diam} = 18'' = 0.457 \text{ m}, \quad \eta_{ap} = 65\%$$

$$\lambda = \frac{c}{f} = 0.0242 \text{ m} \quad \checkmark$$

$$A = \pi R^2 = \pi \left( \frac{\text{Diam}}{2} \right)^2 = 0.164 \text{ m}^2$$

From (14.13)

$$D = \eta_{ap} \frac{4\pi A}{\lambda^2} = (0.65) \frac{4\pi (0.164)}{(0.0242)^2} = 2287 = \underline{\underline{33.6 \text{ dB}}} \quad \checkmark$$

**14.5**  $f = 38 \text{ GHz}, G = 39.0 \text{ dB}, \text{Diam} = 12.0'', \eta_{\text{rad}} = 90\%$

a) From (14.11),  $D = \frac{G}{\eta_{\text{rad}}} = \frac{10^{39/10}}{0.9} = 8,826.$

From (14.13),  $D = \frac{4\pi A}{\lambda^2} \eta_{\text{ap}}$

$$\eta_{\text{ap}} = \frac{\lambda^2 D}{4\pi A} = \left( \frac{C}{\pi f \text{Diam}} \right)^2 D = \underline{\underline{60\%}}$$

b) From (14.9),  $D = \frac{32,400}{\theta_3^2}$

$$\theta_3 = \sqrt{\frac{32,400}{8826}} = \underline{\underline{1.9^\circ}}$$


**14.6**

From (14.18),  $T_A = \eta_{\text{rad}} T_b + (1 - \eta_{\text{rad}}) T_p$   
 $= (T_b - T_p) \eta_{\text{rad}} + T_p$

Thus,

$$\eta_{\text{rad}} = \frac{T_A - T_p}{T_b - T_p} = \frac{105 - 290}{5 - 290} = \underline{\underline{65\%}}$$

**14.7**

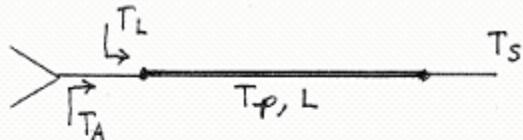

$$T_A = \eta_{\text{rad}} T_b + (1 - \eta_{\text{rad}}) T_p \quad (\text{at antenna}) \quad (14.18)$$

$$T_L = (L-1) T_p \quad (\text{at antenna}) \quad (10.15)$$

$$T_s = \frac{1}{L} (T_A + T_L) \quad (\text{at output})$$

$$= \frac{1}{L} [\eta_{\text{rad}} T_b + (1 - \eta_{\text{rad}}) T_p] + \frac{(L-1)}{L} T_p \quad (14.20) \checkmark$$

**14.8**

$$T = \eta_{\text{rad}} T_b + (1 - \eta_{\text{rad}}) T_p + T_R$$

$$T_b = 50K$$

$$T_p = 290K$$

$$F = 1.1 \text{ dB} = 1.29$$

$$L = 2.5 \text{ dB} = 1.78$$

$$G = 33.5 \text{ dB} = 2240$$

The noise temperature of the receiver is,

$$T_R = (F - 1) T_0 = (1.29 - 1)(290) = 84K$$

The efficiency of the array is,

$$\eta_{\text{rad}} = \frac{1}{L} = \frac{1}{1.78} = 0.56$$

Thus,

$$T = (0.56)(50) + (1 - 0.56)(290) + 84 = \underline{\underline{240K}}$$

$$\text{Then, } \frac{G}{T} (\text{dB}) = 10 \log \frac{2240}{240} = \underline{\underline{9.7 \text{ dB/K}}}$$

This value is well below the desired minimum of 12 dB/K.

**14.9**

Solving (14.23) for G gives,

$$G = \frac{4\pi S R^2}{P_t} = \frac{4\pi (7.5 \times 10^{-3})(300)^2}{85} = 100 = \underline{\underline{20 \text{ dB}}}$$

**14.10**

1) RADIO LINK:  $f = 28 \text{ GHz} \Rightarrow \lambda = 0.0107 \text{ m}$ ;  $G_t = G_r = 25 \text{ dB} = 316$ .

Let  $P_r = 1 \text{ W}$ . Then,

$$P_t = \frac{(4\pi R)^2}{P_r G_t G_r \lambda^2} = \frac{(4\pi)^2 (5000)^2}{(1)(316)^2 (0.0107)^2} = 3.45 \times 10^8 \text{ W}$$

$$\text{ATTENUATION} = 10 \log \frac{P_r}{P_t} = 10 \log \frac{1}{3.45 \times 10^8} = -85.4 \text{ dB } \checkmark$$

2) WIRED LINK:  $\alpha = 0.05 \text{ dB/m} = 0.0057 \text{ nepot/m}$ ;  $4 \times 30 \text{ dB REPEATERS}$ .



$$\begin{aligned} \text{ATTENUATION OF LINE} &= 10 \log e^{-2\alpha R} \\ &= 10 \log e^{-2(0.0057)(5000)} \\ &= -250 \text{ dB} \end{aligned}$$

$$\text{TOTAL LOSS} = -250 + 4(30) = -130 \text{ dB } \checkmark$$

The radio link has much less link loss than the wired link, and will thus require less transmit power.

**14.11**

GSM downlink, 935-960 MHz, EIRP = 20 W,  
 $G_r = 0 \text{ dB} \downarrow$ ,  $T = 450 \text{ K}$ , SNR = 10 dB, LM = 30 dB,  
 $B = 200 \text{ kHz}$ ,  $F_R = 8 \text{ dB}$ .

$$f = 947.5 \text{ MHz} \Rightarrow \lambda = 0.317 \text{ m}, G_r = 0 \text{ dB} \downarrow = 1$$

$$F_R = 8 \text{ dB} = 6.31, \text{ SNR} = 10 \text{ dB} = 10.$$

$$T_{sys} = T_A + T_R = T_A + (F_R - 1)T_o = 450 + (6.31 - 1)(290)$$

$$= 1990 \text{ K}$$

$$N_0 = kT_{sys}B = (1.38 \times 10^{-23})(1990)(200 \times 10^3)$$

$$= 5.5 \times 10^{-15} \text{ W} = -112.6 \text{ dBm} \text{ (at rec. input)}$$

$$S_0(\text{dBm}) = \left( \frac{S_0}{N_0} \right) + N_0 + LM = 10 - 112.6 + 30 = -72.6 \text{ dBm}$$

$$= 5.5 \times 10^{-11} \text{ W}$$

$$R = \sqrt{\frac{P_t G_t G_r \lambda^2}{(4\pi)^2 S_0}} = \sqrt{\frac{(20)(1)(0.317)^2}{(4\pi)^2 (5.5 \times 10^{-11})}} = 15.2 \text{ km}$$

(stated base station range for GSM 900 is 2-20 km)

**14.12** Carrier power at receiver:

$$C = S_i G_A G/L \quad (S_i \text{ ref. to antenna w/ } 0 \text{ dB})$$

at input to amplifier:

$$T_e = T_A + (F-1)T_0 + (L-1)T_0/G$$

The noise power at input to receiver:

$$N = kT_e G/L = \frac{C}{(C/N)}$$

$$L = 25 \text{ dB} = 316.2$$

$$S_i = 1 \times 10^{-16}$$

$$G_A = 5 \text{ dB} = 3.16$$

$$\frac{C}{N} = 32 \text{ dB} = 1580.$$

$$G = 10 \text{ dB} = 10$$

So,

$$T_e = \frac{C L}{k(\frac{C}{N}) G} = \frac{S_i G_A}{k(\frac{C}{N})}$$

$$\begin{aligned} F &= 1 + \frac{T_e}{T_0} - \frac{T_A}{T_0} - \frac{(L-1)}{G} = 1 + \frac{S_i G_A}{k T_0 (\frac{C}{N})} - \frac{T_A}{T_0} - \frac{(L-1)}{G} \\ &= 1 + \frac{(1 \times 10^{-16})(3.16)}{(1.38 \times 10^{-23})(290)(1.58 \times 10^3)} - \frac{300}{290} - \frac{(316.2-1)}{10} \\ &= 18.4 = \underline{\underline{12.6 \text{ dB}}} \end{aligned}$$

**14.13**

$$N_0 = kT_b B = S_0 \quad \text{for } S_0/N_0 = 0 \text{ dB}$$

$$kT_b B = P_r = \frac{P_t G^2 \lambda^2}{(4\pi R)^2}$$

$$R = \sqrt{\frac{P_t G^2 \lambda^2}{16\pi^2 k T_b B}} = \sqrt{\frac{(1000)(2.51)^2 (4.48)^2}{16\pi^2 (1.38 \times 10^{-23})(4)(4 \times 10^6)}} = 1.9 \times 10^9 \text{ m}$$

$$\text{If SNR} = 30 \text{ dB} = 1000, \quad R = 6.0 \times 10^7 \text{ m}$$

$R_{VENUS} = 4.2 \times 10^9 \text{ m}$ , so the signal will not even reach the nearest planet.

14.14

Marsiner 10, PSK,  $P_b = 0.05$ ,  $(E_b/n_0) = 1.4 \text{ dB}$ ,  
 $R = 1.6 \times 10^8 \text{ km}$ ,  $f = 2.295 \text{ GHz}$ .  $G_t = 27.6 \text{ dB}$   
 $P_t = 16.8 \text{ W}$ ,  $G_r = 61.3 \text{ dB}$ ,  $T_{\text{sys}} = 13.5 \text{ K}$


$$\lambda = 0.1307 \text{ m}, P_t = 12.25 \text{ dBW}, E_b/n_0 = 1.38$$

$$L_o = 20 \log (4\pi R/\lambda) = 263.7 \text{ dB}.$$

$$P_r = P_t + G_t - L_o + G_r = -162.6 \text{ dBW} = 5.56 \times 10^{-17} \text{ W} \checkmark$$

$$n_0 = k T_{\text{sys}}$$

$$\text{From (14.36), } R_b = \left( \frac{P_r}{n_0} \right) \left( \frac{n_0}{E_b} \right) = \frac{5.56 \times 10^{-17}}{(1.38 \times 10^{-23})(13.5)} \left( \frac{1}{1.38} \right)$$
$$= \underline{216 \text{ kbps}} \checkmark$$

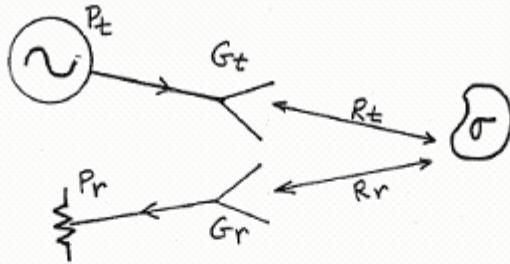**14.15**

From (14.23) the power density incident on the target is,

$$S = \frac{P_t G_t}{4\pi R_t^2}$$


The scattered power density at the receiver is, from (14.40),

$$S_r = \frac{P_t G_t \sigma(\theta_t, \phi_t; \theta_r, \phi_r)}{(4\pi)^2 R_t^2 R_r^2},$$

where  $\sigma(\theta_t, \phi_t; \theta_r, \phi_r)$  is the radar cross-section of the target seen at  $\theta_r, \phi_r$  with an incident wave at  $\theta_t, \phi_t$ .

Then the received power can be found using (14.14):

$$P_r = P_t \frac{G_t G_r \lambda^2 \sigma(\theta_t, \phi_t; \theta_r, \phi_r)}{(4\pi)^3 R_t^2 R_r^2} \quad \checkmark$$

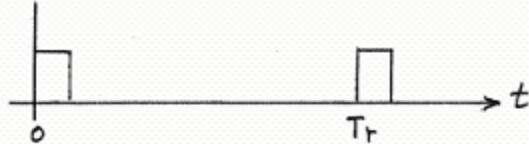**14.16**

When a pulse is transmitted at  $t=0$ , the return pulse must come back before the next pulse is transmitted at  $t=Tr$ , to avoid an ambiguity in range. The round-trip time for a pulse return is,

$$T = 2R/c,$$

so the maximum unambiguous range is,

$$R_{MAX} = \frac{CTr}{2} = \frac{C}{2f_r} \quad \checkmark$$

**14.17**

From (14.43) the doppler frequencies are,

$$f_d(\text{MIN}) = \frac{2V_{\text{MIN}} f_0}{c} = \frac{2(1 \text{ m/sec})(12 \text{ GHz})}{3 \times 10^8 \text{ m/sec}} = 80 \text{ Hz}$$

$$f_d(\text{MAX}) = \frac{2V_{\text{MAX}} f_0}{c} = \frac{2(20 \text{ m/sec})(12 \text{ GHz})}{3 \times 10^8 \text{ m/sec}} = 1.6 \text{ kHz}$$

so the necessary passband is 80-1600 Hz.

**14.18**


From (14.41) the received power is,

$$P_r = P_t \frac{G^2 \lambda^2 \sigma}{(4\pi)^3 R^4} = 1000 \frac{(1000)^2 (0.15)^2 (20)}{(4\pi)^3 (10^4)^4} = 2.27 \times 10^{-11} \text{ W}$$

$$= -76 \text{ dBm}$$

The transmitter power is  $10 \log(10^4)(10^3) = 70 \text{ dBm}$ . So the isolation between receiver and transmitter must be,

$$I = 70 \text{ dBm} - (-76 \text{ dBm}) + 10 \text{ dB} = 156 \text{ dB}$$

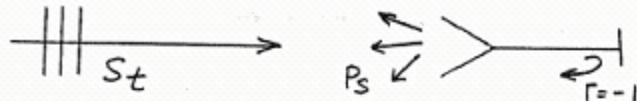**14.19**

Assume an incident plane wave with power density  $S_t$ . Then the received power of the antenna is, from (13.14) and (14.15)

$$P_r = S_t A_e = S_t \frac{\lambda^2 G}{4\pi}$$

Because of the short-circuit termination, all of this power is re-transmitted (assuming a lossless antenna), giving a radiated power in the main beam direction of,  $P_s = G P_r$ . Then the RCS can be found from (14.39) :

$$\sigma = \frac{P_s}{S_t} = \frac{\lambda^2 G^2}{4\pi} \quad \checkmark$$

14.20

$$\Delta T_{\text{TRUE}} = T_p - T_2$$


$$\Delta T_s = T_s \Big|_{T_B=T_1} - T_s \Big|_{T_B=T_2}$$

From (14.19), with  $L=1$ ,  $T_s = (1-\Gamma^2) [\eta_{\text{rad}} T_b + (1-\eta_{\text{rad}}) T_p]$

$$\begin{aligned}\Delta T_s &= (1-\Gamma^2) [\eta_{\text{rad}} T_p + (1-\eta_{\text{rad}}) T_p] \\ &\quad - (1-\Gamma^2) [\eta_{\text{rad}} T_2 + (1-\eta_{\text{rad}}) T_p]\end{aligned}$$

$$\frac{\Delta T_s}{\Delta T_{\text{TRUE}}} = \frac{(1-\Gamma^2)\eta_{\text{rad}}(T_p - T_2)}{T_p - T_2} = (1-\Gamma^2)\eta_{\text{rad}} \quad \checkmark$$

14.21

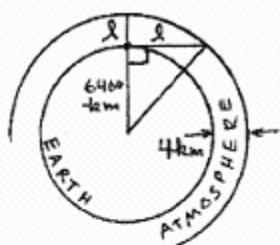

LOOKING TOWARD ZENITH,  $l = 4000 \text{ m.} = 4 \text{ km.}$

LOOKING TOWARD HORIZON,

$$l = \sqrt{(6404)^2 - (6400)^2} = 226 \text{ km.}$$

$$\alpha = 0.005 \text{ dB/km}$$

$$T = \frac{T_0}{4K} \left[ L + L(T_0) \right] \Rightarrow T_e = \frac{4}{L} + (L-1)T_0$$

$$\text{AT ZENITH: } L = (0.005 \text{ dB/km})(4 \text{ km}) = 0.02 \text{ dB} = 1.0046$$

$$T_e = \underline{5.3K}$$

$$\text{AT HORIZON: } L = (0.005 \text{ dB/km})(226 \text{ km}) = 1.13 \text{ dB} = 1.297$$

$$T_e = \underline{89K}$$

**14.22**  $f = 2.8 \text{ GHz} \Rightarrow \lambda_0 = 0.0107 \text{ m}, G = 32 \text{ dB} = 1585, P_E = 5 \text{ W}$

a)  $R = \sqrt{\frac{G P_E}{4\pi S}} = \sqrt{\frac{(1585)(5)}{4\pi(0.01 \text{ W/cm}^2)}} = 251 \text{ cm} = 2.51 \text{ m}$

b)  $G = 32 - 10 = 22 \text{ dB} = 158.5$

$$R = \sqrt{\frac{(158.5)(5)}{4\pi(0.01 \text{ W/cm}^2)}} = 79.5 \text{ cm} = 0.795 \text{ m}$$

c)  $d = \sqrt{\frac{\lambda^2 D}{\pi^2}} = 0.175 \text{ m}$  (use  $D = \frac{G}{\eta_{ap}} = 2641$ )

$$R_{ff} = \frac{2d^2}{\lambda} = 5.7 \text{ m}$$

(neither distance is in the far-field of the antenna)

**14.23**

$$S = 1300 \text{ W/m}^2 = \frac{1}{2} |\bar{E}| |\bar{H}| = \frac{1}{2\eta_0} |\bar{E}|^2 = \frac{\eta_0}{2} |\bar{H}|^2$$

$$|\bar{E}| = \sqrt{2\eta_0 S} = \sqrt{2(377)(1300)} = 990 \text{ V/m}$$

$$|\bar{H}| = \sqrt{\frac{2S}{\eta_0}} = \sqrt{\frac{2(1300)}{377}} = 2.6 \text{ A/m}$$

check:  $\frac{1}{2} |\bar{E}| |\bar{H}| = \frac{1}{2}(990)(2.6) = 1300 \text{ W/m}^2 \checkmark$

6.26

The unperturbed  $TE_{101}$  cavity fields are,

$$E_y = A \sin \frac{\pi x}{a} \sin \frac{\pi z}{d}$$

$$H_x = \frac{-jA}{z} \sin \frac{\pi x}{a} \cos \frac{\pi z}{d} ; \quad z = kn/\beta$$

$$H_z = \frac{j\pi A}{k\eta a} \cos \frac{\pi x}{a} \sin \frac{\pi z}{d}$$

Then the numerator in (6.95) is,

$$\begin{aligned} \int_{v_0}^v (\Delta\epsilon |\bar{E}_0|^2 + \Delta\mu |\bar{H}_0|^2) dv &= (\mu_r - 1) \mu_0 \int_{x=0}^a \int_{y=0}^b \int_{z=0}^t (|H_x|^2 + |H_z|^2) dz dy dz \\ &= \mu_0 (\mu_r - 1) \frac{ab}{2} A^2 \int_{z=0}^t \left( \frac{1}{z^2} \cos^2 \frac{\pi z}{d} + \frac{\pi^2}{k^2 \eta^2 a^2} \sin^2 \frac{\pi z}{d} \right) dz \\ &= \mu_0 (\mu_r - 1) \frac{ab}{2} A^2 \left[ \frac{1}{2} \left( \frac{3}{2} + \frac{\sin \frac{2\pi z}{d}}{4\pi/d} \right) \Big|_0^t + \frac{\pi^2}{k^2 \eta^2 a^2} \left( \frac{3}{2} - \frac{\sin \frac{2\pi z}{d}}{4\pi/d} \right) \Big|_0^t \right] \\ &= \mu_0 (\mu_r - 1) \frac{ab}{2} A^2 \left[ \frac{t}{2\eta^2} + \frac{\beta^2 - \pi^2/a^2}{k^2 \eta^2} \frac{d}{4\pi} \sin \frac{2\pi t}{d} \right] \end{aligned}$$

The denominator in (6.95) is  $\frac{abd\epsilon_0 A^2}{2}$ , so

$$\begin{aligned} \frac{\omega - \omega_0}{\omega_0} &= \frac{-(\mu_r - 1) ab \eta^2 [ \cdot ]}{abd} \\ &= \frac{-(\mu_r - 1)}{d} \left( \frac{t}{2} + \frac{\beta^2 - \pi^2/a^2}{k^2} \frac{d}{4\pi} \sin \frac{2\pi t}{d} \right) \end{aligned}$$

For  $t \ll d$  this simplifies to,

$$\frac{\omega - \omega_0}{\omega_0} \approx -(\mu_r - 1) \left( \frac{t}{d} \right) \left( \frac{\beta^2}{k^2} \right)$$

**6.27**

Following Example 6.8 :

at  $x = a/2, z = 0 : E_y = 0$

$$H_x = \frac{-jA}{z}, z = k_0 \eta_0 / \beta$$

$$H_y = 0$$

Then,

$$\int_{\Delta V} (u |\bar{H}_0|^2 - \epsilon |\bar{E}_0|^2) dV = M_0 \frac{A^2}{z^2} \Delta V ; \Delta V = \pi \ell r_0^2$$

$$\int_{\Delta V} (u |\bar{H}_0|^2 + \epsilon |\bar{E}_0|^2) dV = \frac{V_0 \epsilon_0 A^2}{2}$$

So (6.102) reduces to,

$$\frac{\omega - \omega_0}{\omega_0} = \frac{2M_0 \Delta V}{z^2 \epsilon_0 V_0} = \frac{2\eta_0^2 \Delta V \beta^2}{k_0^2 \eta_0^2 V_0} = \frac{2\beta^2}{k_0^2} \frac{\Delta V}{V_0}$$

(an increase in resonant frequency)